
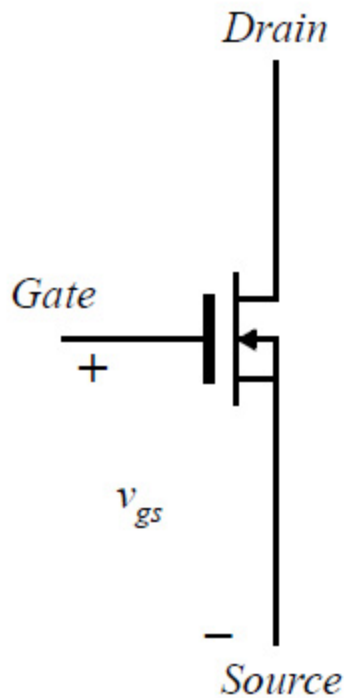

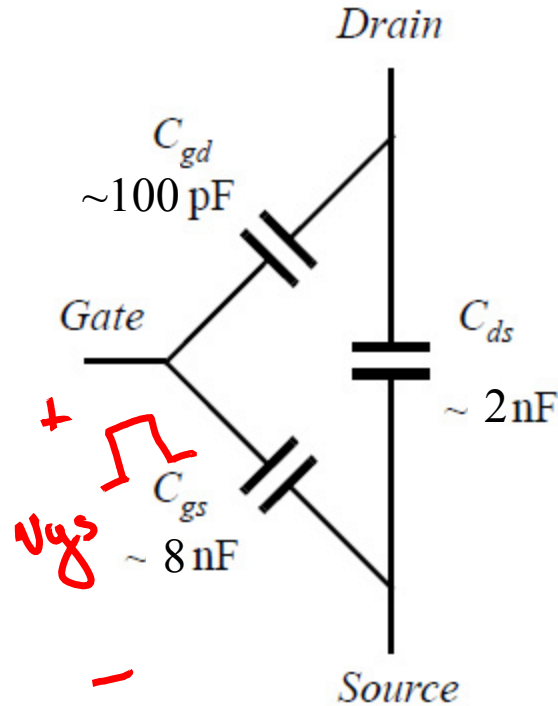
# Driving a Power MOSFET Switch

- MOSFET is off when  $v_{gs} < V_{th} \approx 3 \text{ V}$
- MOSFET fully on when  $v_{gs}$  is sufficiently large (10-15 V)
- Warning: MOSFET gate oxide breaks down and the device fails when  $v_{gs} > 20 \text{ V}$ .
- Fast turn on or turn off (10's of ns) requires a large spike (1-2 A) of gate current to charge or discharge the gate capacitance
- MOSFET gate driver is a logic buffer that has high output current capability




Power MOSFET




MOSFET capacitances

# Driving a Power MOSFET Switch

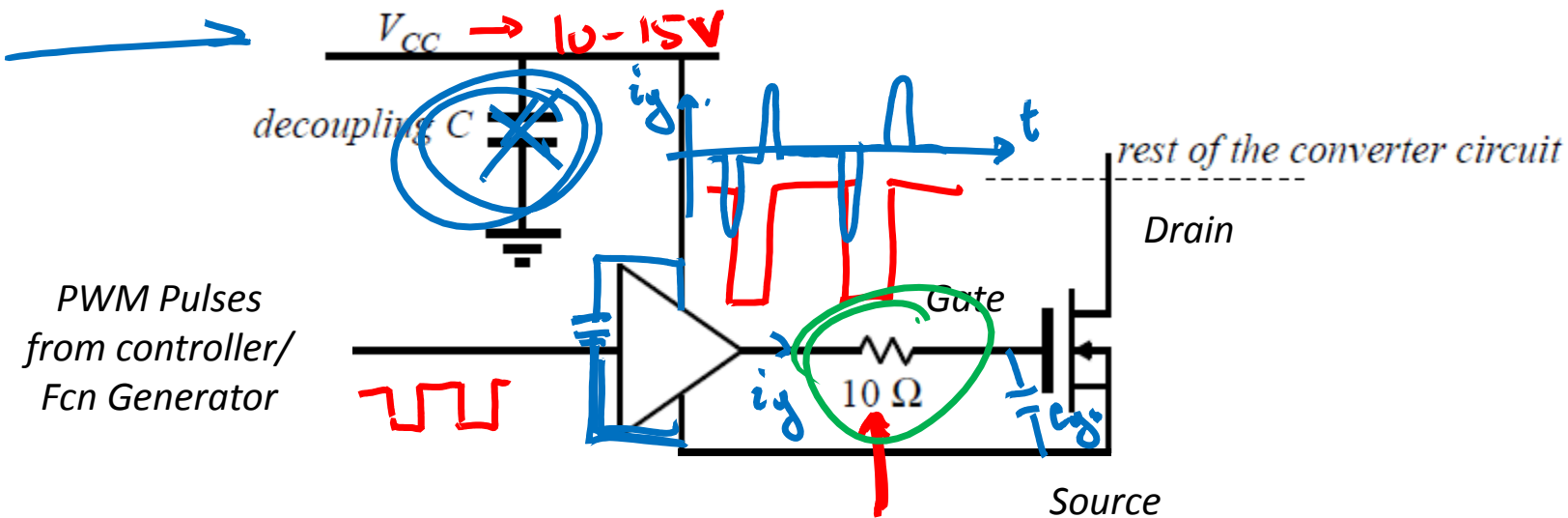

- MOSFET gate driver is used as a logic buffer with high output current ( $\sim 1.8\text{ A}$ ) capability
- The amplitude of the gate voltage equals the supply voltage  $V_{CC}$
- Decoupling capacitors are necessary at all supply pins of LM5104 (and all ICs)
- Gate resistance used to slow  $dv/dt$  at switch node

# Gate Drive Implementation

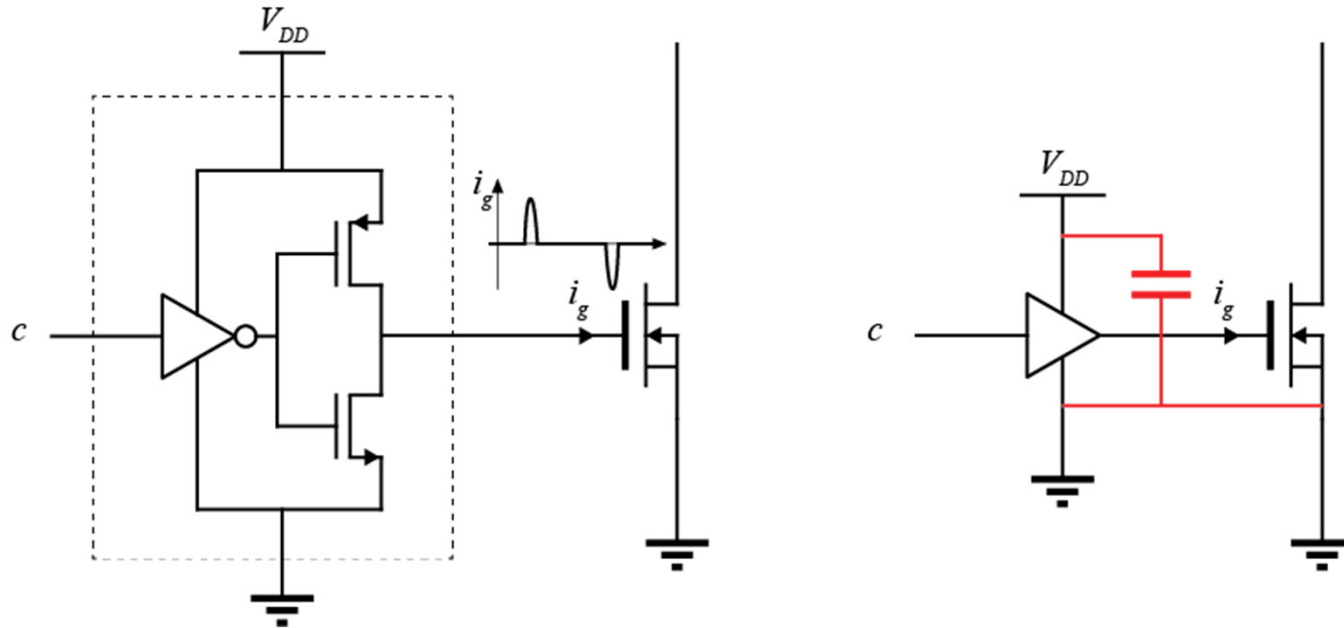

- Gate driver is cascaded half-bridges of increasing size to obtain quick rise times
- Reminder: keep loops which handle pulsating current small by decoupling and making close connections

# Capacitor Sizing – Pulsed Caps



Most Important Loops in Power converter layout

1

Power Loop

2

Each gate drive Loop

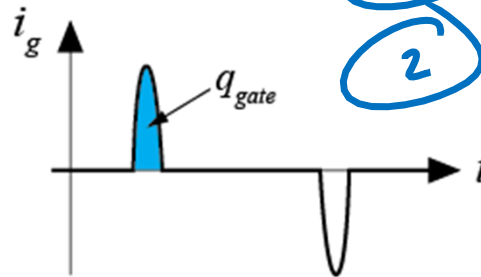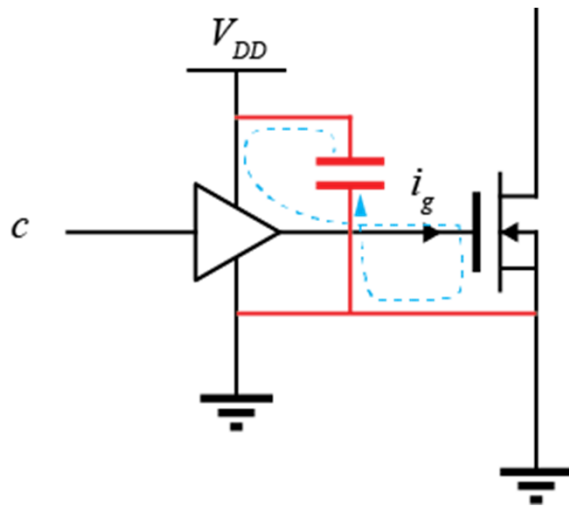


$$\frac{q_{gate}}{\Delta V_{DD}} = C$$

everything else



- Area of current pulse is total charge supplied to gate of capacitor
- All charge must be supplied from gate drive decoupling capacitor

# High Side Signal Ground

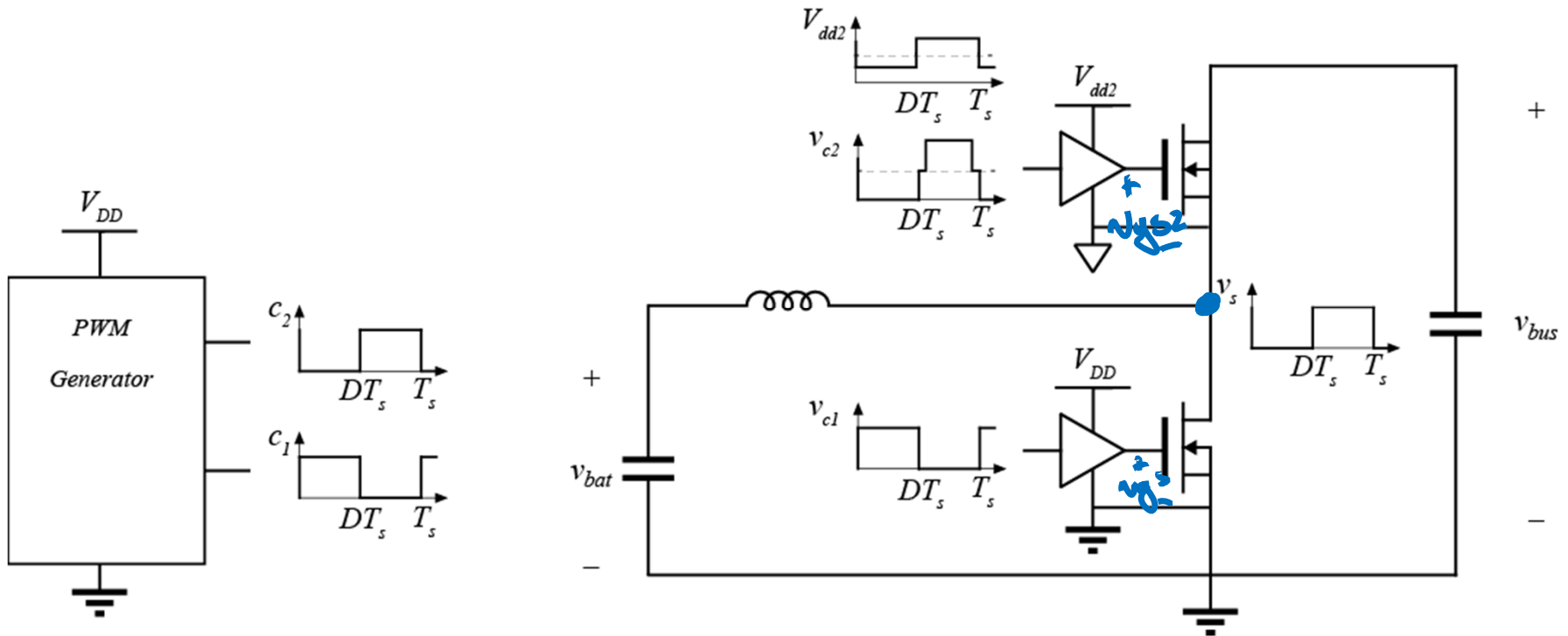


- Gate driver chip must implement  $v_{gs}$  waveforms
- Issue: source of  $Q_2$  is not grounded

# Generating Floating Supply

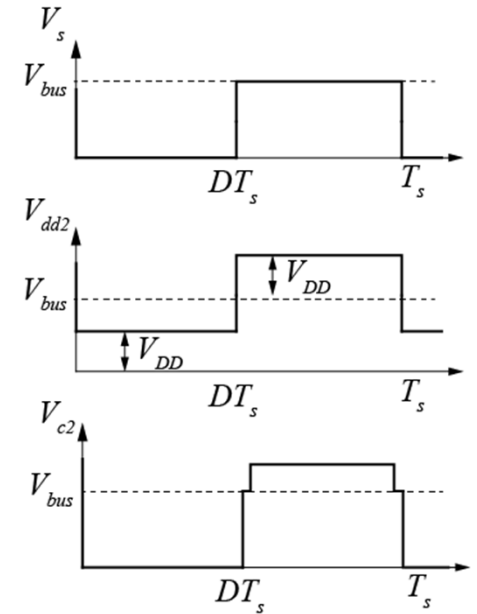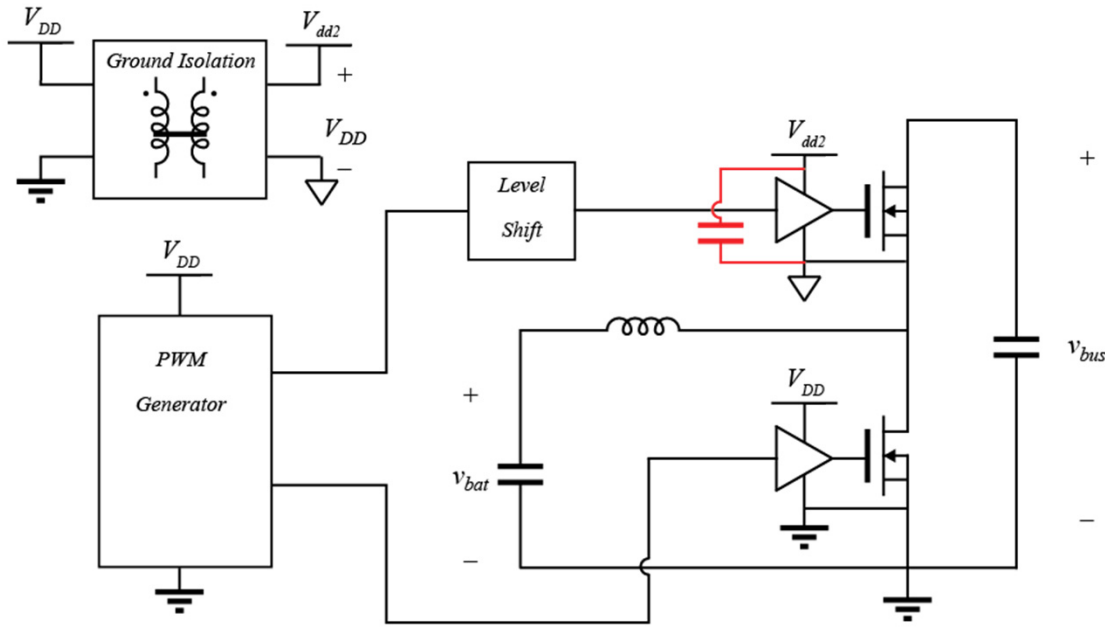

- Isolated supplies sometimes used; Isolated DC-DC, batteries
- Bootstrap concept: capacitor can be charged when  $V_s$  is low, then switched


Direct Drive

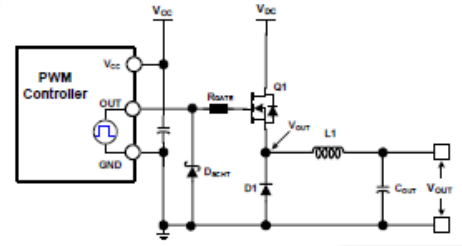

Easiest high-side application the MOSFET and can be driven directly by the PWM controller or by a ground referenced driver, but it must meet two conditions, as follows:


$$V_{CC} < V_{GS,MAX} \quad \text{and} \quad V_{DC} < V_{CC} - V_{GS,Miller}$$

Floating Supply Gate Drive

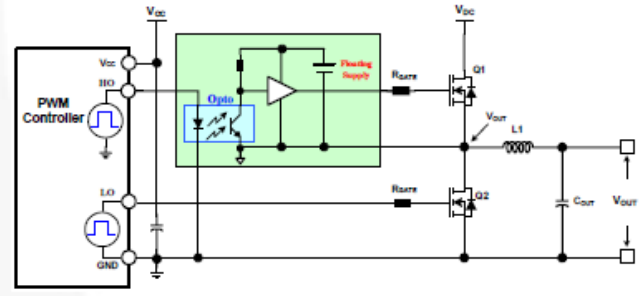


Cost impact of isolated supply is significant. Optocoupler tends to be relatively expensive, limited in bandwidth, and noise sensitive.

Transformer Coupled Drive

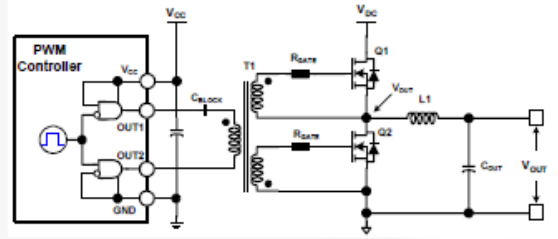


Gives full gate control for an indefinite period of time, but is somewhat limited in switching performance. This can be improved with added complexity.

Charge Pump Drive

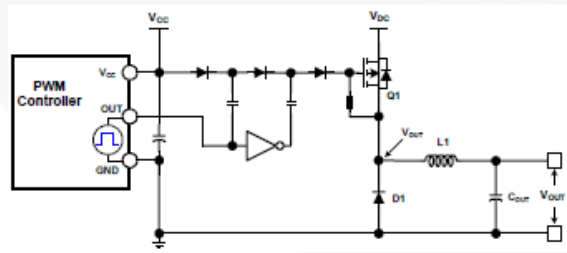

The turn-on times tend to be long for switching applications. Inefficiencies in the voltage multiplication circuit may require more than low stages of pumping.

Bootstrap Drive

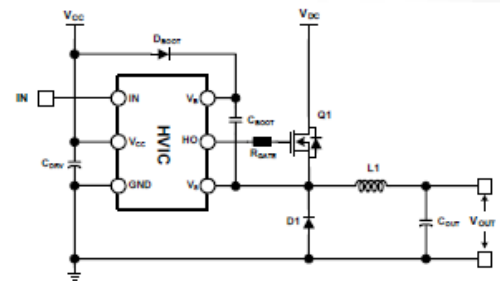

Simple and inexpensive with limitations; such as, the duty cycle and on-time are both constrained by the need to refresh the bootstrap capacitor. Requires level shift, with the associated difficulties.

# UCC27712 Internal Diagram

