


Complete Routing of Signal

- Always consider return path
- Ground plane can help, but still need to consider the path and optimize

Decoupling


- Always add bypass capacitor at power supply for any IC/reference
- Use small-valued ($\sim 100\text{nf}$), low ESR and ESL capacitors (ceramic)
- Limit loop for any di/dt

Decoupling

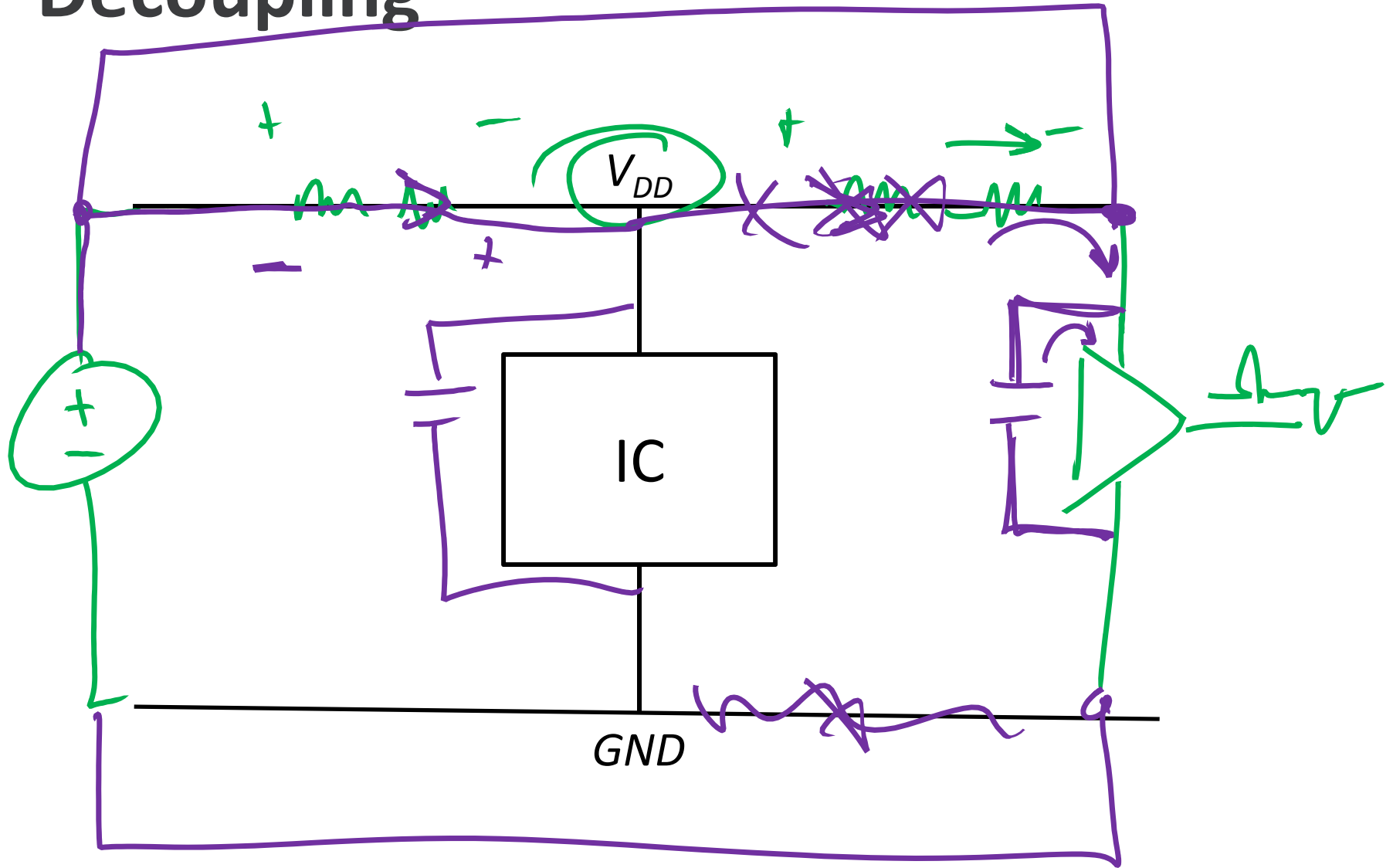


Star-Grounding Vs. Daisy Chain

Undesired

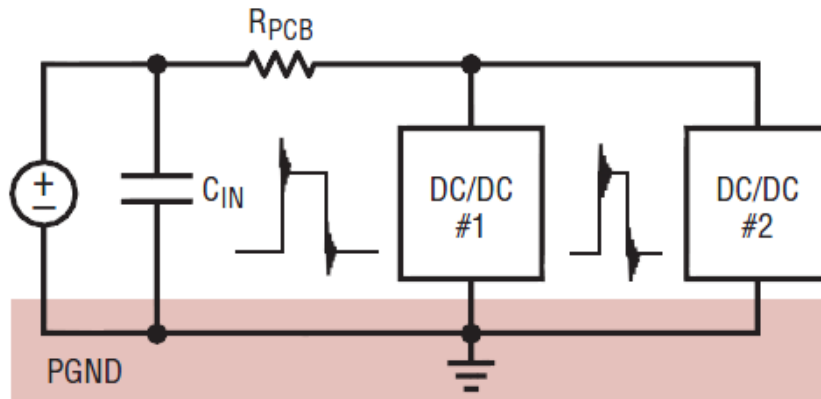

Desired

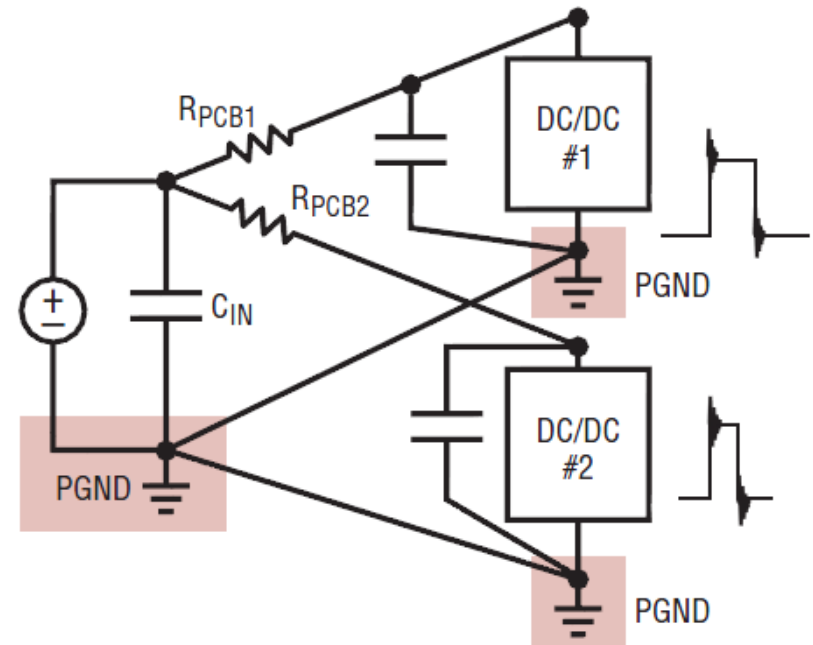

AN136 F09

Figure 9. Separate the Input Current Paths Among Supplies

Capacitor Sizing – Filter Caps


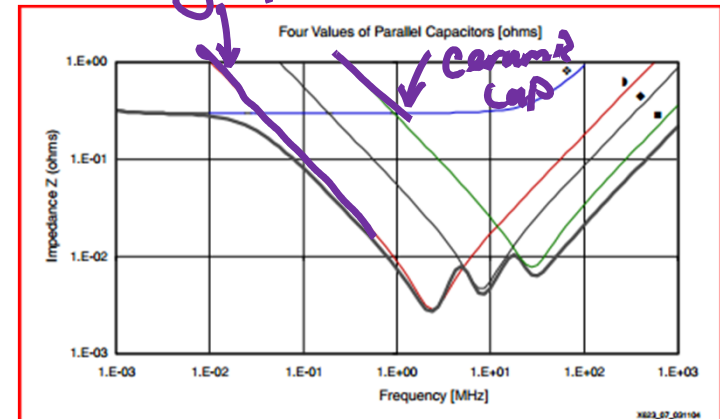
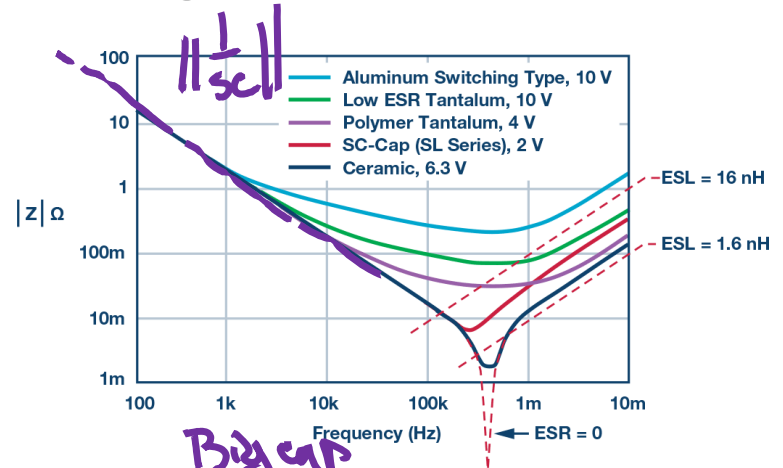


Figure 8: PDS Impedance Versus Frequency Plot


Table 8: Values Used in Impedance Plot of Figure 8

Quantity	Symbol	Package	Capacitive Values (μF)	Parasitic Inductance (nH)	Parasitic Resistance (ohms)
2	◇	E	680	2.8	0.57
7	▶	0805	2.2	2.0	0.02
13	◆	0603	0.22	1.8	0.06
26	■	0402	0.022	1.5	0.20


Kelvin Connection

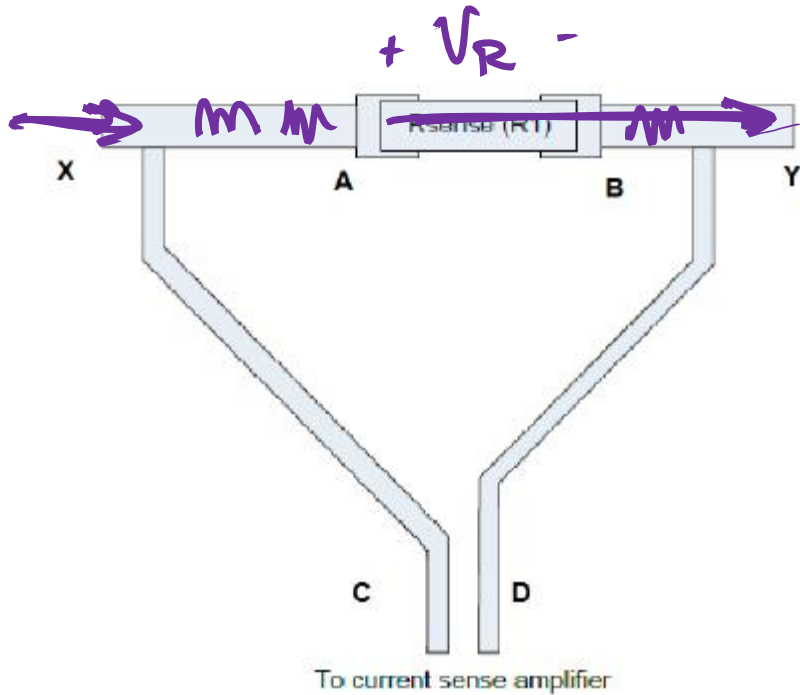

$+ V_R +$
 $- V_{parasitic}$

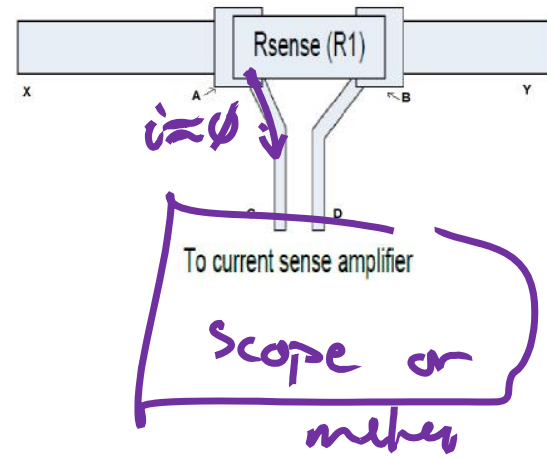

Efficiency Measurement

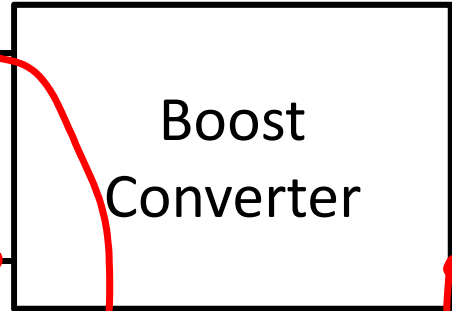

i_{in}

v_{g1}

v_{g2}

i_{out}

v_{out}



High Impedance Nodes

