

Motor Control

- Motor control is open-loop
- User throttle monotonically increases power
 - Controlled as BLDC motor
- Two options to change throttle
 - Alter boost output voltage
 - Alter duty cycle of motor drive

Motor Driver: Trapezoidal Control

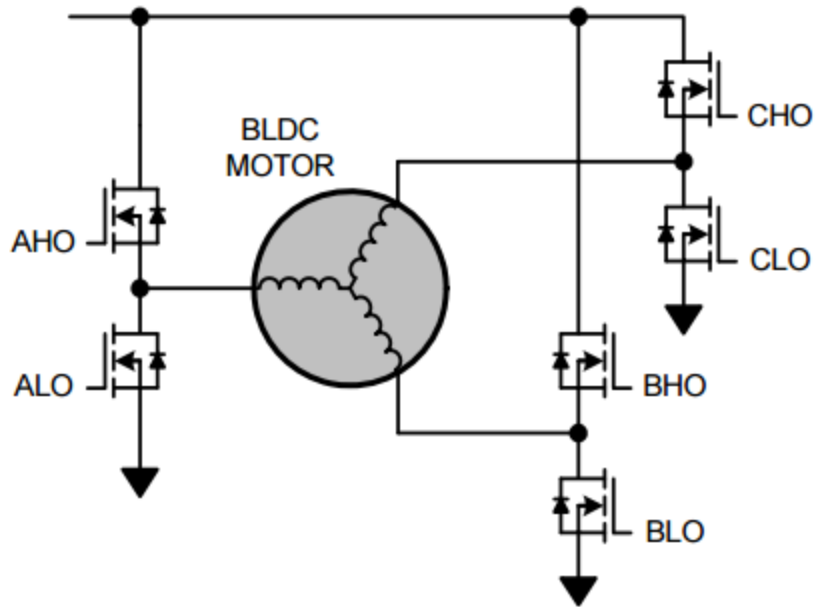


FIGURE 3. BASIC BLDC MOTOR POWER TOPOLOGY

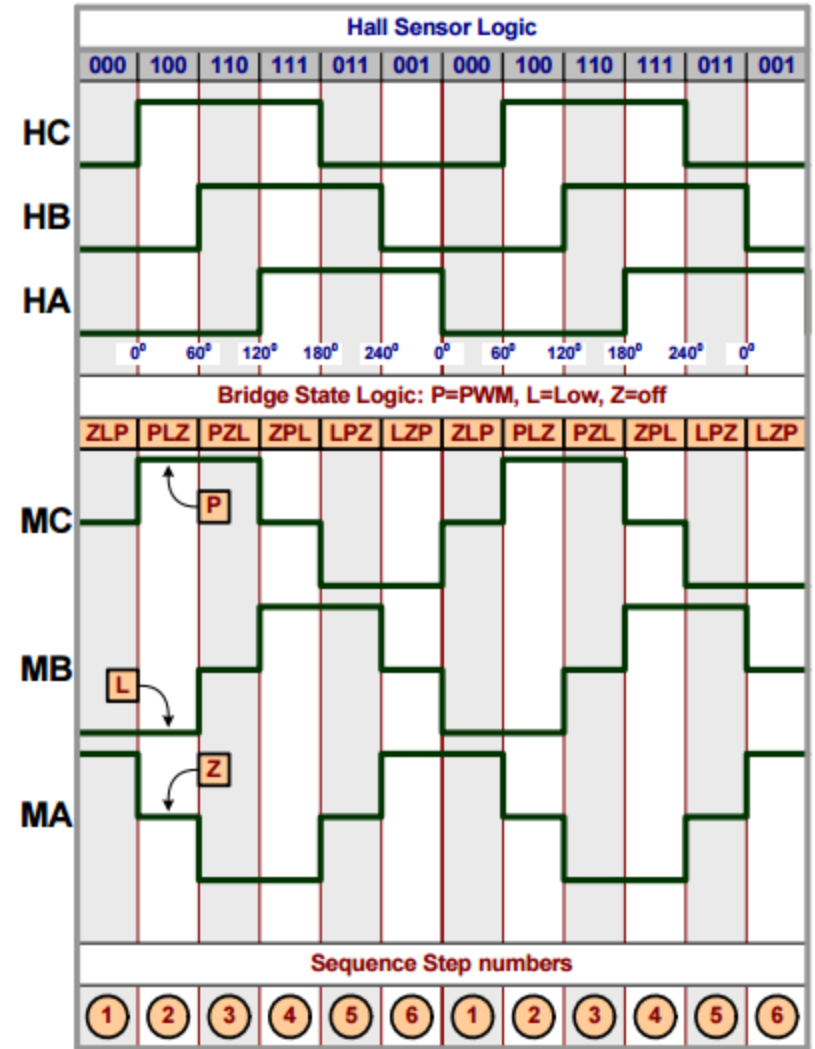


FIGURE 4. HALL SENSOR LOGIC vs BRIDGE STATE LOGIC

Trapezoidal Control: HF PWM

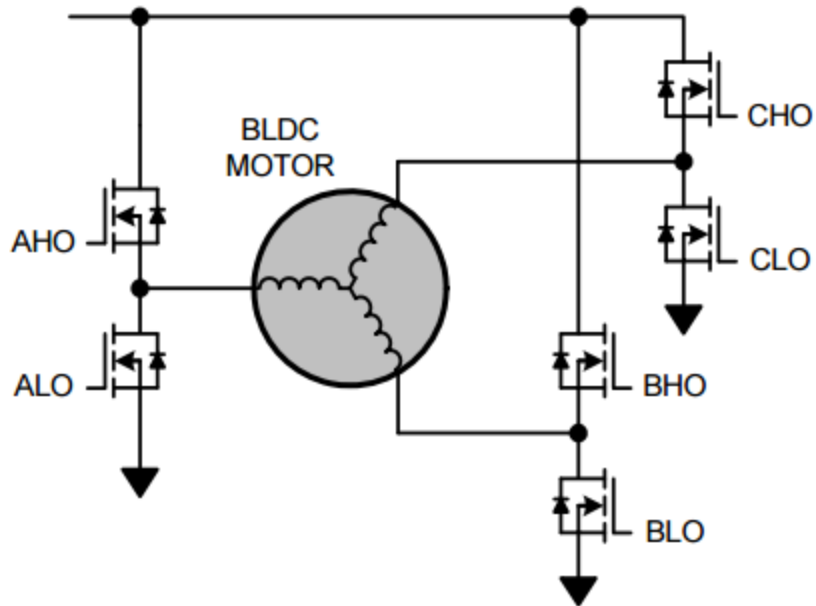


FIGURE 3. BASIC BLDC MOTOR POWER TOPOLOGY



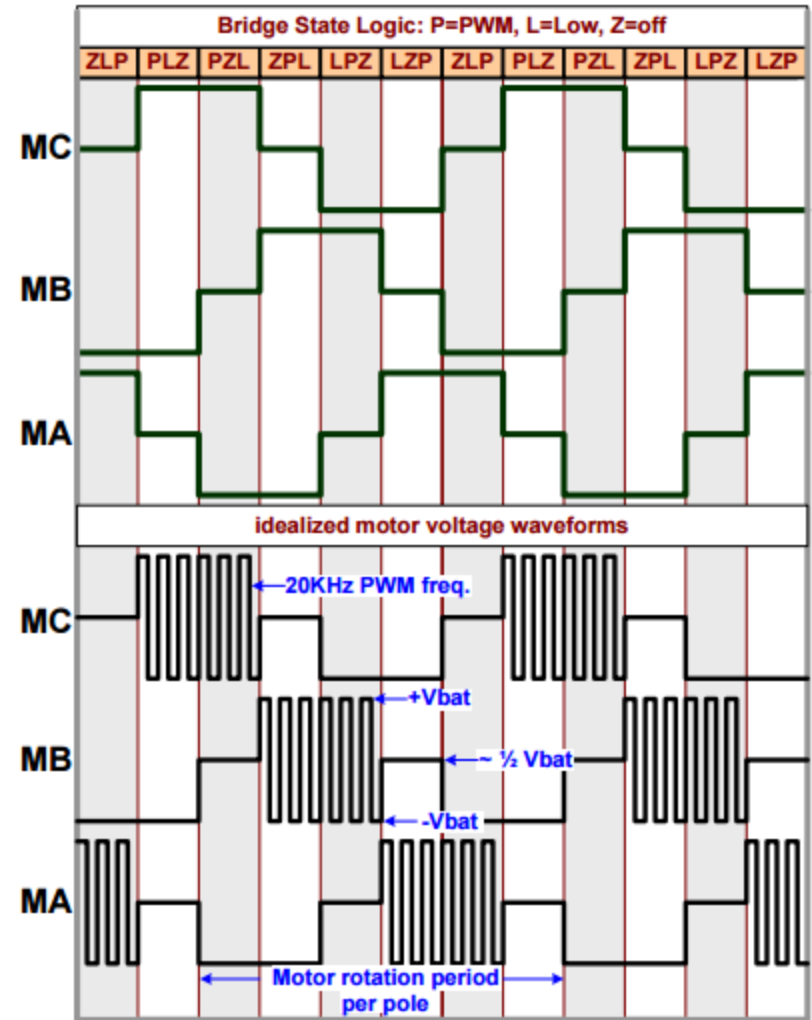


FIGURE 5. BRIDGE STATE LOGIC vs MOTOR VOLTAGE


A Note: Reflected Voltages

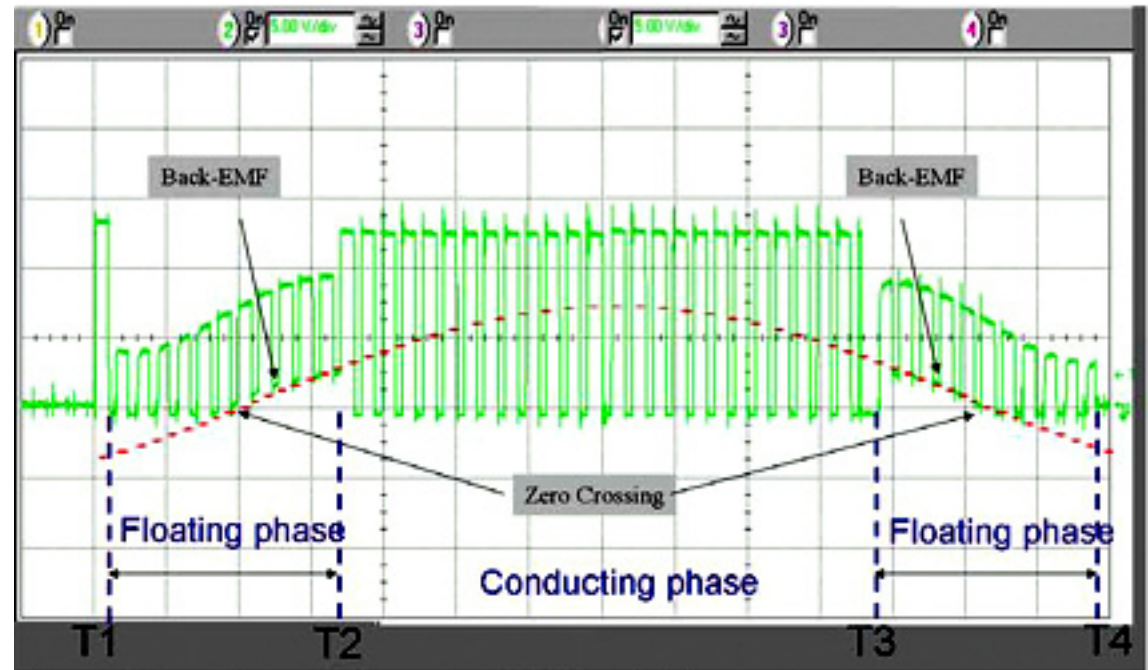


Sinusoidal (Vector) Control

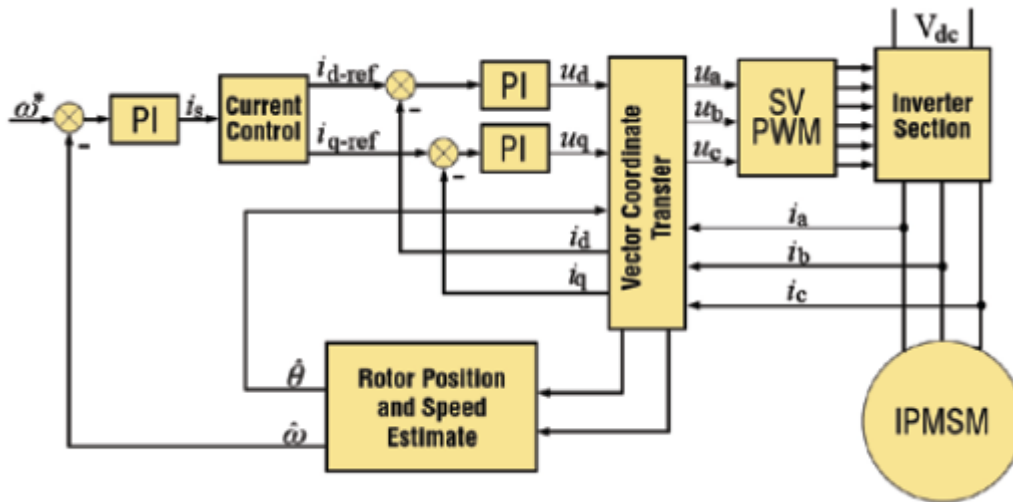

"Trapezoidal"

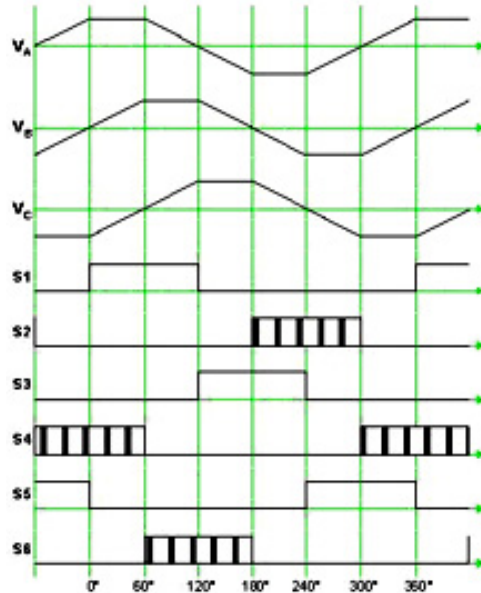


"Sinewave"

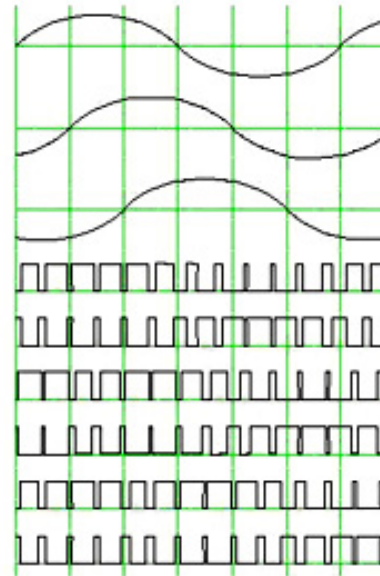


DC Bus Ripple – Trapezoidal Control

- $C_{DC} = 100\mu\text{F}$

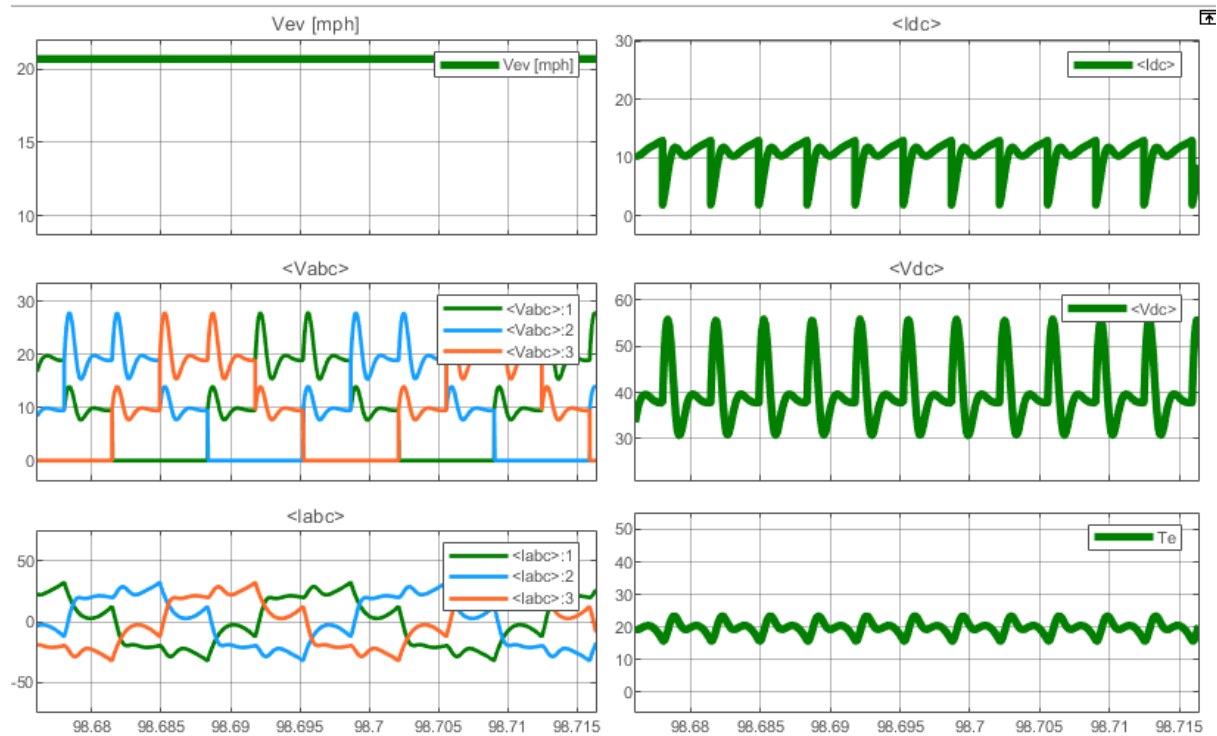


DC Bus Ripple – Sinusoidal Control

- $C_{DC} = 100\mu\text{F}$

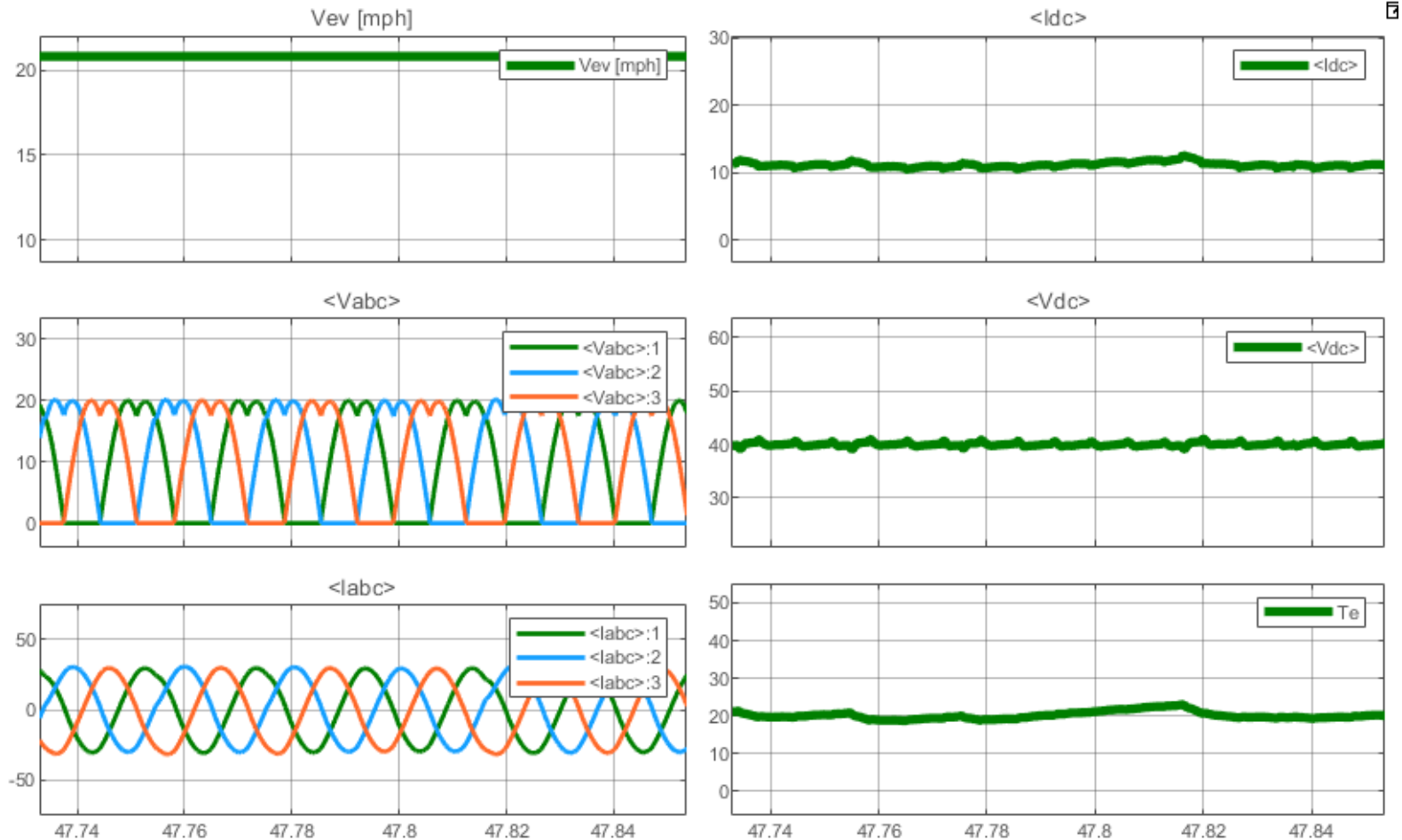

Reference Filtering

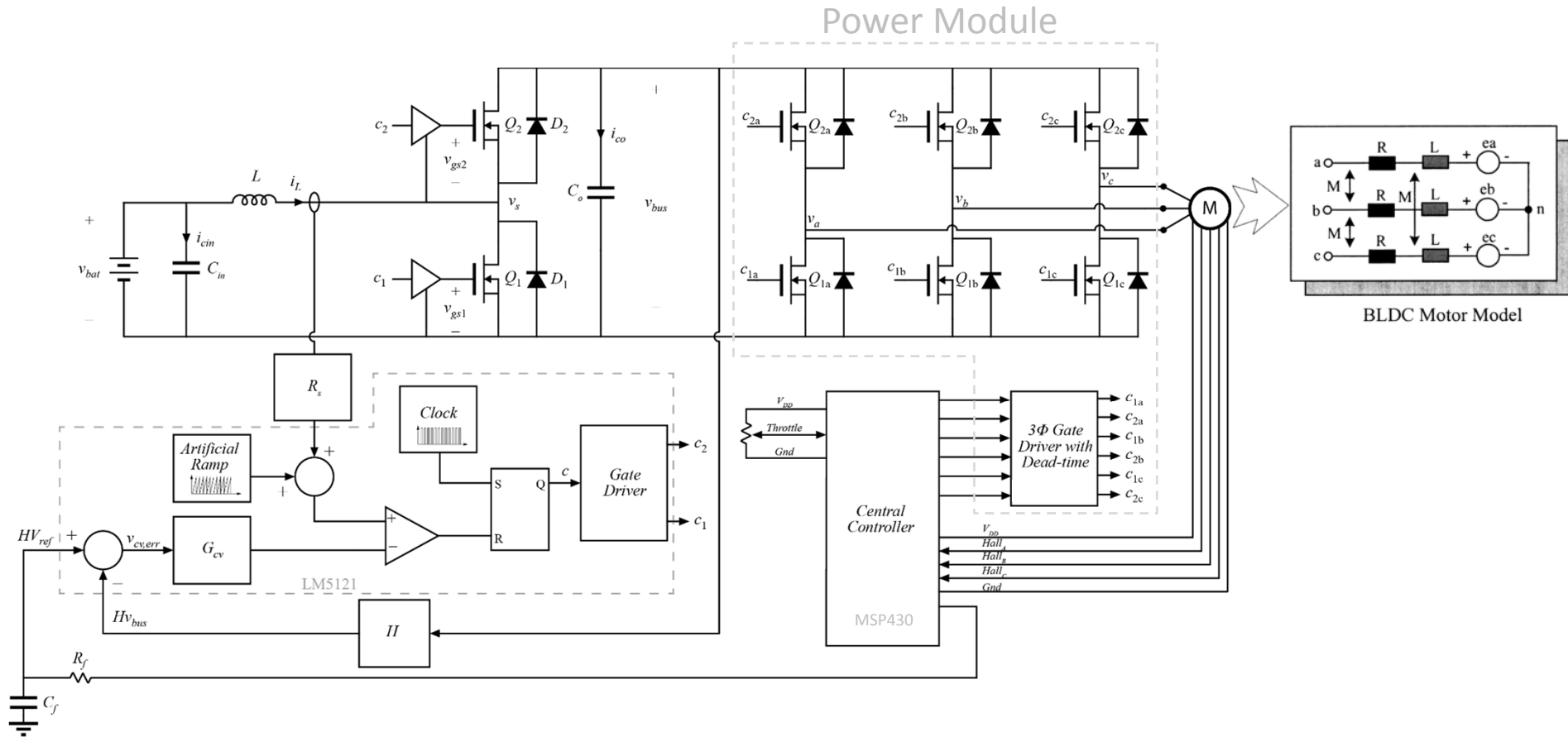


Motor Control Bandwidth

Throttle
Release


No Filter

May require braking circuit

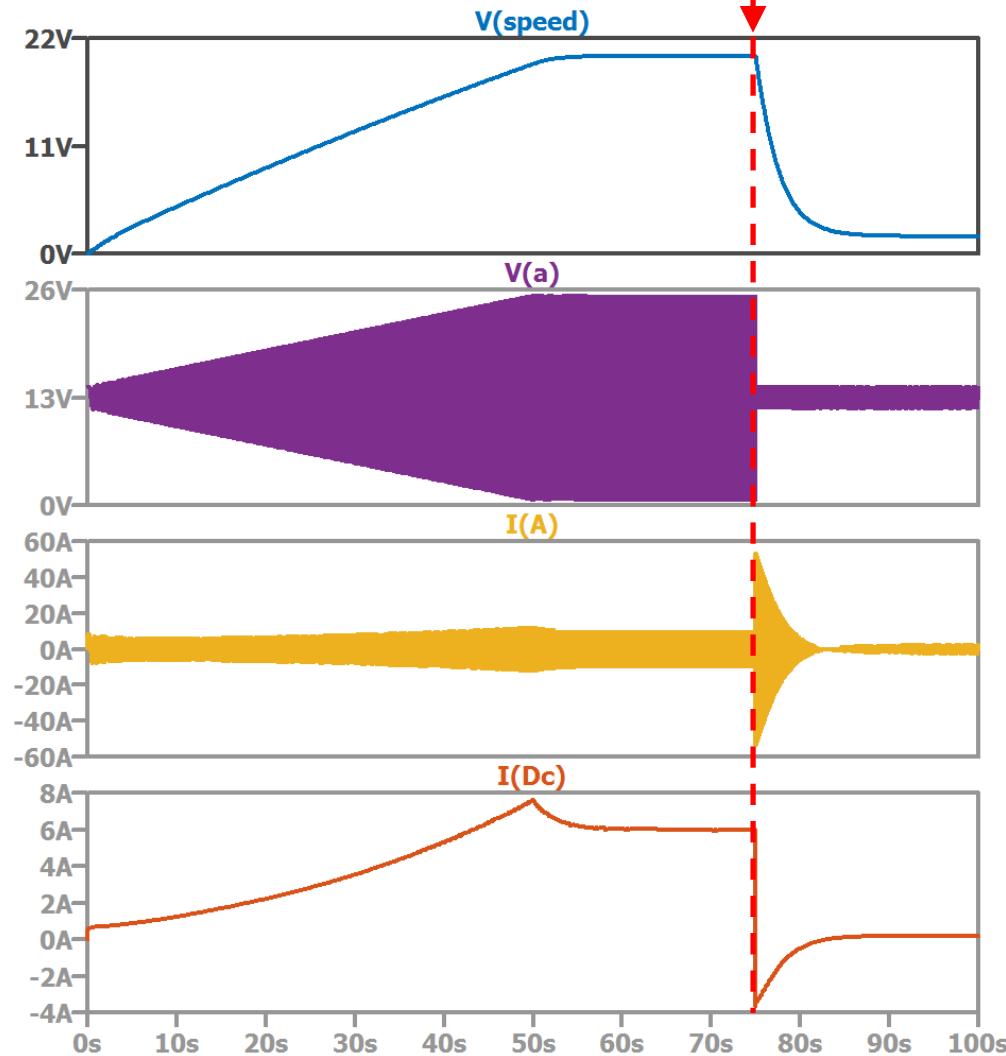

Motor Control Bandwidth

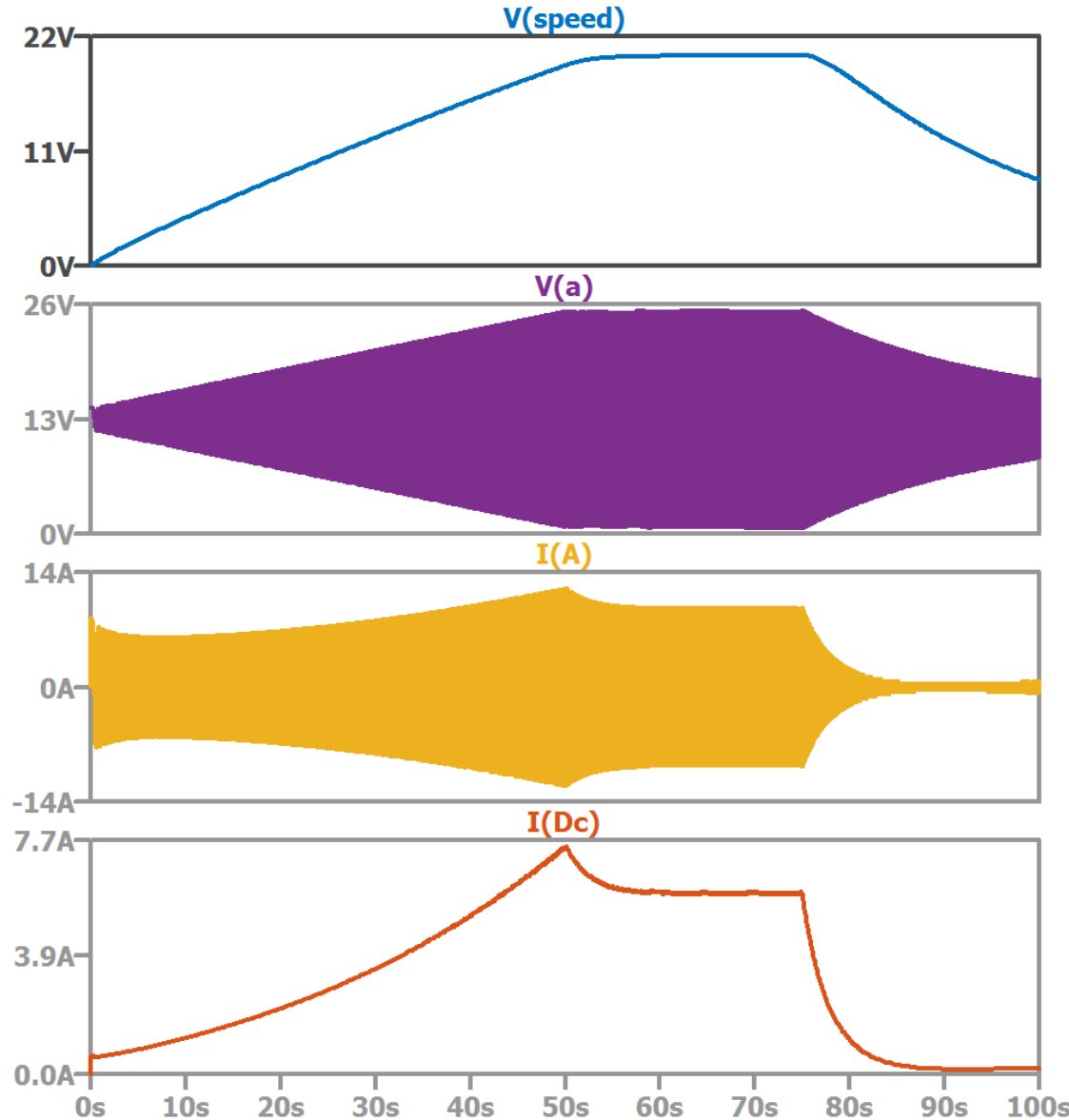$f_c = 8 \text{ mHz} + \text{ antiparallel diode}$



Motor Drive

- Power Stage
 - Power module
 - Integrated devices, and/or drivers
 - 3 Φ bridge (e.g. MTI85W100GC, IRAM136-3023B)
 - Half bridge (e.g. SQJ974EP, IPG20N10S4L)
 - Individual FETs
- Controller
 - Allegro A4915
 - Toshiba TB6551FAG
 - **TI DRV8308**
 - Other options
- Example Schematics in Starter Files for Experiment 5