

PCB Layout for Experiment 5

- Include test points for voltages/currents to aid debugging
- Where possible, give yourself “backup options”
- Include option for heatsink
- Fans available, but consider power consumption
- Make sure parts you select are available and have sufficient stock
 - even if some get ordered in the interim




Basic PCB Layout Concepts

- Kelvin Connection
- Parasitic Capacitances and Decoupling
- Loop Inductances / Complete Routing
- Decoupling
- Ground Plane / Return Currents
- Partitioning

Trace Parasitics

$$R = \frac{\rho Z}{XY}$$

ρ = RESISTIVITY

 

SHEET RESISTANCE CALCULATION FOR 1 OZ. COPPER CONDUCTOR:

$$\rho = 1.724 \times 10^{-6} \Omega\text{cm}, Y = 0.0036\text{cm}$$

$$R = 0.48 \frac{Z}{X} \text{m}\Omega$$


$$\frac{Z}{X} = \text{NUMBER OF SQUARES}$$

$$R = \text{SHEET RESISTANCE OF 1 SQUARE (Z=X)} \\ = 0.48\text{m}\Omega/\text{SQUARE}$$



$$\text{WIRE INDUCTANCE} = 0.0002L \left[\ln \left(\frac{2L}{R} \right) - 0.75 \right] \mu\text{H}$$

 
EXAMPLE: 1cm of 0.5mm o.d. wire has an inductance of 7.26nH
($2R = 0.5\text{mm}$, $L = 1\text{cm}$)



$$\text{STRIP INDUCTANCE} = 0.0002L \left[\ln \left(\frac{2L}{W+H} \right) + 0.2235 \left(\frac{W+H}{L} \right) + 0.5 \right] \mu\text{H}$$

EXAMPLE: 1cm of 0.25 mm PC track has an inductance of 9.59 nH
($H = 0.038\text{mm}$, $W = 0.25\text{mm}$, $L = 1\text{cm}$)

Figure 12.18: Wire and Strip Inductance Calculations

 

$$C = \frac{0.00885 E_r A}{d} \text{pF}$$

A = plate area in mm^2

d = plate separation in mm

E_r = dielectric constant relative to air

- ▼ Most common PCB type uses 1.5mm glass-fiber epoxy material with $E_r = 4.7$
- ▼ Capacitance of PC track over ground plane is roughly 2.8 pF/cm²

Figure 12.24: Capacitance of two parallel plates

Figure 12.2: Calculation of Sheet Resistance and Linear Resistance
for Standard Copper PCB Conductors

Kelvin Connection

 


Figure 1. Kelvin Connection

Decoupling

- Always add bypass capacitor at power supply for any IC/reference
- Use small-valued ($\sim 100\text{nf}$), low ESR and ESL capacitors (ceramic)
- Limit loop for any di/dt

Decoupling Capacitance

 
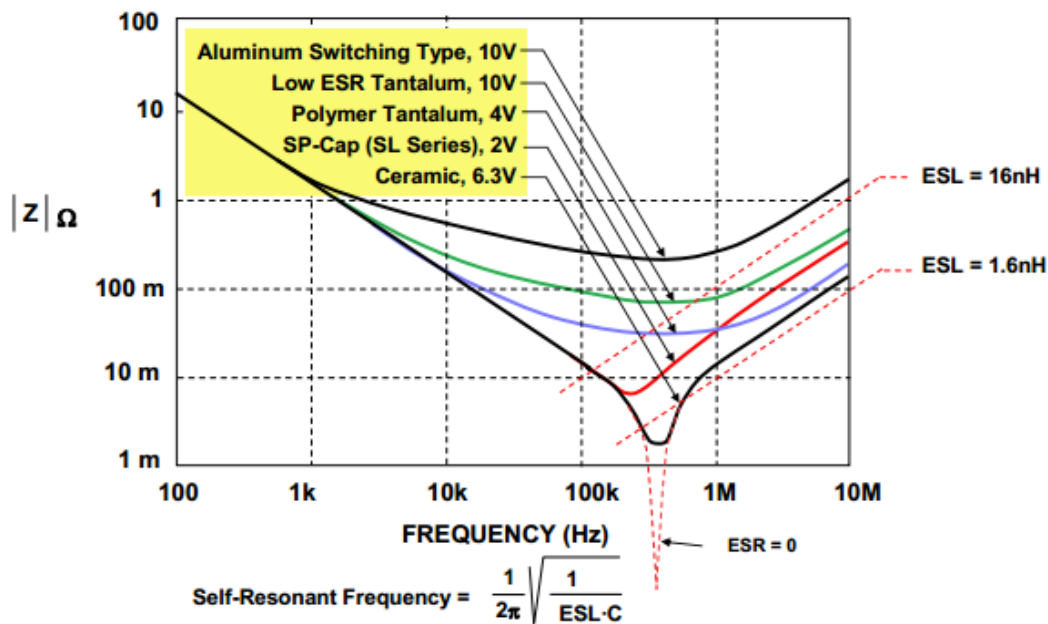


Figure 4: Impedance of Various 100 μF Capacitors

High Impedance Nodes and Capacitive Coupling

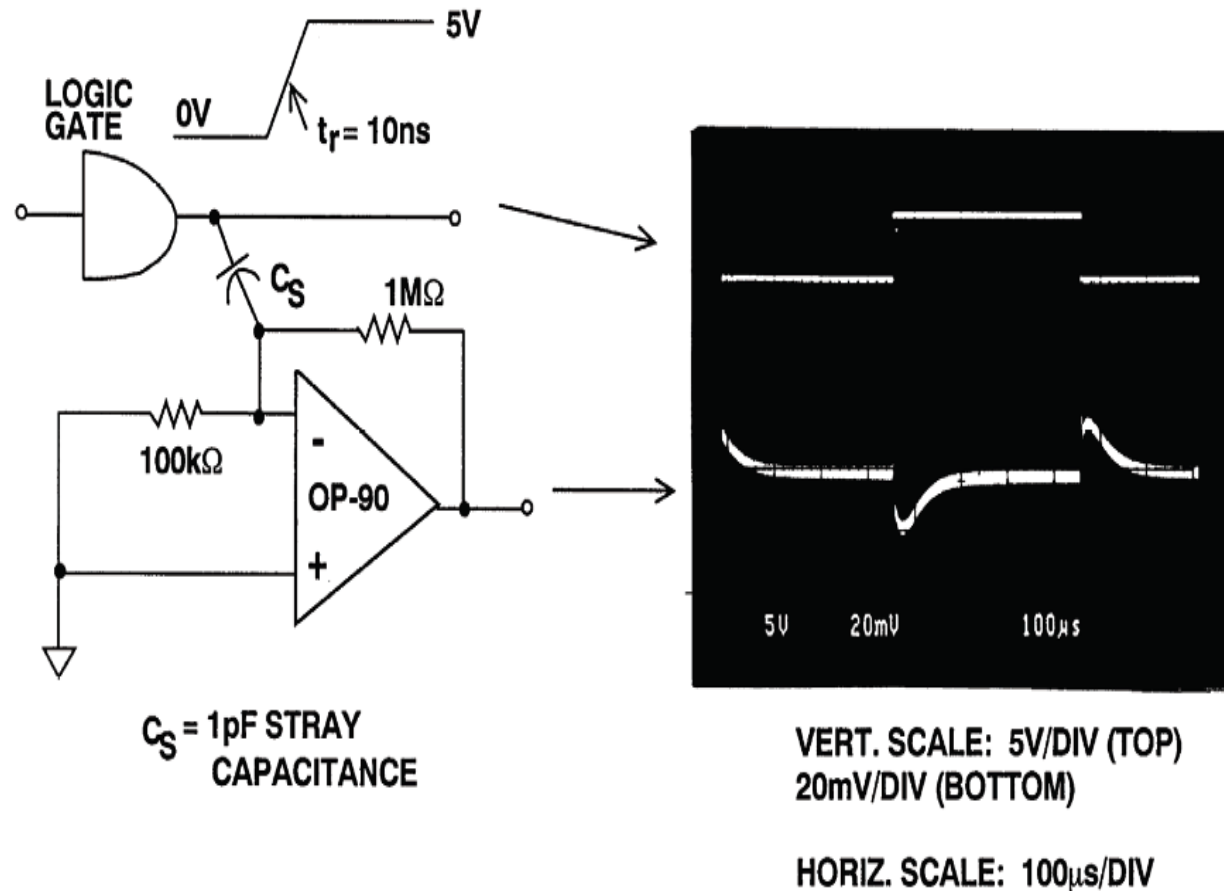


Figure 12.29 High Circuit Impedances Increase Susceptibility to Noise Pickup

Capacitive Shielding


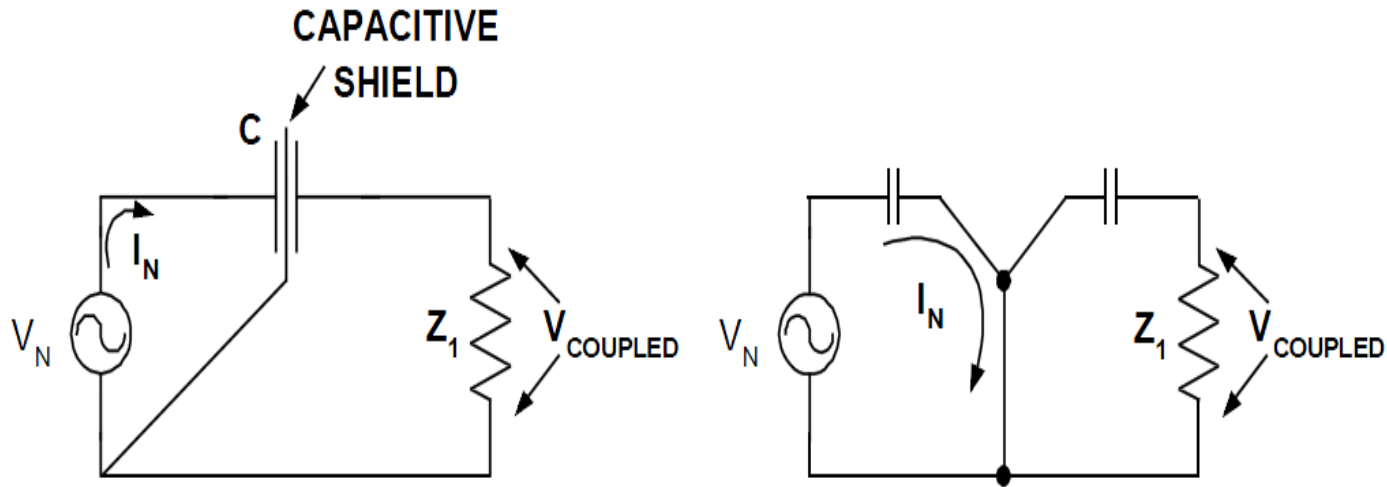



Figure 12.26: An Operational Model of a Faraday Shield

 

Loop Inductances



 
Bad practice: wide separation of signal and return





Good practice: close coupling of signal and return

Ground Plane

 - Benefits:
 - Common reference
 - Shielding
 - Heat dissipation
 - Reduced inductance (increased capacitance)
- Resist urge to cut ground plane as much as possible; consider paths of return currents when cuts are unavoidable





Ground Plane Cuts

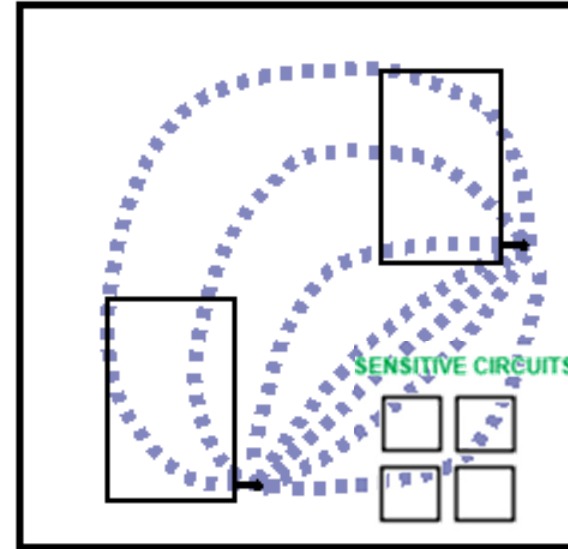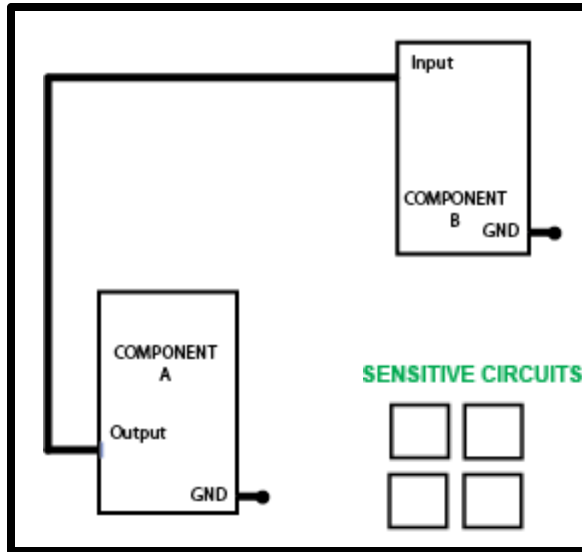

Ground return current path

Ground Plane Cuts

 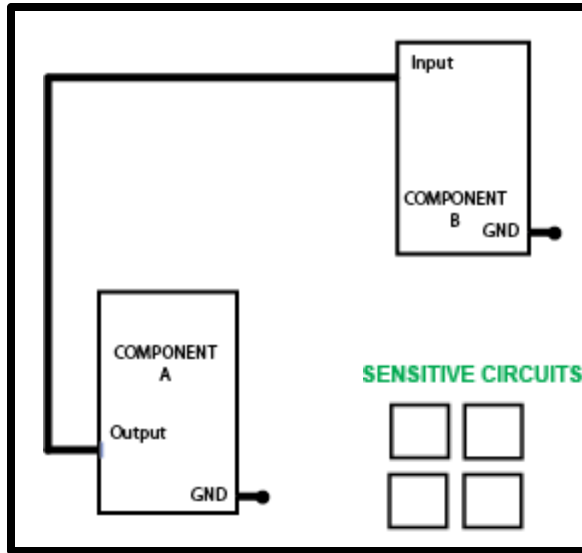

Ground return current path


Cuts in Ground Plane

- Goals:
 - minimize inductance/loops
 - Minimize ground interference
- Routing cuts should be kept short and out of the path of any significant (high frequency) return paths
- Cuts can be used effectively for ground isolation, and to reduce noise coupled between digital/analog/power circuitry
- Reducing parasitic capacitance in sensitive signal locations (i.e. op-amp circuitry)


Ground Plane Example

Half Bridge Loop Inductance

 Parasitic inductances of input loop explicitly shown:




 Addition of bypass capacitor confines the pulsating current to a smaller loop:




high frequency currents are shunted through capacitor instead of input source

 
Even better: minimize area of the high frequency loop, thereby minimizing its inductance




Bridge Layout

 

Half Bridge Layout: Another Example

 


(a)

 


(a)




(b)

 


(a)

 


(b)

 

Lateral


 


Vertical

 

“Optimal”

Layout Impact Measurements

  

- Smallest Loop Area results in
 - Smaller overvoltage
 - Lower switching loss