
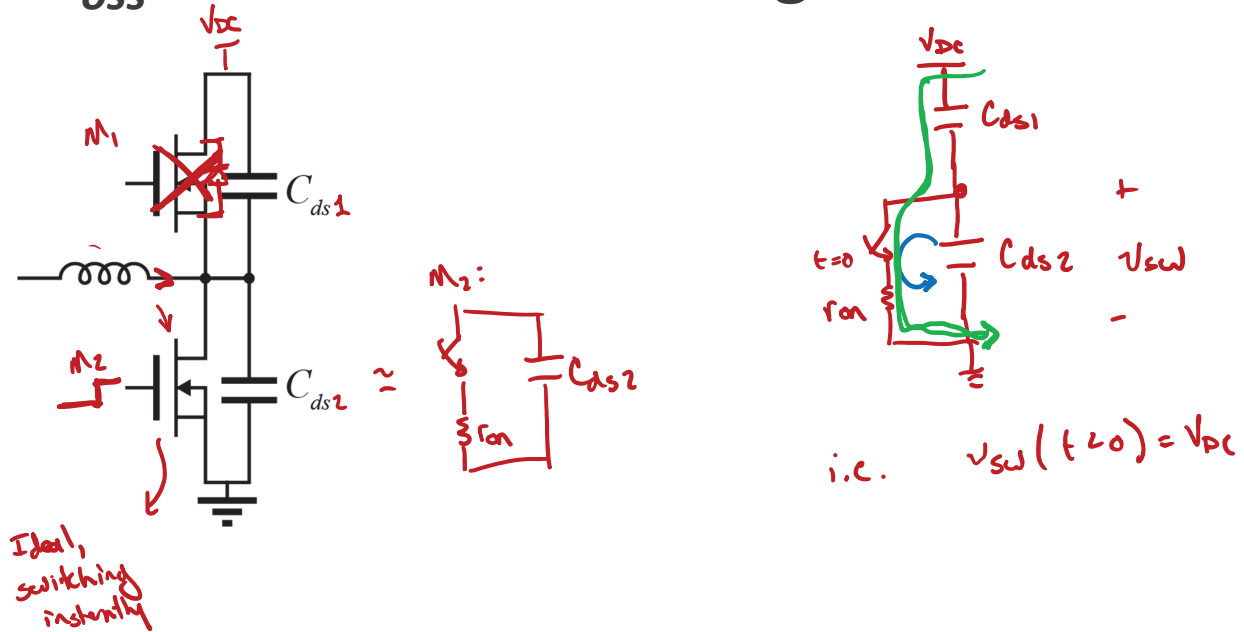


C_{oss} Losses in a Half Bridge

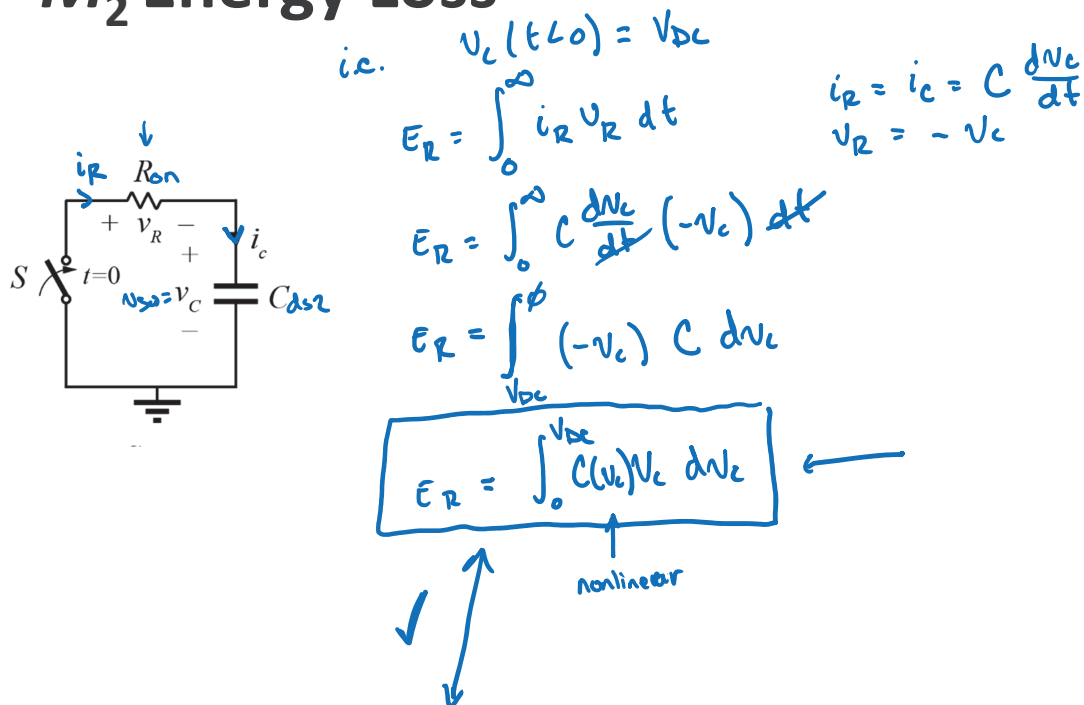


M_2 Energy Loss



Insight: $E_R = \frac{1}{2} C_{eq} V_{DC}^2$

M₁ Energy Loss

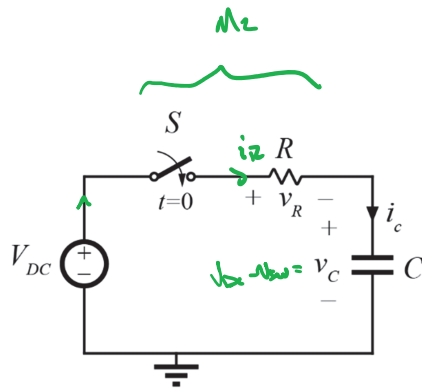

i.e. $v_C(t=0) = 0$

$$E_R = \int_0^\infty i_R v_R dt$$

$$i_R = i_C = C \frac{dv_C}{dt}$$

$$v_R = V_{DC} - v_C$$

cas1 $E_R = \int_0^\infty C \frac{dv_C}{dt} (V_{DC} - v_C) dt$

$$E_R = \int_0^{V_{DC}} V_{DC} C dv_C - \int_0^{V_{DC}} C v_C dv_C$$

$$E_R = V_{DC} \int_0^{V_{DC}} C dv_C - \int_0^{V_{DC}} C v_C dv_C$$

\checkmark \uparrow \uparrow
 Q E

Insight: $E_R = V_{DC} (V_{DC} C_{eq,a}) - \frac{1}{2} C_{eq,E} V_{DC}^2$

Total Half Bridge C_{oss} Loss


$$E_{tot} = \frac{1}{2} C_{eq,E(M_2)} V_{DC}^2 + V_{DC}^2 C_{eq,a(M_1)} - \frac{1}{2} C_{eq,E(M_1)} V_{DC}^2$$

If M_1 & M_2 are identical $C_{ds1} = C_{ds2}$


then $E_{tot} = V_{DC}^2 C_{eq,a}$!

total energy lost depends only on charge-equivalent.

Energy Equivalent

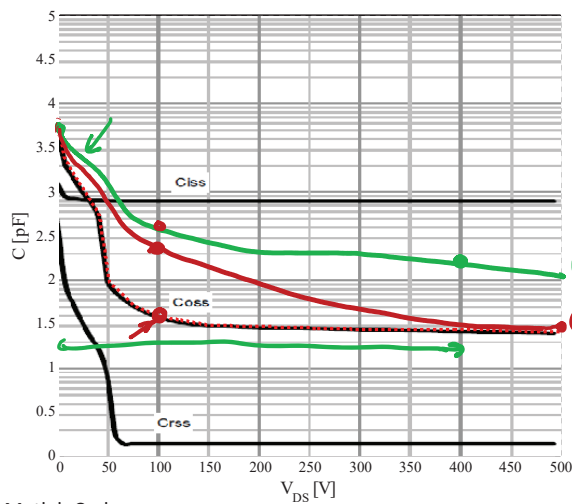

Almost always in datasheet

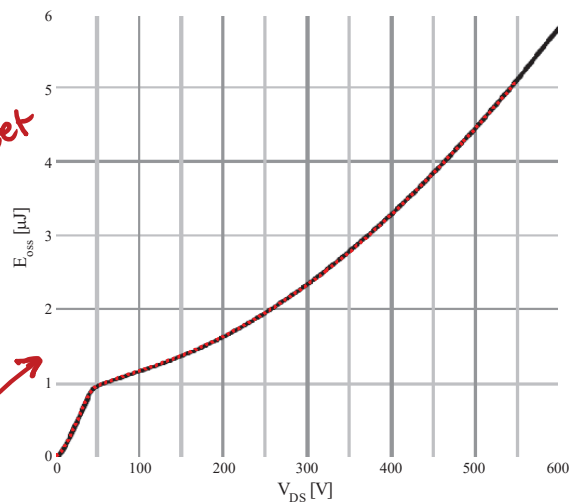

Matlab Code:

Vdc = 550;

Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];

Coss = [5500 2500 1900 550 95 50 38 30 29 27 27 25 24]*1e-12;

vx = 0.01:0.01:Vdc;

Cx = 10.^interp1(Vds, log10(Coss), vx, 'linear'); ← Interpolate

E = cumtrapz(vx, Cx.*vx); ← $\int C_V dv_V = E$

Ceq_e = 2*(E)./vx.^2;

Nonlinear Capacitance Extraction

- <http://web.eecs.utk.edu/~dcostine/personal/PowerDeviceLib/DigiTest/index.html>

Datasheet Reported Capacitance


Dynamic characteristics

Input capacitance	C_{iss}	$V_{GS}=0\text{ V}, V_{DS}=100\text{ V}$	-	790	-	pF
Output capacitance	C_{oss}	$f=1\text{ MHz}$	-	38	-	
Effective output capacitance, energy related ⁶⁾	$C_{o(er)}$	$V_{GS}=0\text{ V}, V_{DS}=0\text{ V}$ to 480 V	-	36	-	
Effective output capacitance, time related ⁷⁾	$C_{o(tr)}$		-	96	-	
Turn-on delay time	$t_{d(on)}$	$V_{DD}=400\text{ V},$ $V_{GS}=10\text{ V}, I_D=5.2\text{ A},$ $R_G=3.3\ \Omega$	-	10	-	ns
Rise time	t_r		-	5	-	
Turn-off delay time	$t_{d(off)}$		-	40	-	
Fall time	t_f		-	5	-	


⁶⁾ $C_{o(er)}$ is a fixed capacitance that gives the same stored energy as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

⁷⁾ $C_{o(tr)}$ is a fixed capacitance that gives the same charging time as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

Example Simulation

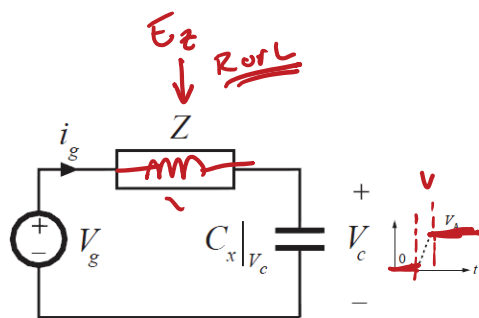

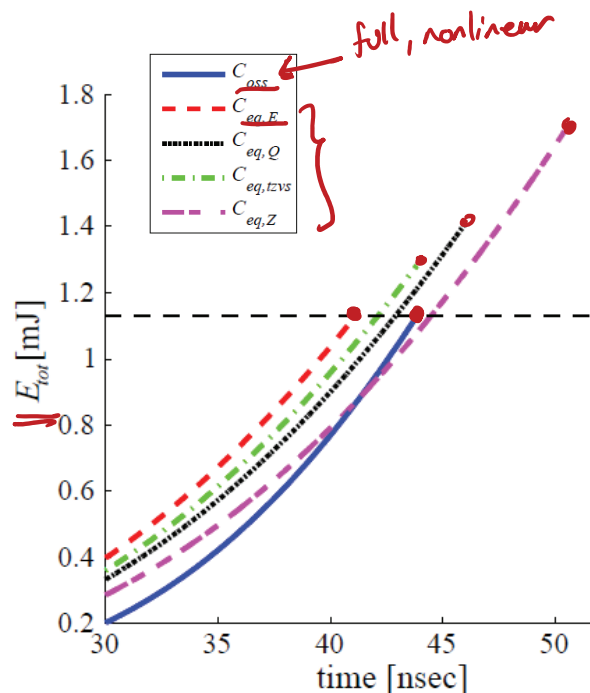$C_{eq,Q} = 70.5\text{ pF}$
 $C_{eq,tzvs} = 64.1\text{ pF}$
 $C_{eq,E} = 56.4\text{ pF}$
 $C_{eq,Z} = 84.5\text{ pF}$



Further Simulation

