

Example Analysis

What is i_{Lpk} ?

$$j_{Lpk} = \frac{i_{Lpk}}{I_{base}} = \frac{i_{Lpk}}{V_{base}/R_0}$$

$$j_{Lpk} = j_{DC} + r$$

$$j_{Lpk} = j_{DC} + \sqrt{(M_{DC} - M_0)^2 + (j_{DC} - j_0)^2}$$


$$i_{Lpk} = \frac{V_{base}}{R_0} \left(j_{DC} + \sqrt{(M_{DC} - M_0)^2 + (j_{DC} - j_0)^2} \right)$$

When (t) does i_{Lpk} occur? (first)

$$\theta_{pk} = \omega_0 t_{pk}$$

$$\theta_{pk} = \frac{\pi}{2} + \phi = \frac{\pi}{2} + \tan^{-1} \left(\frac{j_{DC} - j_0}{M_{DC} - M_0} \right)$$
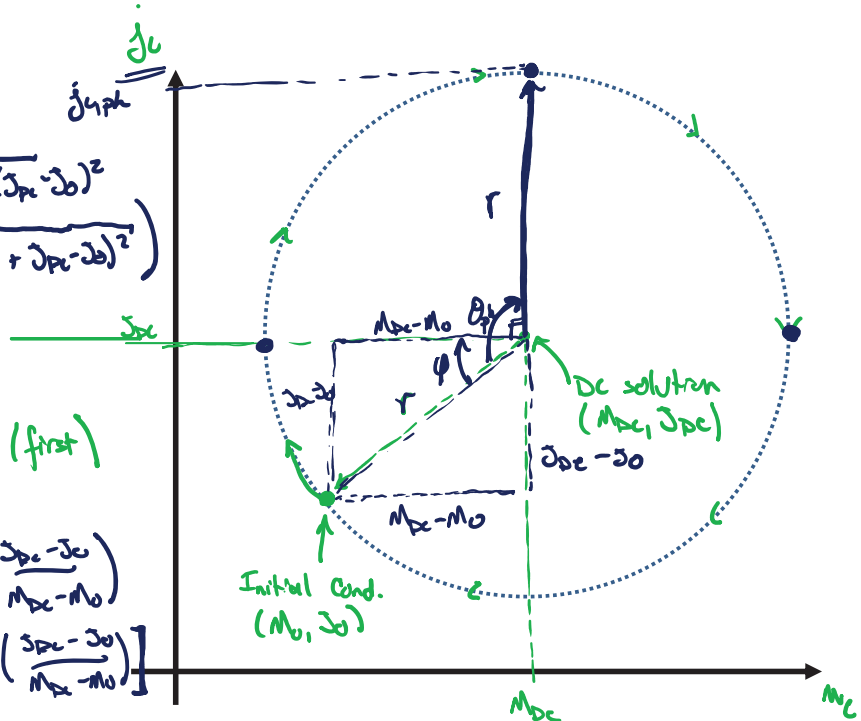
$$t_{pk} = \frac{\theta_{pk}}{\omega_0} = \frac{1}{\omega_0} \left[\frac{\pi}{2} + \tan^{-1} \left(\frac{j_{DC} - j_0}{M_{DC} - M_0} \right) \right]$$



State Plane Algorithm

Manipulate circuit into ac equivalent w/ 1L, 1C & (possibly) DC sources, only.
- May require some approximation

(1) Normalize waveforms & time

V_{base} = anything, you choose

$$I_{base} = \frac{V_{base}}{R_0}$$

$$M_x(t) = \frac{V_x(t)}{V_{base}}$$

$$j_x(t) = \frac{i_x(t)}{I_{base}}$$

$$\theta_x = \omega_0 t_x$$


(2) Plot trajectory on the $M_L - j_L$ axes

Form a circle


- center at (M_{DC}, j_{DC}) → the DC solution
- point on circle at (M_0, j_0) → initial condition
- Direction of state plane comes from i.e. on first derivative

(3) Solve parameters of interest on state plane

(4) Denormalize

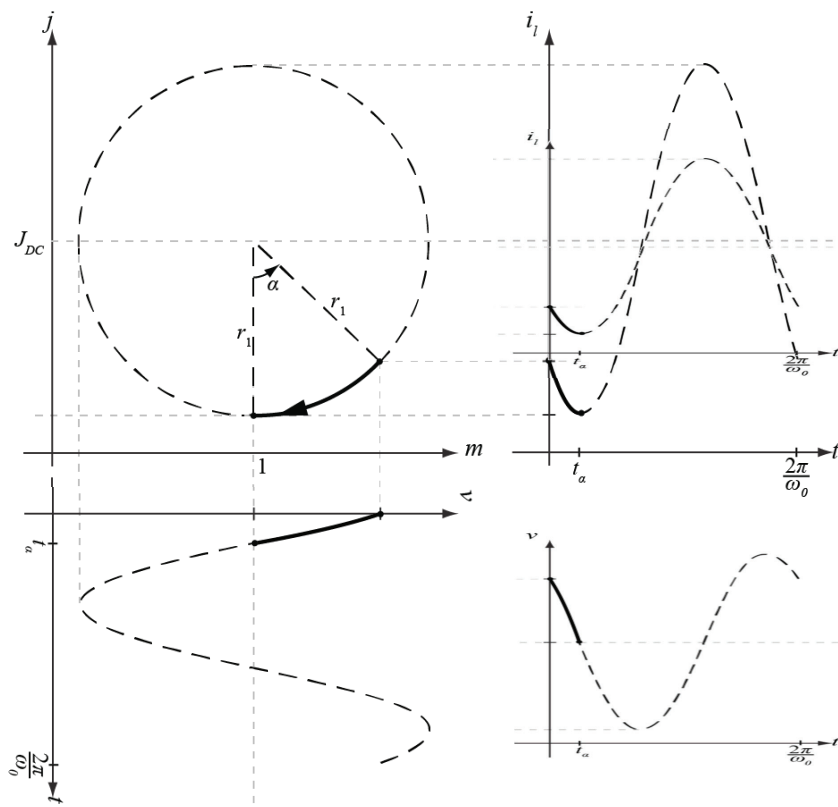

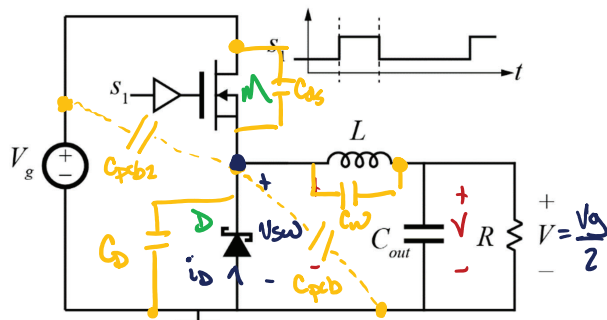DCM Buck Converter Example ($M=1/2$) = $\frac{V}{V_g}$



when both M & D off, ac equivalent:



$C_{sw} = C_{gs} || C_{gd} || C_{oss} || C_{sw}$...

← not unique

DC solution

$$\begin{aligned} V_{sw} &= V \\ i_L &= \phi \end{aligned}$$

Initial Conditions

$$\begin{aligned} @ t = \phi \quad \left\{ \begin{aligned} V_{sw} &= \phi \\ i_L &= \phi \\ \frac{dV_{sw}}{dt} &= \phi \\ \frac{di_L}{dt} &= -\frac{V}{L} \end{aligned} \right.$$

