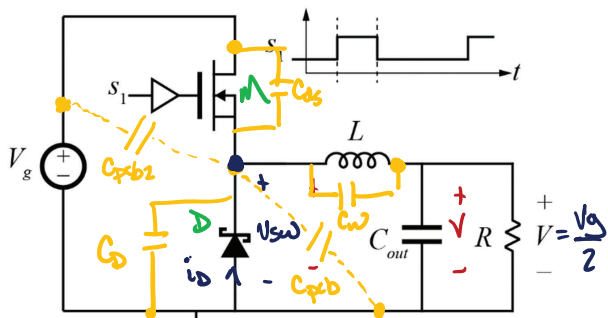


DCM Buck Converter Example ($M=1/2$) = $\frac{V}{V_g}$



when both \bar{M} & D off, ac equivalent:


$$C_{\omega} = C_{\omega_1} \parallel C_{\omega_2} \parallel C_{\omega_3} \dots$$

← not unique

DC solution

$$V_{k,s} = V$$
 $i = 6$

Initial Conditions
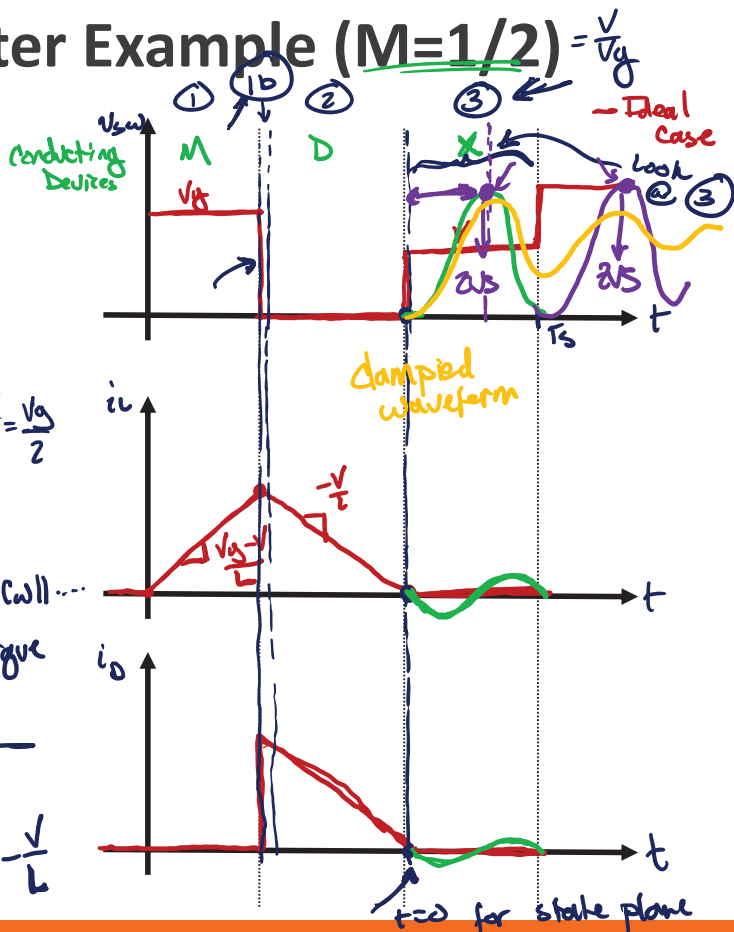
$$\textcircled{a} \quad \left\{ \begin{array}{l} N_{sw} = \phi \\ i_L = \phi \\ \frac{dN_{sw}}{dt} = \phi \end{array} \right.$$
$$N_{\omega} = \emptyset$$
$$i_L = \emptyset$$
$$\frac{dI_{SW}}{dt} = 0 \quad \frac{dI_C}{dt} = -\frac{V}{L}$$


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



DCM Buck State Plane $V_{base} = V_g$ $I_{base} = \frac{V_g}{R_o}$

DC solution → center

$$N_{\text{wo}} = \sqrt{\quad} \rightarrow n_c = \frac{\sqrt{\quad}}{\Delta} = N \quad (\text{ratio})$$
$$i_L = \phi \rightarrow j_L = \phi$$

Initial conditions \rightarrow starting point

$$V_{SO} = 0 \rightarrow \pi_c = 0$$
$$i_L = 0 \rightarrow j_L = 0$$


$\frac{d}{dt}$ Initial values \rightarrow direction
done!

$$\left. \frac{dN_{\text{sw}}}{dt} \right|_{t=0} = 0 \quad \rightarrow \quad \left. \frac{dN_{\text{sw}}}{dt} \right|_{t=\infty} = 0$$
$$\left. \frac{dj_c}{dt} \right|_{t=0} = \frac{-V}{L} \rightarrow \left. \frac{dj_c}{dt} \right|_{t=0} < 0$$

zvs switching times:

$$t = (\pi + n2\pi) \frac{1}{\omega_0}$$


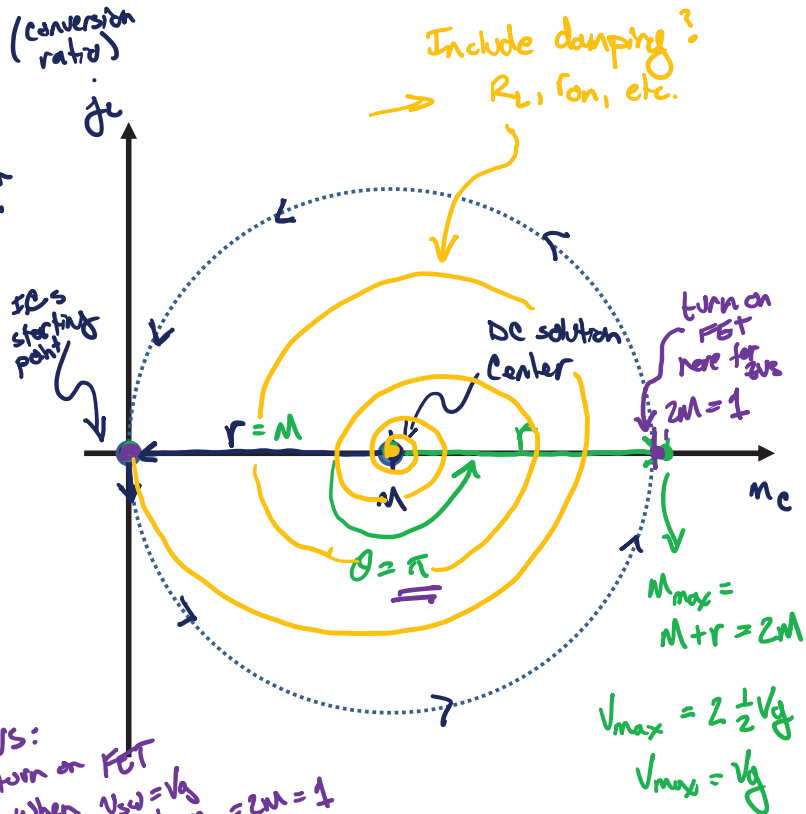
2Vs:
turn on FET
when $V_{sw} = V_g$
 $\hookrightarrow m_c = 2m = 1$



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



DCM Buck $M \neq 1/2$

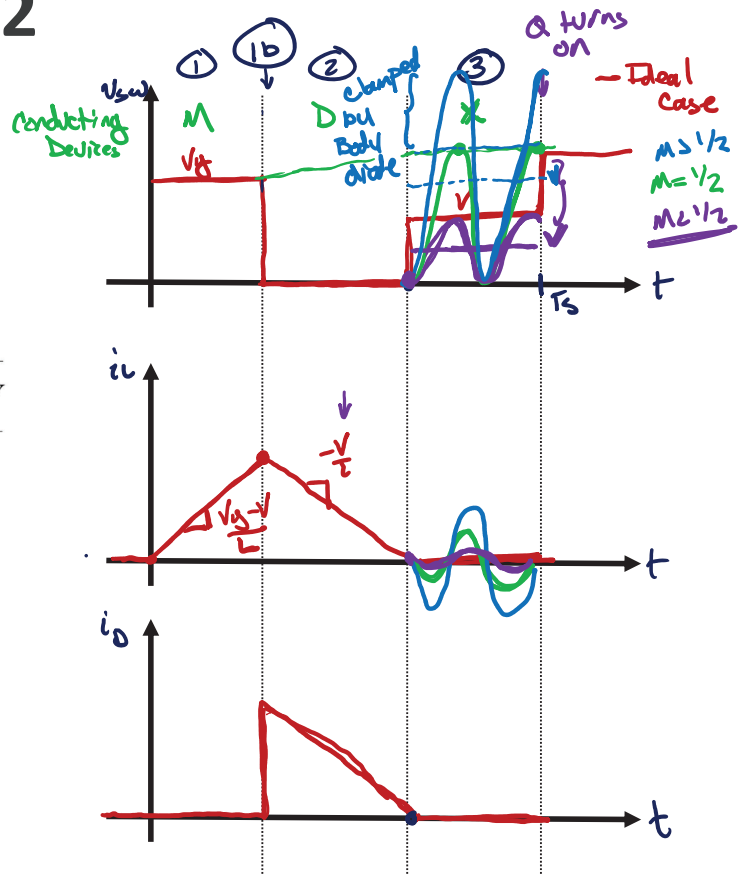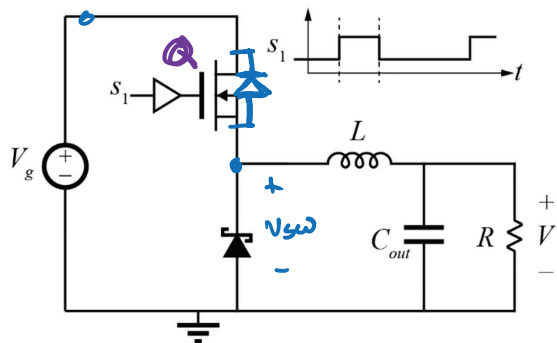

DCM Buck State Plane ($M < 1/2$)


I.C.'s still zero
DC op point & Initial values of $\frac{d}{dt}$ expressions unchanged

ZVS condition:

$$M_{max} = M + r = 2M \geq 1$$

$$M \geq \frac{1}{2}$$

$$V \geq \frac{V_g}{2}$$

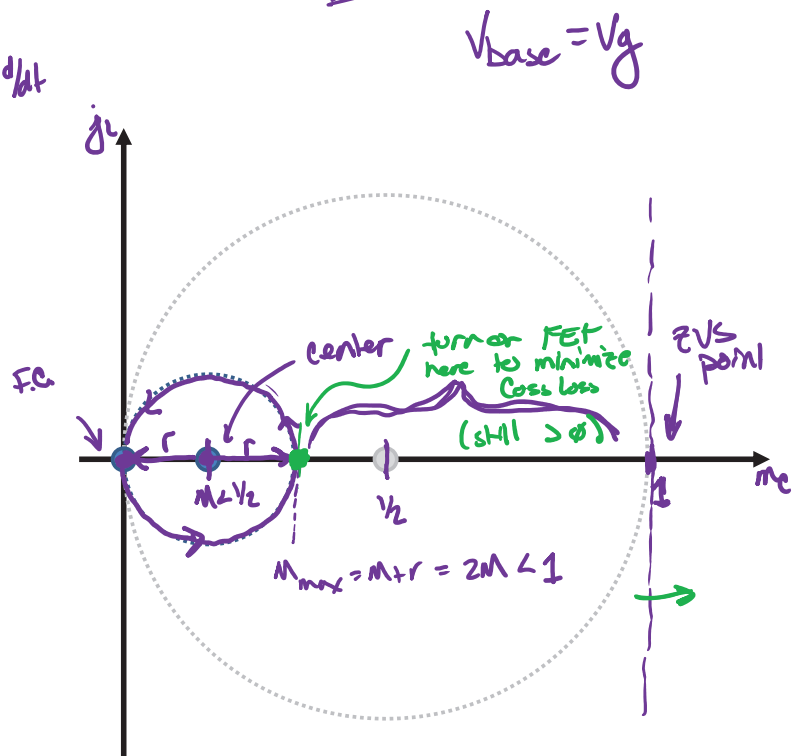

DCM Buck State Plane ($M > 1/2$)

③

