
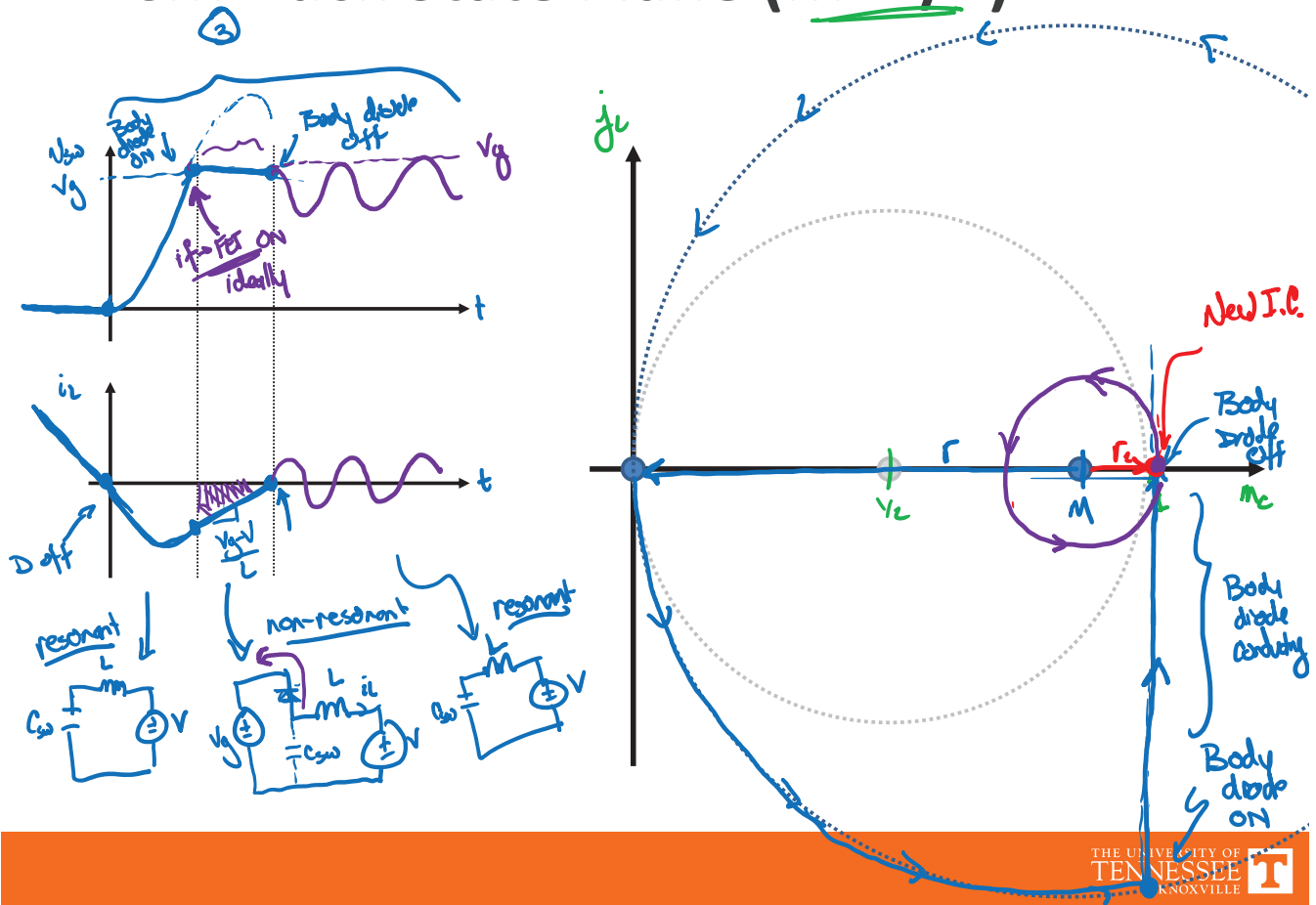


DCM Buck State Plane ($M > 1/2$)

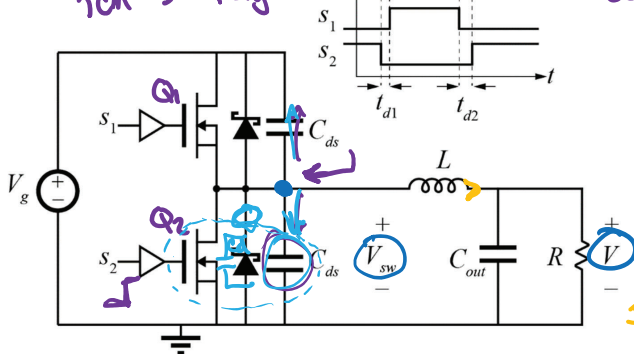


Synchronous Buck Converter

2V_{sw} Buck converter
CRM → Critical Cond. mode
BCM → Boundary " "
TCM → Triangular " "




② & ④ equivalent ac circuit:

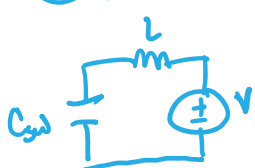


DC: $v_{sw} = V$, $i_L = 0$
 $m_L = M$, $j_L = 0$
w/ $V_{base} = V_g$

IC: vary by interval

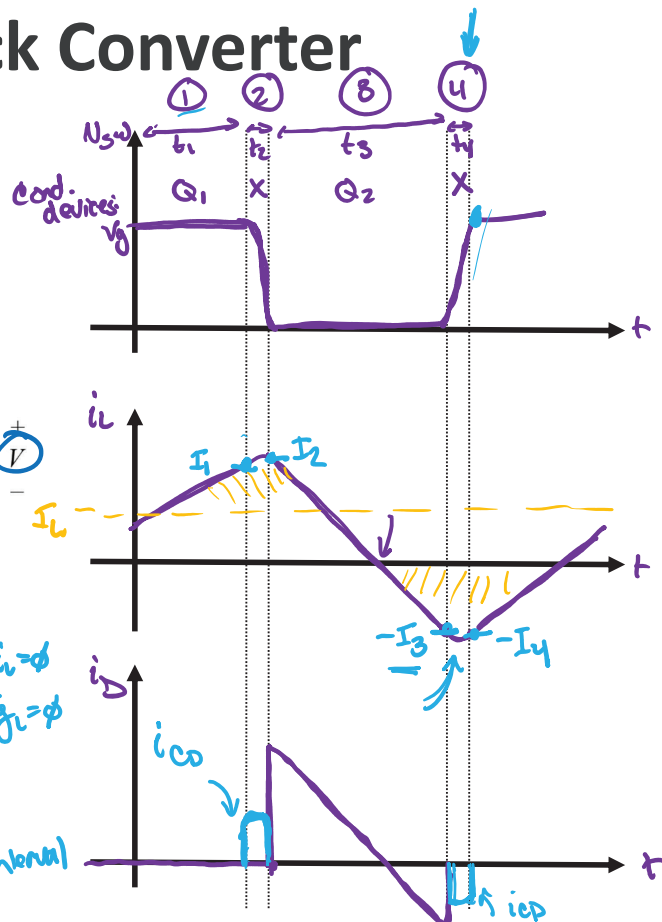

During ④

$$j_2 = -j_3, \quad m_c = \phi$$

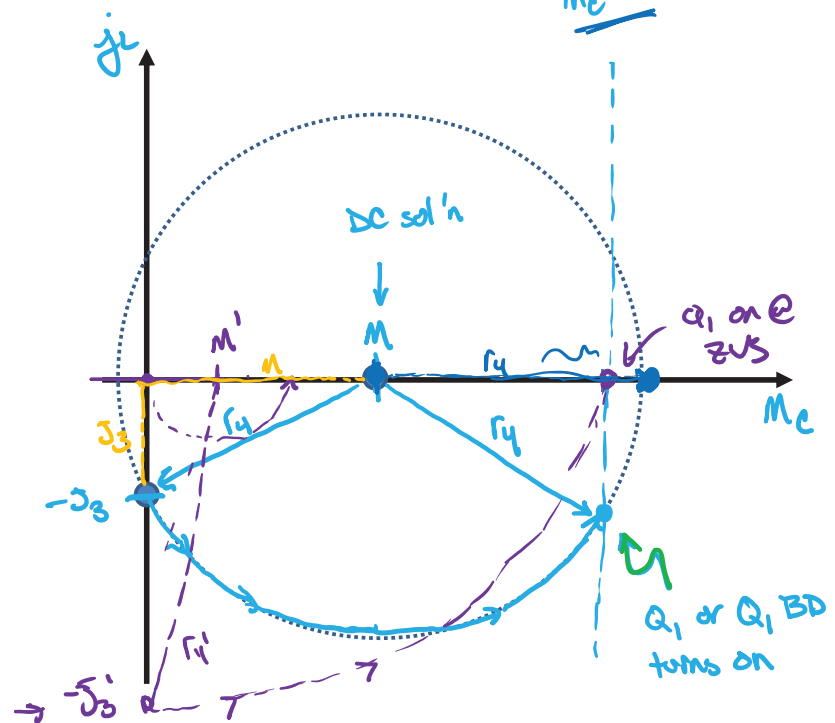

for ZVS turn-on of Q_1 .

$$r_y = \sqrt{M^2 + J^2}$$

$$m + \sqrt{m^2 + j_3^2} \geq 1 \quad \leftarrow$$

$$\frac{v}{v_g} + \sqrt{\left(\frac{v}{v_g}\right)^2 + \left(\frac{I_3}{v_g R_0}\right)^2} \geq 1$$

$$v^2 + \frac{I_3^2 L}{C_{sw}} \geq (v_g - v)^2, \quad R_0 = \sqrt{\frac{L}{C_{sw}}}$$


$$C_{sw}V^2 + LI_3^2 \geq C_{sw}(V_g - V)^2$$

$$\frac{1}{2} L I_3^2 \geq \frac{1}{2} C_{sw} (V_g - V)^2 - \frac{1}{2} C_{sw} V^2$$

↖ initial energy

Sync-Buck State Plane (Ring out)

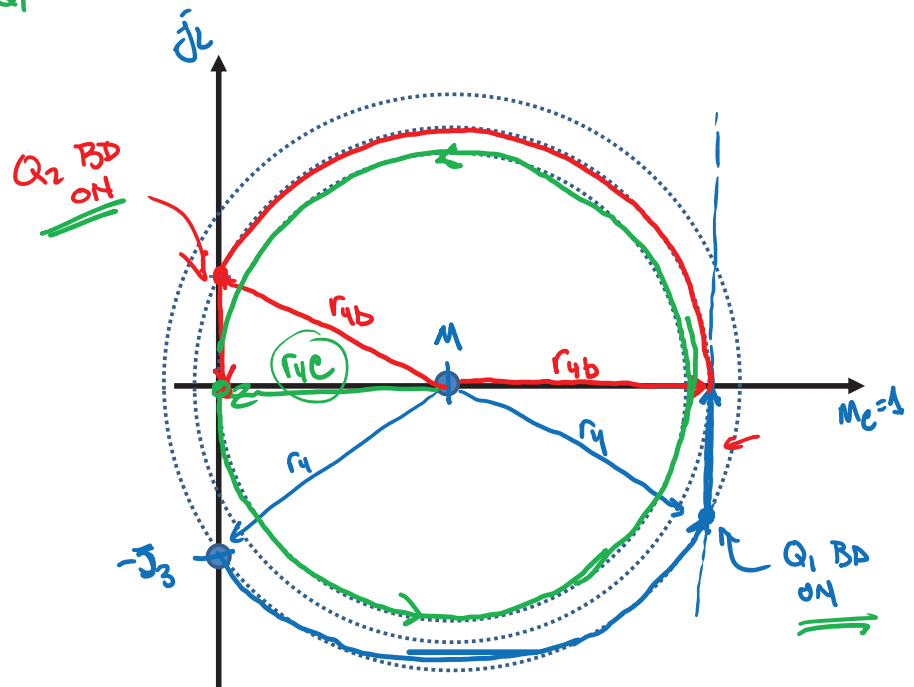If we never turn Q_1 on after interval (4)



Sync-Buck Complete State Plane

②: $I_c: i_L = I_1 \quad N_{sw} = V_g$
 $j_L = J_1 \quad m_c = 1$

