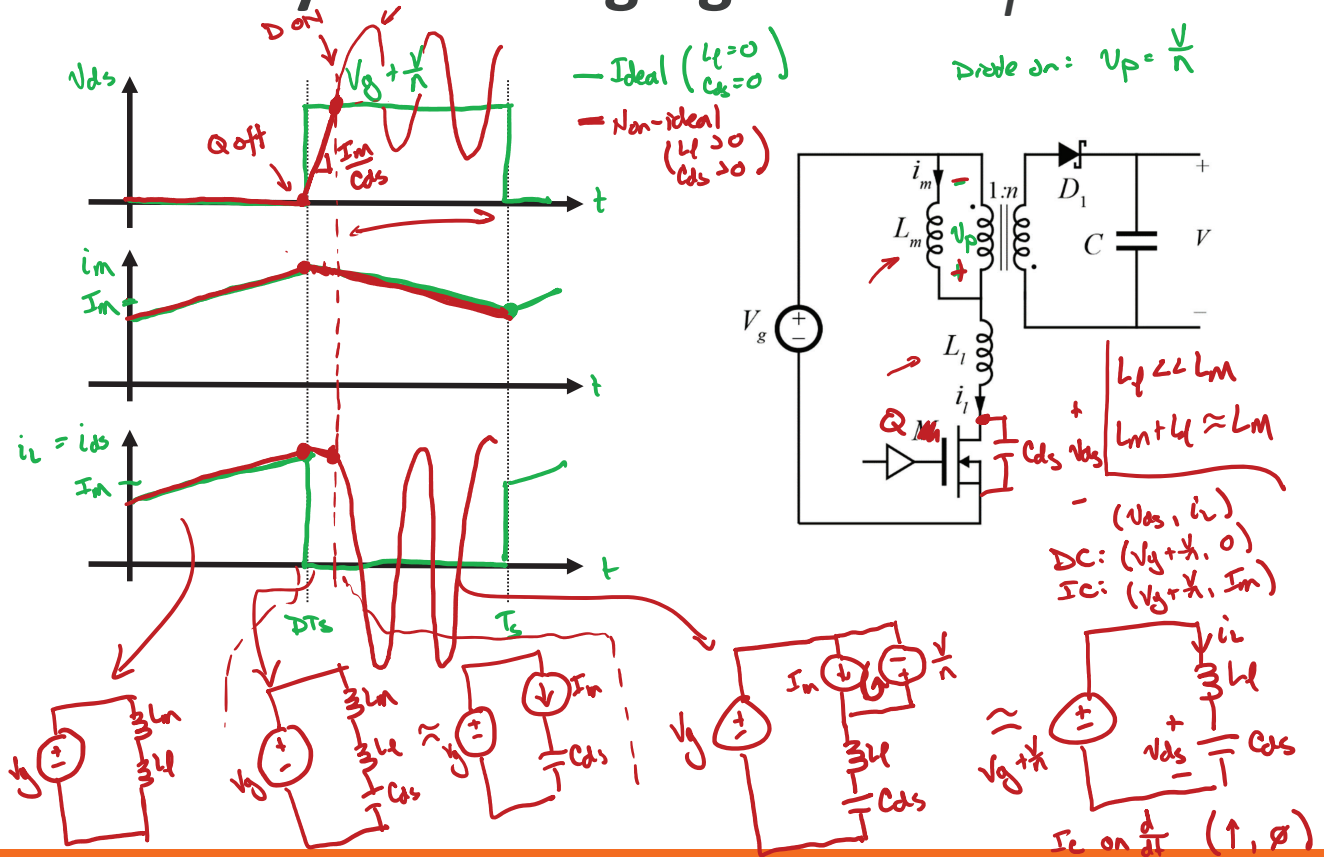



CCM Flyback: Ringing Due to L_l



MOSFET Turn-off

$$V_{base} = V_g + \frac{V}{N}, \quad I_{base} = \frac{V_{base}}{R_o}$$

$$R_o = \sqrt{\frac{L_l}{C_{ds}}}$$

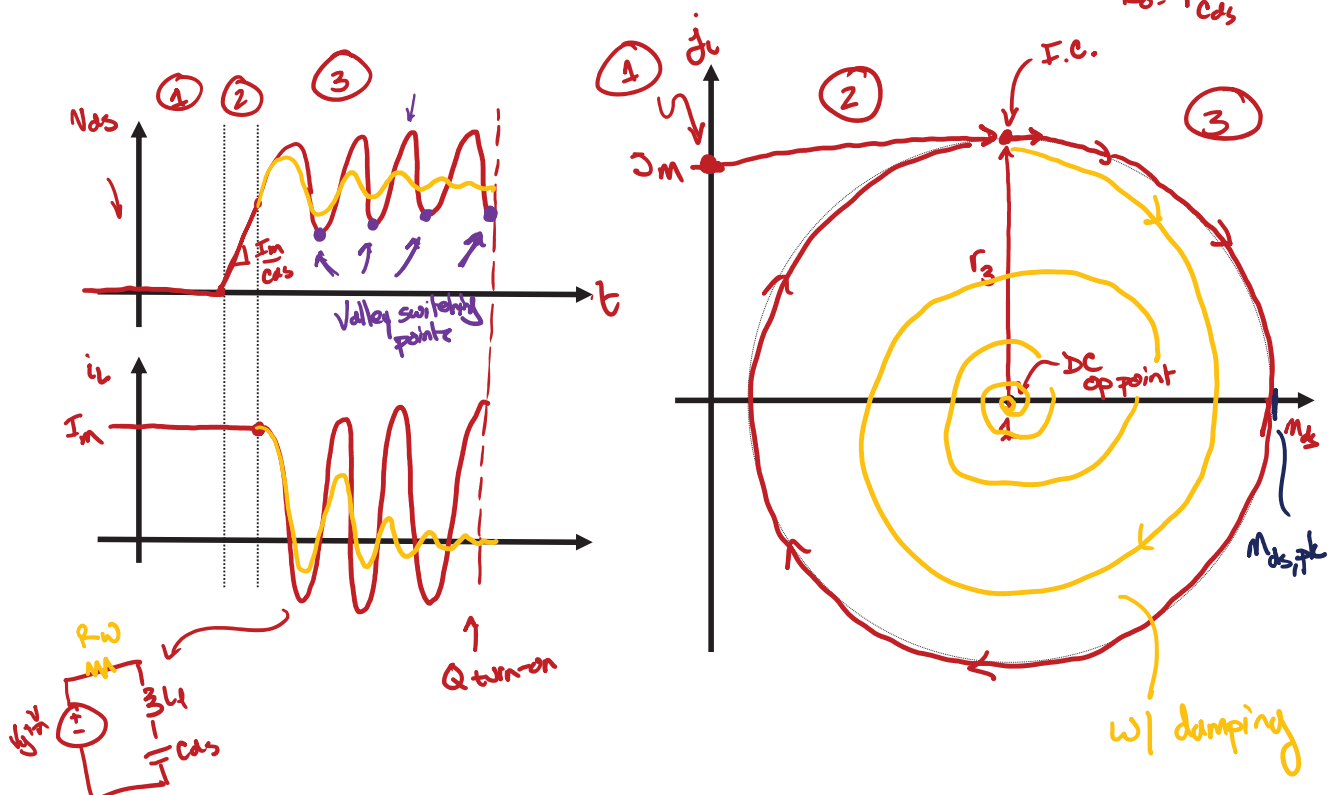

Leakage Voltage Stress

$$M_{ds,ph} = 1 + r_3 = 1 + J_m$$

$$V_{ds,ph} = V_g + \frac{V}{n} + I_m R_o$$

$$J_m = \frac{I_m}{V_g + V_h} R_o$$

example design:

$$V_g = 400V$$

$$V = 10V$$

$$P = 100W$$

$$f_s = 1MHz$$

$$n = \frac{1}{40}, D = 0.5$$

$$C_{ds} = 100pF$$

$$L_m = 1.5mH$$

$$L_l = 35\mu H$$

(2% of L_m)

$$R_o = \sqrt{\frac{L_l}{C_{ds}}} = 600\Omega$$

$$I_m = \frac{1I_{out}}{D'} = 500mA$$

$$V_{base} = V_g + \frac{V}{n} = 800V$$

$$V_{ds,ph} = 800V + (0.5A)(600\Omega)$$

$$= \underline{\underline{1.1kV!}}$$

Leakage Switching Loss

For the fully damped case (i.e. ringing dies out before Q turns on)

From state plane:

$$E_{start} = \frac{1}{2} C_{ds} (V_g + \frac{V}{n})^2 + \frac{1}{2} L_l I_m^2$$

$$E_{end} = \frac{1}{2} C_{ds} (V_g + \frac{V}{n})^2$$



$$\rightarrow E_{loss} = \frac{1}{2} L_l I_m^2$$

Note: be careful \rightarrow where did the energy go?

$$E_{loss} = 4.4\mu J$$

$$\rightarrow P_{loss} = E_{loss} f_s = \underline{\underline{4.4W}}$$

CCM Flyback: Clamping Circuit

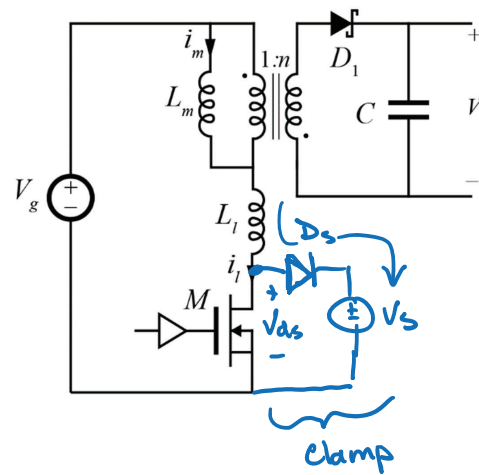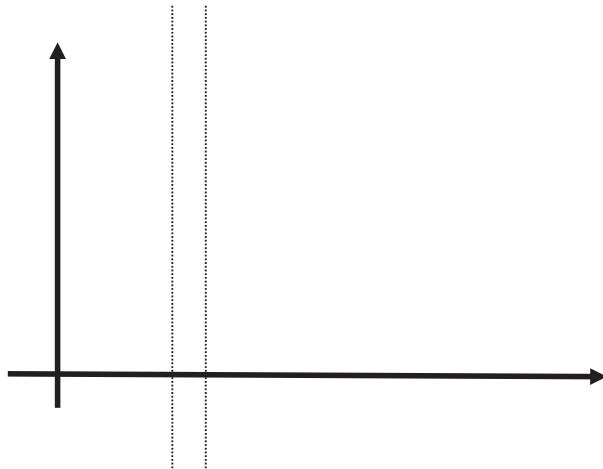

$$V_g + \frac{V}{n} \leq V_s \leq V_{s,ph} \quad (\text{from unclamped case})$$

Clamped State Plane

