
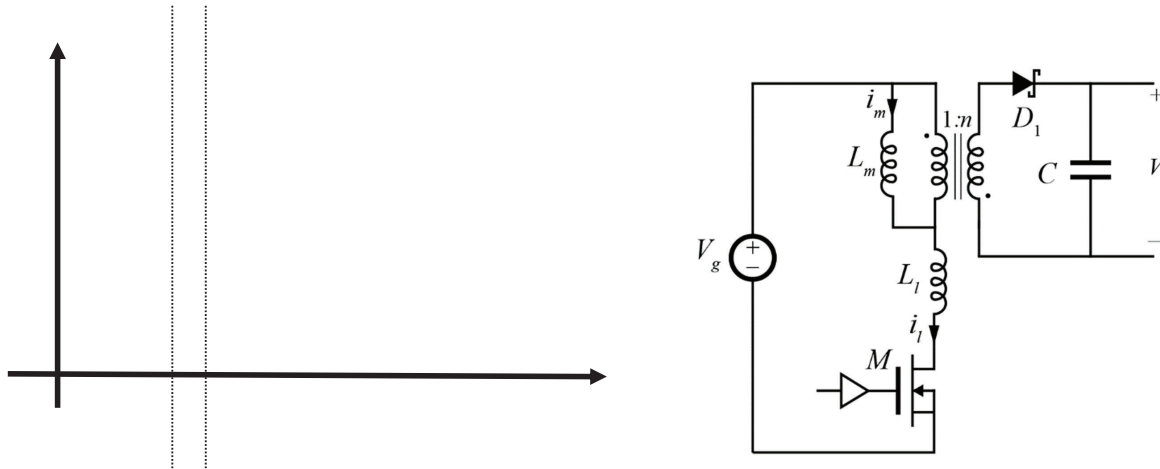


## CCM Flyback: Ringing Due to $L_f$

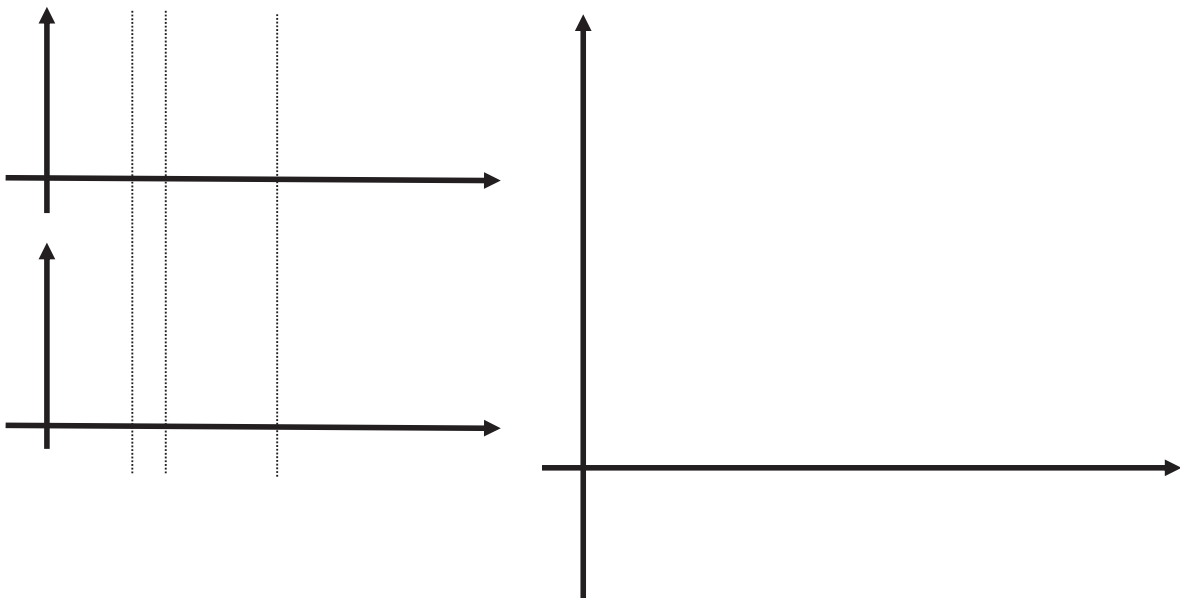



# MOSFET Turn-off





# Leakage Voltage Stress

# Leakage Switching Loss

# CCM Flyback: Clamping Circuit

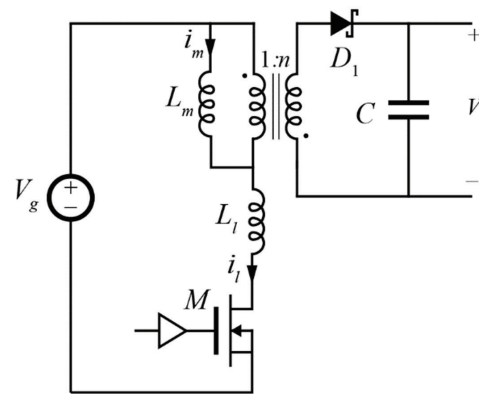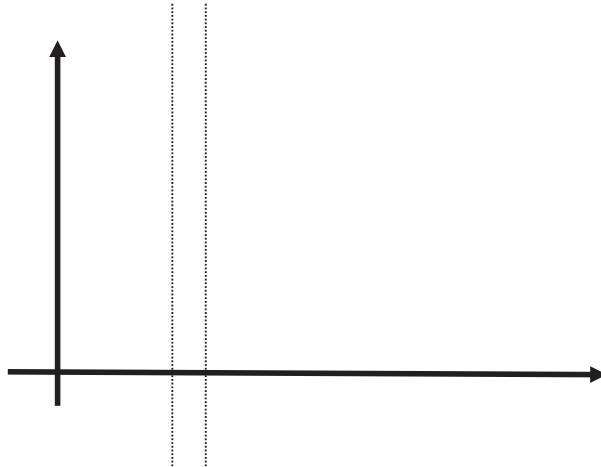

## Clamped State Plane

 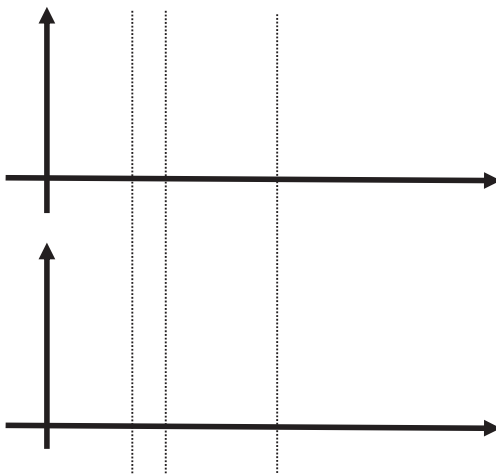

# Loss Comparison

## Snubber Implementations

