

Analysis: Intervals 1-3

$$\textcircled{1} \quad \text{Nothing yet.} \rightarrow T_S = \sum_{i=1}^6 t_i \rightarrow \boxed{\frac{2\pi}{F} = \theta_1 + \theta_2 + \theta_3 + \theta_4 + \theta_5 + \theta_6}$$

$$\textcircled{2} \quad \left(\frac{1}{R_0 C_{ds}}\right) \frac{I_m}{C_{ds}} t_2 = V_g + \frac{V}{n} \left(\frac{1}{I_{base}}\right)$$

$$J_m \frac{1}{R_0 C_{ds}} t_2 = \frac{V_g + \frac{V}{n}}{V_{base}} = 1$$

$$\boxed{J_m \theta_2 = 1}$$

$$\frac{1}{R_0 C_{ds}} = \sqrt{\frac{C_{ds}}{T_0}} \frac{1}{C_{ds}} = \frac{1}{T_0 C_{ds}} = \omega_b$$

$$\textcircled{3} \quad \left. \begin{array}{l} r_2^2 = J_m^2 \\ r_3^2 = J_3^2 + (m_s - 1)^2 \end{array} \right\} \quad \boxed{J_m^2 = J_3^2 + (m_s - 1)^2}$$

$$\boxed{\theta_3 = \tan^{-1} \left(\frac{m_s - 1}{J_3} \right)}$$



Analysis: Intervals 4-6

$$\textcircled{4} \quad \left(\frac{V_g + \frac{V}{n} - V_s}{L_f} \right) t_4 = I_3 + I_4$$

$$\boxed{-(1-m_s) \theta_4 = J_3 + J_4}$$

$$\textcircled{5} \quad \left. \begin{array}{l} (m_s - 1)^2 + J_4^2 = 1 + J_5^2 \\ \theta_4 = \pi - \tan^{-1} \left(\frac{J_5}{1} \right) - \tan^{-1} \left(\frac{J_4}{m_s - 1} \right) \end{array} \right\} \quad \text{from } r_5^2 = r_5^2$$

$$\textcircled{6} \quad \left(\frac{V_g + \frac{V}{n}}{L_f} \right) t_6 = I_5 + I_M$$

$$\boxed{(1) \theta_6 = J_5 + J_M}$$



Analysis: Averaging

Get one additional equation from applying averaging to every filter element.

$$C_S \rightarrow \text{Cap-Q balance}$$

$$\langle i_{CS} \rangle_{T_S} = \phi$$

$$I_3 = I_4$$

$$J_2 = J_4$$


$$L_m \rightarrow \text{volt-sec balance}$$

$$\langle V_m \rangle_{T_S} = \phi$$

$$\langle V_m \rangle_{T_S} = \frac{1}{T_S} \int_0^{T_S} V_m(t) dt$$

$$\phi = \frac{1}{T_S} \left[V_g t_1 + t_2 \frac{V_g - \frac{V}{n}}{2} + -\frac{V}{n} (t_3 + t_4 + t_5 + t_6) \right]$$
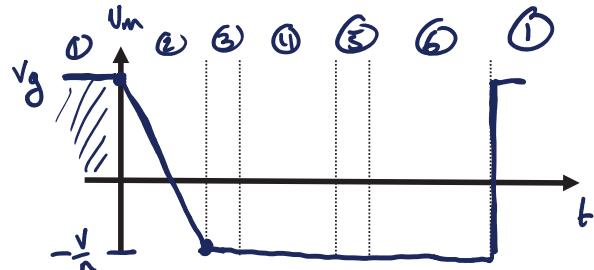
$$V_g(t_1 + \frac{t_2}{2}) = \frac{V}{n} \left(\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6 \right) \rightarrow \boxed{\frac{V_g}{V_g} = M = n \frac{\frac{t_1 + \frac{t_2}{2}}{T_S}}{\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6} \approx n \frac{D}{D}}$$



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Average Output Current

$$\text{Output cap } C \rightarrow \text{cap-Q balance}$$

$$\langle i_{cS} \rangle_{T_S} = \phi = \langle i_{p1} - i_{out} \rangle_{T_S}$$

$$\langle i_{out} \rangle_{T_S} = \langle i_{p1} \rangle_{T_S} = \frac{1}{T_S} \int_0^{T_S} (I_m - i_L) \frac{1}{n} dt$$

$$n I_{out} = \frac{1}{T_S} \int_0^{T_S} I_m - i_L dt$$


$$= \frac{1}{T_S} [g_1 + g_2 + g_3 + g_4 + g_5 + g_6]$$

$$g_3 = I_m t_3 - C_{ds} \left(V_S - V_g - \frac{V}{n} \right)$$

$$g_4 = t_4 \left(\frac{(I_m - I_S) + (I_m + I_u)}{2} \right) = I_m t_4$$

$$g_5 = I_m t_5 + C_{ds} V_S$$

$$g_6 = t_6 \frac{I_m + I_S}{2}$$

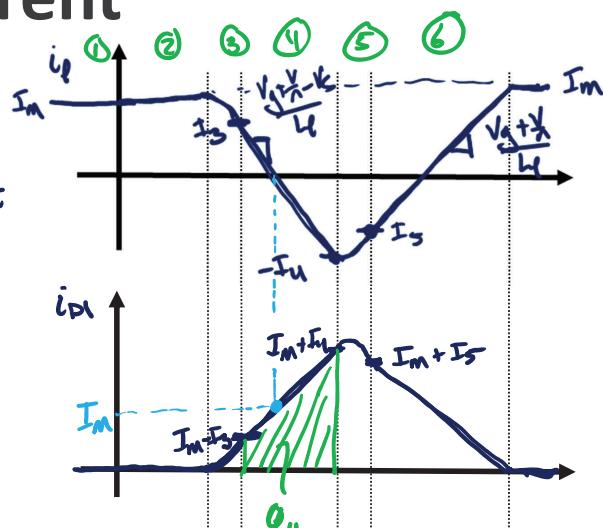

$$\frac{n I_{out}}{I_{base}} = n J_{out} = \frac{1}{T_S} \left[J_m t_3 + 1 C_{ds} R + J_m t_4 + J_m t_5 + \frac{J_m + J_S}{2} t_6 \right]$$

$$J_{out} = \frac{F}{2\pi} \left[J_m \left(\delta + \theta_4 + \epsilon + \frac{\theta_6}{2} \right) + J_S \frac{\theta_6}{2} + 1 \right]$$

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE