

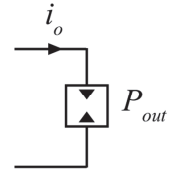
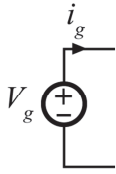



Introduction to AC-link topologies

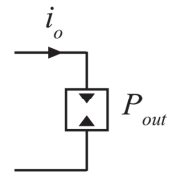


DC-Transformer (DCX)

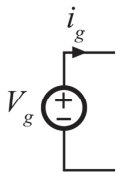


Dual Active Bridge

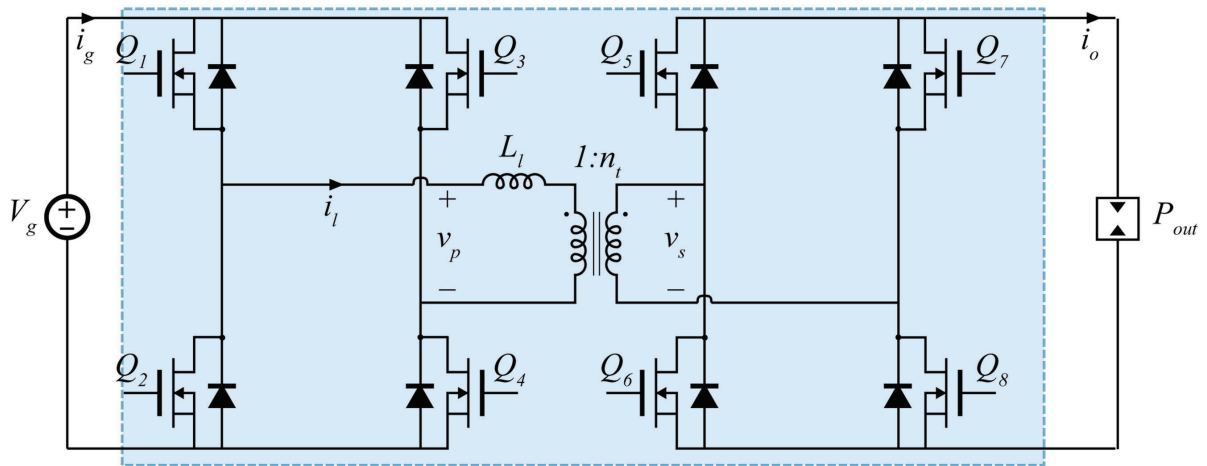


Switching Behavior (PSM)

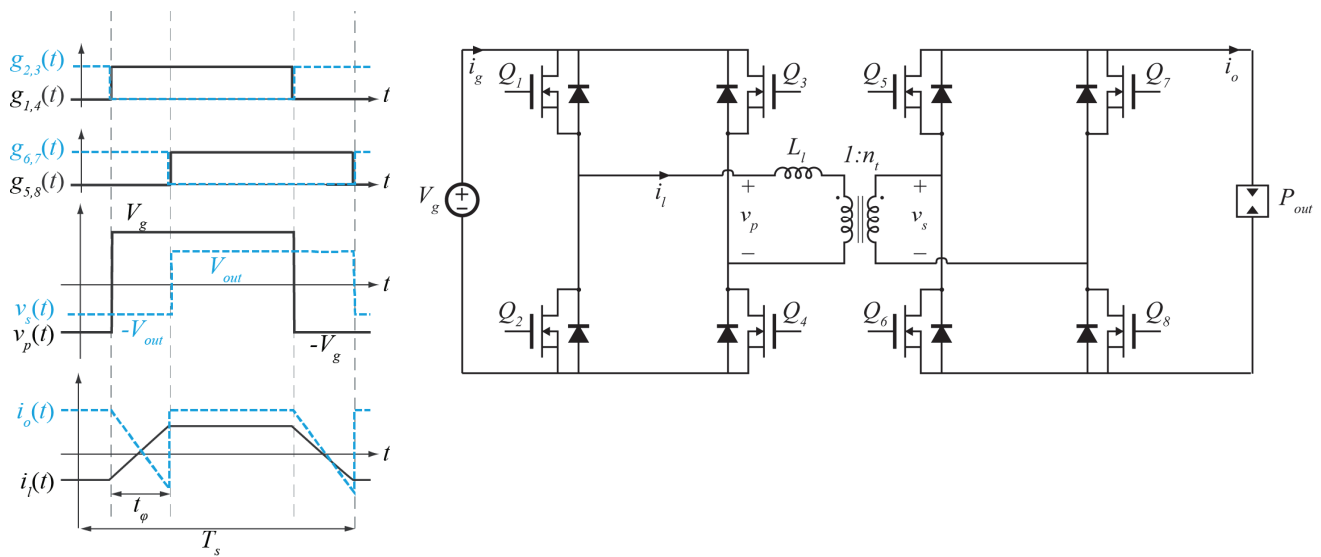

DAB Operation Analysis

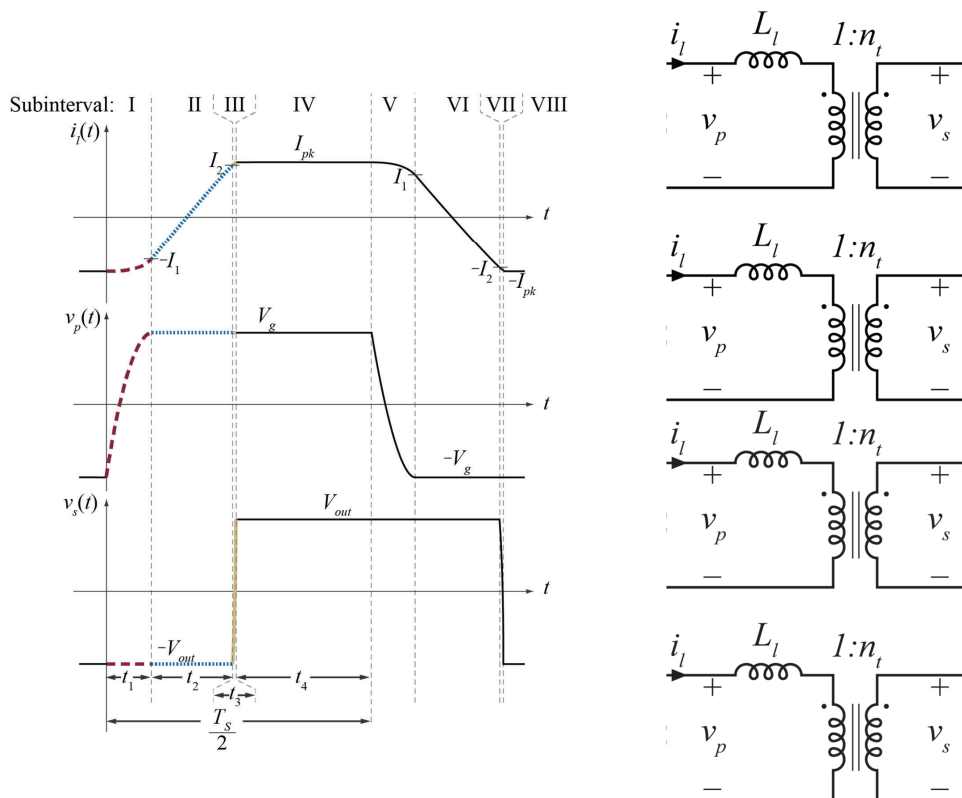

DAB State Plane

 

ZVS Condition