

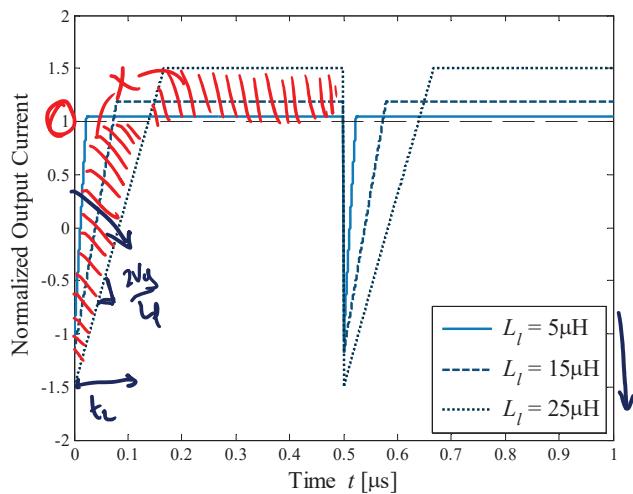



# Output Current Vs. Inductance

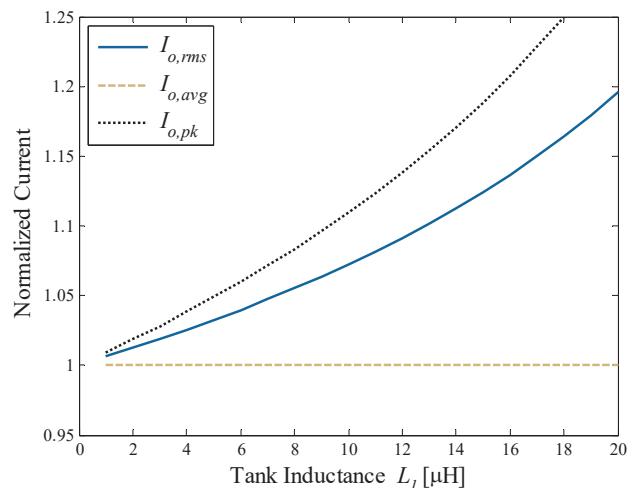

# Output Current Vs. Inductance




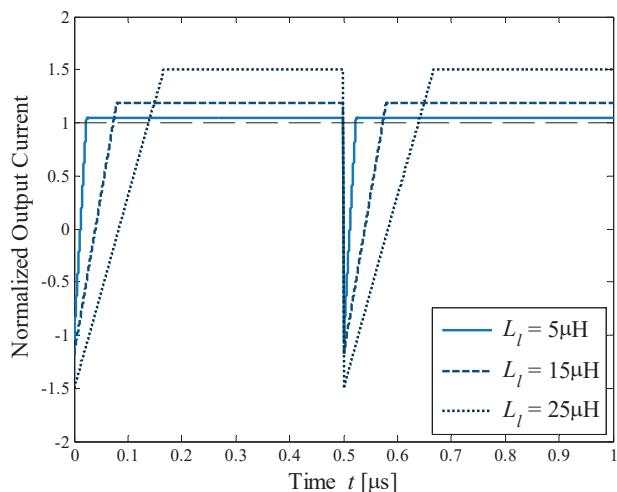


# Constraints on Inductance


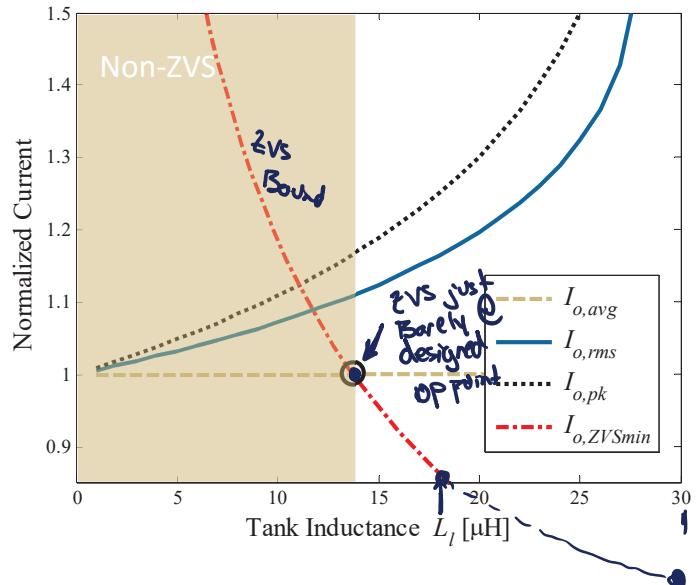


## DAB: Experimental Results

ISO-to-12V, now DAB  
@ 1MHz

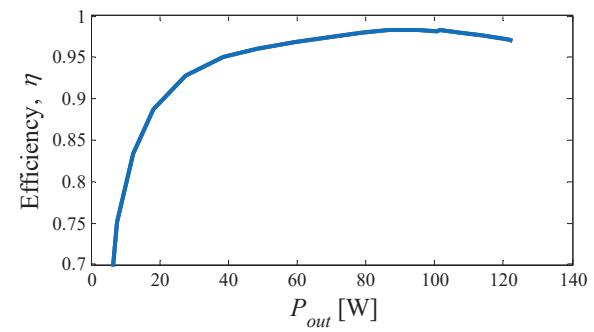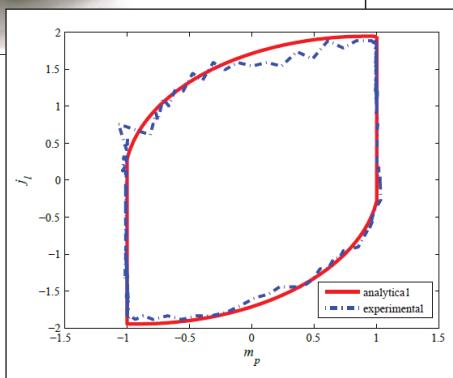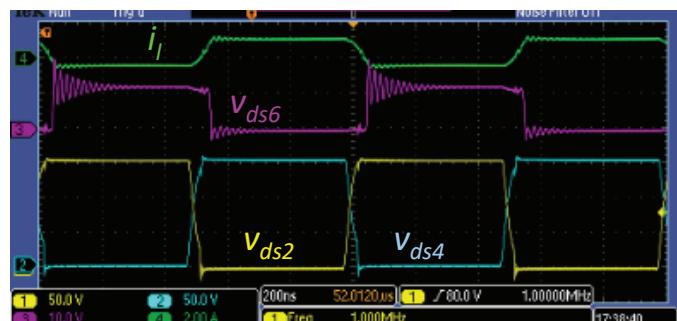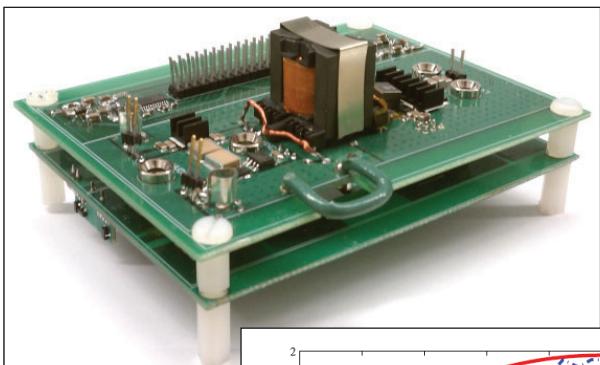


# Operation with $V \neq nV_g$

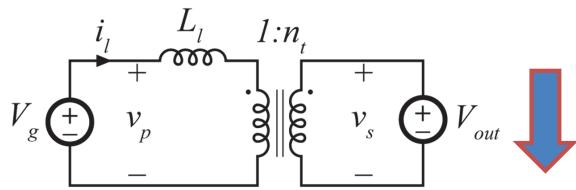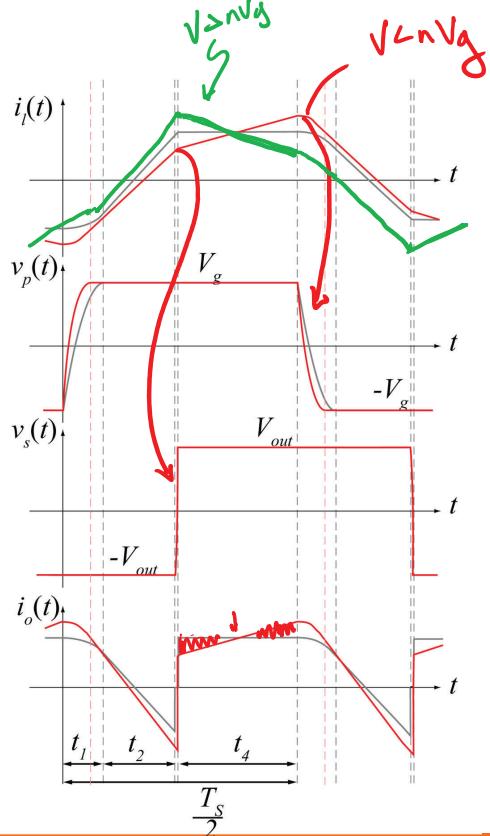

- E.g. Decrease to  $\frac{V}{nV_g} = M_N < 1$  by decreasing output voltage
- Current now ramping, causing more energy available for primary ZVS, but higher RMS currents
- Can use behavior to extend ZVS range of one bridge

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE
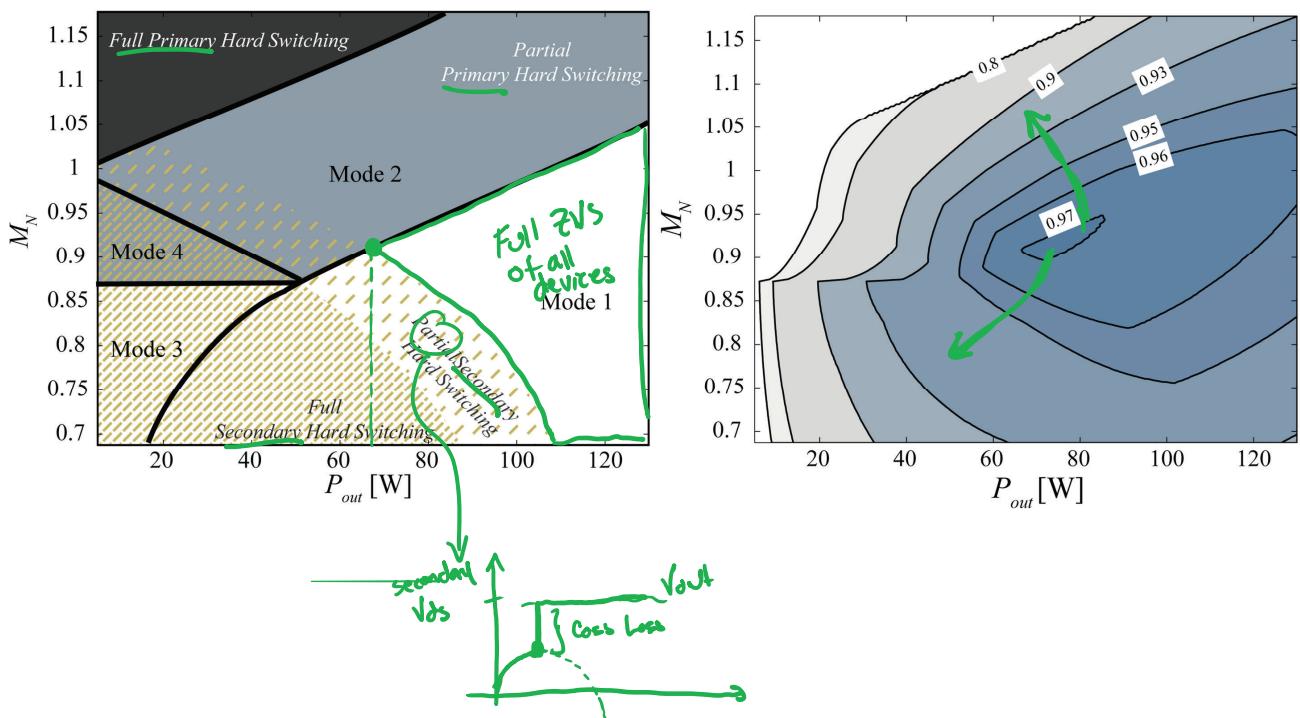
## Soft Switching Range with Varying $V_{out}$



# Application Example: Automotive

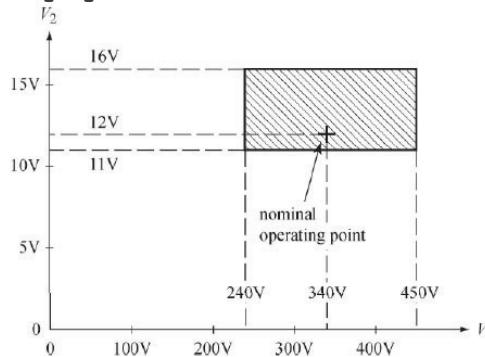


Fig. 1. Converter operating voltage ranges required for automotive application.

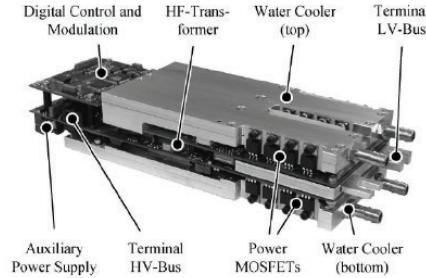


Fig. 3. Automotive DAB converter ( $273 \times 90 \times 53$  mm).


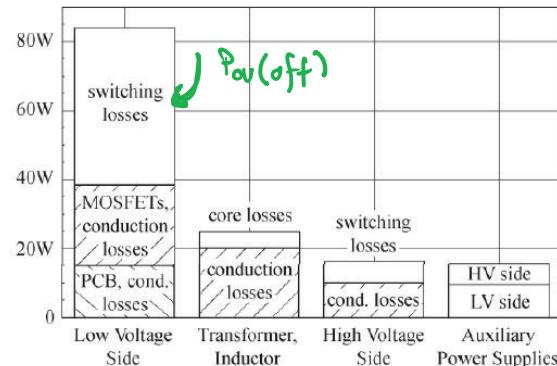
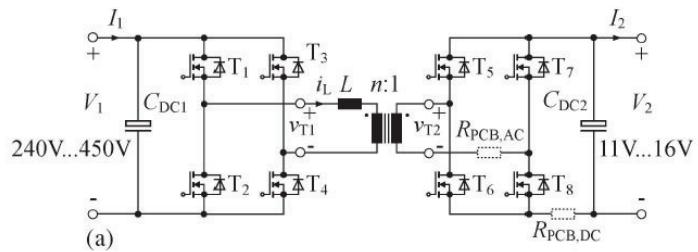


Fig. 13. Calculated distribution of the power losses for operation at  $V_1 = 340$  V,  $V_2 = 12$  V, and  $P_2 = 2$  kW.


\*F. Krismer, J.W.Kolar, "Accurate Power Loss Model Derivation of a High-Current Dual Active Bridge Converter for an Automotive Application, IEEE Trans. On Industrial Electronics, March 2010

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE


## Alternate Modulation Schemes

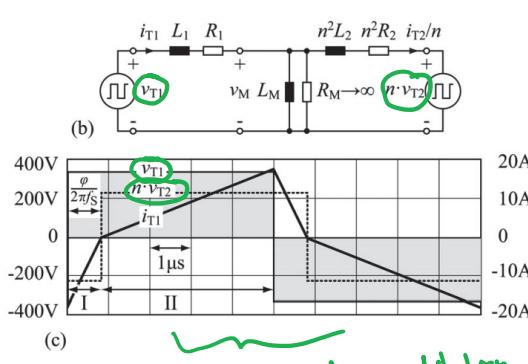

Phase shift modulation

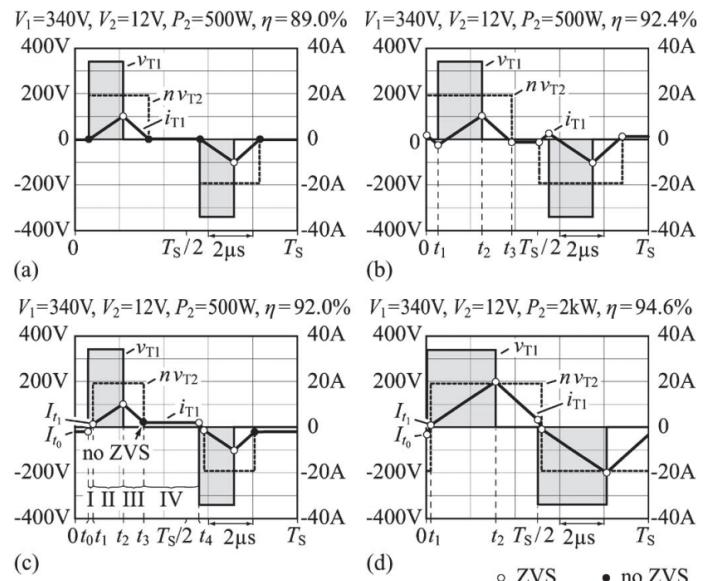



# DAB: Transformer Saturation

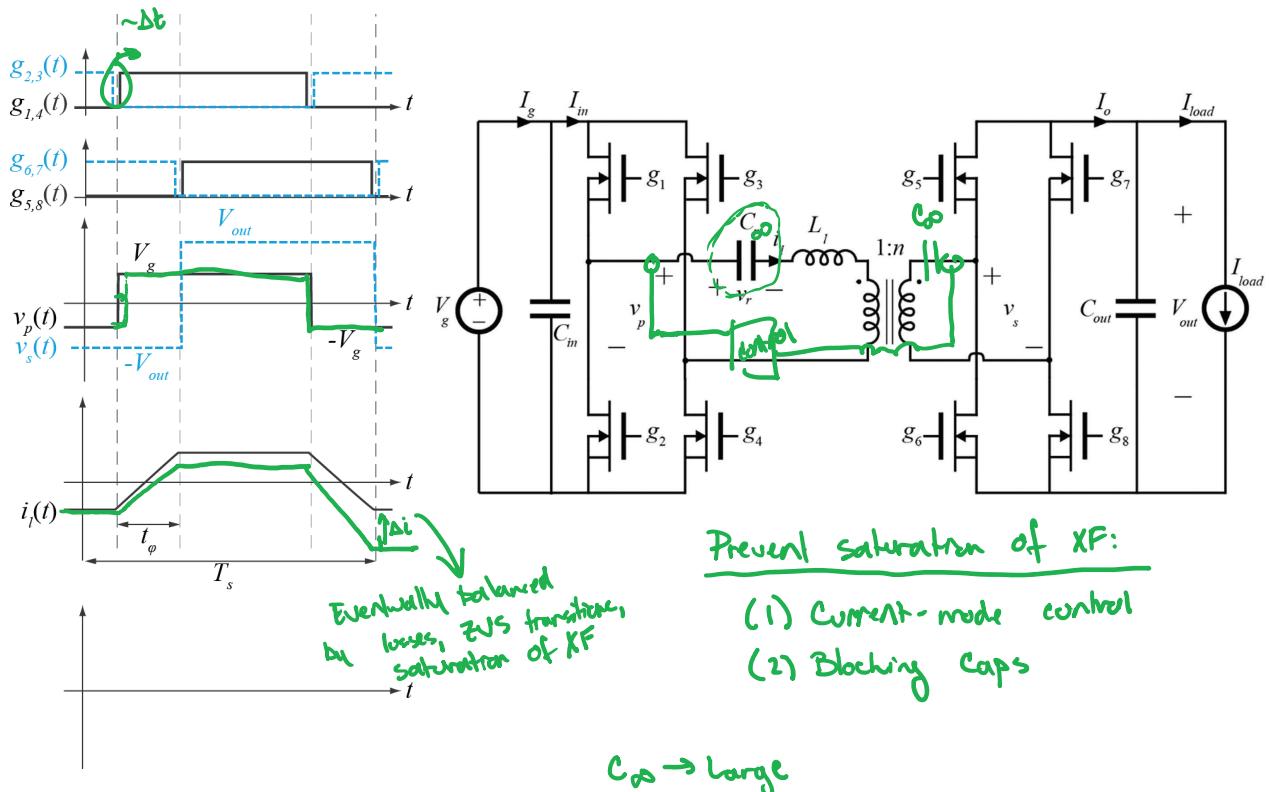

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE


## Series Resonant Converter

Phase-shift Modulation

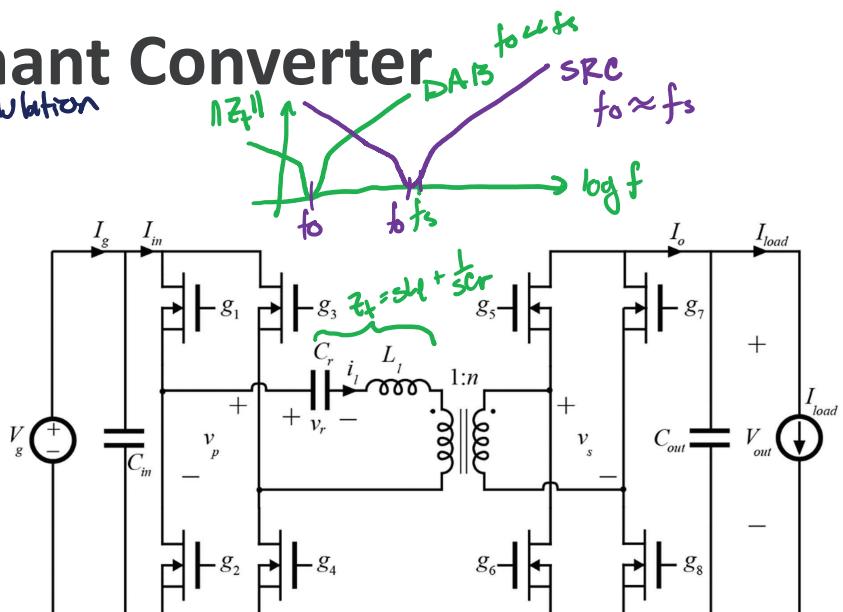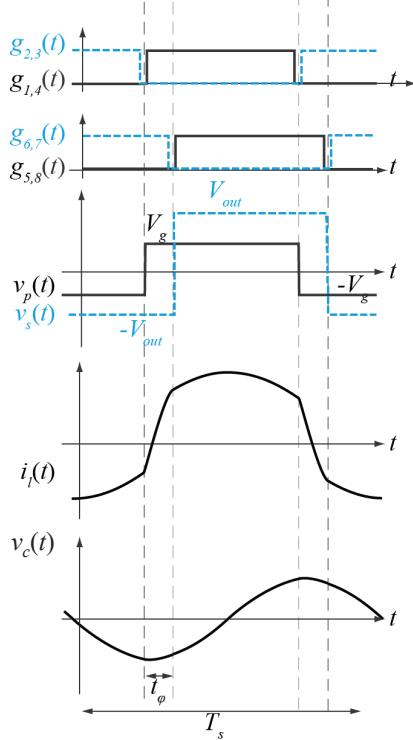

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

# Subinterval Equivalent Circuits

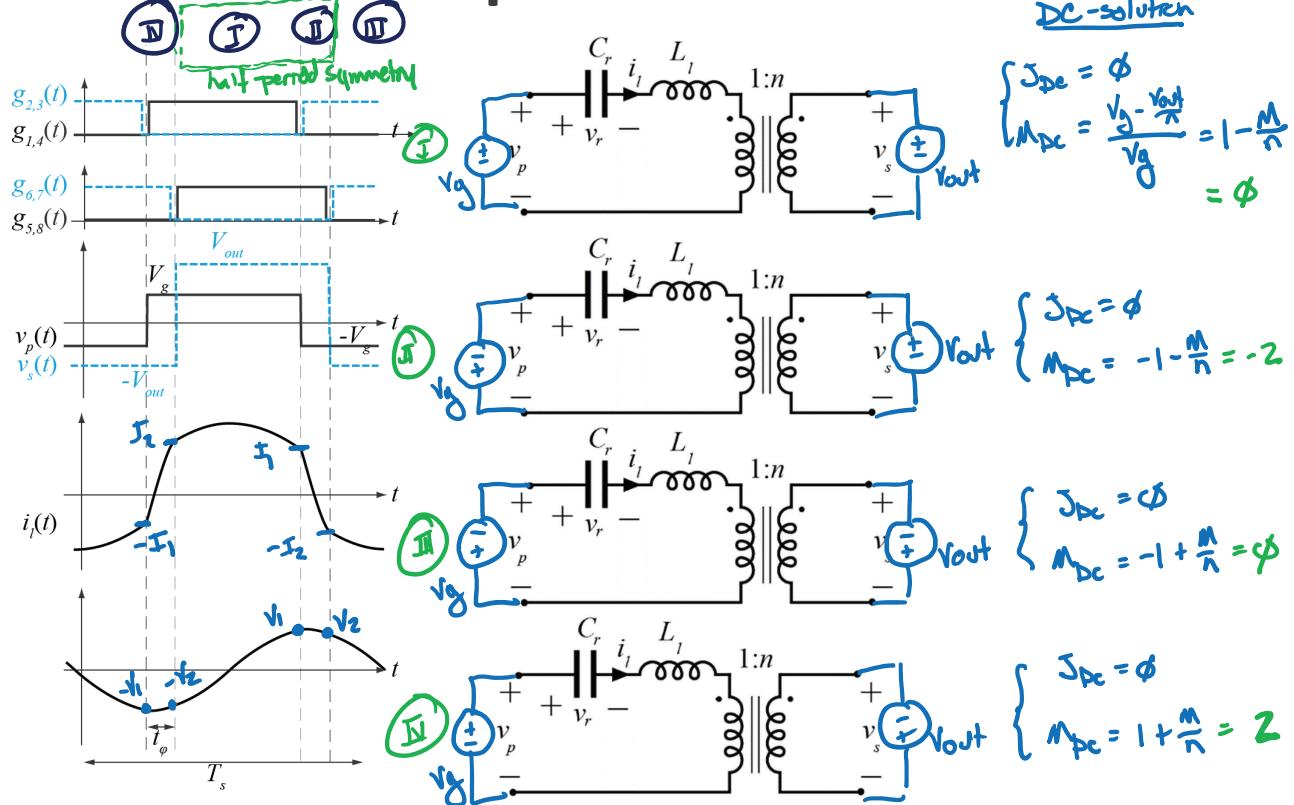

## Complete State Plane – Phase Shift Modulation

