

State Plane Solution

$$\textcircled{I} \quad r_1^2 = M_1^2 + S_1^2 = \underline{M_1^2 + S_1^2}$$

Period:

$$\frac{T_0}{2} = t_1 + t_2$$

$$\alpha = \tan^{-1}\left(\frac{M_1}{S_1}\right) + \tan^{-1}\left(\frac{M_2}{S_2}\right)$$

$$\textcircled{II} \quad r_2^2 = (z + M_1)^2 + S_1^2 = (z + M_2)^2 + S_2^2$$

$$\beta = \tan^{-1}\left(\frac{S_1}{z + M_1}\right) + \tan^{-1}\left(\frac{S_2}{z + M_2}\right)$$

$$\boxed{\frac{I}{F} = \alpha + \beta}$$

$$\frac{q + 4M_1 + \underline{M_1^2 + S_1^2}}{-\underline{(M_1^2 + S_1^2)}} = \frac{q + 4M_2 + \underline{M_2^2 + S_2^2}}{-\underline{(M_2^2 + S_2^2)}}$$

$$q + 4M_1 = q + 4M_2$$

$$\boxed{M_1 = M_2}$$


$$\beta \quad \boxed{S_1 = S_2}$$

specific simplification for PSM $\Rightarrow V_{out} = nV_g$

Averaging Step

$$\hat{n} \langle i_{out} \rangle \Big|_{T_0/2} = \frac{2}{T_0} \int_0^{T_0/2} i_{in}(t) dt$$

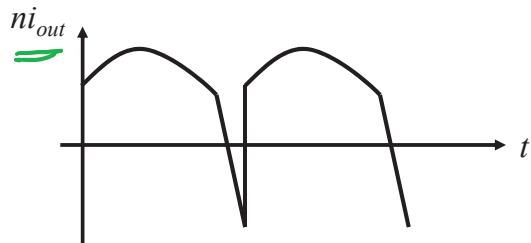$i_{in}(t) = i_{in}^{\textcircled{I}}(t) + i_{in}^{\textcircled{II}}(t)$



$$\hat{n} I_{out} = \frac{2}{T_0} [g_1 + g_2]$$

$$\hat{n} I_{out} = \frac{2}{T_0} \left[\underbrace{C_r(V_1 + V_2)}_{C_r 2V_1 = C_r 2V_2} + \underbrace{C_r(V_1 - V_2)}_{\phi} \right]$$

Recall: $M_1 = M_2$
 $V_1 = V_2$

$$\hat{n} I_{out} = \frac{2}{T_0} C_r 2V_1$$

$$\hat{n} S_{out} = \boxed{S = \frac{F}{\pi} 2 M_1}$$

Closed-Form Solution

$$\zeta = \frac{F}{\pi} 2m$$

$$\left| \begin{array}{l} \frac{\pi}{F} = \alpha + \beta \\ \alpha = \frac{\pi}{F} - \beta \end{array} \right.$$

$$\alpha = 2 \tan^{-1} \left(\frac{m_1}{z_1} \right)$$

$$\beta = 2 \tan^{-1} \left(\frac{z_1}{z+m_1} \right)$$

$$m_1 = \zeta_1 \tan \left(\frac{\alpha}{2} \right) \quad \curvearrowleft \quad \zeta_1 = \tan \left(\frac{\beta}{2} \right) (z+m_1)$$

$$m_1 = \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right) (z+m_1)$$

$$m_1 = \frac{2 \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right)}{1 - \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right)}$$


$$\boxed{\zeta = 4 \frac{F}{\pi} \frac{\tan \left(\frac{\pi}{2F} - \frac{\beta}{2} \right) \tan \left(\frac{\beta}{2} \right)}{1 - \tan \left(\frac{\pi}{2F} - \frac{\beta}{2} \right) \tan \left(\frac{\beta}{2} \right)}}$$

SRC Control Trajectory


Normally, $F > 1$ in SRC

$$F = \frac{f_s}{f_o} > 1 \rightarrow f_s > f_o$$

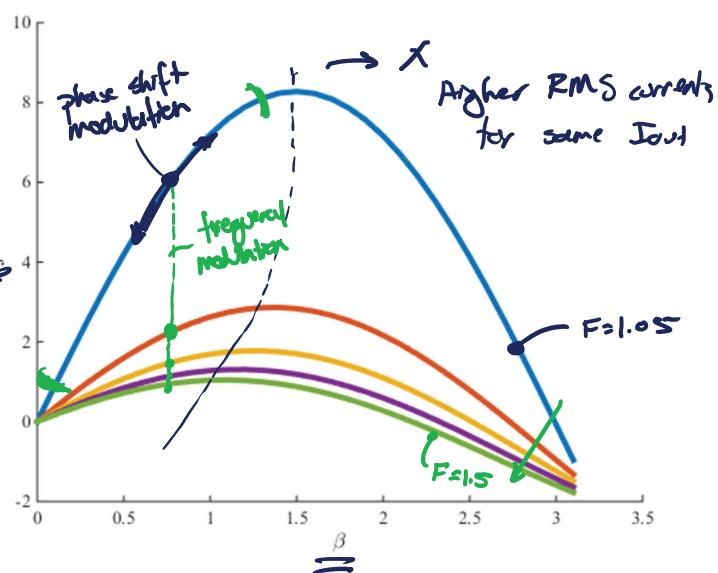Gives the possibility of getting ZVS
(subject to further analysis)



SRC Current Stress

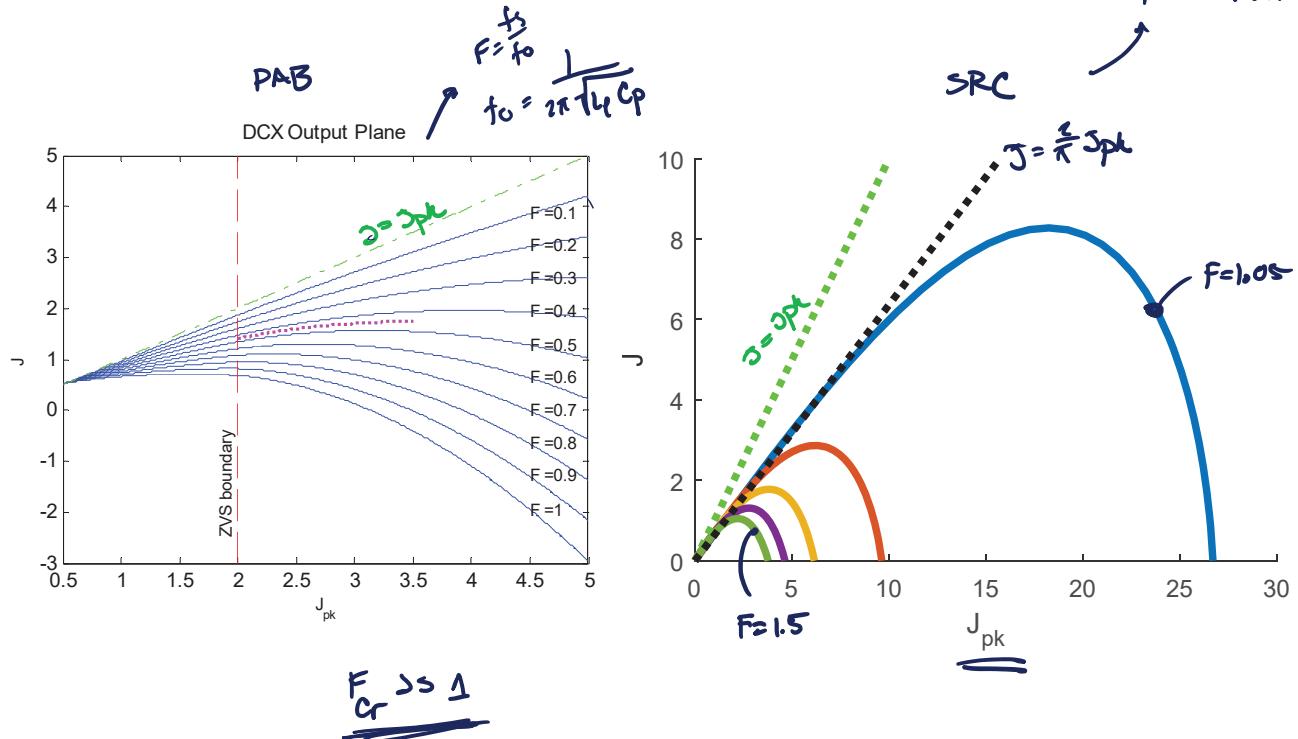


Example Simulation

```



.param Cr={150n} Ro={(L/Cr)**.5} td=70n phi={Ts/2+150n} Rop={(L/Cp)**.5}
.param fs=750k Ts={1/fs} Vg=100 V={Vg} C={100u} Cp=200p Cs={Cp} L={10u}

```

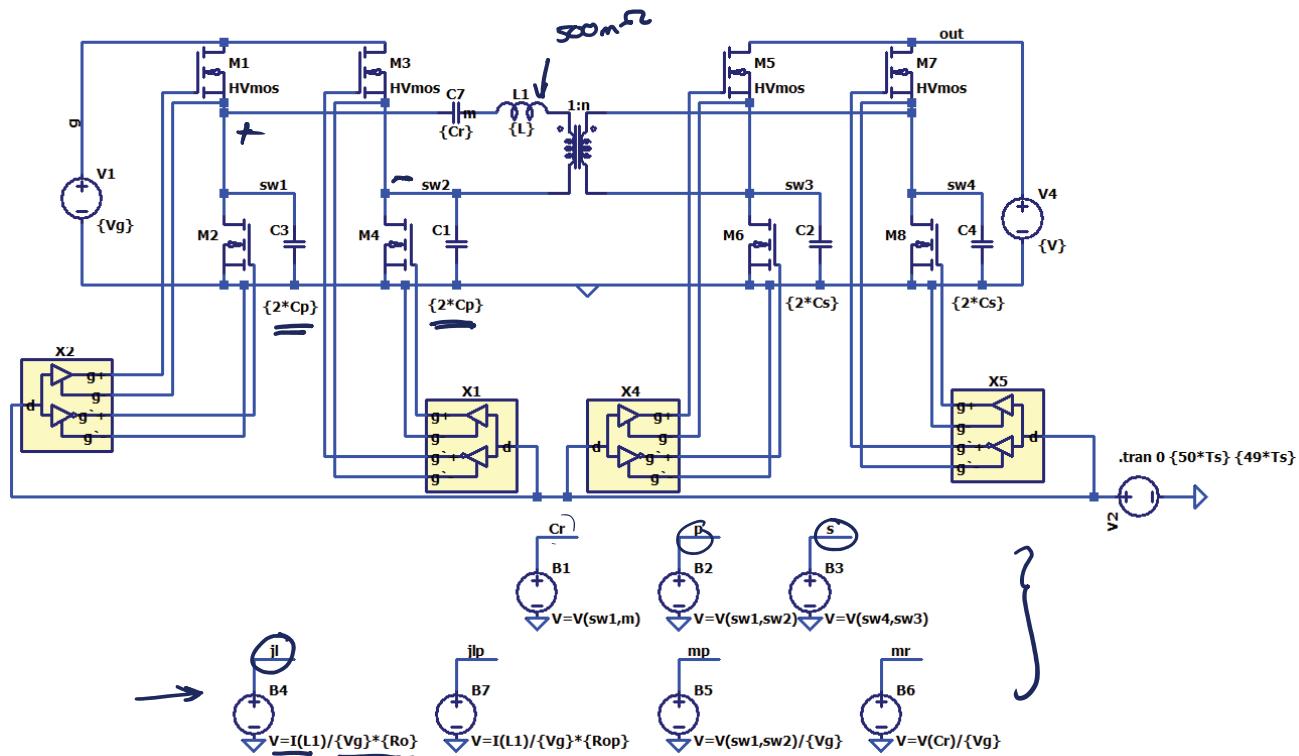



SRC Simulation

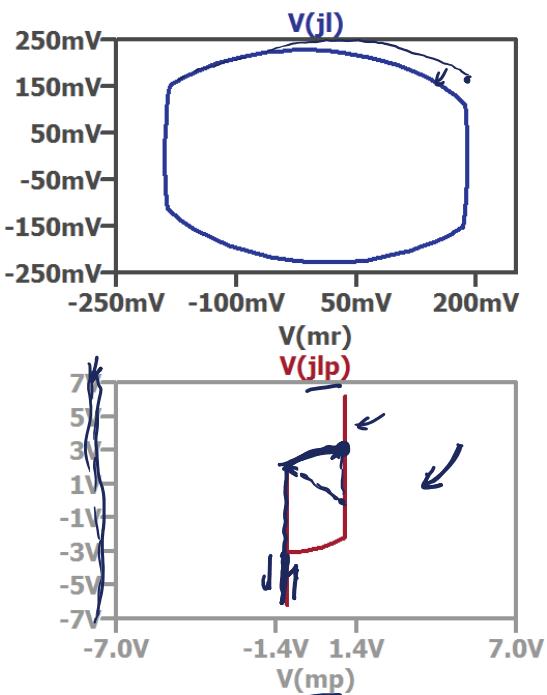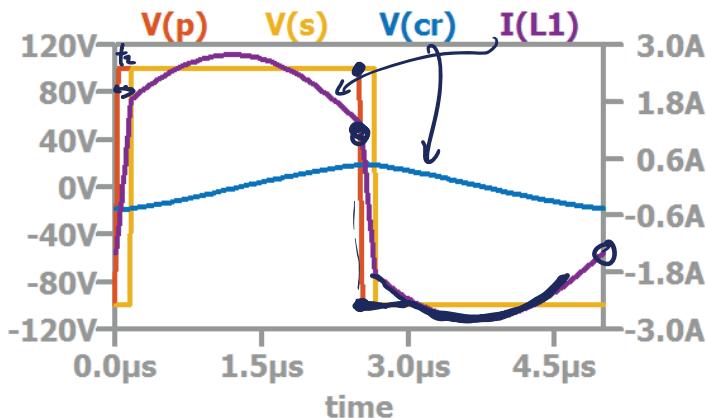$I_{out} = 2A$
 $\rightarrow f_s = 200\text{kHz}$
 $\rightarrow f_o = 130\text{kHz}$
 $V_g = 100V$
 $V_{out} = 100V$



SRC Simulation

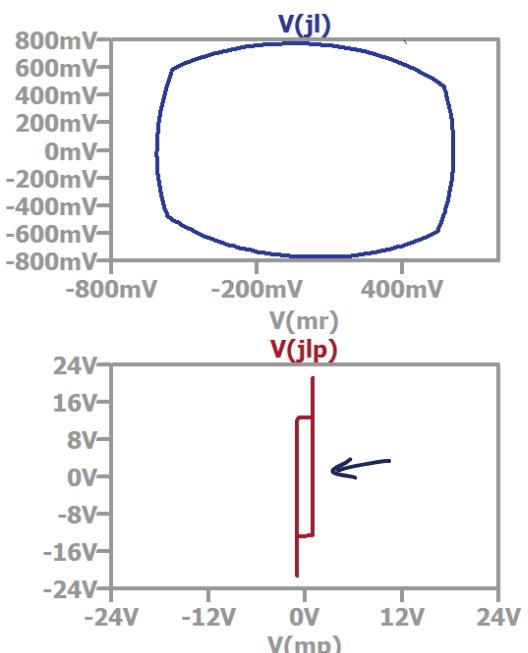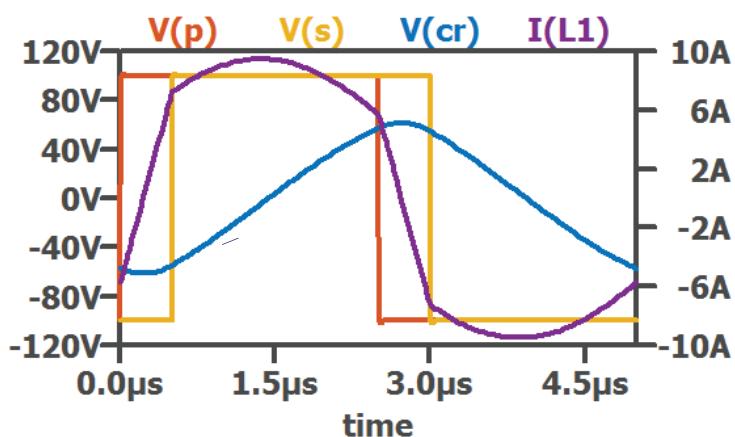$I_{out} = 6.5A$ ←
 $f_s = 200\text{kHz}$
 $f_o = 130\text{kHz}$
 $V_g = 100V$
 $V_{out} = 100V$



SRC Simulation




$$I_{out} = 500\text{mA}$$

$$f_s = 200\text{kHz}$$

$$f_o = 130\text{kHz}$$

$$V_g = 100\text{V}$$

$$V_{out} = 100\text{V}$$

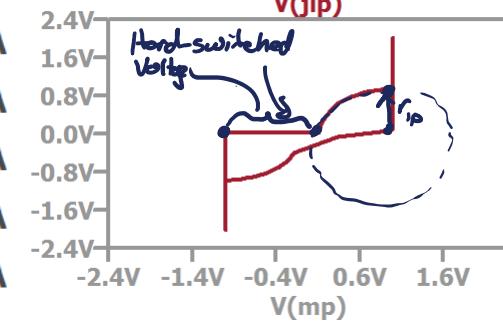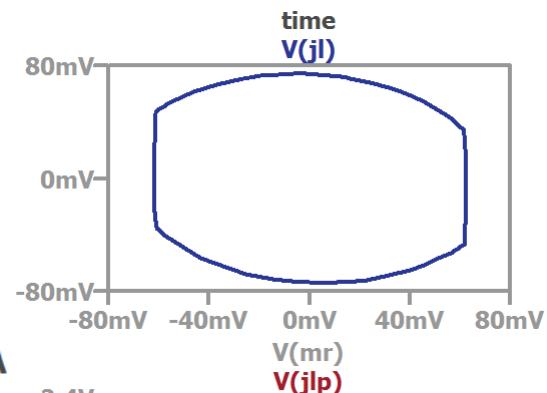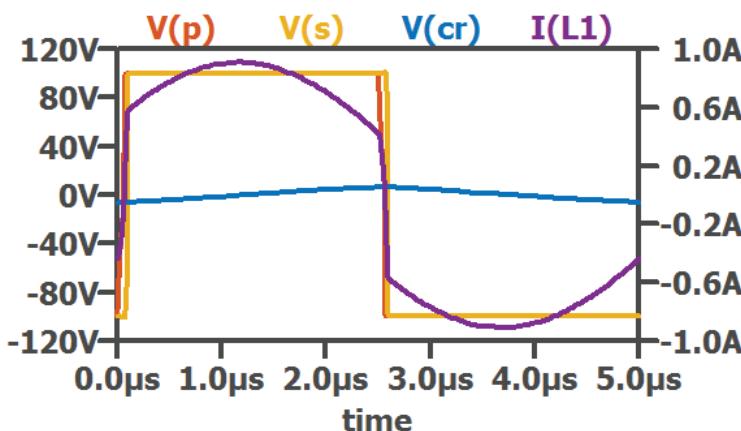




SRC Simulation

$$I_{out} = 1.2\text{A}$$

$$\left\{ \begin{array}{l} f_s = 130\text{kHz} \\ f_o = 130\text{kHz} \end{array} \right. \quad f=1$$



$$V_g = 100\text{V}$$

$$V_{out} = 100\text{V}$$

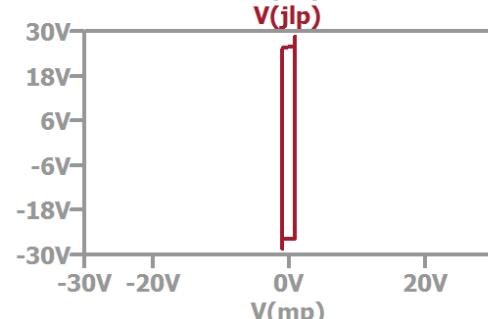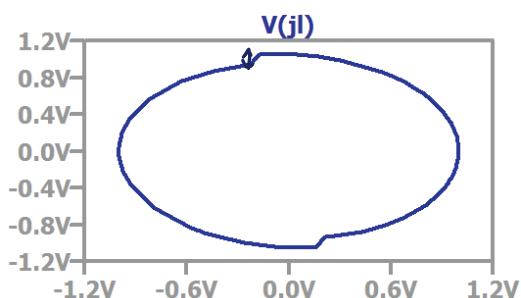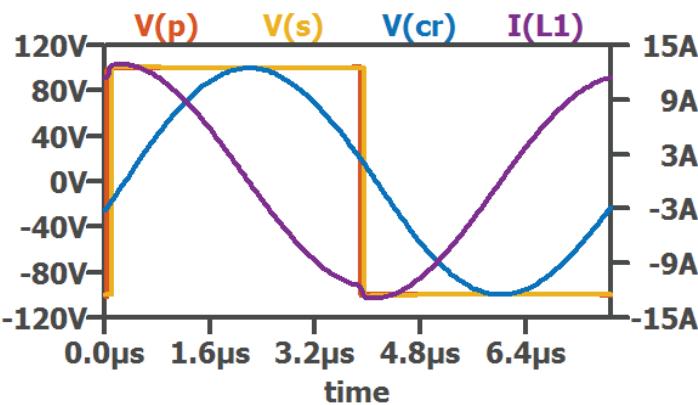



SRC Simulation

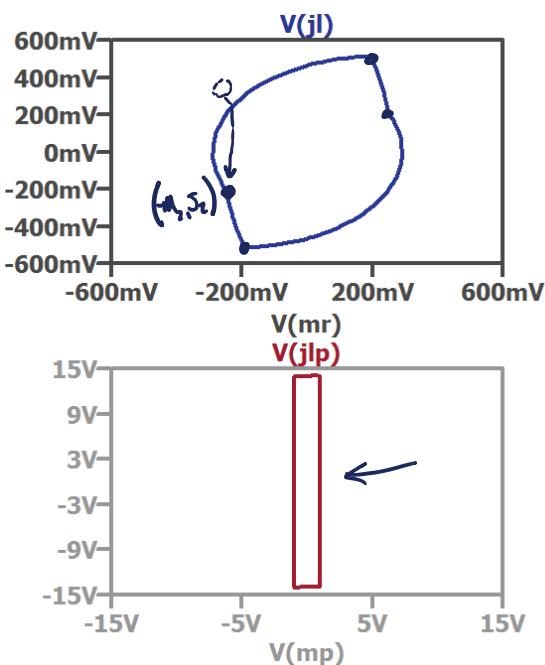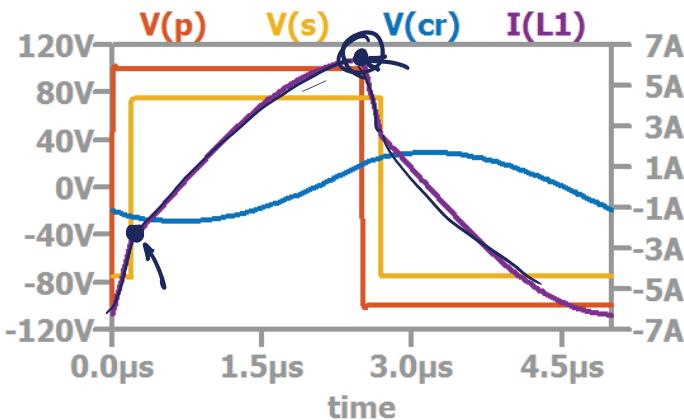$I_{out} = 3A$
 $f_s = 200\text{kHz}$
 $f_o = 130\text{kHz}$
 $V_g = 100V$
 $V_{out} = 75V$ ←




SRC Simulation

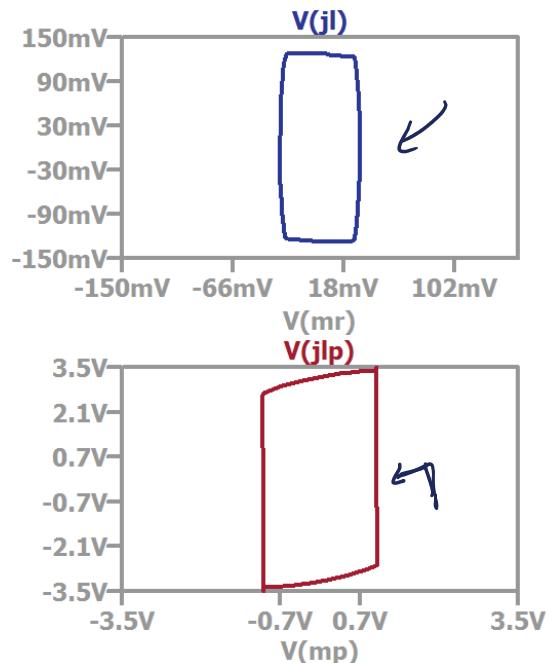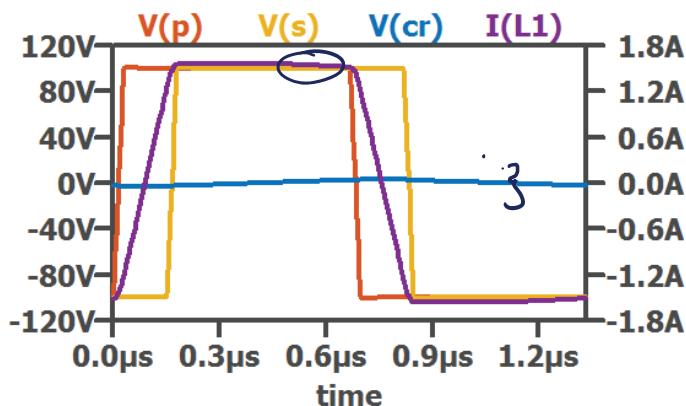
$I_{out} = 1A$
 $f_s = 750\text{kHz}$ ← $f_s \gg f_o$
 $f_o = 130\text{kHz}$
 $V_g = 100V$
 $V_{out} = 100V$



DAB vs SRC

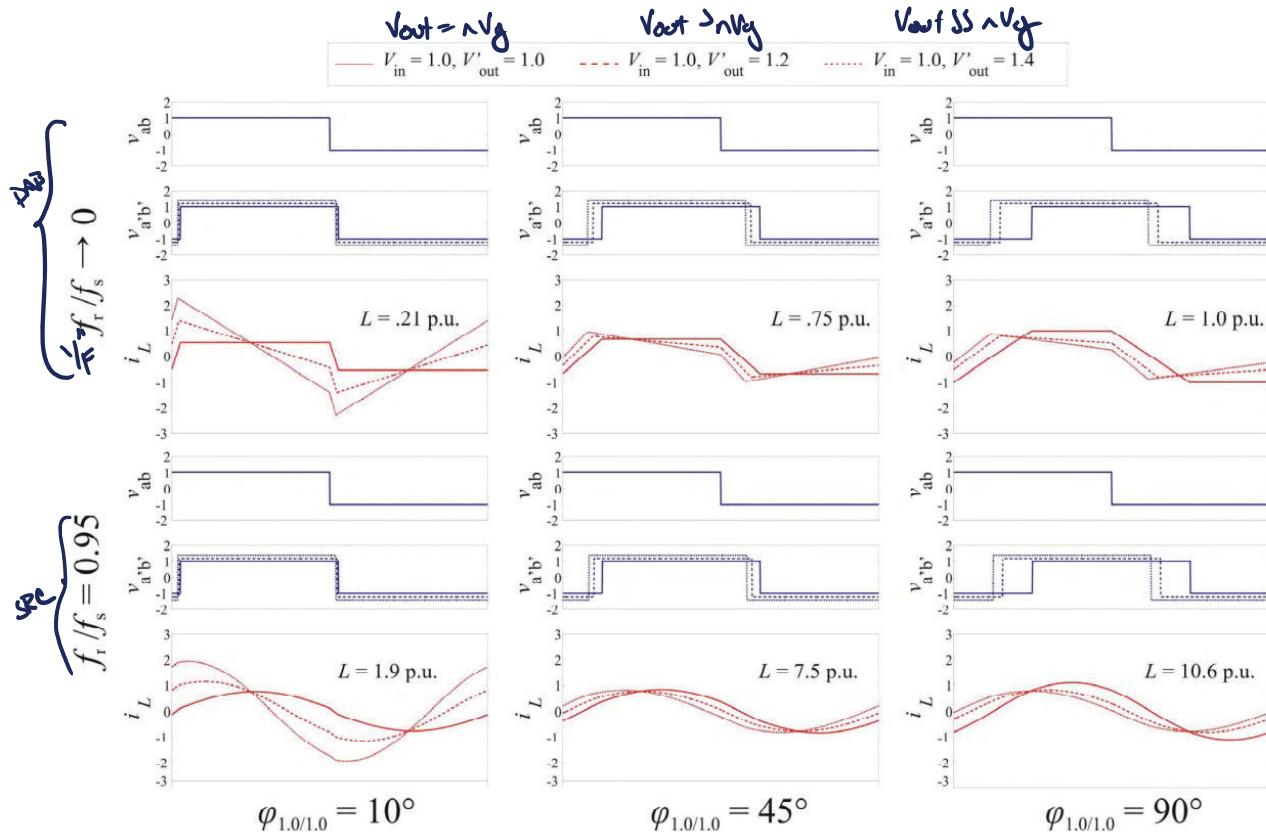

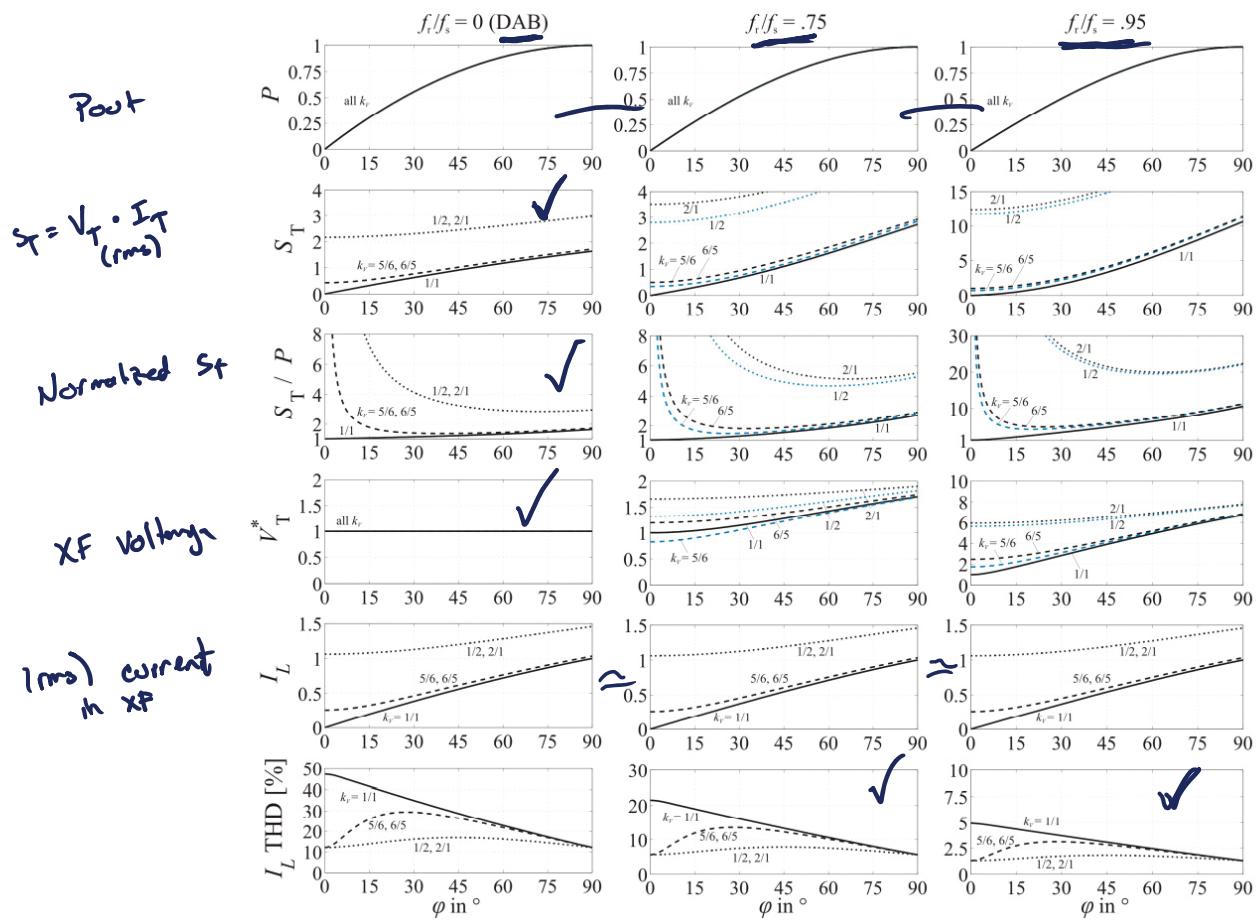R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"



R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"



DAB vs SRC: Conclusions

- | <u>DAB</u> | <u>SRC</u> |
|------------------------------|---|
| + Smaller resonant tank | + Can be designed with larger XF inductance |
| + Smaller RMS currents | + Lower AC winding losses |
| + Wider Soft-switching range | + Reduced device <u>turn-off losses</u> |

R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"

