
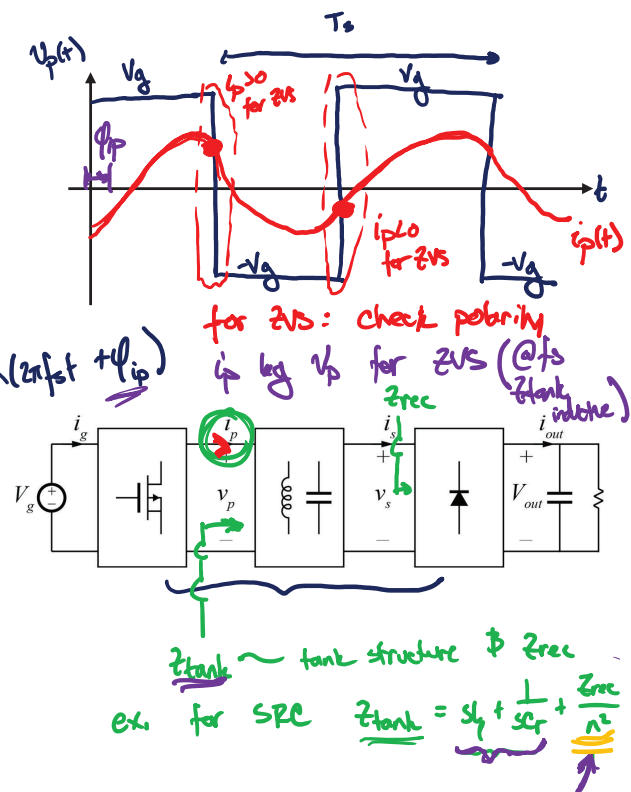

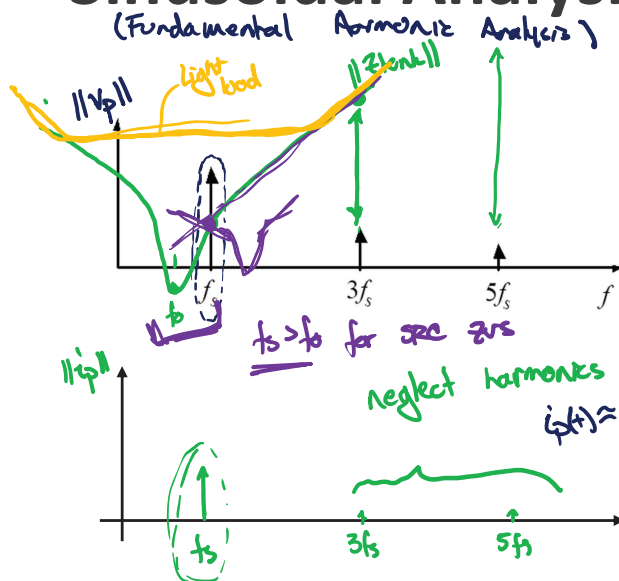
# Sinusoidal Analysis (Ch 19)


Erickson & Maksimovic 2nd ed.  
ch 22 in 3rd edition



Good approximation if tank has good bandpass characteristics
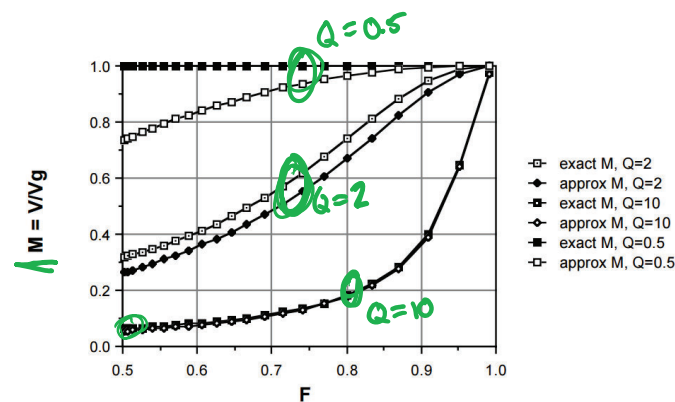
## Sinusoidal Analysis: Comments


- Generally most accurate when operating near resonance with a high  $Q$
- Effective quality factor  $Q_e$  depends not only on resonant tank, but also on loading
- Analysis neglects switching intervals; can only predict where ZVS **cannot** be obtained



"exact" = state plane  
"approx" = sinusoidal analysis

Fig. 2.14. Comparison of exact and approximate series resonant converter characteristics, below resonance.


# AC Link Waveforms

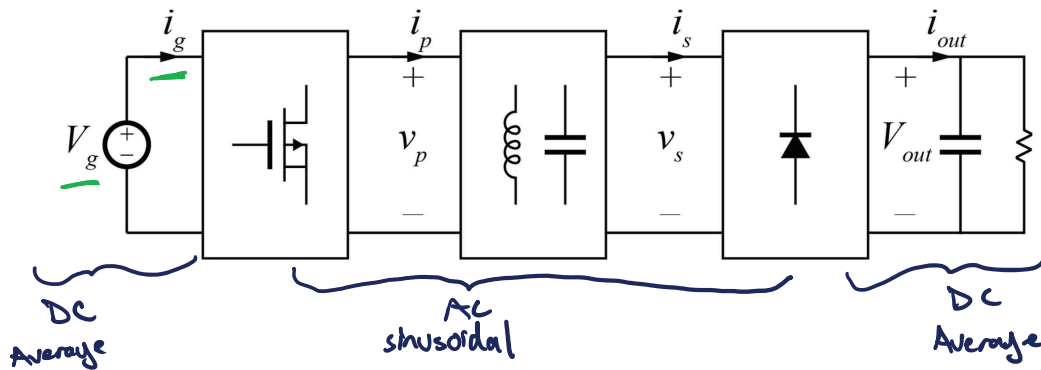

$v_p(t) \rightarrow$  full signal

$v_{p1}(t) \rightarrow$  fundamental component

## Switch Network Sinusoidal Analysis

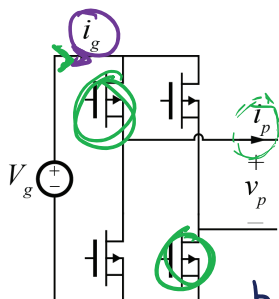

Fourier Series

$$b_1 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(x) dx$$

For  $v_p(t)$ :

$$b_1 = \frac{2}{T_s} \int_0^{T_s} v_p(t) \sin(2\pi f_s t) dt$$


$$= \frac{4}{T_s} \int_0^{T_s/2} V_g \sin(2\pi f_s t) dt$$

$$= \frac{4}{T_s} V_g \int_0^{\pi} \sin(\theta) \frac{1}{2\pi f_s} d\theta$$

$$= \frac{4}{T_s} V_g \frac{1}{2\pi f_s} [-\cos(\theta)]_0^{\pi}$$

$$= \frac{4}{T_s} V_g \frac{1}{2\pi f_s} (2) = \boxed{\frac{4}{\pi} V_g}$$

$$\approx 1.27 V_g$$

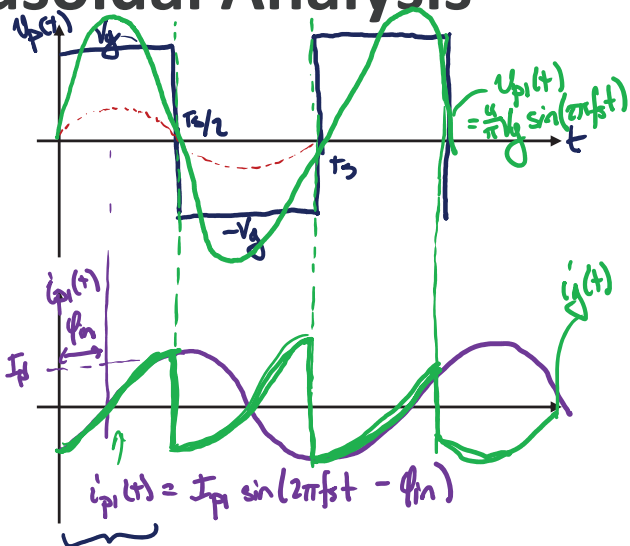

# Input Current


$$i_p(t) = I_{p1} \sin(2\pi f_s t - \phi_{in}) \quad \leftarrow \text{Generic definition at the moment}$$

$$\begin{aligned} \langle i_g \rangle_{T_s} &= \frac{2}{T_s} \int_0^{T_s/2} i_p(t) dt \\ &= \frac{2}{T_s} \int_0^{T_s/2} I_{p1} \sin(2\pi f_s t - \phi_{in}) dt \\ &= \frac{2}{T_s} I_{p1} \int_{-\phi_{in}}^{\pi - \phi_{in}} \sin \theta \frac{1}{2\pi f_s} d\theta \\ &= \frac{2}{T_s} I_{p1} \frac{1}{2\pi f_s} \left[ -\cos \theta \right]_{-\phi_{in}}^{\pi - \phi_{in}} \\ &= \frac{2}{T_s} I_{p1} \frac{1}{2\pi f_s} \left[ 2 \cos \phi_{in} \right] \end{aligned}$$

$$\begin{aligned} \theta &= 2\pi f_s t - \phi_{in} \\ d\theta &= 2\pi f_s dt \end{aligned}$$

$$\langle i_g \rangle_{T_s} = \frac{2}{\pi} I_{p1} \cos(\phi_{in})$$

## Switch Network Equivalent Circuit

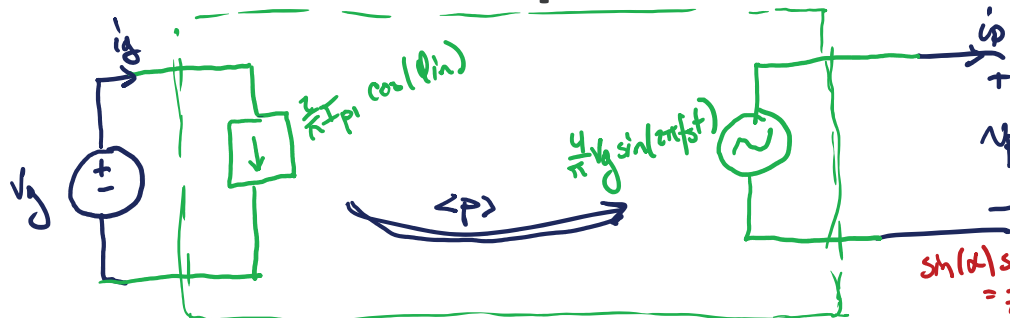

$$P_g = V_g \langle i_g \rangle_{T_s} = V_g I_{p1} \frac{2}{\pi} \cos \phi_{in} \checkmark$$

$$P_p(t) = V_p(t) \cdot i_p(t)$$

$$\langle P_p \rangle_{T_s} = \frac{1}{T_s} \int_0^{T_s} \frac{4}{\pi} V_g \sin(\omega_s t) \cdot I_{p1} \sin(\omega_s t - \phi_{in}) dt$$

$$\langle P_p \rangle_{T_s} = \frac{1}{T_s} \frac{4}{\pi} V_g I_{p1} \frac{1}{2} \int_0^{T_s} (\cos(\omega_s t - \omega_s t + \phi_{in}) - \cos(\omega_s t + \omega_s t - \phi_{in})) dt$$

$$= \frac{1}{T_s} \frac{4}{\pi} V_g I_{p1} \frac{1}{2} \left[ \cancel{T_s \cos(\phi_{in})} - \phi \right]$$

$$= \frac{2}{\pi} V_g I_{p1} \cos \phi_{in} \checkmark$$