

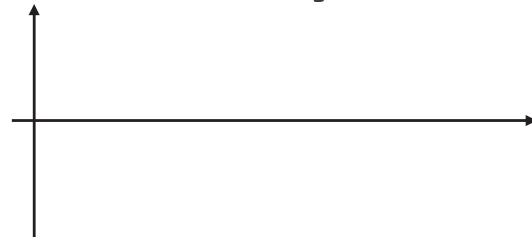
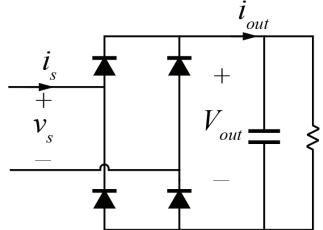


# Diode Rectifier Sinusoidal Analysis

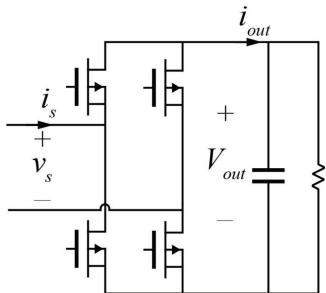


## Diode Rectifier Equivalent Circuit


# Other Implementations

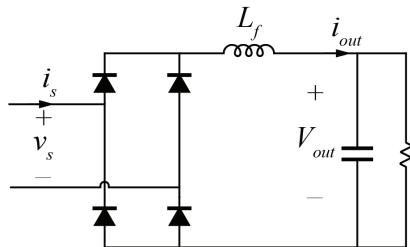

## Complete Equivalent Circuit

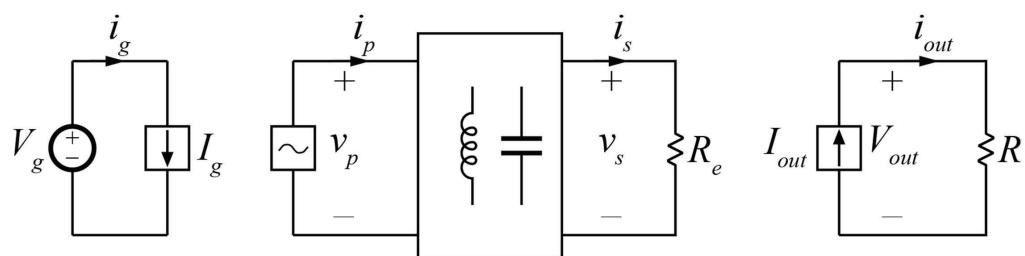

# Output Characteristic

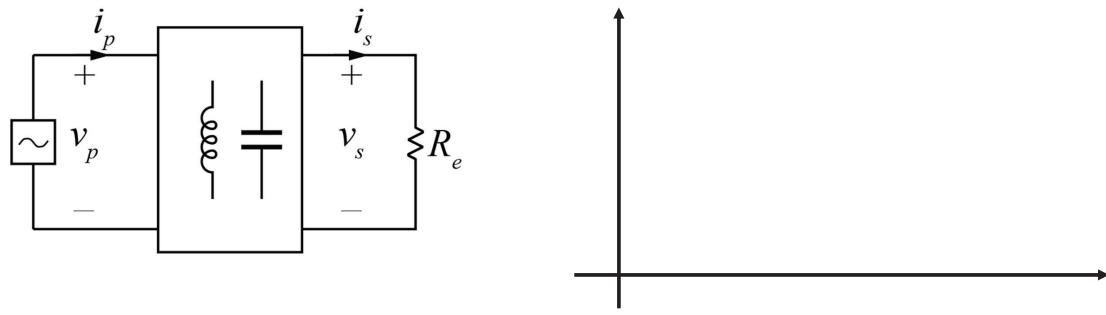

## Construction of Tank Transfer Function

# Tank Input Impedance

