
Tank Input Impedance


TENNESSEE KNOXVILLE

Series Resonant Tank

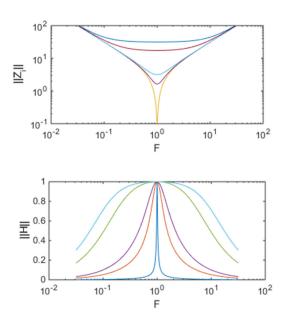





Parallel Resonant Converter

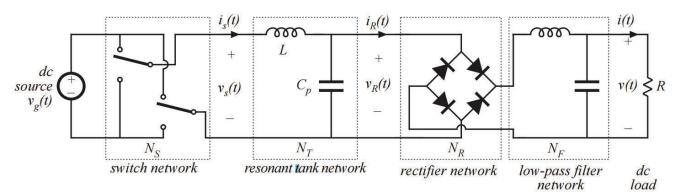

TENNESSEE KNOXVILLE


PRC Tank Input Impedance

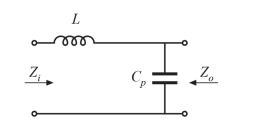

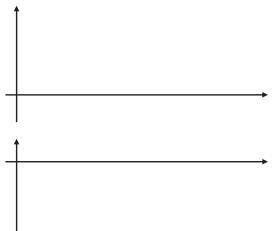





PRC Tank

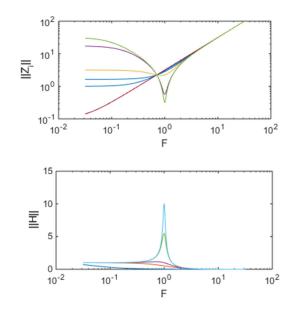

TENNESSEE KNOXVILLE


LCC

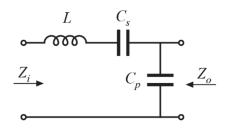

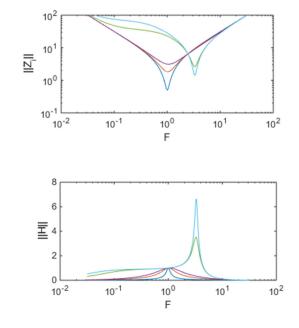




LLC

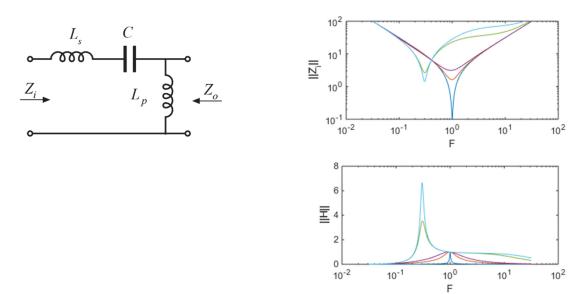




Tank Summary (1/2)

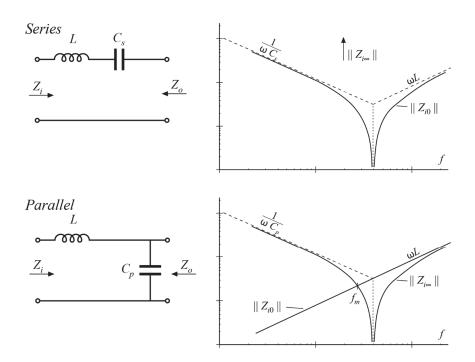




Tank Summary (2/2)

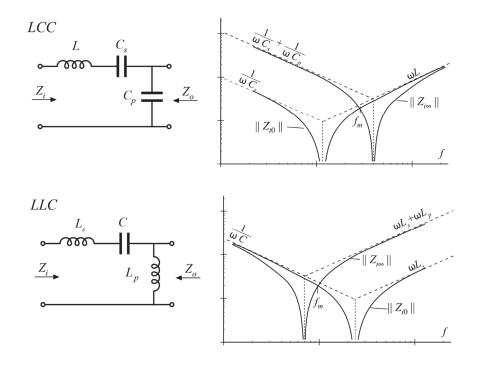




Series Resonant Tank – Subharmonic Modes

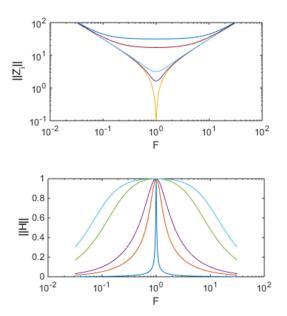




Subharmonic Modes - High Q

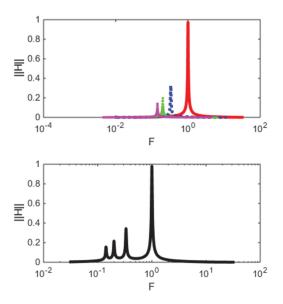


TENNESSEE KNOXVILLE

Subharmonic Modes – Low Q

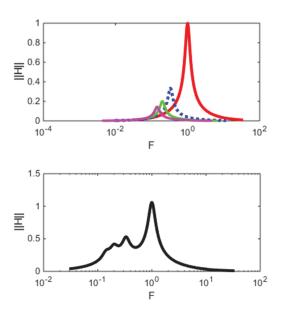



SRC Control Plane

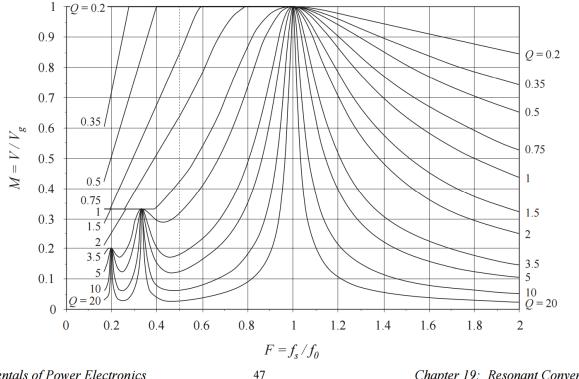


Fundamentals of Power Electronics

Chapter 19: Resonant Conversion



SRC Mode Boundaries

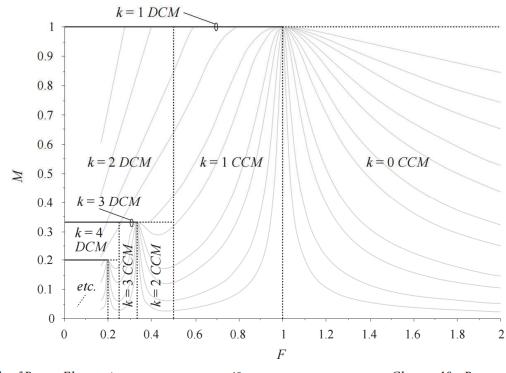

Fundamentals of Power Electronics

48

Chapter 19: Resonant Conversion

