
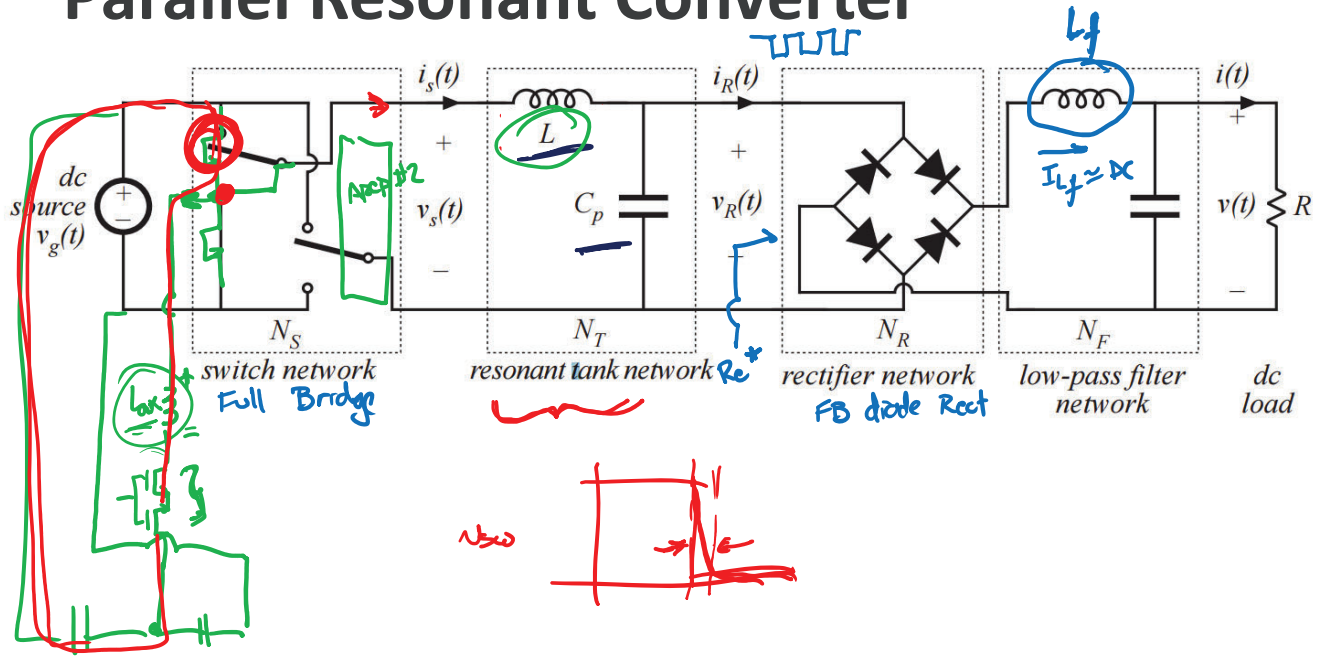


Parallel Resonant Converter

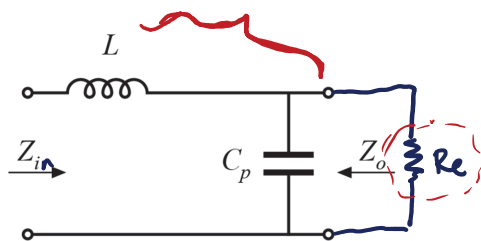


PRC Tank Input Impedance



$$Z_{in} = sL + \frac{1}{sC_p} \parallel Re$$

$$H(s) = \frac{\frac{1}{sC_p} \parallel Re}{Z_{in}}$$

$$Q_e = \frac{Re}{R_o}$$

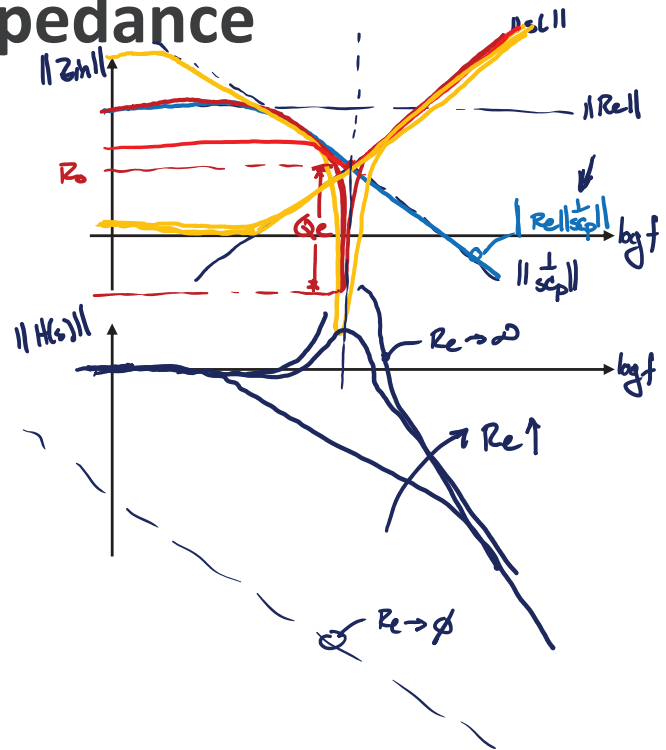


PRC Tank

Textbook Theorem 1
 section 19.4.2 in 2nd edition
 section 22.4 in 3rd edition



If tank is purely reactive, $\|Z_i(j\omega_x)\|$
 is a purely monotonic function of R_e

Can really just look at $Z_i|_{R_e \rightarrow 0}$ &
 $Z_i|_{R_e \rightarrow \infty}$, all other curves of different R_e
 are monotonic in between.


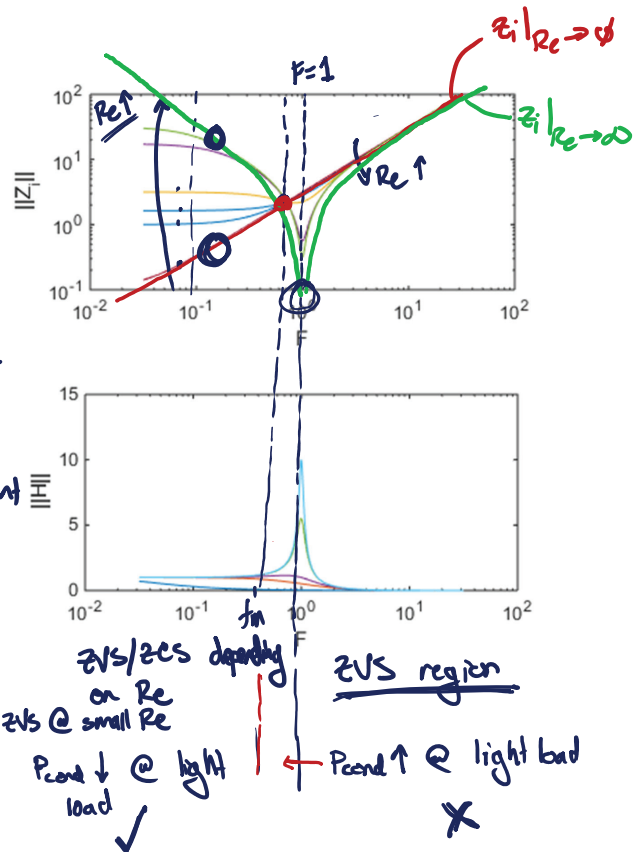
Q $F=1$, no problem w/ short circuit but
 open circuit results in very high current
 stress.



LCC

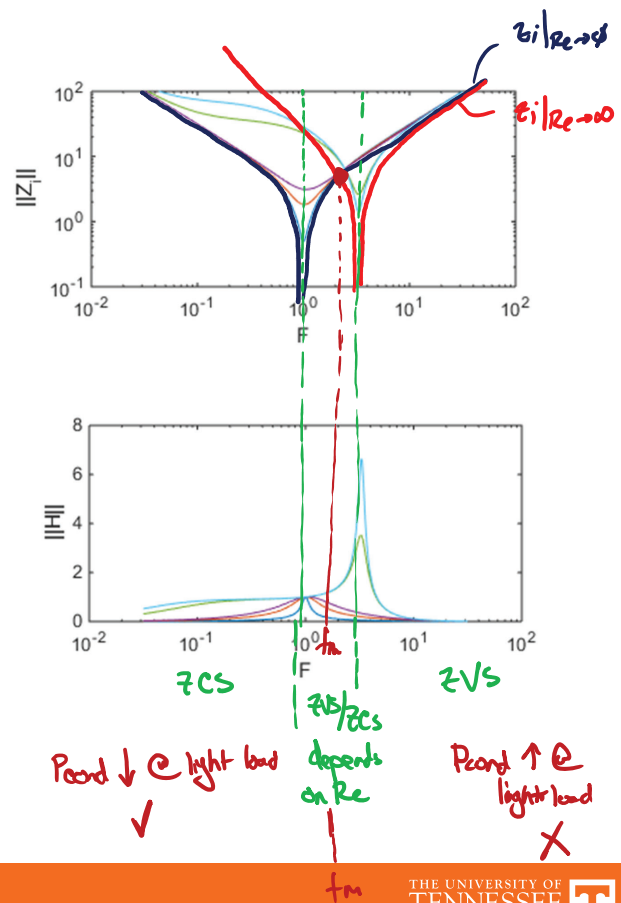
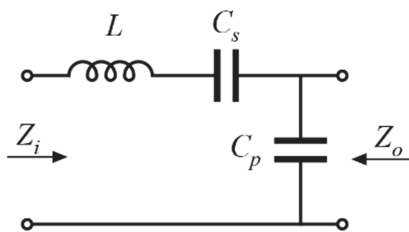


LLC

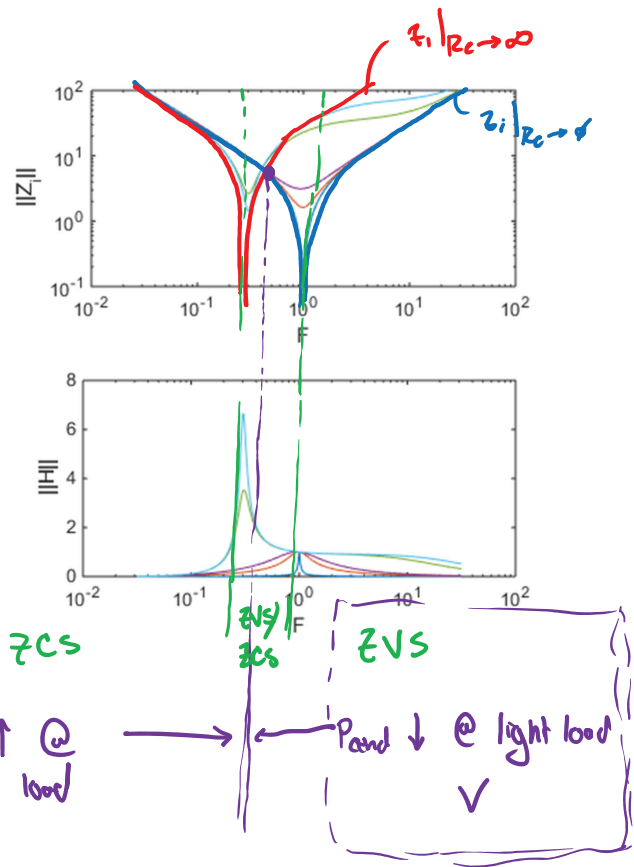
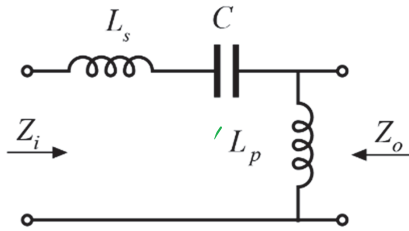


Tank Summary (1/2)

Series

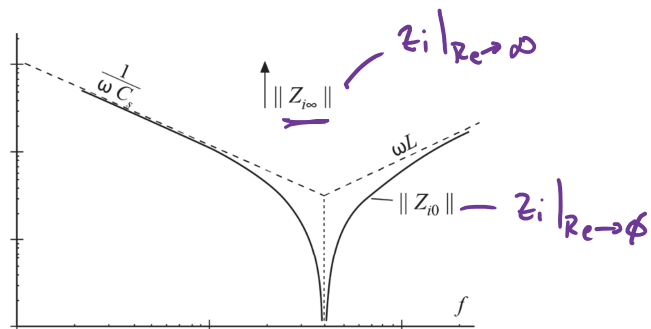
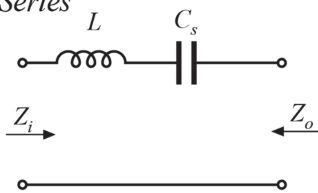


Parallel

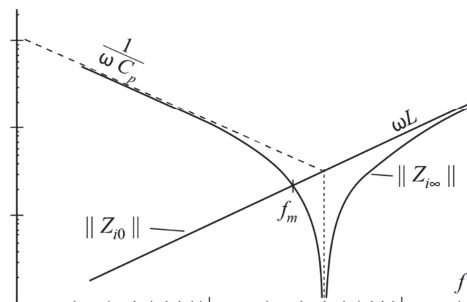
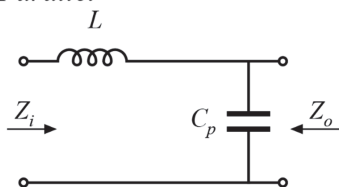


Tank Summary (2/2)



LCC

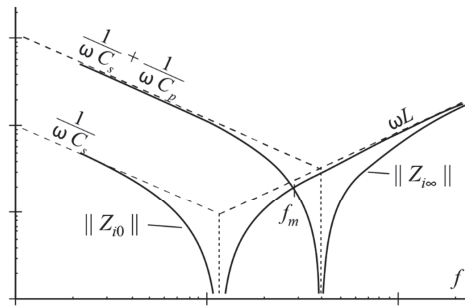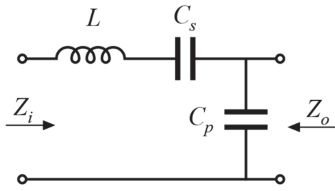

LLC

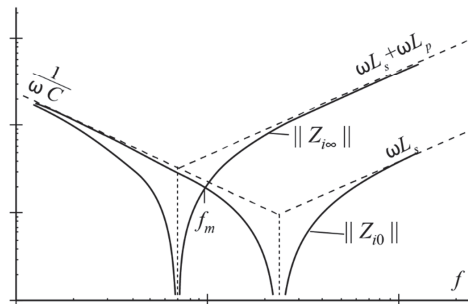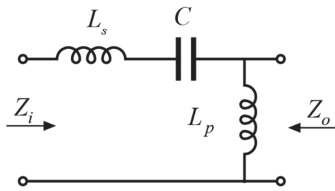


Series Resonant Tank – Subharmonic Modes

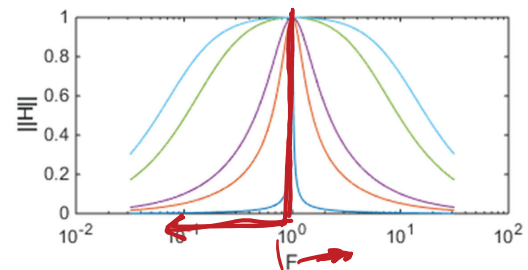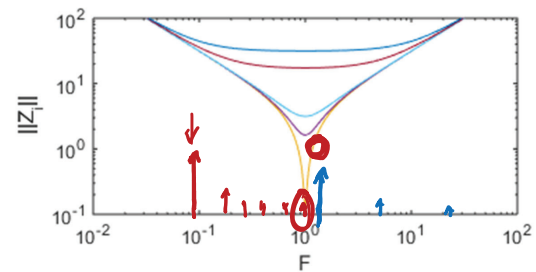


$\uparrow f_s \uparrow V_{out} \leftarrow \rightarrow \uparrow f_s \downarrow V_{out}$


Subharmonic Modes

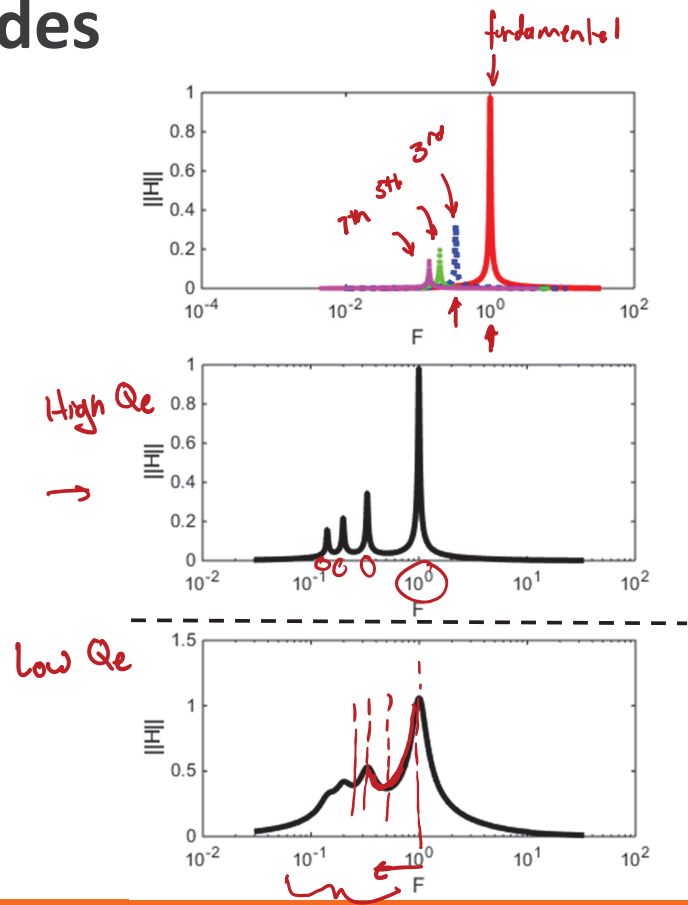


SRC Control Plane

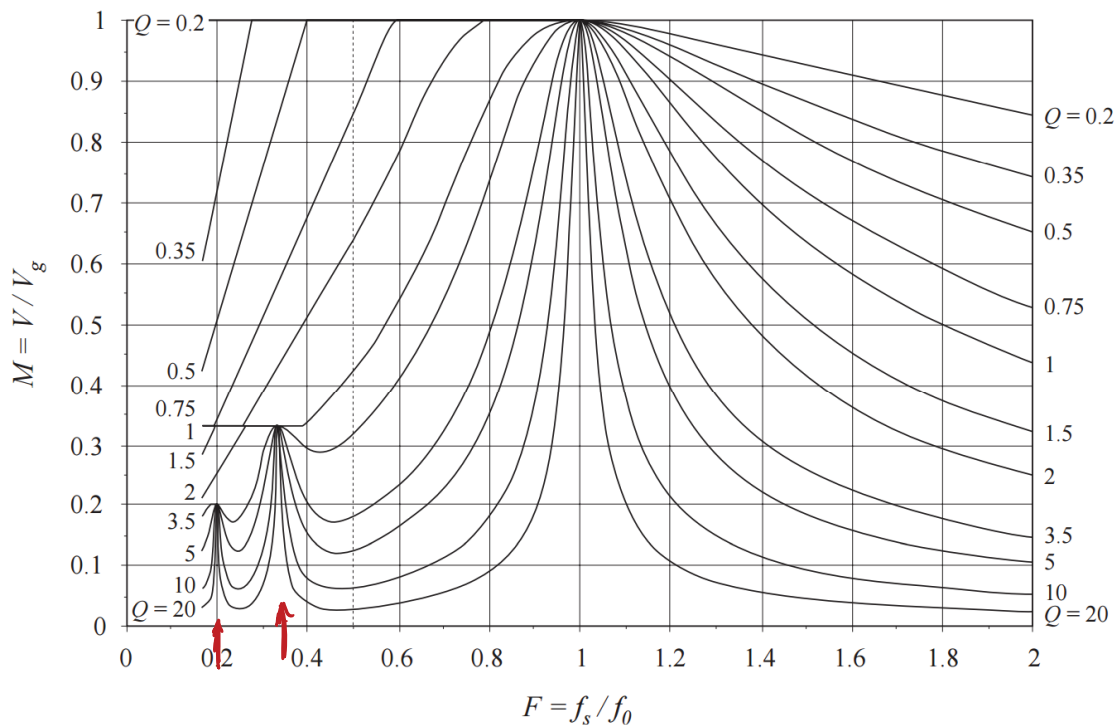

SRC Mode Boundaries

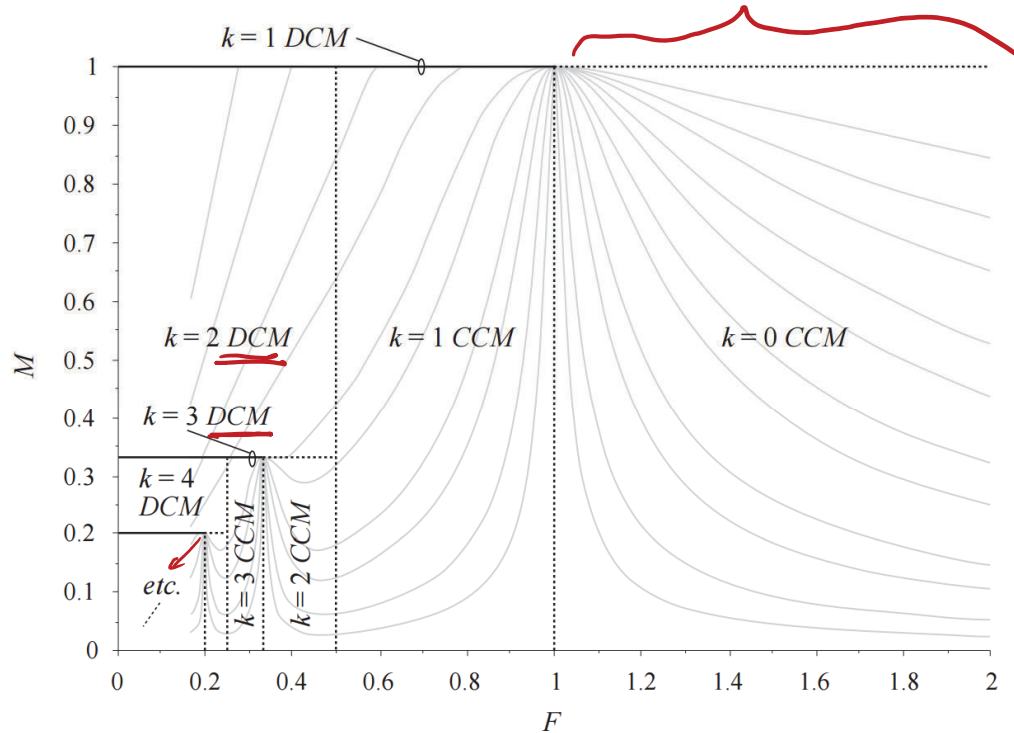

ZVS Assist Circuits

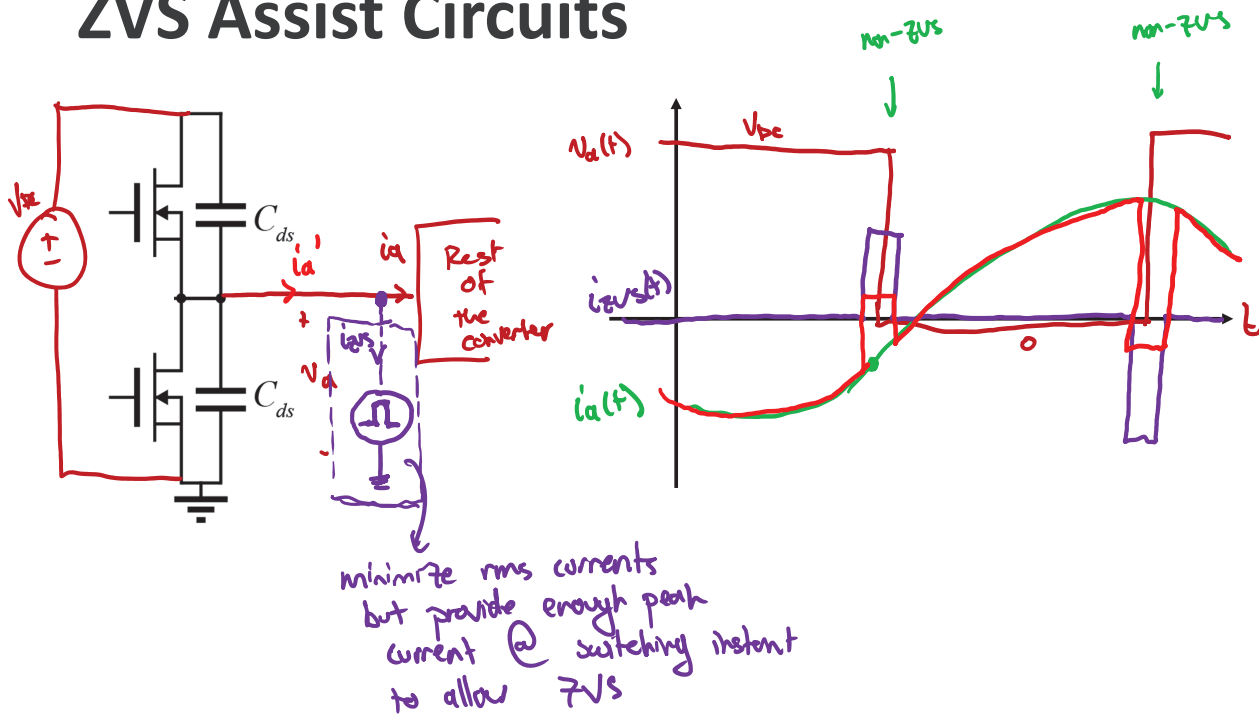

ZVS Tank Examples

