

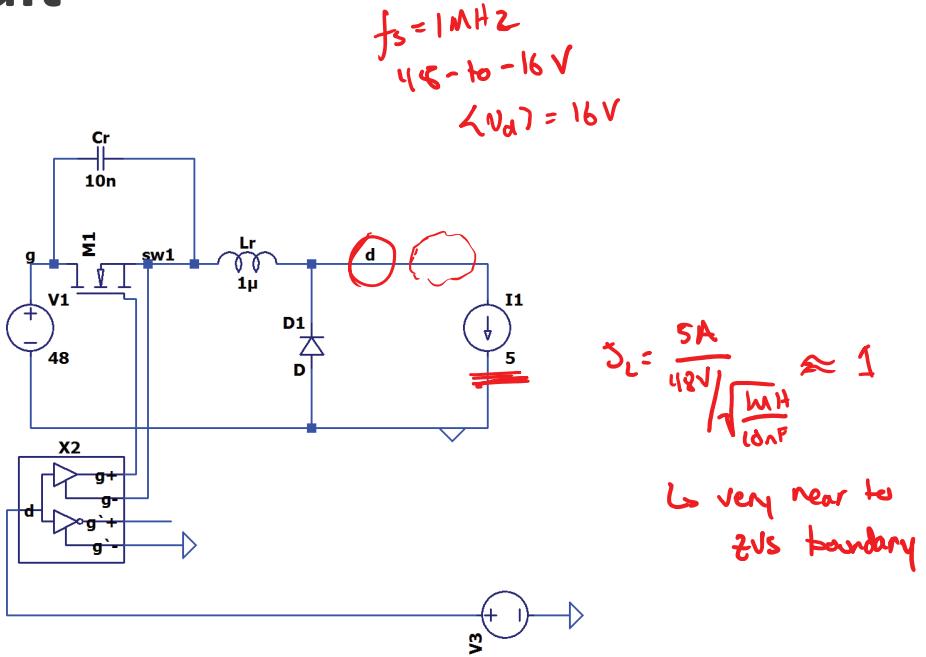



Test Circuit

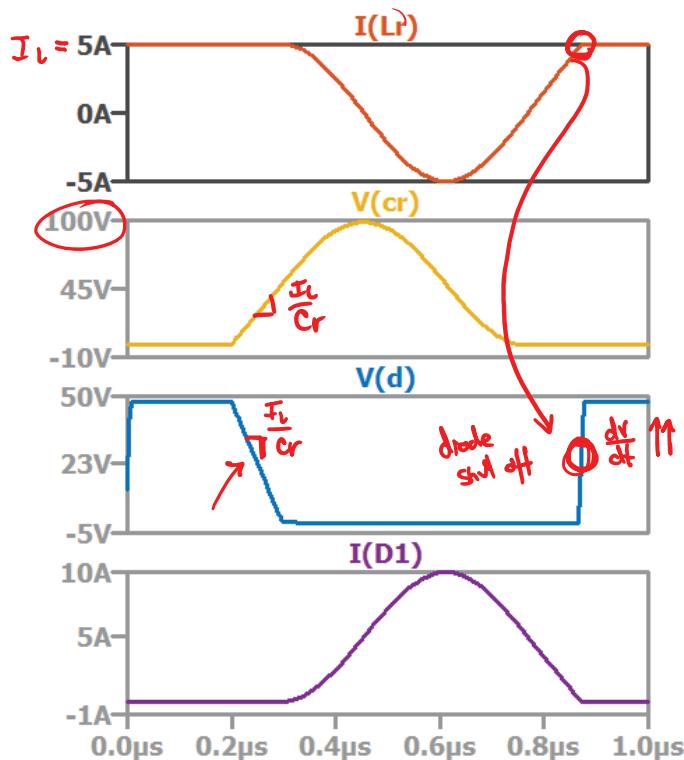

Simulation Results

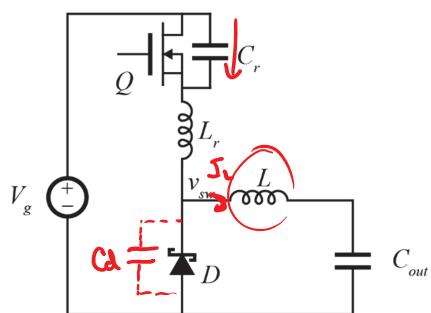


Diode Capacitance

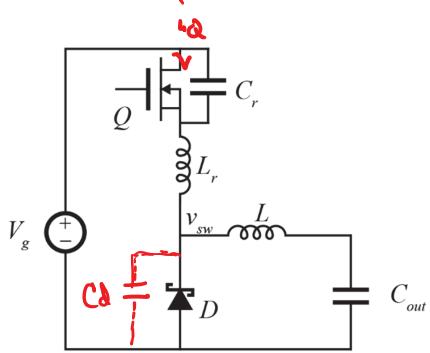

Handwritten notes:



v_g $\frac{1}{j\omega} C_d$ $3L_r$ I_L

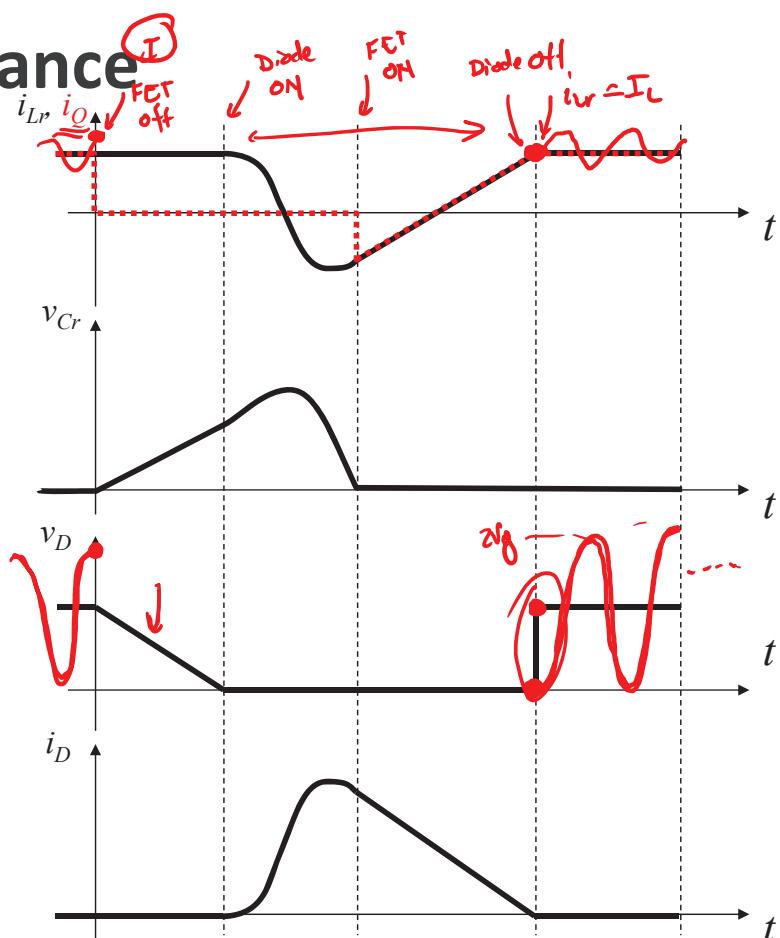DC solution:
 $N_{SW} = \frac{V_g}{V_D}$
 $i_{ur} = I_L$




THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Simulation Results: Diode Capacitance

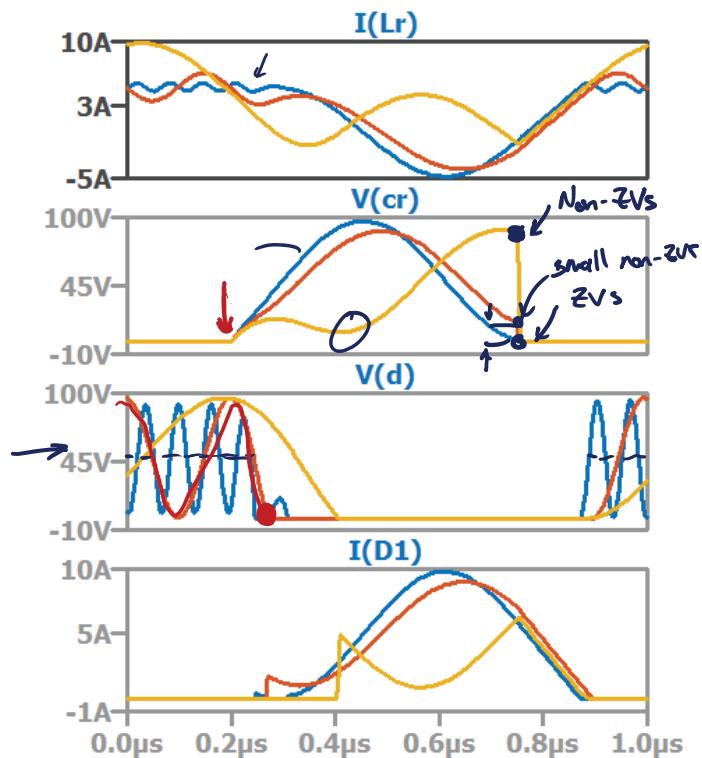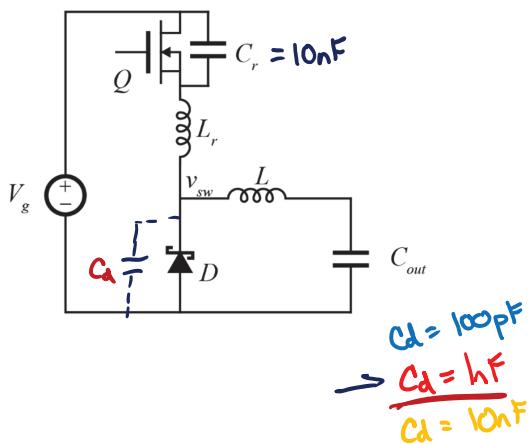


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Wishlist: Multi-Resonant

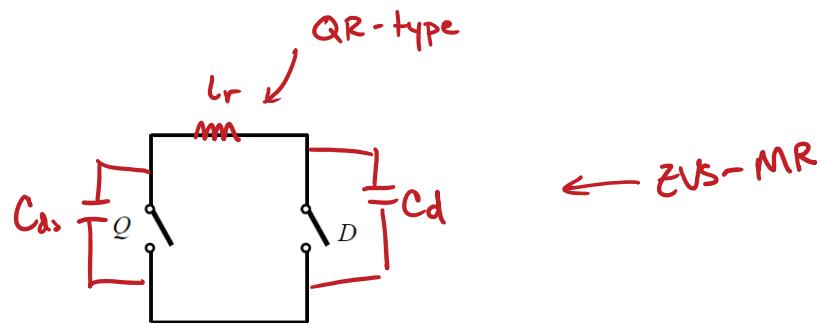


QSW :

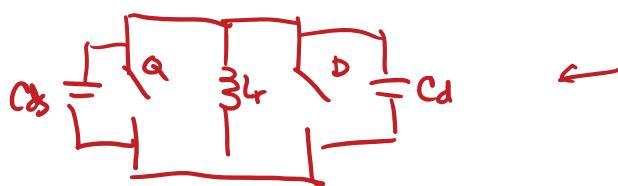


THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

ZVS-MR Buck

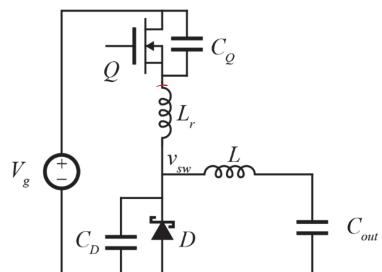


Conducting

Q

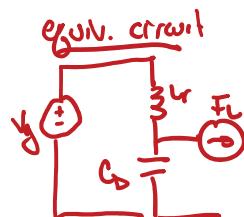


$$\frac{R_o}{\sqrt{L_r/C_d}}$$

D

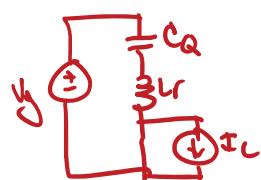


$$\sqrt{L_r/C_d}$$

Q&D

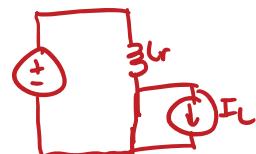

X
(linear "substitution")

X

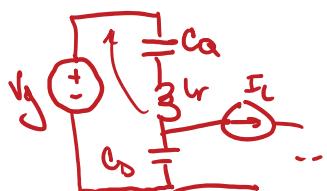

$$C_{eq} = \frac{C_Q C_D}{C_Q + C_D}$$

$$I_{eq} = \pm \sqrt{\frac{L_r}{C_Q C_D}}$$

$$R_o = \sqrt{\frac{L_r}{k_{eq}}}$$

Operating Modes


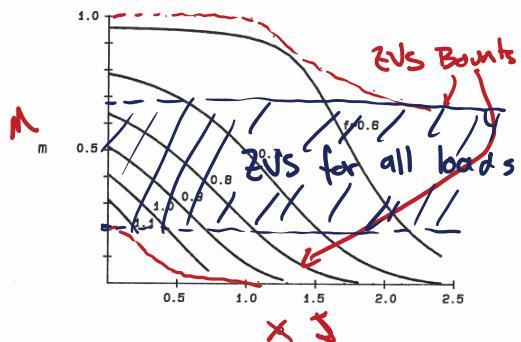


Figure 10.7: Load-to-output DC characteristics of a ZV-MR converter operating in modes (I, II).

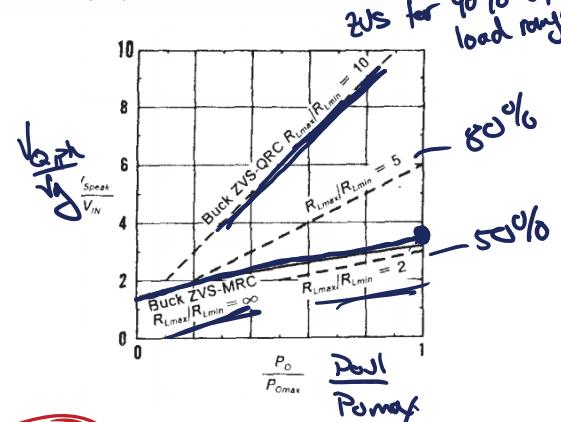

D Maksimovic, "Synthesis of PWM and Quasi-Resonant DC-to-DC Power Converters," Ph.D. Thesis, CalTech 1989



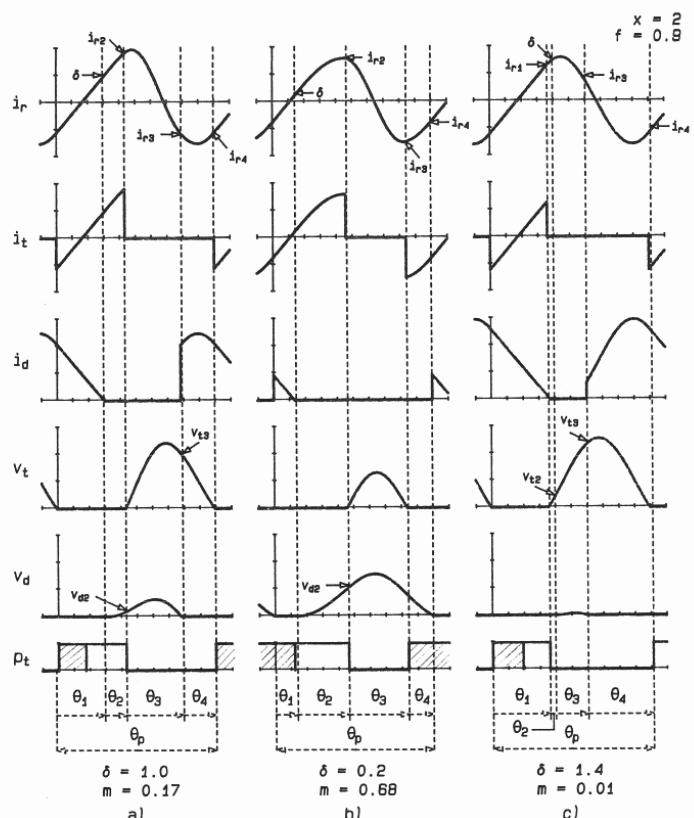


Figure 10.2: Typical waveforms for a ZV-MR converter operating in modes I₁ (a), II₁ (b) or III₁ (c).

Identification of Resonant Switch

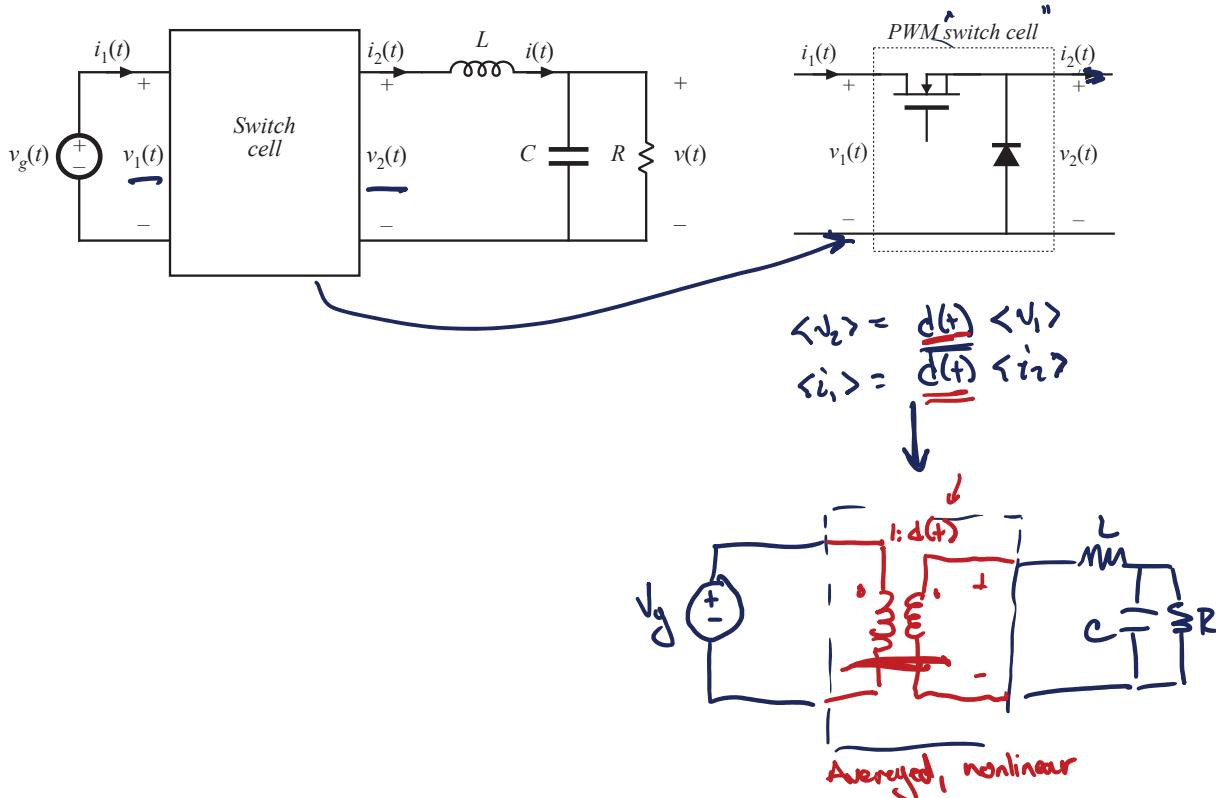

Switching Cell Conversion Ratio

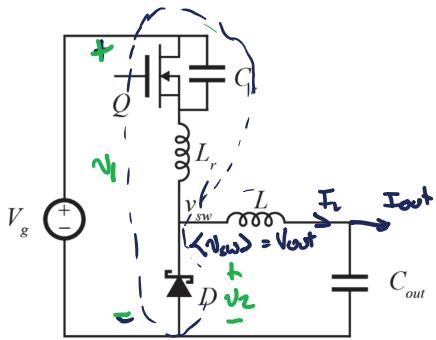

$$M = f(F, S_L)$$

derived by: $V = \frac{N_{sw}}{N_{out}}$
 M is also $\frac{N_{sw}}{N_{out}}$

$$\langle V_2 \rangle = M \langle V_1 \rangle, \quad \langle i_1 \rangle = M \langle i_2 \rangle$$

Unique to Buck converter

More generally:

$$M = \text{switch cell conversion ratio}$$

$$\langle V_2 \rangle = M \langle V_1 \rangle, \quad \langle i_1 \rangle = M \langle i_2 \rangle$$

Buck is a special case, where $M = m$
 for any other parent PWM topology $M \neq m$

Take PWM averaged analysis to replace $d(t)$ w/ $M(t)$ to
 get overall conversion ratio

$$\text{Boost } M > \frac{1}{1-D} \quad \xrightarrow{\text{resonant}} \quad M = \frac{1}{1-\lambda}$$

Conversion Ratios of Various Switch Cells

$$\rightarrow P_{1/2}(x) = \frac{1}{2\pi} \left[\frac{1}{2}x + \pi + \sin^{-1}x + \frac{1}{x} \left(1 - \sqrt{1-x^2} \right) \right]$$

$$P_1(x) = \frac{1}{2\pi} \left[\frac{1}{2}x + 2\pi + \sin^{-1}x + \frac{1}{x} \left(1 - \sqrt{1-x^2} \right) \right] \approx 1$$

Switch Cell	Conv. Ratio μ	Current Range	Conv. Ratio Range	Requirements on Q
PWM	D	N/A	$0 \leq \mu \leq 1$	
ZVS-QR (half)	$1 - F \cdot P_{\frac{1}{2}} \left(\frac{1}{J_L} \right)$	$1 \leq J_L \leq \infty$	$0 \leq \mu \leq 1$	
ZVS-QR (full)	$1 - F P_1 \left(\frac{1}{J_L} \right)$	$1 \leq J_L \leq \infty$	$0 \leq \mu \leq 1$	Bidirectional voltage
{ ZCS-QR (half) }	$F P_{\frac{1}{2}}(J_L)$	$0 \leq J_L \leq 1$	$0 \leq \mu \leq 1$	Unidirectional Current*
ZCS-QR (full)	$F P_1(J_L)$	$0 \leq J_L \leq 1$	$0 \leq \mu \leq 1$	

Resonant Switch Identification Examples

