


Test Circuit

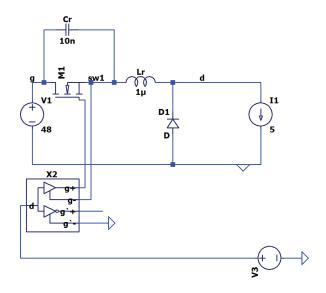

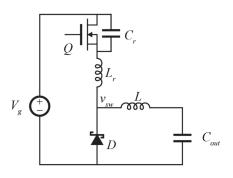


Simulation Results

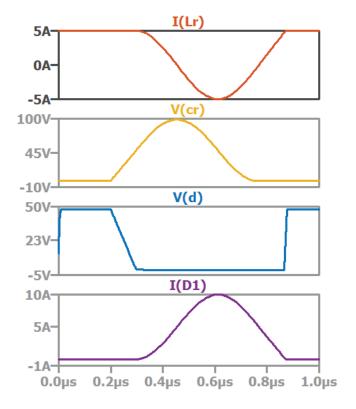





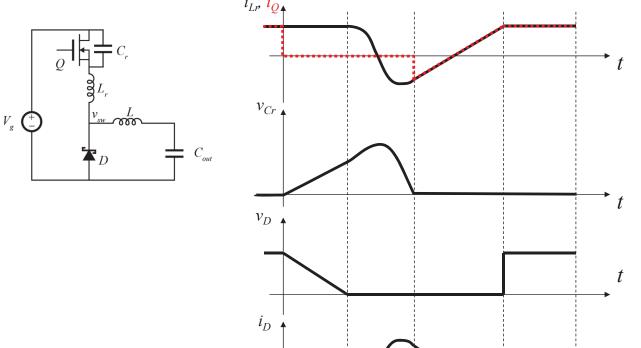Diode Capacitance i_{L_r} $i_{Q\uparrow}$




Simulation Results: Diode Capacitance

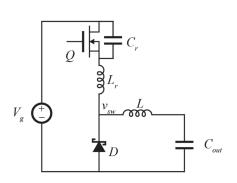

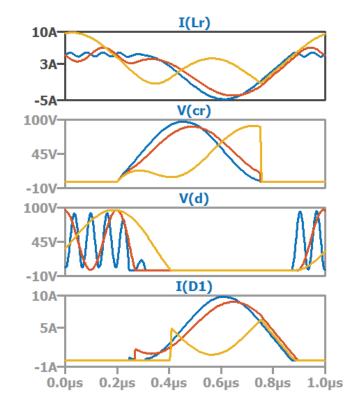


Wishlist: Multi-Resonant

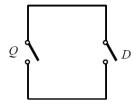



ZVS-MR Buck

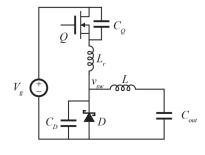

Operating Modes


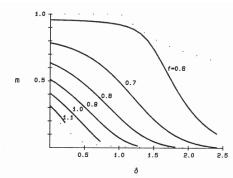


Figure 10.7: Load-to-output DC characteristics of a ZV-MR converter operating in modes (I.II).

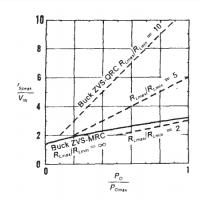

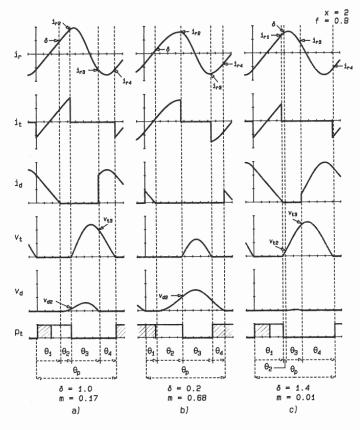



Figure 10.2: Typical waveforms for a ZV-MR converter operating in modes I_1 (a), II_1 (b) or III_1 (c).


D Maksimovic, "Synthesis of PWM and Quasi-Resonant DC-to-DC Power Converters," Ph.D. Thesis, CalTech 1989



\mathbf{T}

Identification of Resonant Switch

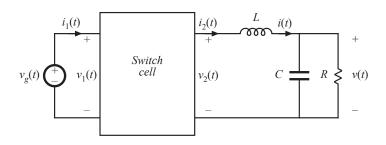

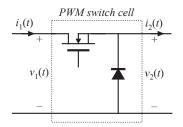

Switching Cell Conversion Ratio

