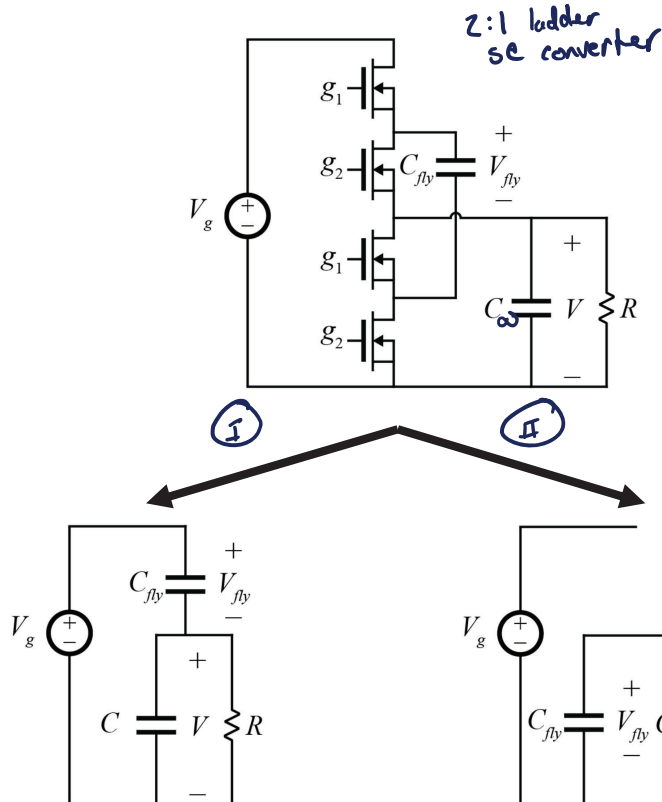


# A 2:1 SC Converter



Assume:

- $V \approx$  constant output voltage
- $f_n \text{ (I) } \neq \text{ (II)}$ ,  $V_{fly}$  reaches a final value before the next switching action

(I)  $V_{fly} = V$

(II)  $V_{fly} = V_g - V$

If  $C_{fly}$  large,  $\Delta V_{fly} \approx 0$

$$V = V_g - V$$


$$2V = V_g$$

$$\frac{V}{V_g} = \frac{1}{2} = M$$

## SC Converters


- Fixed conversion ratio
  - No regulation (except linear) i.e. lossy
- Not lossless, even with ideal elements
- Can be very small, fully integrated
  - Discrete caps can be small & efficient in many applications
  - Integrated on-chip caps much better than on-chip inductors
- **Resonant** versions can reduce loss
- **Hybrid** versions can allow regulation

# Capacitor Charging: Voltage Source

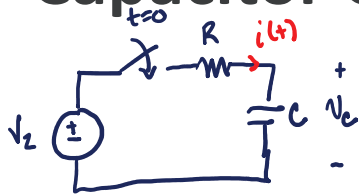

$$V_c(t=0) = V_1$$

$$V_2 > V_1$$

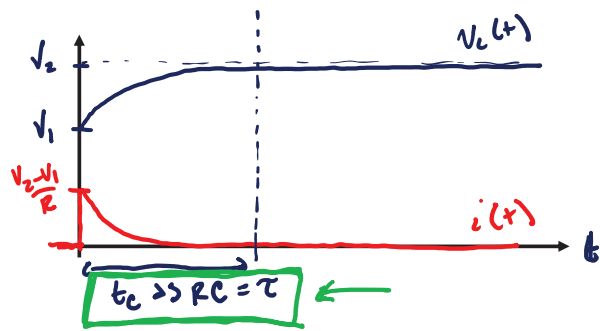

$$\Delta E_c = \frac{1}{2} C V_2^2 - \frac{1}{2} C V_1^2$$

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2)$$

$$\Delta E_v = \int_0^{t_c} V_2 i(t) dt \approx \int_0^{\infty} V_2 i(t) dt = V_2 \underbrace{C (V_2 - V_1)}_{\Delta Q_c}$$

$$\Delta E_v = C V_2 (V_2 - V_1)$$

$$E_{\text{loss}} = \Delta E_v - \Delta E_c = C V_2 (V_2 - V_1) - \frac{1}{2} C (V_2^2 - V_1^2)$$

$$= C V_2^2 - C V_2 V_1 - \frac{1}{2} C V_2^2 + \frac{1}{2} C V_1^2$$

$$= \frac{1}{2} C V_2^2 + \frac{1}{2} C V_1^2 - C V_2 V_1 = \frac{1}{2} C [V_2^2 + V_1^2 - 2 V_2 V_1]$$

$$E_{\text{loss}} = \frac{1}{2} C (V_2 - V_1)^2 = \frac{1}{2} C (\Delta V_c)^2$$

$$\eta = \frac{\Delta E_c}{\Delta E_v} = \frac{\frac{1}{2} C (V_2^2 - V_1^2)}{C V_2 (V_2 - V_1)} = \frac{1}{2} \frac{V_2^2 - (V_2 - \Delta V_c)^2}{V_2 (V_2 - (V_2 - \Delta V_c))}$$

$$\eta = \frac{1}{2} \frac{\cancel{V_2^2} - \cancel{V_2^2} - (\Delta V_c)^2 + 2 V_2 \Delta V_c}{\cancel{V_2^2} - \cancel{V_1^2} + V_2 \Delta V_c}$$

$$= \frac{1}{2} \frac{2 V_2 \Delta V_c - (\Delta V_c)^2}{V_2 \Delta V_c}$$


$$= \frac{1}{2} \left( 2 - \frac{\Delta V_c}{V_2} \right)$$

$$\eta = 1 - \frac{\Delta V_c}{2 V_2}$$

No dependence on R  
except  $t_c \gg RC$

↓  
Slow-switching limit  
(SSL)

# Capacitor Charging: Current Source

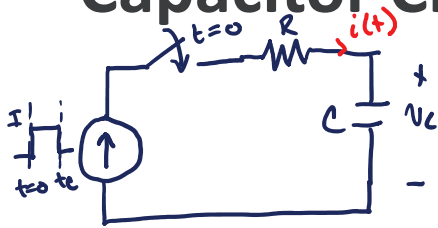

$$v_c(t < 0) = v_1$$

