
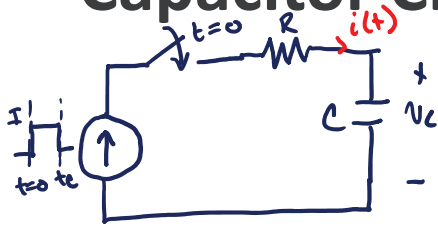


Capacitor Charging: Current Source

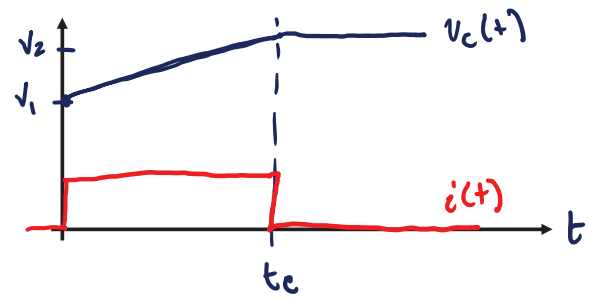

$$v_c(t < 0) = v_1$$



Capacitor Charging: Resonant



Comparison of Capacitor Charging

2:1 SC Revisited

