
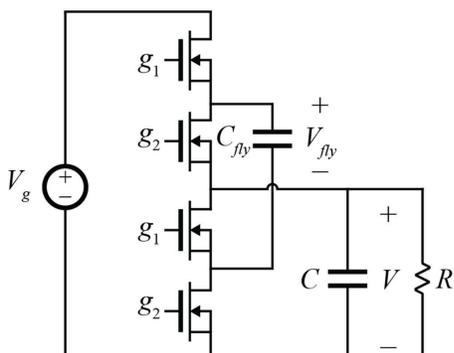


Generalized Equivalent Circuit

2:1 – Current Loaded

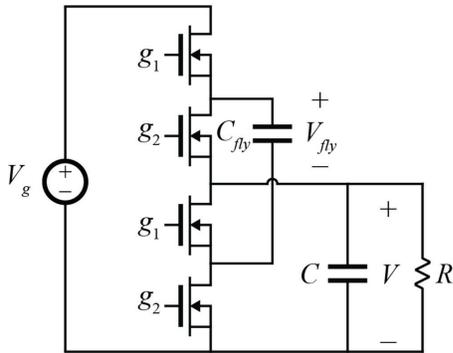

2:1 – Resonant Implementation



Slow and Fast Switching Limits

2:1 SC – FSL Model

SC Converter Topologies

