

Tellegen's Theorem

For any valid circuit (KVL & KCL)

$$\sum_{i \in \text{element}} v_i I_i = 0$$

Voltage across current through

Passive sign convention held everywhere

For our 2-subinterval SC converter:

$$\bar{a}^I \bar{v}^I = 0 \quad \neq \quad \bar{a}^II \bar{v}^II = 0$$

so, $\bar{a}^I \bar{v}^I + \bar{a}^II \bar{v}^II = 0$

$$\underbrace{V_g(a_{in}^I + a_{in}^{II})}_{\text{when testing } R_o = 0} + \bar{a}_c^I \bar{v}_c^I + \bar{a}_c^{II} \bar{v}_c^{II} + V_{out} \underbrace{(a_{out}^I + a_{out}^{II})}_{=1, \text{ by normalization}} = 0$$

SSL Output Resistance

$$\bar{a}_c^I \bar{v}_c^I + \bar{a}_c^{II} \bar{v}_c^{II} = -V_{out}$$

$\bar{a}_c^I = -\bar{a}_c^{II}$, by charge balance in 2-subinterval SC conv.

$$\bar{a}_c^I (\bar{v}_c^I - \bar{v}_c^{II}) = -V_{out}$$

$$\bar{v}_c^I - \bar{v}_c^{II} = \Delta \bar{v}_c \quad \Delta V_{ci} = \frac{g_i}{C_i} \quad \neq \quad a_{ci} = \frac{g_i}{g_{out}}$$

$$-V_{out} = \sum_{i \in \text{caps}} \left(\frac{g_i}{g_{out}} \right) \left(\frac{g_i}{C_i} \right) = \sum_{i \in \text{caps}} \frac{(g_i)^2}{g_{out}} \frac{1}{C_i}$$

$$\frac{-V_{out}}{g_{out} f_s} = \sum_{i \in \text{caps}} (a_{ci})^2 \frac{1}{C_i f_s}$$


$$g_{out} f_s = I_{out}$$

$$\frac{-V_{out}}{I_{out}} = R_o = \sum_{i \in \text{caps}} \frac{(a_{ci})^2}{C_i f_s}$$

for 2-subinterval SC converters


$$\boxed{R_{o,ssl} = \sum_{i \in \text{caps}} \frac{(a_{ci})^2}{C_i f_s}}$$

Output Resistance

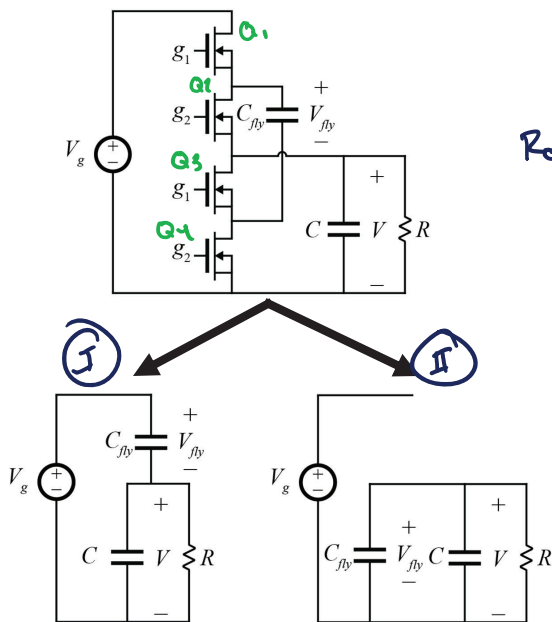

$$\bar{a}^I = \begin{bmatrix} -\frac{1}{2} & \frac{1}{2} & \frac{1}{2} \end{bmatrix} \quad \bar{a}^{II} = \begin{bmatrix} 0 & \frac{1}{2} & \frac{1}{2} \end{bmatrix}$$
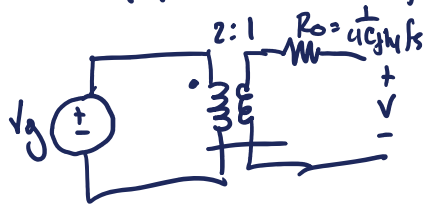
$$R_{o,ssL} = \sum_{i=1}^1 \frac{(a_{ci})^2}{C_i f_s} = \frac{(1/2)^2}{C_{jfy} f_s} = \frac{1}{4C_{jfy} f_s}$$




$$\bar{a}_r = \begin{bmatrix} 1/2 & 1/2 & 1/2 & 1/2 \\ g_1 & g_2 & g_3 & g_4 \end{bmatrix}$$

$$R_{o,FSL} = \sum_{i=trans} (a_{ri})^2 \cdot 2R_{on,i}$$

if all $R_{on,i}$ are the same

$$R_{o,FSL} = 2R_{on}$$

Dickson Charge Vector Analysis

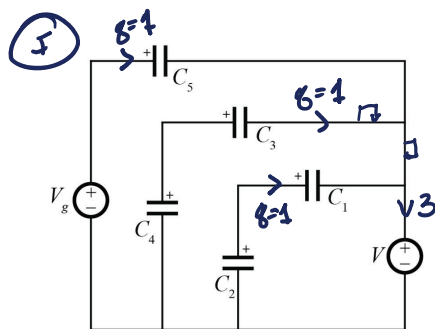


$$\bar{a}^I = \begin{bmatrix} -1 & 1 & -1 & 1 & -1 & 1 & 3 \\ i_n & q_1 & q_2 & q_3 & q_4 & q_5 & out \end{bmatrix} / g_{out}$$

$$\bar{a}^I = \begin{bmatrix} -1/6 & 1/6 & -1/6 & 1/6 & -1/6 & 1/6 & 1/2 \end{bmatrix}$$

$$\bar{a}^{II} = \begin{bmatrix} 0 & -1 & 1 & -1 & 1 & -1 & 3 \end{bmatrix} / g_{out}$$
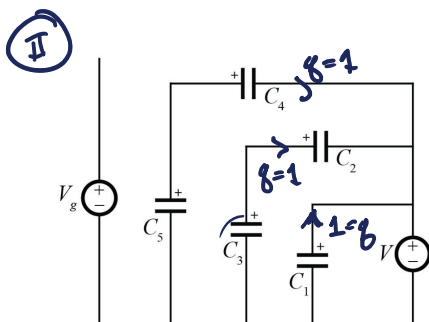
$$\bar{a}^{II} = \begin{bmatrix} 0 & -1/6 & 1/6 & -1/6 & 1/6 & -1/6 & 1/2 \end{bmatrix}$$



$$g_{out} = g_{out}^I + g_{out}^{II} = 6$$

$$g_{in} = -1/6$$

$$g_{out} = 1$$

$$M = \frac{1}{6} = \frac{g_{in}}{g_{out}} = \frac{V_{out}}{V_g}$$



Dickson Output Resistance

$$R_{o,ssl} = \sum_{i \in caps} \frac{(a_{ci})^2}{C_i f_s}$$

Assume all $C_i = C_{fH}$

$$R_{o,ssl} = 5 \frac{(1/6)^2}{C_{fH} f_s} = \boxed{\frac{5}{36} \frac{1}{C_{fH} f_s} = R_{o,ssl}}$$

Charge Vector Analysis in ESL

$$\bar{a}_r = \frac{\bar{q}_r}{q_{out}}$$

where q_{ri} is the charge flowing through transistor i when it is conducting

No superscript because each transistor only conducts in one interval

Find \bar{a}_r by inspection a) some linear combination $\bar{a}_c \neq \bar{a}_c^T$

i_{ri} = transistor current when conducting

$$i_{ri} = q_{ri} \cdot \frac{2}{T_s}$$

assume 2-subinterval SC converter @ $D=50\%$

$$P_{ri} = (i_{ri})^2 R_{on,i} \cdot \left(\frac{1}{2}\right)$$

$$i_{ri} = a_{ri} q_{out} \frac{2}{T_s}$$

$$P_{ri} = \left(a_{ri} q_{out} \frac{2}{T_s}\right)^2 R_{on,i} \left(\frac{1}{2}\right) = (a_{ri})^2 q_{out}^2 f_s^2 \cdot 2 \cdot R_{on,i}$$

$$P_{ri} = I_{out}^2 (a_{ri})^2 \cdot 2 R_{on,i}$$

Doesn't include ESR or other resistances

$$R_{o,ESL} = \sum_{i \in transistors} (a_{ri})^2 \cdot 2 R_{on,i}$$