


Dickson Output Resistance

$$R_{o,ssl} = \sum_{i \in caps} \frac{(aci)^2}{c_i f_s}$$

Assume all $c_i = C_{f14}$


$$R_{o,ssl} = 5 \cdot \frac{(1/6)^2}{C_{f14} f_s} = \boxed{\frac{5}{36} \cdot \frac{1}{C_{f14} f_s} = R_{o,ssl}}$$

6:1 Dickson Converter Simulation

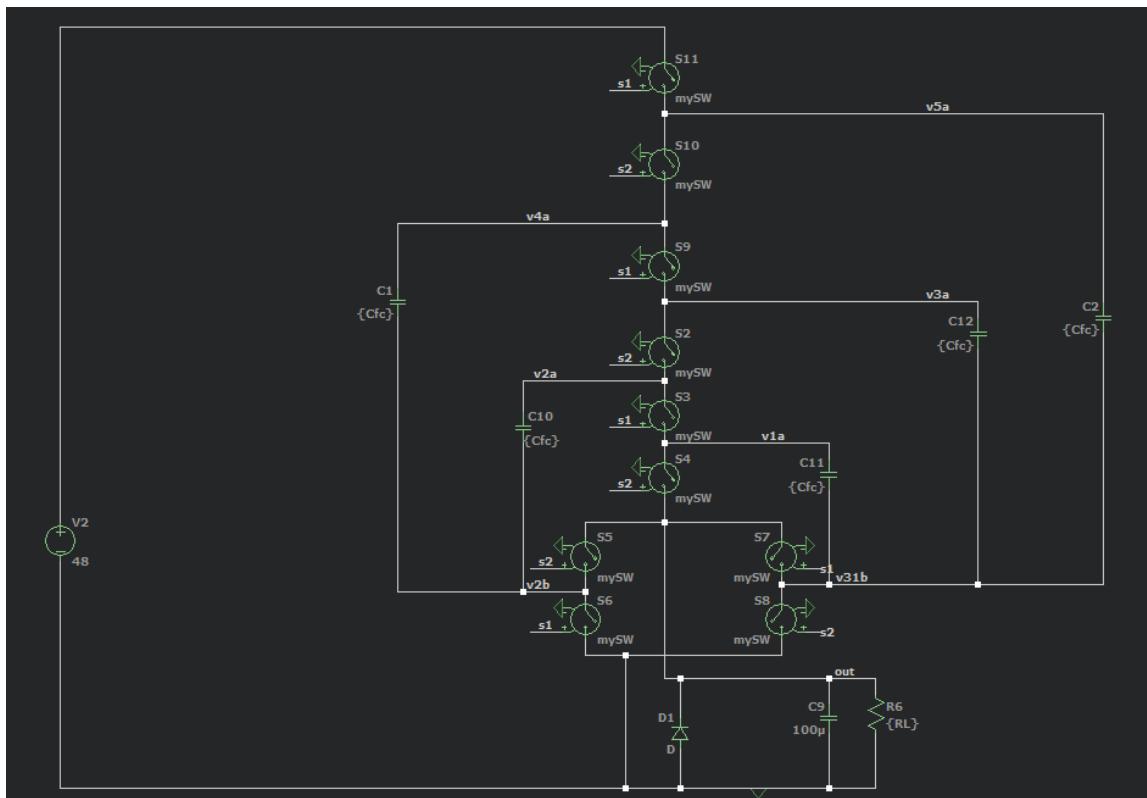


Simulation Comparison to Model

fixed $f_s = 1\text{MHz}$

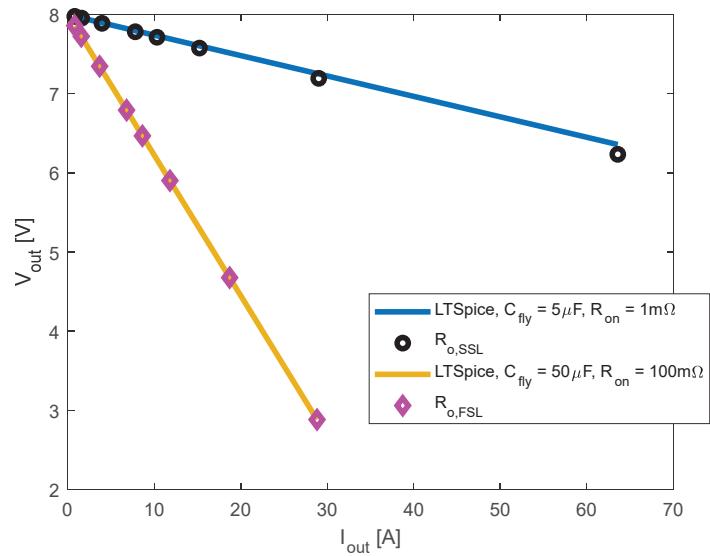

R_o vs Switching Frequency


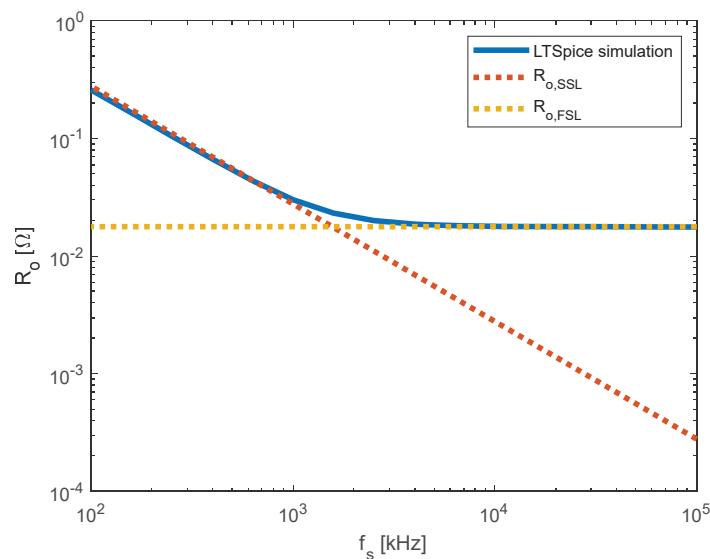
fixed $R_{on} = 10\text{m}\Omega$, $C_{fly} = 5\mu\text{F}$





Switching Losses in SC Converters



Hybrid Dickson converter

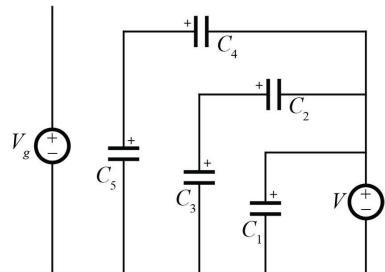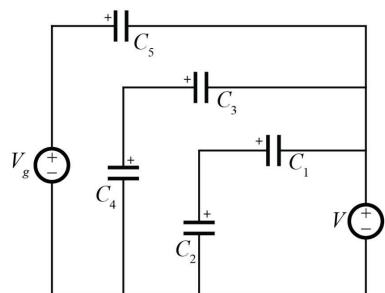

Split-Phase Control

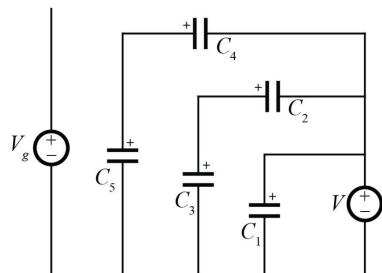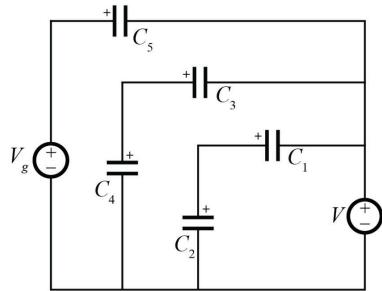

Y. Lei, R. May, and R. Pilawa-Podgurski, "Split-Phase Control: Achieving Complete Soft-Charging Operation of a Dickson Switched-Capacitor Converter," 2016



LTSpice Simulation

