

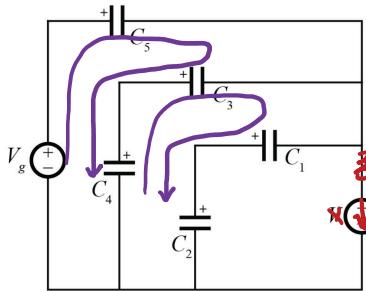


Hybrid Dickson converter

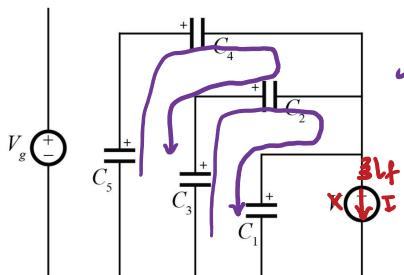

In either subinterval, DC solution is

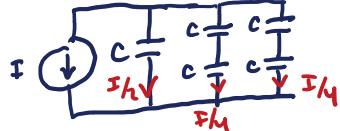

However, there are also pure V-C loops. If any current flows in the V-C loops, there will still be charge-sharing loss.

Assume current is only I_{out} DC solution:



$$\bar{\alpha}^I = \begin{bmatrix} -\frac{1}{4} & \frac{1}{8} & \frac{1}{8} & \frac{1}{8} & \frac{1}{4} & \frac{1}{2} \end{bmatrix} \begin{matrix} I_{out} T_3 \\ I_{out} T_3 \end{matrix}$$

in C_1 C_2 C_3 C_4 C_5 out


$$\bar{\alpha}^{II} = \begin{bmatrix} \emptyset & -\frac{1}{4} & \frac{1}{8} & \frac{1}{8} & \frac{1}{8} & \frac{1}{2} \end{bmatrix}$$



Split-Phase Control

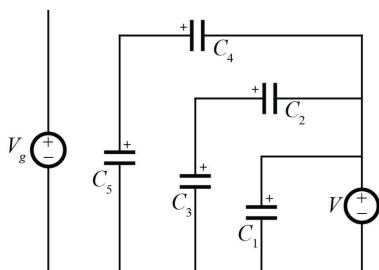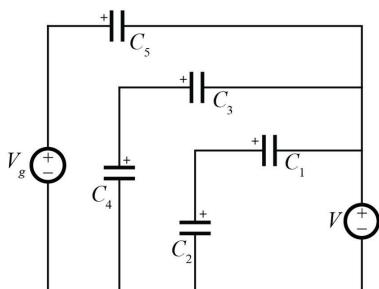

LTSlice Simulation

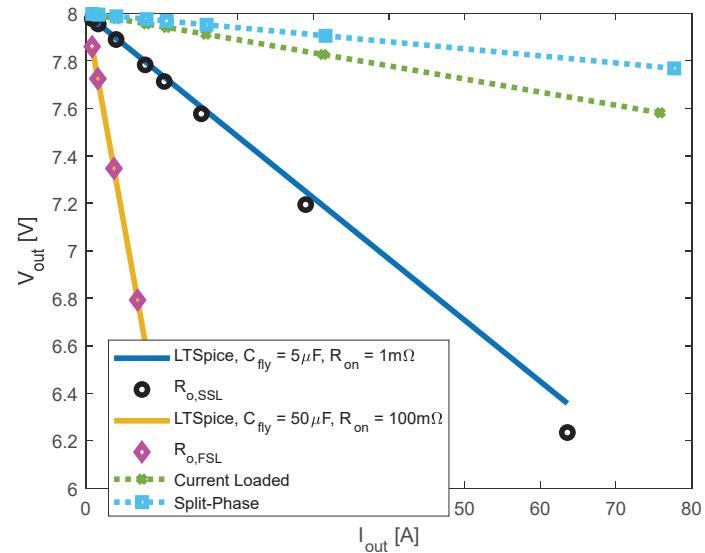

Switching Losses in SC Converters