Announcements

- HW9 posted
- PCBs ordered for all planning to complete the design challenge
- TNvoice available
 - https://utk.campuslabs.com/eval-home/
 - Currently, 1/6 completed
 - Closes 12/1



The Averaged System

This equation is now the model of a new, equivalent linear system

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$

where


$$A = DA_1 + D'A_2$$
$$B = DB_1 + D'B_2$$


which has averaged behavior over one switching period

This approximation is perhaps valid, if

- State waveforms are dominantly linear
- Dynamics of interest are at $f_{bw} \ll f_s$

Buck State Space Averaging

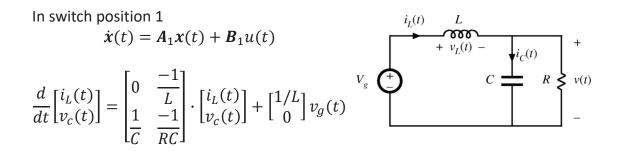

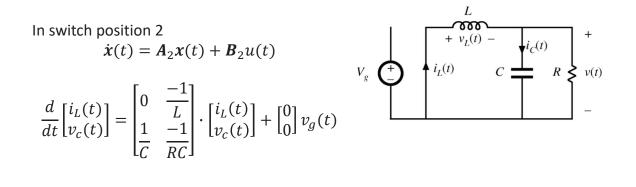


TENNESSEE KNOXVILLE

Buck Averaged Model

So, our average model is


$$\begin{split} \langle \dot{\mathbf{x}}(t) \rangle &= (DA_1 + D'A_2) \langle \mathbf{x}(t) \rangle + (DB_1 + D'B_2) \langle u(t) \rangle \\ \langle \dot{\mathbf{x}}(t) \rangle &= \left(D \begin{bmatrix} 0 & -1 \\ 1 & -1 \\ c & Rc \end{bmatrix} + D' \begin{bmatrix} 0 & -1 \\ 1 & -1 \\ c & Rc \end{bmatrix} \right) \langle \mathbf{x}(t) \rangle + \left(D \begin{bmatrix} 1/L \\ 0 \end{bmatrix} + D' \begin{bmatrix} 0 \\ 0 \end{bmatrix} \right) V_g \\ \langle \dot{\mathbf{x}}(t) \rangle &= \begin{bmatrix} 0 & -1 \\ 1 & -1 \\ c & Rc \end{bmatrix} \langle \mathbf{x}(t) \rangle + \begin{bmatrix} D/L \\ 0 \end{bmatrix} V_g \\ \\ \text{Longe-signul} \quad \left(\text{sheadly-the} \right) \\ \begin{cases} DV_g - \langle v_c(t) \rangle = L \frac{d\langle i_L(t) \rangle}{dt} = \mathcal{A} & \text{vertex} \\ \langle i_L(t) \rangle - \frac{\langle v_c(t) \rangle}{R} = C \frac{d\langle v_c(t) \rangle}{dt} = \mathcal{A} & \text{J}_L = \frac{V}{R} \end{cases}$$

Averaging: Discussion

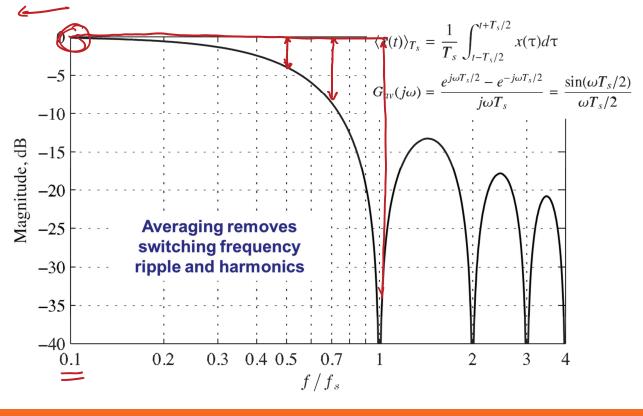


TENNESSEE KNOXVILLE

Discrete Time Nature of PWM

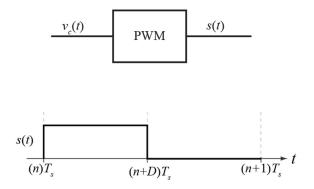




Discrete Time Nature of PWM

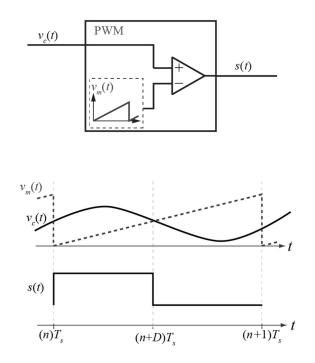



Discrete Time Nature of PWM

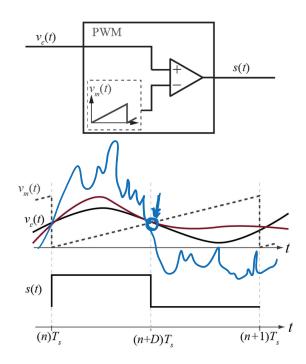



Historical Perspective



Robert D Middlebrook

PhD, Standford, 1955 CalTech Professor, 1955-1998

Slobodan Cúk PhD CalTech, 1976 CalTech Prof, 1977-1999



Modelling, analysis, and design of switching converters

Model a switched system as an averaged, time-invariant system with

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$

where

 $A = DA_1 + D'A_2$ $B = DB_1 + D'B_2$

Discrete modeling and analysis of switching regulators

Dennis John Packard

PhD, CalTech 1976

Model a switched system as a discrete-time system with

$$\boldsymbol{x}[n+1] = \boldsymbol{\Phi}\boldsymbol{x}[n] + \boldsymbol{\Psi}\boldsymbol{U}[n]$$


where

$$\boldsymbol{\Phi} = \left(\prod_{i=n_{sw}}^{1} e^{A_{i}t_{i}}\right)$$
$$\boldsymbol{\Psi} = \sum_{i=1}^{n_{sw}} \left\{ \left(\prod_{k=n_{sw}}^{i+1} e^{A_{k}t_{k}}\right) A_{i}^{-1} (e^{A_{i}t_{i}} - \boldsymbol{I}) \boldsymbol{B}_{i} \right\}$$

A. R. Brown and R. D. Middlebrook, "Sampled-data Modeling of Switching Regulators" PESC 1981

TENNESSEE TENNESSEE

Large Signal Modeling of SMPS

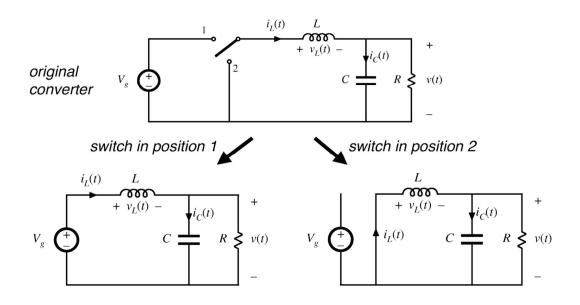

Discrete Time Modeling

- Every subcircuit is a passive, linear circuit
- Passive, linear circuits can be solved in closedform
 - Can model states at discrete times without averaging
- Only assumptions required
 - Independent inputs are DC or slowly varying

TENNESSEE KNOXVILLE

Solution to State Space Equation

Closed form solution to state space equation

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$

Multiply both sides by e^{-At}

$$e^{-At}\dot{\boldsymbol{x}}(t) - e^{-At}\boldsymbol{A}\boldsymbol{x}(t) = e^{-At}\boldsymbol{B}\boldsymbol{u}(t)$$

Left-hand side is

$$\frac{d}{dt} \left(e^{-At} \boldsymbol{x}(t) \right) = e^{-At} \boldsymbol{B} u(t)$$

Solution to State Space Equation

$$\frac{d}{dt} \left(e^{-At} \boldsymbol{x}(t) \right) = e^{-At} \boldsymbol{B} u(t)$$

Can now be solved by direct integration

$$e^{-At}\boldsymbol{x}(t) - \boldsymbol{x}(0) = \int_{0}^{t} e^{-A\tau} \boldsymbol{B} u(\tau) \, d\tau$$

Rearranging

ing
Natural response

$$x(t) = e^{At}x(0) + \int_{0}^{t} e^{-A(t-\tau)}Bu(\tau) d\tau$$

$$convolution$$
integral


TENNESSEE

Matrix Exponential

Matrix exponential defined by Taylor series expansion

$$e^{At} = I + At + \frac{(At)^2}{2!} + \dots + \frac{(At)^N}{N!} = \sum_{k=0}^N \frac{(At)^k}{k!}$$

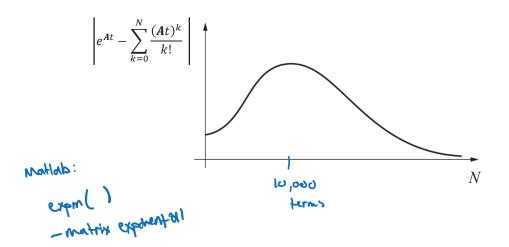Well-known issue with convergence in many cases





Properties of the Matrix Exponential


- Matrix exponential always exists
 - i.e. summation will always converge
- Exponential of any matrix is always invertible, with

$$e^A e^{-A} = I$$

TENNESSEE KNOXVILLE

First Order Taylor Series Expansion

Linear ripple approximation

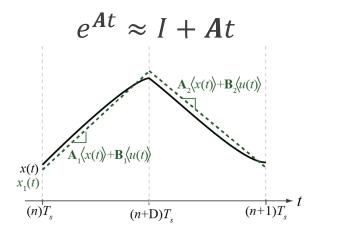

Valid only if switching frequency much faster than system modes

Simplification for Slow-Varying Inputs


$$\boldsymbol{x}(t) = e^{At}\boldsymbol{x}(0) + \int_{0}^{t} e^{-A(t-\tau)}\boldsymbol{B}\boldsymbol{u}(\tau) \, d\tau$$

If A is invertible and $u(\tau) \approx U$

$$\boldsymbol{x}(t) = e^{At}\boldsymbol{x}(0) + A^{-1}(e^{At} - \boldsymbol{I})\boldsymbol{B}\boldsymbol{U}$$


TENNESSEE KNOXVILLE

Application to Switching Converter

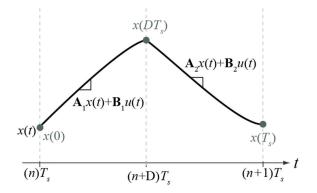




Application to Switching Converter

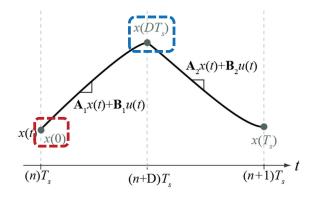




Application to Switching Converter

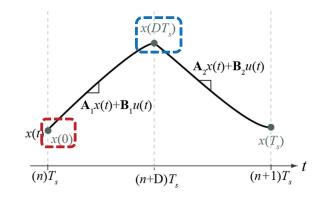

 $\mathbf{x}(DT_{s}) = e^{A_{1}DT_{s}}\mathbf{x}(0) + A_{1}^{-1}(e^{A_{1}DT_{s}} - I)B_{1}U$



Application to Switching Converter

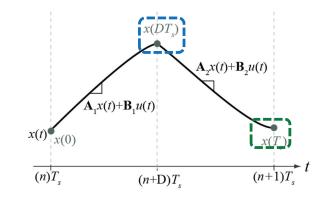


 $\mathbf{x}(DT_{s}) = e^{A_{1}DT_{s}}\mathbf{x}(0) + A_{1}^{-1}(e^{A_{1}DT_{s}} - \mathbf{I})B_{1}U$

 $\mathbf{x}(T_{s}) = e^{A_{2}D'T_{s}}\mathbf{x}(DT_{s}) + A_{2}^{-1}(e^{A_{2}D'T_{s}} - I)B_{2}U$

TENNESSEE KNOXVILLE

Application to Switching Converter

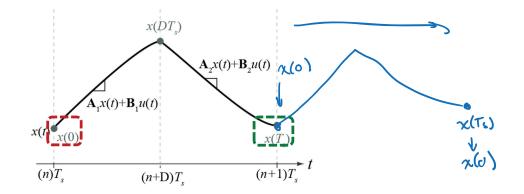

 $\boldsymbol{x}(DT_{s}) = e^{A_{1}DT_{s}}\boldsymbol{x}(0) + A_{1}^{-1}(e^{A_{1}DT_{s}} - \boldsymbol{I})\boldsymbol{B}_{1}\boldsymbol{U}$

$$\boldsymbol{x}(T_{s}) = e^{A_{2}D'T_{s}}\boldsymbol{x}(DT_{s}) + A_{2}^{-1}(e^{A_{2}D'T_{s}} - \boldsymbol{I})\boldsymbol{B}_{2}\boldsymbol{U}$$

 $\mathbf{x}(T_s) = e^{A_2 D' T_s} e^{A_1 D T_s} \mathbf{x}(0) + A_2^{-1} (e^{A_2 D' T_s} - \mathbf{I}) \mathbf{B}_2 U + e^{A_2 D' T_s} A_1^{-1} (e^{A_1 D T_s} - \mathbf{I}) \mathbf{B}_1 U$

General Form

Generally, for n_{sw} separate switching positions

$$\mathbf{x}(T_{s}) = \left(\prod_{i=n_{sw}}^{1} e^{A_{i}t_{i}}\right) \mathbf{x}(0) + \sum_{i=1}^{n_{sw}} \left\{ \left(\prod_{k=n_{sw}}^{i+1} e^{A_{k}t_{k}}\right) A_{i}^{-1}(e^{A_{i}t_{i}} - I) B_{i} \right\} U$$

Equation is in the form of a discrete-time system with
$$\mathbf{x}[n+1] = \mathbf{\Phi}\mathbf{x}[n] + \mathbf{\Psi}U[n] \leftarrow \mathsf{LTE} \quad \mathsf{DT} \text{ system}$$

Again, the effect of changing modulation (i.e. t_i) is hidden in nonlinear terms

$$\widehat{\boldsymbol{x}}[n+1] = \boldsymbol{\Phi}\widehat{\boldsymbol{x}}[n] + \boldsymbol{\Psi}\widehat{\boldsymbol{u}}[n] + \boldsymbol{\Gamma}\widehat{\boldsymbol{d}}[n]$$

Find Γ by small-signal modeling

THE UNIVERSITY OF TENNESSEE

Aside: Comparison to Averaged Modeling

$$\boldsymbol{x}(T_{s}) = \left(\prod_{i=n_{sW}}^{1} e^{A_{i}t_{i}}\right)\boldsymbol{x}(0) + \sum_{i=1}^{n_{sW}} \left\{ \left(\prod_{k=n_{sW}}^{i+1} e^{A_{k}t_{k}}\right)A_{i}^{-1}(e^{A_{i}t_{i}} - \boldsymbol{I})\boldsymbol{B}_{i} \right\} U$$
Approximate with straight-line waveforms, $e^{At} \approx \boldsymbol{I} + At$

$$\boldsymbol{x}(T_{s}) = \left(\boldsymbol{I} + \sum_{i=n_{sW}}^{1} A_{i}t_{i} + \cdots \right)\boldsymbol{x}(0) + \sum_{i=1}^{n_{sW}} \left\{ \left(\boldsymbol{I} + \sum_{k=n_{sW}}^{i+1} A_{k}t_{k} + \cdots \right)t_{i}\boldsymbol{B}_{i} \right\} U$$

Neglect all terms with product of two ore more t_i

$$x(T_s) = \left(I + \sum_{i=1}^{n_{SW}} A_i t_i\right) x(0) + \sum_{i=1}^{n_{SW}} (t_i B_i) U$$

Continuous time conversion
$$\dot{x}_{DT}(t) = \frac{x(T_s) - x(0)}{T_s} = \sum_{i=1}^{n_{SW}} \left(A_i \frac{t_i}{T_s}\right) x + \sum_{i=1}^{n_{SW}} \left(B_i \frac{t_i}{T_s}\right) U$$



Aside: Discrete vs Averaged Modeling

So, averaged and discrete time formulations are equivalent if

- Ripple in states is
 - 1. Dominantly straight-line, so $e^{A_i t_i} \approx (I + A_i t_i)$
 - 2. Low frequency, such that $t_i t_j \ll \left\| \boldsymbol{A}_i \boldsymbol{A}_j \right\|$

