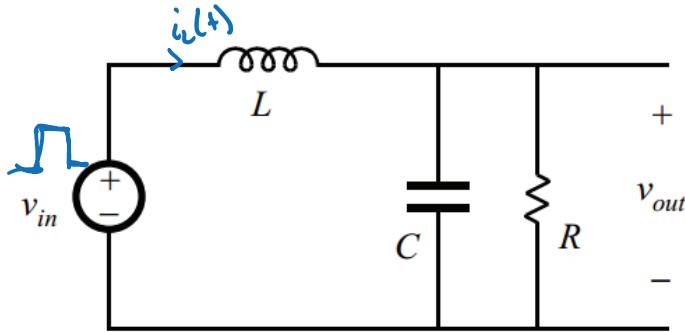


Resonant Circuits



ECE481:
 $i_L(t) \approx I_L$
 $v_C(t) \approx V$

} X does not generally apply


↓ transient analysis

$$LC \frac{d^2v_{out}}{dt^2} + \frac{L}{R} \frac{dv_{out}}{dt} + (V_{out} - V_{in}) = 0$$

} (will develop new techniques in class)






Resonant Circuit Analysis

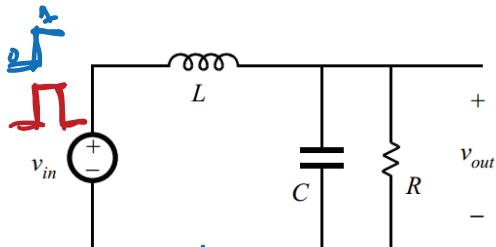

$$||H(s)|| = \frac{V_{out}}{V_{in}} = \frac{1}{s^2LC + sR^2 + 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



$$R_0 = \sqrt{\frac{L}{C}}$$

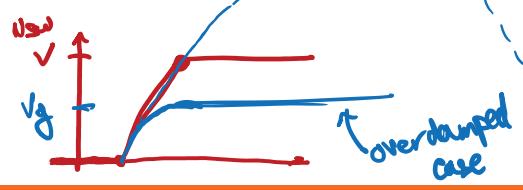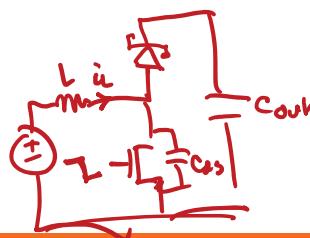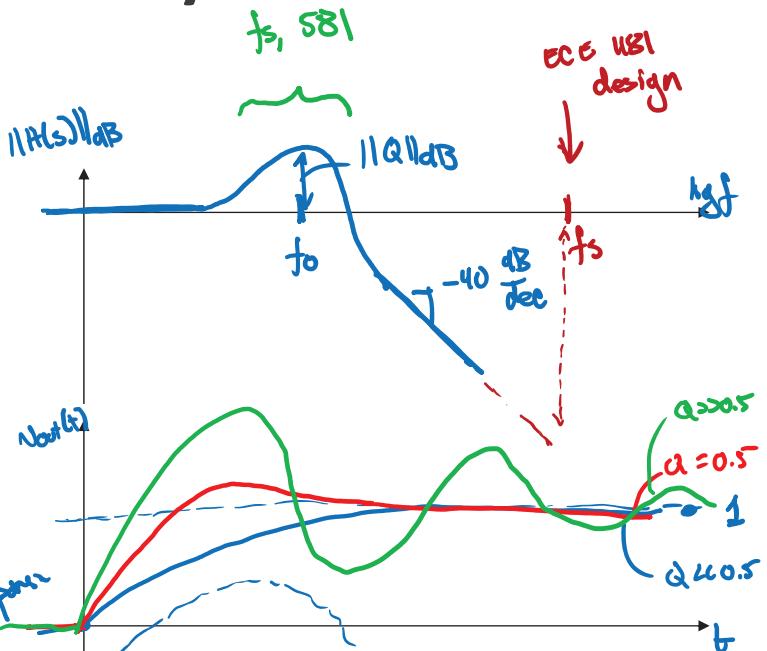


Soft Switching

- Advantages
 - Reduced switching loss
 - Possible operation at higher switching frequency
 - Lower EMI
- Disadvantages
 - Increased current and/or voltage stresses due to circulating current
 - Higher peak and rms current values
 - Complexity of analysis and modeling

Limitations: Gate Drive


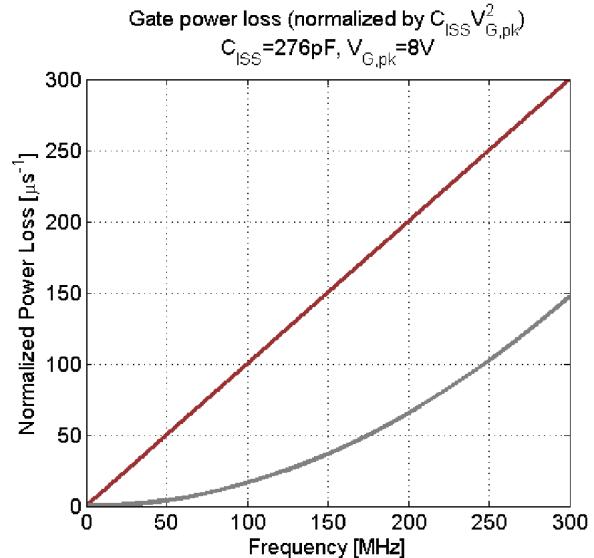
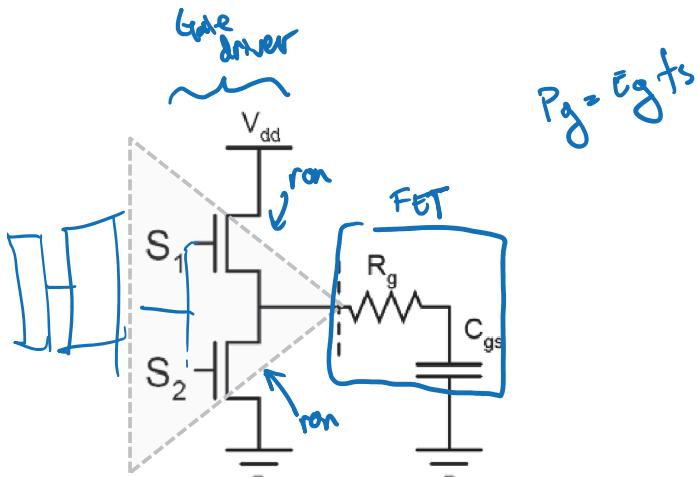


Limitations: t_d/T_s


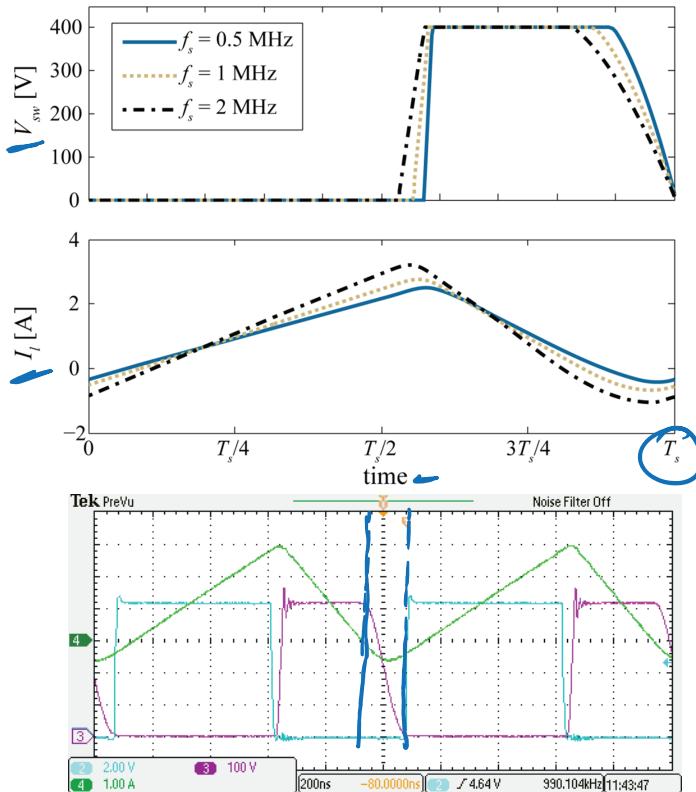


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Limitations: Thermal

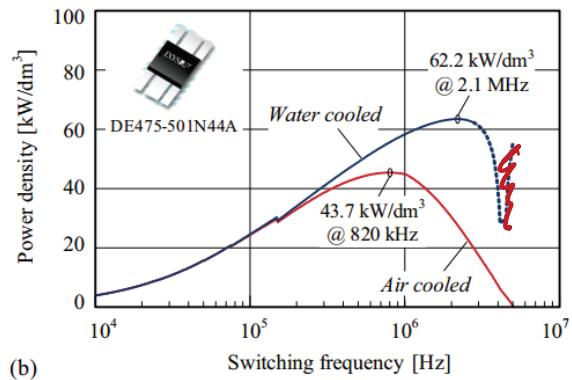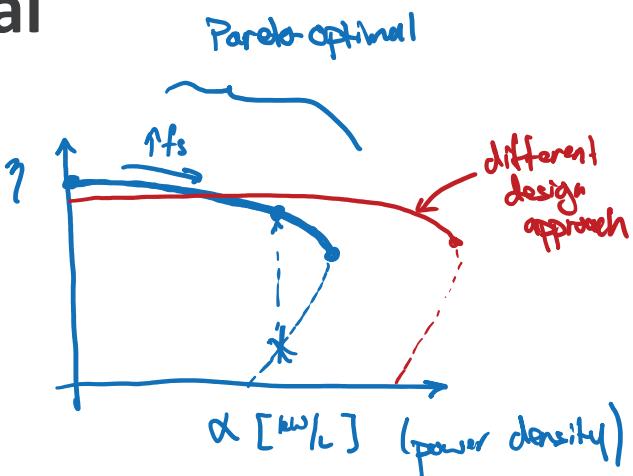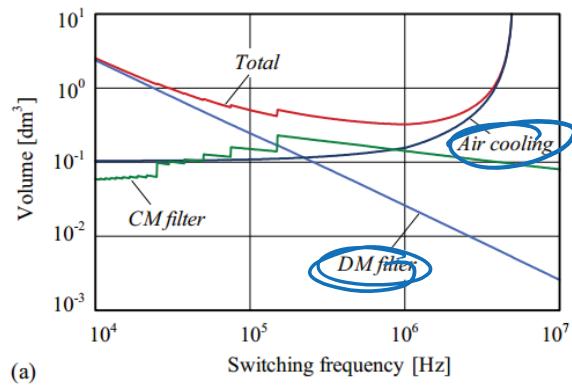

Limitations: Magnetics Design

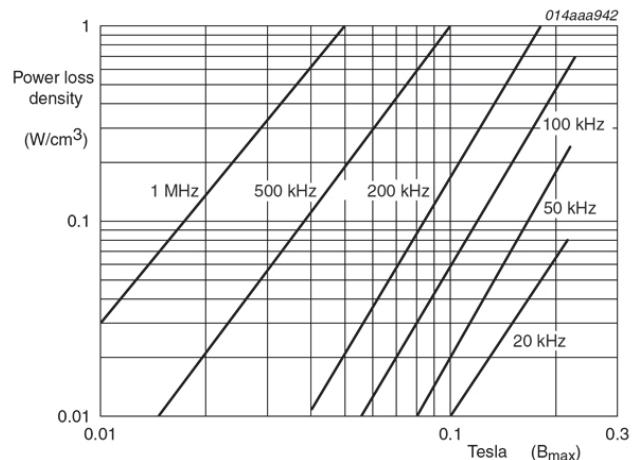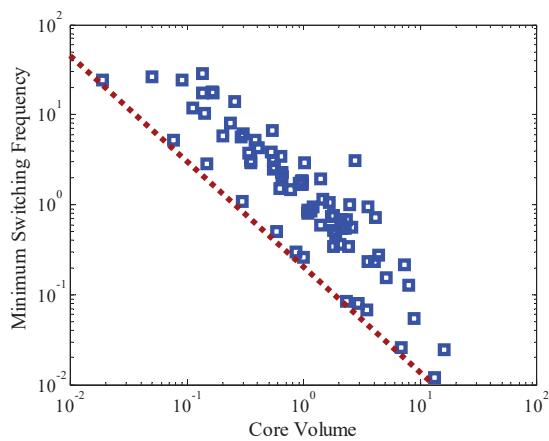

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Limitations: Circuit Modeling

