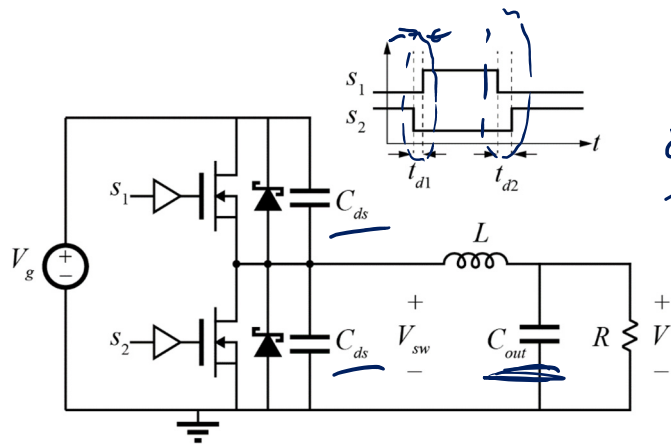



# Time-Domain Analysis of Switching Transitions

(1) Assume  $C_{out}$  is a filter element with small ripple







(2) Assume  $C_{ds}$  is linear




during dead time

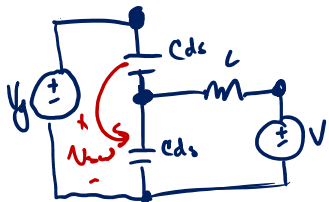

ac-equivalent

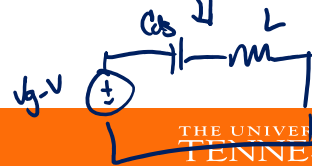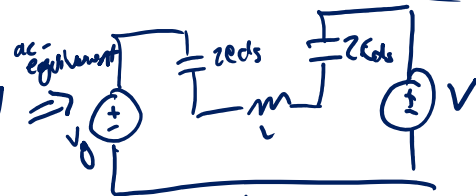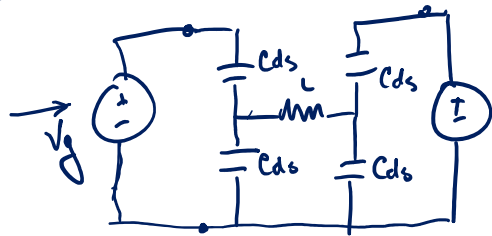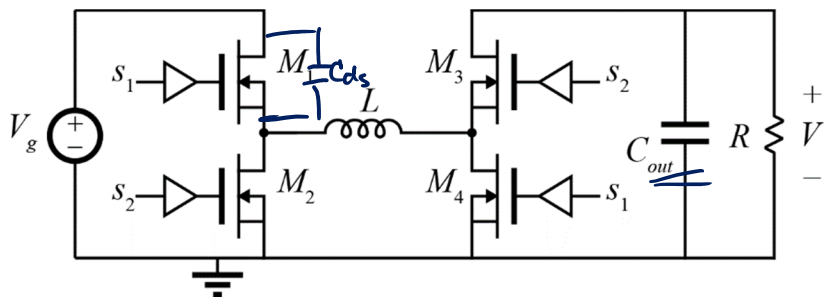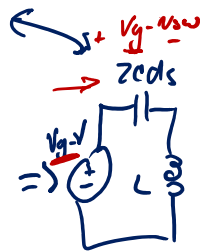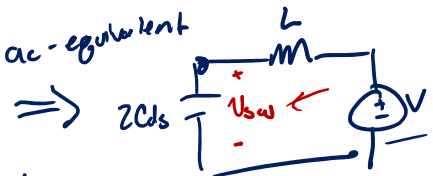

# Resonant Circuit Solution

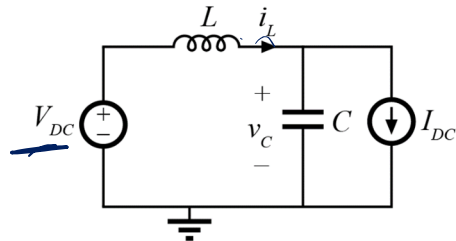

Initial Conditions:

$$v_C(t=0) = V_0$$

$$i_L(t=0) = I_0$$

$$\left. \begin{array}{l} \textcircled{1} \quad C \frac{di_L}{dt} = i_L - I_{DC} \\ \textcircled{2} \quad L \frac{dv_C}{dt} = V_{DC} - v_C \end{array} \right\} \rightarrow L \frac{d}{dt} \left( C \frac{di_L}{dt} + I_{DC} \right) = V_{DC} - v_C$$

$$= LC \frac{d^2 v_C}{dt^2} + v_C - V_{DC} = 0$$

$$v_C = \begin{cases} A \sin(\omega t) + B \cos(\omega t), & \text{homogeneous} \\ \underline{v_C = V_{DC}}, & \text{particular} \end{cases}$$

$$v_C(t) = V_{DC} + \underbrace{(V_0 - V_{DC})}_{\cos} \left( \frac{t}{\sqrt{LC}} \right) + \underbrace{(I_0 - I_{DC})}_{\sqrt{\frac{L}{C}} \sin} \left( \frac{t}{\sqrt{LC}} \right)$$

$$i_L(t) = I_{DC} + \underbrace{(I_0 - I_{DC})}_{\cos} \left( \frac{t}{\sqrt{LC}} \right) + \underbrace{(V_{DC} - V_0)}_{\sqrt{\frac{C}{L}} \sin} \left( \frac{t}{\sqrt{LC}} \right)$$

# Normalization and Notation

Notation:  $\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$        $R_0 = \sqrt{L/C}$

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0}(V_{DC} - V_0) \sin(\omega_0 t)$$

Normalization:

$$m(t) = \frac{v(t)}{V_{base}}$$

$V_{base} \rightarrow$  anything you want (constant)  
(some choices better than others)

$\rightarrow j(t) = \frac{i(t)}{I_{base}}$

$$I_{base} = \frac{V_{base}}{R_0}$$

$\theta = \omega_0 t$

$$V_{base} = V_{pc}$$

$$I_{base} = \frac{V_{pc}}{R_0}$$

$$\begin{cases} v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t) \\ i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0}(V_{DC} - V_0) \sin(\omega_0 t) \end{cases}$$

$$R_0 \frac{I_0 - I_{DC}}{V_{pc}} = (J_0 - J_{pc})$$

$$\begin{cases} m_c(\theta) = \frac{v_c(t)}{V_{pc}} = M_{pc} + \underbrace{(M_0 - M_{pc})}_{A} \cos \theta + \underbrace{R_0 \frac{I_0 - I_{DC}}{V_{pc}}}_{B} \sin \theta \\ j_c(\theta) = \frac{i_L(t)}{I_{base}} = \frac{i_L(t)}{V_c/R_0} = J_{pc} + \underbrace{(J_0 - J_{pc})}_{B} \cos \theta + \underbrace{(M_{pc} - M_0)}_{A} \sin \theta \end{cases}$$

$$(M_{pc} = 1)$$

$$A = M_0 - M_{pc}$$

$$B = J_0 - J_{pc}$$

$$\begin{cases} m_c(\theta) = M_{pc} + A \cos \theta + B \sin \theta \\ j_c(\theta) = J_{pc} + B \cos \theta - A \sin \theta \end{cases}$$

Try looking at  $(m_c(\theta) - M_{pc})^2 + (j_c(\theta) - J_{pc})^2 =$

$$= A^2 \cos^2 \theta + B^2 \sin^2 \theta + \cancel{2AB \cos \theta \sin \theta} + B^2 \cos^2 \theta + A^2 \sin^2 \theta - \cancel{2AB \cos \theta \sin \theta}$$

$$= A^2 (\cos^2 \theta + \sin^2 \theta) + B^2 (\sin^2 \theta + \cos^2 \theta)$$

$$= A^2 + B^2 = (M_0 - M_{pc})^2 + (J_0 - J_{pc})^2$$


$$(m_c(\theta) - m_{pc})^2 + (j_c(\theta) - j_{pc})^2 = (m_0 - m_{pc})^2 + (j_0 - j_{pc})^2$$

This is the equation for a circle

$$x^2 + y^2 = r^2$$

$$r = \sqrt{(m_0 - m_{pc})^2 + (j_0 - j_{pc})^2}$$

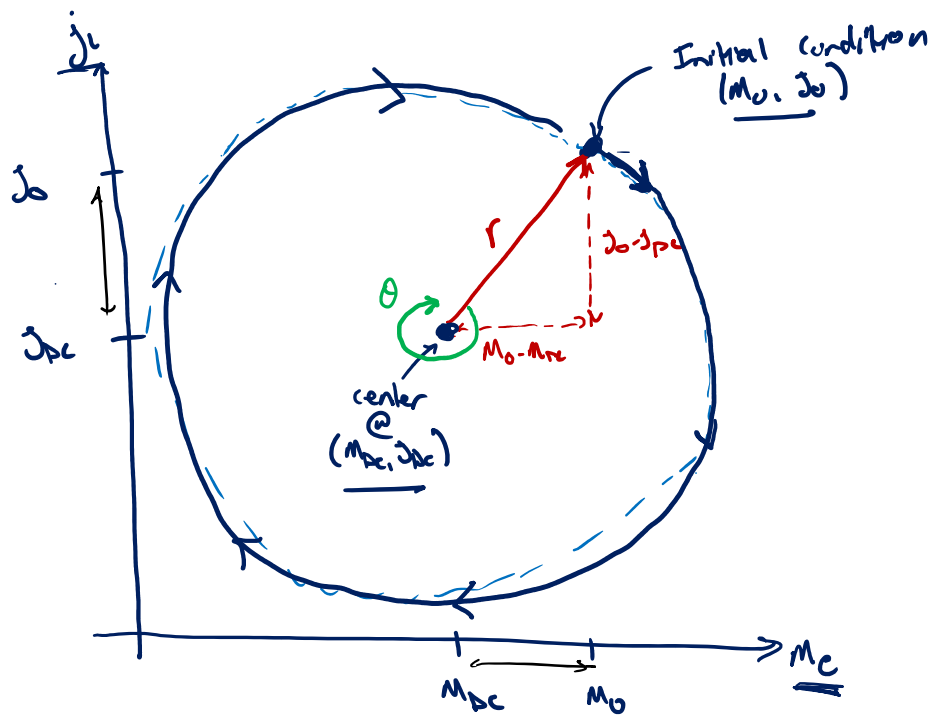
Is a defined direction associated with the state plane  
 - Defined by I.C. on first derivatives of  $j_c$  &  $m_c$



State Plane

- Transforms diff Eq solution into trig solution
- Limited to 1-L, 1-C subcircuits

# State Plane Analysis

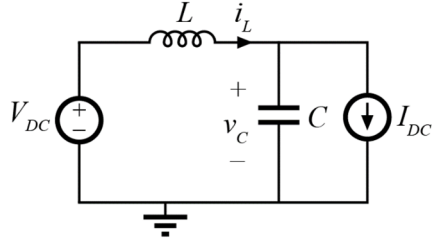

$$V_{base} = \underline{\hspace{2cm}}$$

$$I_{base} = \frac{V_{base}}{R_D}$$

DC solution:

$$V_C = V_{DC} \rightarrow m_c = M_{PC}$$


$$i_L = I_{DC} \rightarrow j_c = J_{PC}$$

Initial conditions:

$$V_C(0) = V_0 \rightarrow m_c = M_0$$

$$i_L(0) = I_0 \rightarrow j_c = J_0$$

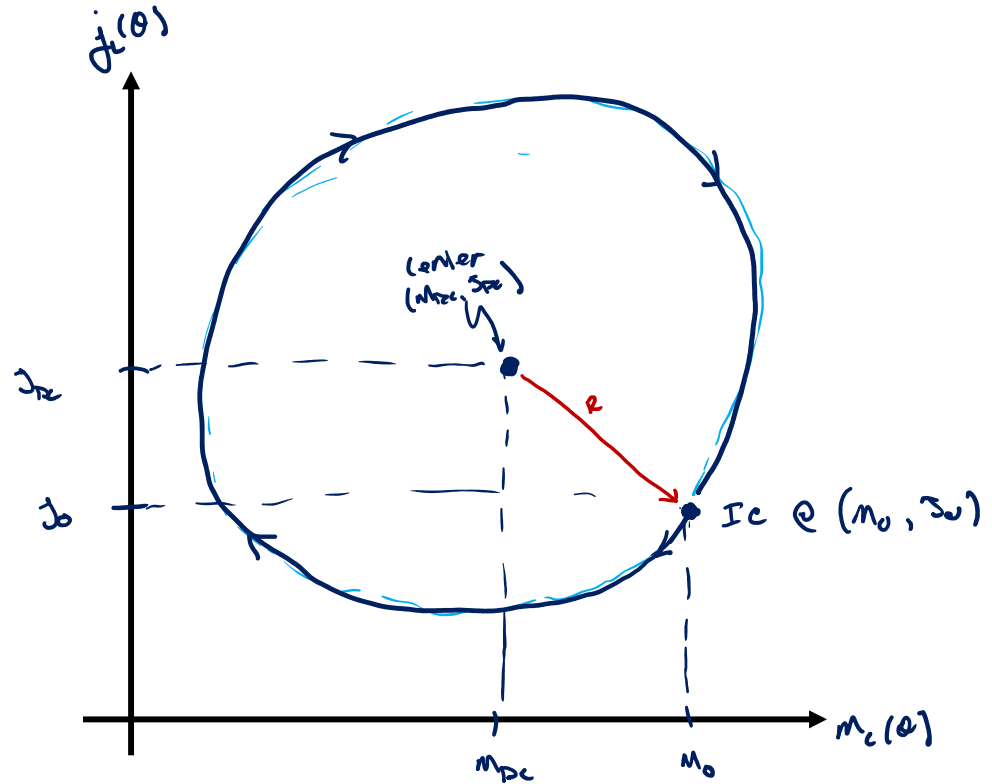Direction from  $I_c$  on first derivatives



[1] R. Oruganti and F. C. Lee, "Resonant Power Processors, Part I – State Plane Analysis", Industry Applications, IEEE

Tran. on, vol. 21, no. 6, nov 1985.

[2] D. P. Atherton, Nonlinear Control Engineering, London: Van Nostrand Reinhold, 1982, Ch. 2.

# Example Analysis

What is  $i_{ipt}$ ?

$$j_{ipt} = \frac{i_{ipt}}{I_{base}} = \frac{i_{ipt}}{V_{base}/R_0}$$

$$j_{ipt} = j_{pc} + r$$

$$j_{ipt} = j_{pc} + \sqrt{(M_0 - M_{pc})^2 + (j_0 - j_{pc})^2}$$

$$i_{ipt} = I_{pc} + \frac{V_{base}}{R_0} \sqrt{(M_0 - M_{pc})^2 + (j_0 - j_{pc})^2}$$

When does  $i_{ipt}$  occur?

$$\theta = \omega_0 t \quad t = \frac{\theta}{\omega_0}$$

$$\theta_{pt} = \frac{\pi}{2} + \tan^{-1} \left( \frac{j_0 - j_0}{M_{pc} - M_0} \right)$$

$$t_{ph} = \frac{\pi}{2\omega_0} + \frac{1}{\omega_0} \tan^{-1} \left( \frac{j_{pc} - j_0}{M_{pc} - M_0} \right)$$

