

State Plane Algorithm

Manipulate the circuit (during a subinterval) into 1-L, 1-C ac-equivalent w/ (possibly) DC bias sources

- May require same approximation

(1) Normalize waveforms & time

$$\left\{ \begin{array}{l} m_x(t) = \frac{v_x(t)}{V_{base}} \\ j_x(t) = \frac{i_x(t)}{I_{base}} \end{array} \right.$$

V_{base} = anything you choose

$$I_{base} = \frac{V_{base}}{R_0}$$

$$\theta_x = \omega_0 t_x$$

(2) Plot the (m_c, j_L) trajectory on the state plane

- will form a circle with

- center at $(M_{pc}, J_{pc}) \rightarrow$ the DC solution


- initial point at $(M_0, J_0) \rightarrow$ the initial condition

- Direction (CW or CCW) from I.C. on first derivative of m_c & j_L

(3) Solve parameters of interest (using geometry & trig)

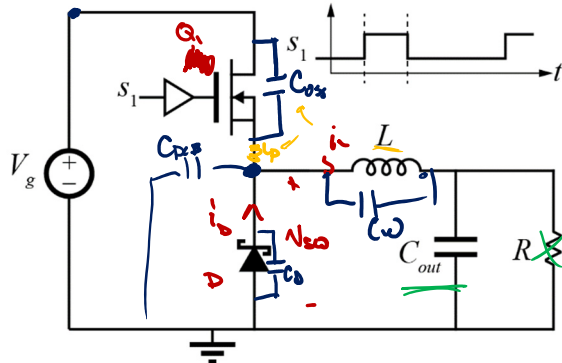(4) Denormalize $(m, j, \theta) \rightarrow (v, i, t)$

DCM Buck Converter Example ($M=1/2$) $= \frac{V}{V_g}$



$$V_{base} = V_g$$

$$I_{base} = \frac{V_g}{R_0}$$

When both Q_1 & D are off:



$$C_{eq} = C_{sw} \parallel C_p \parallel C_w \parallel C_{gs}$$

Initial Conditions:


$$i_L = \phi \rightarrow j_L = \phi$$

$$V_{sw} = \phi \rightarrow V_{sw} = \phi$$

DC solution:

$$i_L = \phi \rightarrow I_{DC} = \phi$$
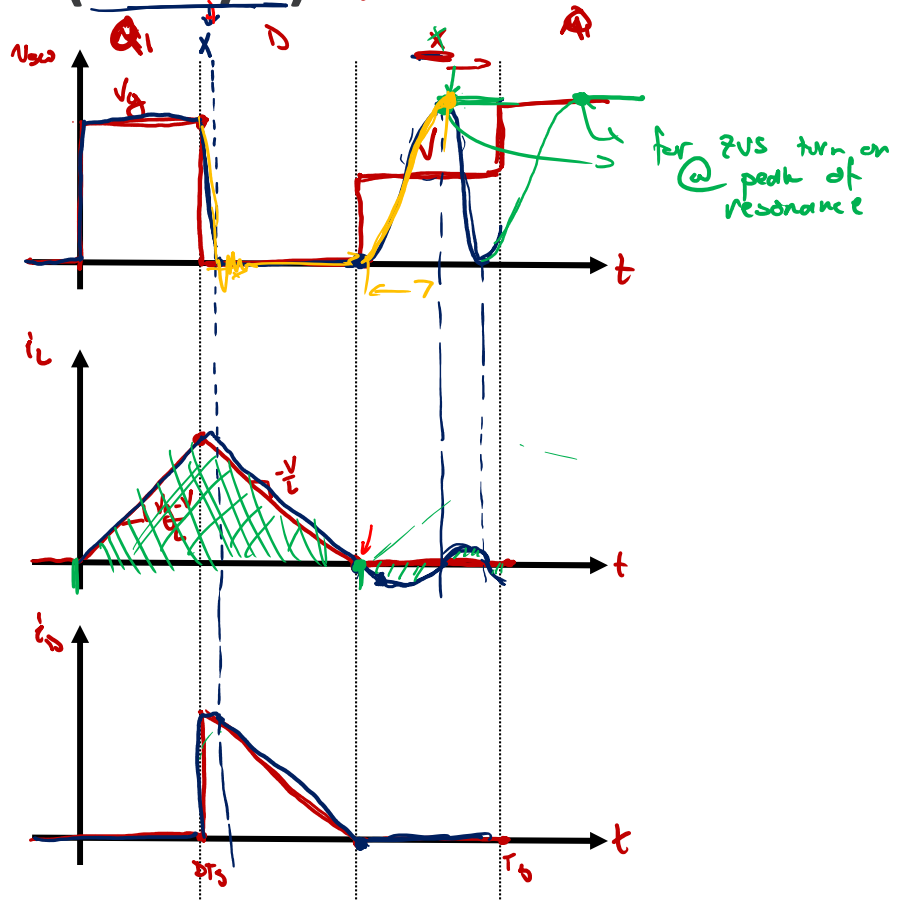
$$V_{sw} = V \rightarrow M_{DC} = \frac{V}{V_g} = M$$



DCM Buck State Plane

$$V_{base} = V_g \quad I_{base} = V_g / R_o$$

$$M_{max} = \frac{V}{V_g} - M = \frac{1}{2}$$


$$J_{re} = \phi$$

$$M_o = \phi$$



$$J_o = \phi$$

IC on 1st derivative

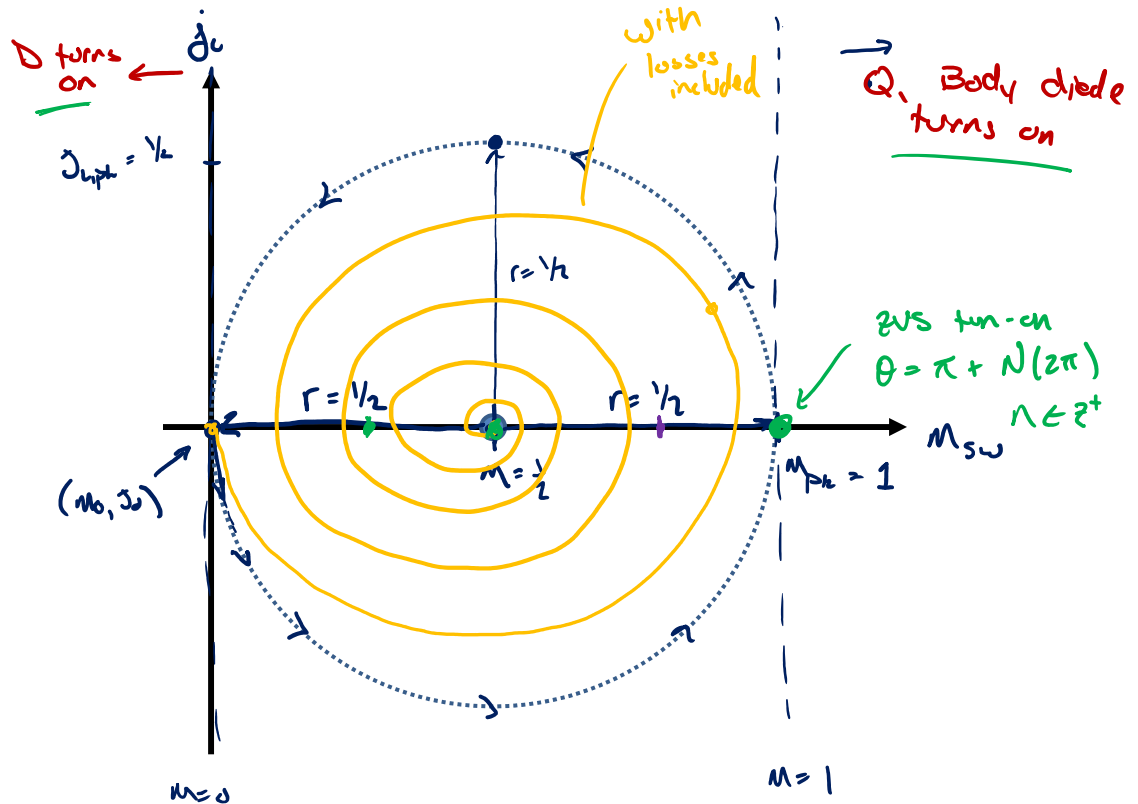- m_{sw} is increasing
- i_c is decreasing



DCM Buck M≠1/2

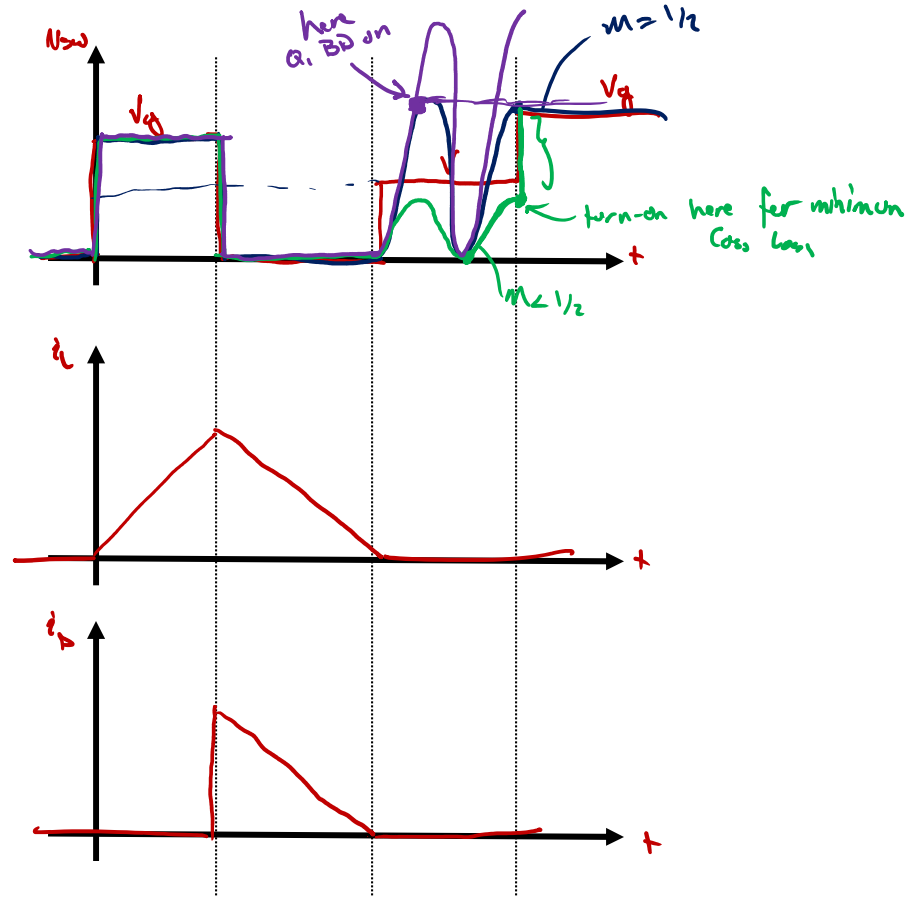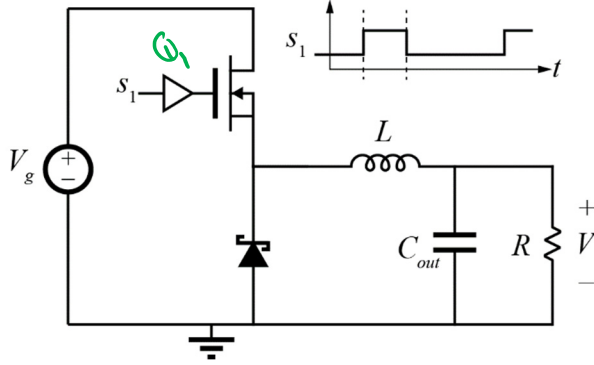

DCM Buck State Plane ($M < 1/2$)

