
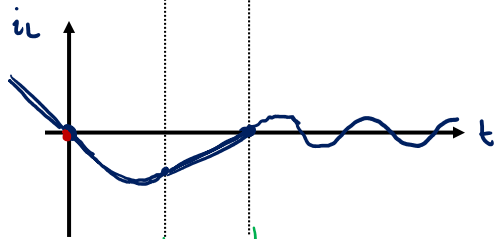



DCM Buck State Plane ($M > 1/2$)

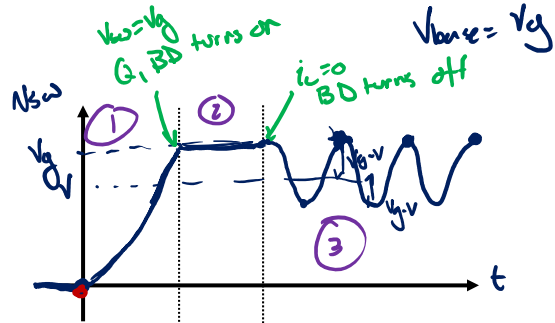


Resonant

Non-resonant

Resonant

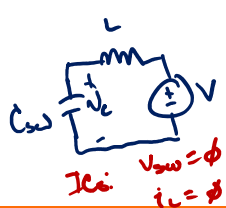


ICs: $V_{sw} = V_g$
 $i_c = 0$

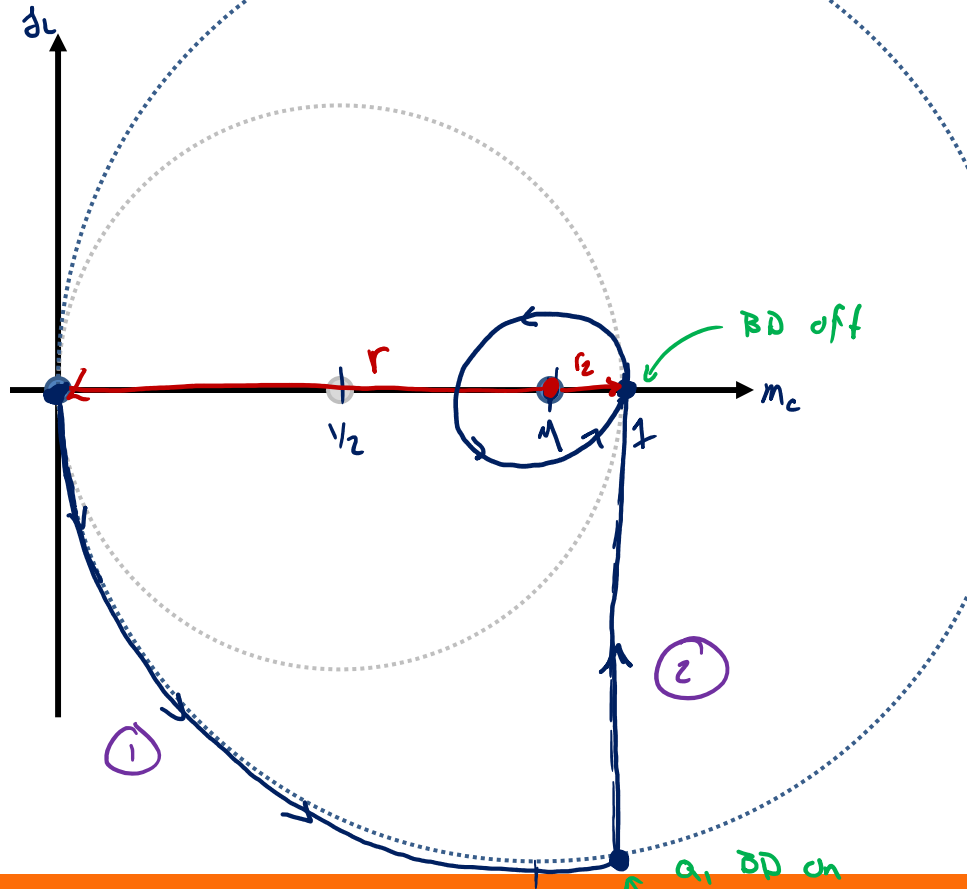

Synchronous Buck Converter

7NS-QSCW Buck Converter

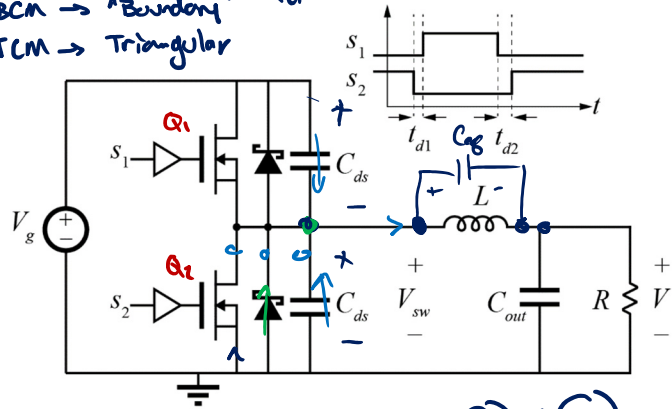- CRM → Critical conduction mode
- BCM → "Boundary"
- TCM → Triangular



↓ During dead times (2) & (4)


$V_{base} = V_g$



DC solution

$V_{sw} = V$
 $i_L = 0$
 $M_{sw} = \frac{V}{V_g} = M_{or} = M_{Q2}$
 $i_e = 0 = i_{pr}$

ICs:
vary by interval

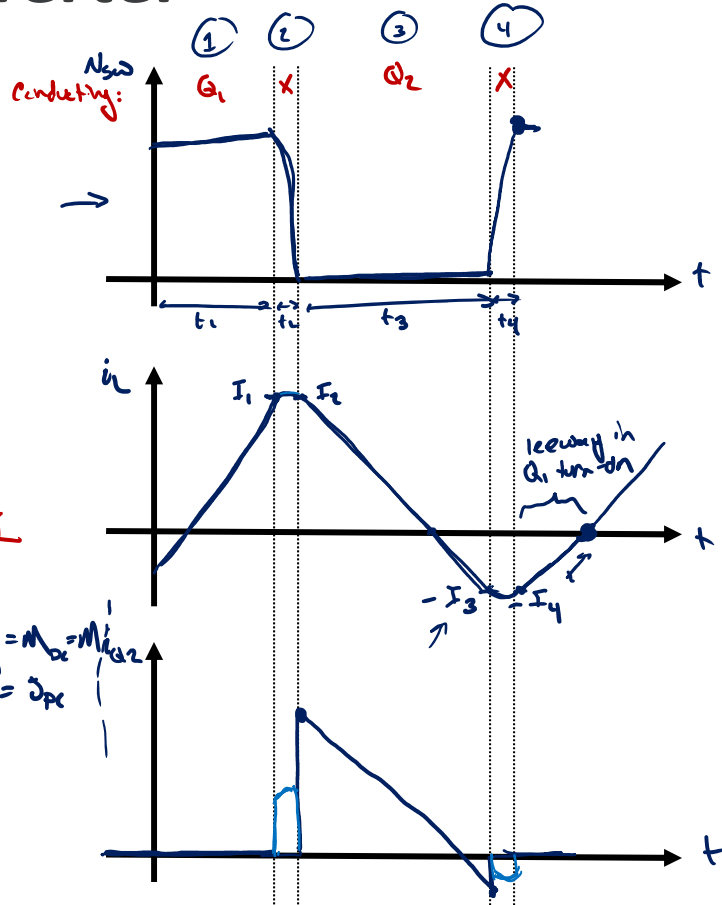


Sync-Buck State Plane

Denny 4

$$V_{base} = V_g \quad I_{base} = \frac{V_g}{R_o}$$

$$DC: (M, 0)$$
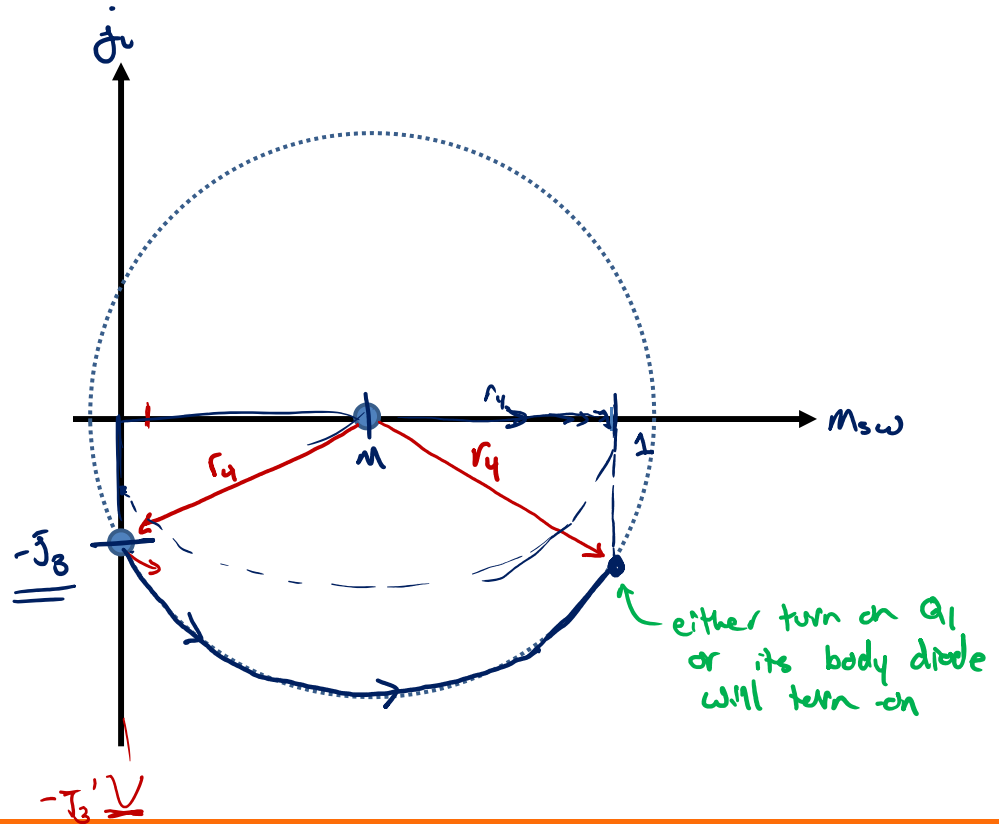
$$FC: i_L = -I_3, \quad v_{sw} = 0$$
$$(0, -I_3)$$



Sync-Buck ZVS Condition

During (1)

To get ZVS turn-on of Q_1 , we need

$$M + r_4 \geq 1$$

$$r_4 = \sqrt{J_3^2 + M^2}$$

$$\rightarrow \boxed{M + \sqrt{M^2 + J_3^2} \geq 1}$$

Denormalize:

$$\frac{V}{V_g} + \sqrt{\left(\frac{V}{V_g}\right)^2 + \left(\frac{I_3}{V_g} R_0\right)^2} \geq 1$$

$$R_0 = \sqrt{\frac{L}{C_{sw}}}$$

$$V^2 + I_3^2 \frac{L}{C_{sw}} \geq (V_g - V)^2$$

$$\rightarrow \boxed{\frac{1}{2} I_3^2 L \geq \frac{1}{2} C_{sw} (V_g - V)^2 - \frac{1}{2} C_{sw} V^2}$$

Initial energy
in L

Add'l energy
required

DC source
Bla

contributed energy

Sync-Buck State Plane (Ring out)

If we never turn Q_1 on
after 4

