
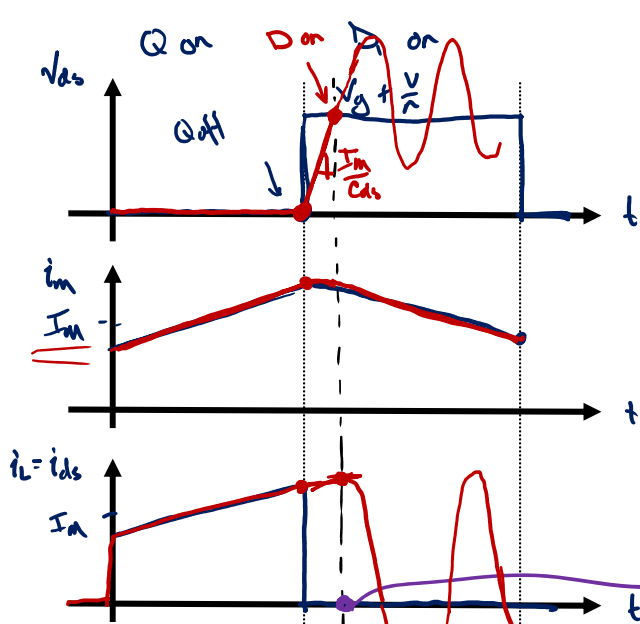


CCM Flyback: Ringing Due to L_l

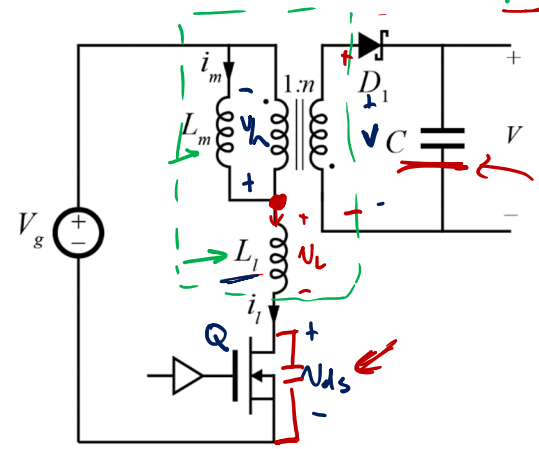


Ideal ($L_l = 0, \neq C_{ds} = \phi$)
 $L_l \neq \phi \neq C_{ds} \neq 0$

Assume L_m & C are filter elements
 Assume $L_l \ll L_m$
 $L_l + L_m \approx L_m$



DCs
 $N_l = \phi$
 $V_{ds} = V_g + \frac{V}{n}$
 $i_L = I_m$

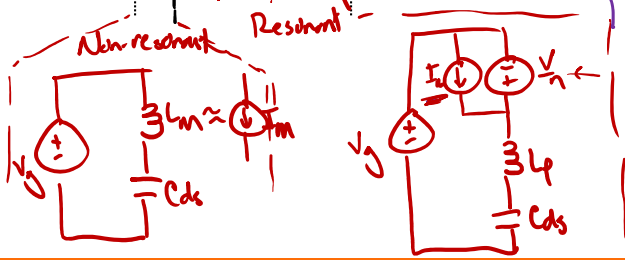DC:
 $V_{ds} = V_g + \frac{V}{n}$
 $i_L = \phi$





MOSFET Turn-off

$$V_{base} = V_g + \frac{V}{n}$$

$$I_{base} = \frac{V_{base}}{R_0}$$

$$R_0 = \sqrt{\frac{L_1}{C_{gs}}}$$

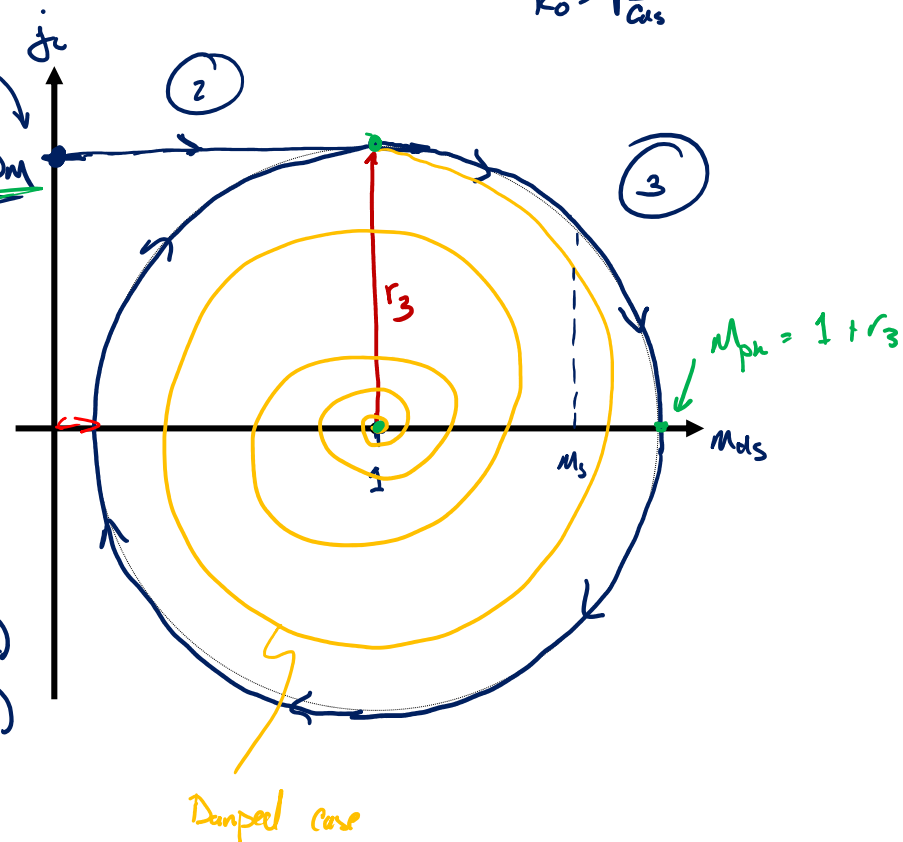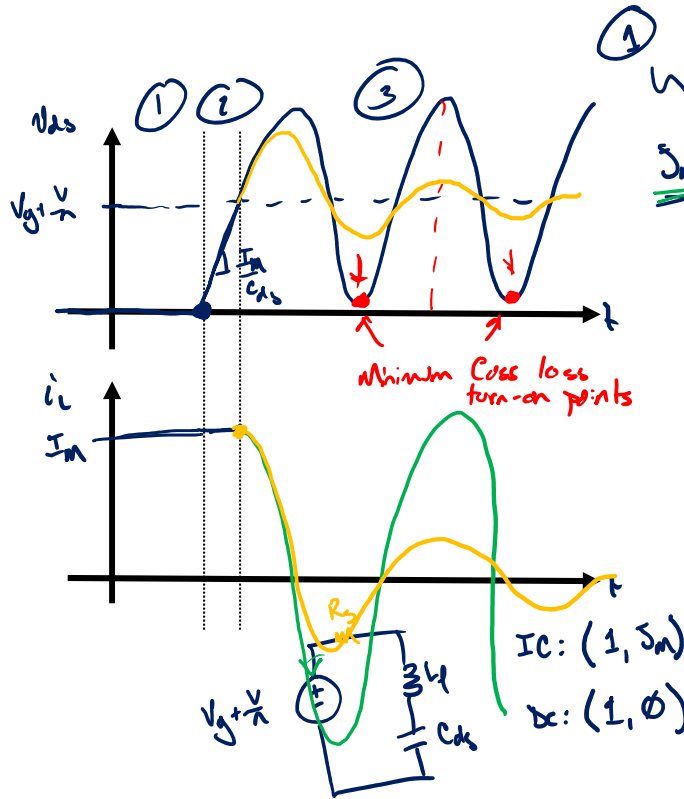

Leakage Voltage Stress

$$M_{pk} = 1 + r_3 = 1 + \Delta_m$$

$$V_{ds, pk} = V_g + \frac{V}{n} + I_m R_o$$

$$\Delta_m = \frac{I_m}{I_{base}} = \frac{I_m R_o}{V_{base}}$$

Example Numbers

$$V_g = 400V$$

$$V = 10V$$

$$P = 100W$$

$$f_s = 1MHz$$

$$n = \frac{1}{40} \quad D = 0.5$$

$$C_{ds} = 100pF$$

$$L_m = 1.2mH$$

$$L_l = 35\mu H$$

(2% of L_m)

$$R_o = \sqrt{\frac{L_l}{C_{ds}}} = 600\Omega$$

$$I_m = \frac{n I_{out}}{D} = 500mA$$

$$V_{base} = V_g + \frac{V}{n} = 800V$$

$$V_{ds, pk} = 800V + (0.5)(600)$$

$$= \underline{\underline{1.1kV!}}$$

Leakage Switching Loss

For the damped case where we converge to the DC operating point in $\textcircled{3}$

From the state plane:

$$E_{\text{start}} = \frac{1}{2} C_{ds} \left(V_g + \frac{V}{n} \right)^2 + \frac{1}{2} L_e I_m^2$$

$$E_{\text{end}} = \frac{1}{2} C_{ds} \left(V_g + \frac{V}{n} \right)^2$$

$$E_{\text{removed}} = \frac{1}{2} L_e I_m^2$$


Note: E_{removed} could be loss or recovered into a source

In this case, $E_{\text{source}} = \emptyset$, $E_{\text{removed}} = E_{\text{loss}}$

$$E_{\text{loss}} = 4.4 \mu\text{J}$$

$$P_{\text{loss}} = \underline{4.4 \text{ W}}$$

CCM Flyback: Clamping Circuit

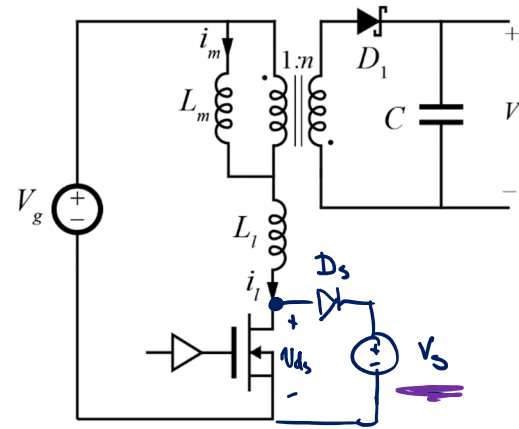

design $V_s \approx \frac{V}{n} < V_s < V_{ds,peak}$

Clamped State Plane

