

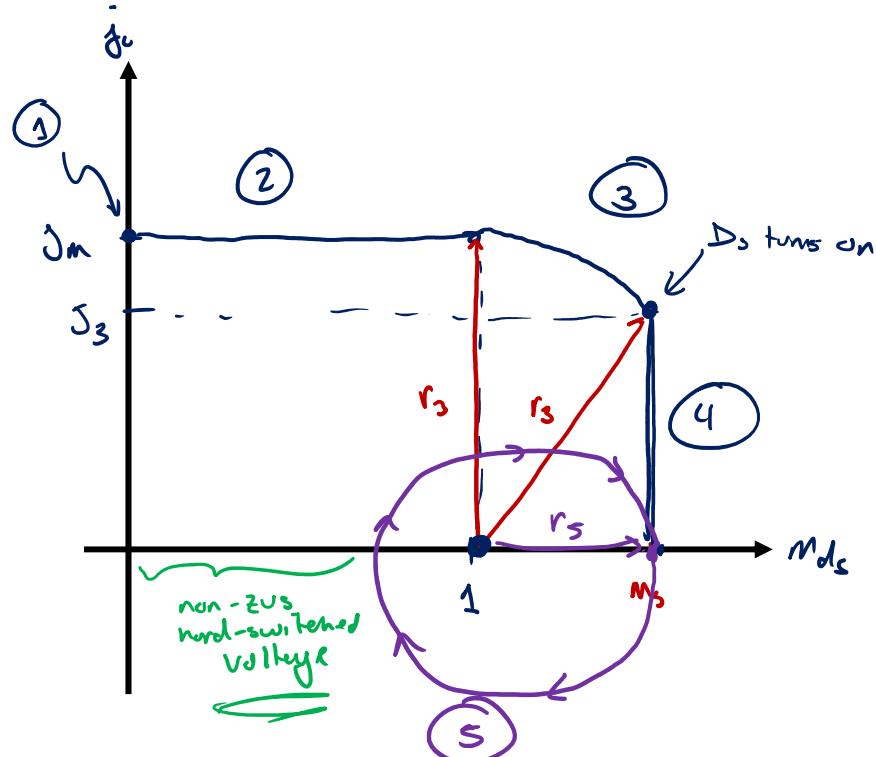


Clamped State Plane

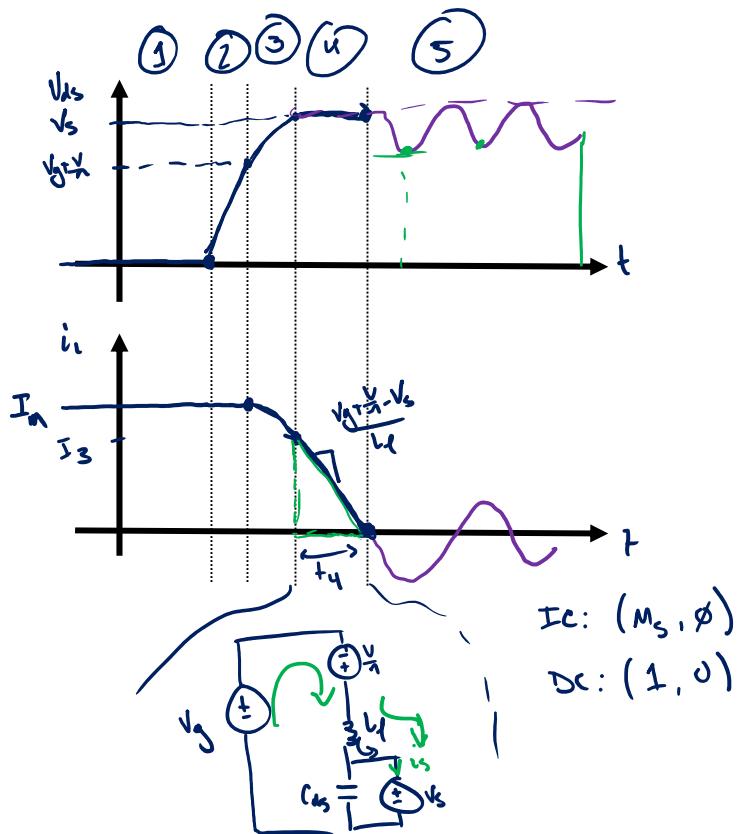

Loss Comparison

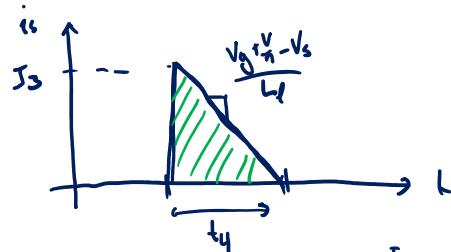


$$\mathcal{J}_3 = \sqrt{\mathcal{J}_m^2 - (m_s - 1)^2}$$

$$\begin{aligned} P_s &= E_s f_s = f_s \int_0^{t_4} V_s \cdot i_s dt = f_s V_s \int_{t_4}^0 i_s dt \\ &= f_s V_s \frac{1}{2} t_4 I_3 = f_s V_s \frac{1}{2} I_3 \left[\frac{I_3 L_s}{V_g + \frac{V}{n} - V_s} \right] \end{aligned}$$



Plug in from previous design with $V_s = 850V$

$$E_s = 72mS$$

$$P_s = 72W \rightarrow \text{Huge!}$$

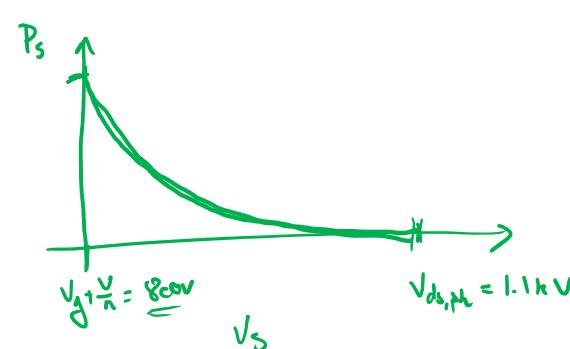


Snubber Implementations

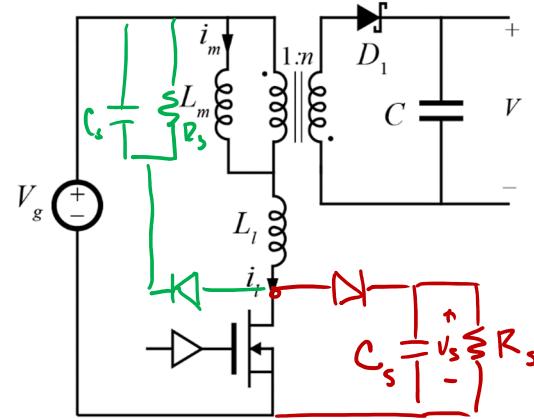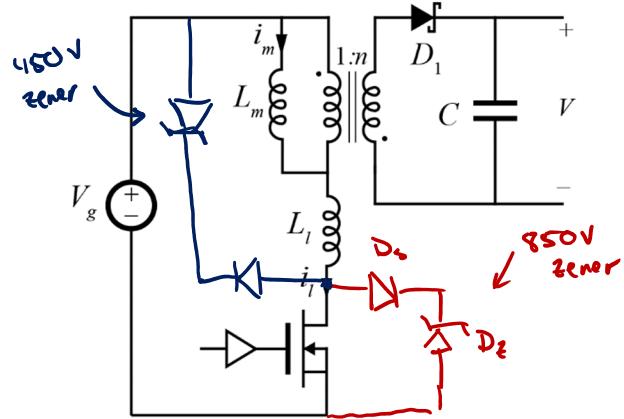

$C_s \rightarrow$ large filter element

$$P_s = \frac{V_s^2}{R_s}$$


Active Clamping

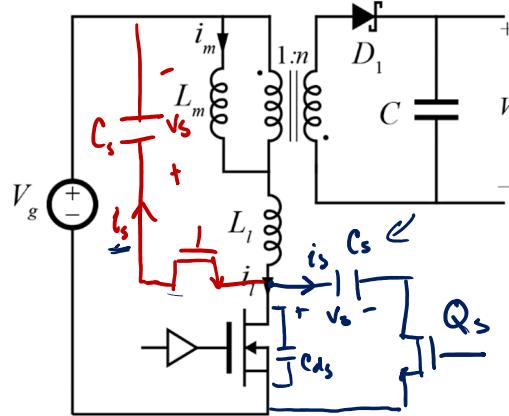


C_s ($\& L_m + C$) \rightarrow large filter elements

Active Clamping

Conducting device



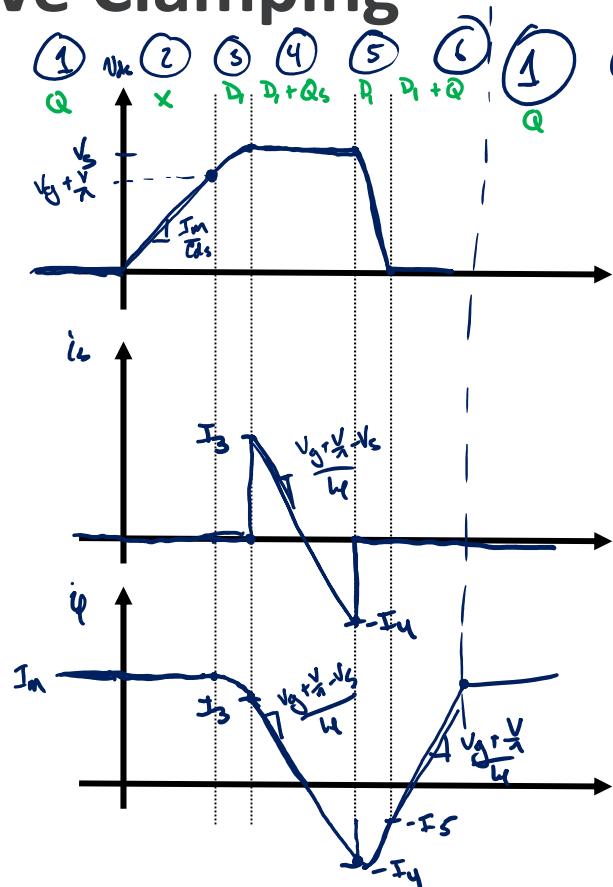


$$V_{basec} = V_g + \frac{V}{n}$$



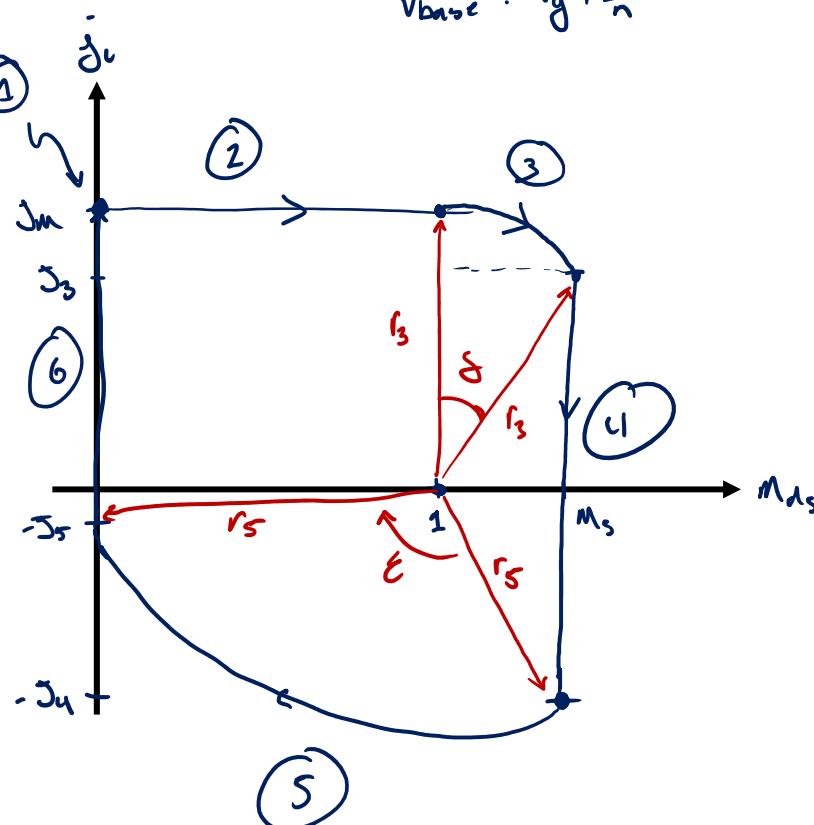


Subinterval Equivalent Circuits

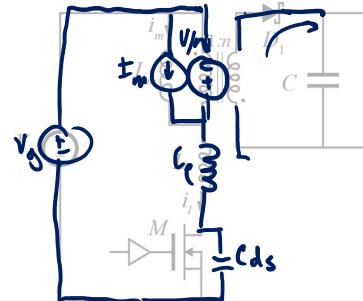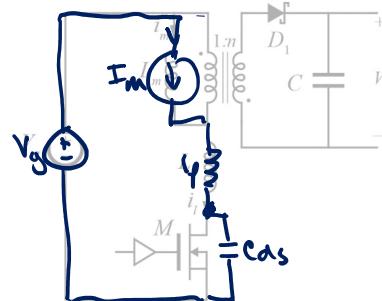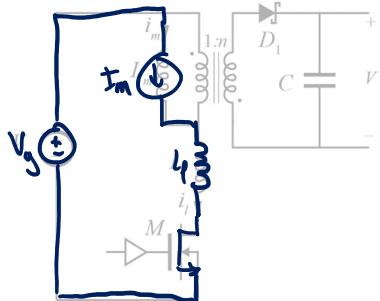① → Q_1 off → ② → D_1 turns on → ③ → turn on Q_S



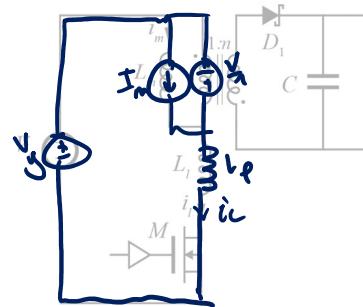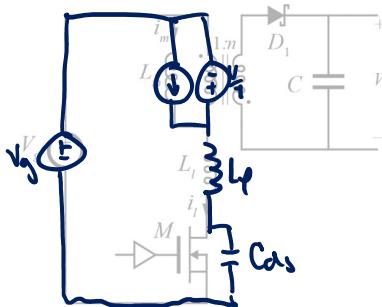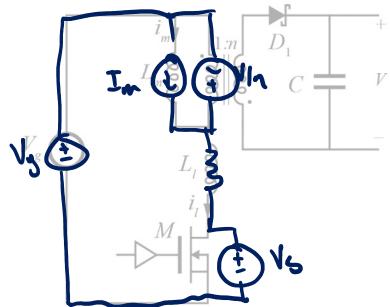④ → shut off Q_S → ⑤ → Turn on Main FET → ⑥ → D_1 off →



ZVS Conditions

3

$$r_3 \geq m_s - 1$$

$$\boxed{r_m \geq m_s - 1}$$

\rightarrow Only violated clamp of $V_{ds,pl} < V_s \rightarrow$ No need for

5

ZVS of Q

$$r_5 \geq 1$$

$$\boxed{\sqrt{s_1^2 + (1-m_s)^2} \geq 1}$$

Analysis: Intervals 1-3

① No equation from state plane or time domain

$$T_5 = t_1 + t_2 + \dots + t_6$$

$$\frac{2\pi}{F} = \theta_1 + \theta_2 + \delta + \theta_4 + \epsilon + \theta_6$$

② $\left(\frac{1}{I_{base}}\right) \frac{J_m}{Cds} t_2 = V_g + \frac{V}{n} \left(\frac{1}{I_{base}} \right)$

$$J_m \frac{t_2}{Cds} = 1 \cdot R_o$$

$$J_m t_2 \frac{1}{Cds R_o} = 1 \rightarrow J_m \theta_2 = 1$$

$$\frac{1}{Cds R_o} = \frac{1}{Cds \sqrt{L/Cds}} = \frac{1}{\sqrt{L/Cds}} = \omega_o$$

③ $r_3^2 = J_m^2 = (M_s - 1)^2 + J_3^2$

$$\delta = \tan^{-1} \left(\frac{M_s - 1}{J_3} \right)$$