

Analysis: Intervals 4-6

$$V_{base} = V_g + \frac{V}{n}$$

$$(4) \quad -\left(\frac{V_g + \frac{V}{n} - V_s}{L_e}\right) t_4 = I_3 + I_4$$

$$-(1 - m_s) \theta_4 = \mathcal{J}_3 + \mathcal{J}_4$$

(5)

$$(m_s - 1)^2 + \mathcal{J}_4^2 = 1 + \mathcal{J}_s^2$$
$$\mathcal{E} = \pi - \tan^{-1}\left(\frac{\mathcal{J}_4}{m_s - 1}\right) - \tan^{-1}\left(\frac{\mathcal{J}_s}{1}\right)$$

(6)

$$\frac{V_g + \frac{V}{n}}{L_e} t_6 = I_m + I_s$$

$$(1) \theta_6 = \mathcal{J}_m + \mathcal{J}_s$$



Analysis: Averaging

Apply volt-sec / cap-Q balance to all filter elements
 In Active Comp Flyback: C, Lm, Cs

Cap-Q balance to Cs

$$\langle i_s \rangle T_s = \phi$$

$$\int_0^{T_s} i_s dt = \phi$$

$$\frac{I_3 - I_4}{2} t_4 = \phi \rightarrow \boxed{I_3 = I_4}$$


Volt-sec Balance on Lm

$$\int_0^{T_s} v_{Lm} dt = \phi$$

$$\phi = \left[V_g t_1 + \frac{V_g - V}{2} t_2 + (-\frac{V}{n}) (t_3 + t_4 + t_5 + t_6) \right]$$

$$\boxed{\frac{V}{V_g} = M = n \frac{t_1 + \frac{t_2}{2}}{\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6}}$$

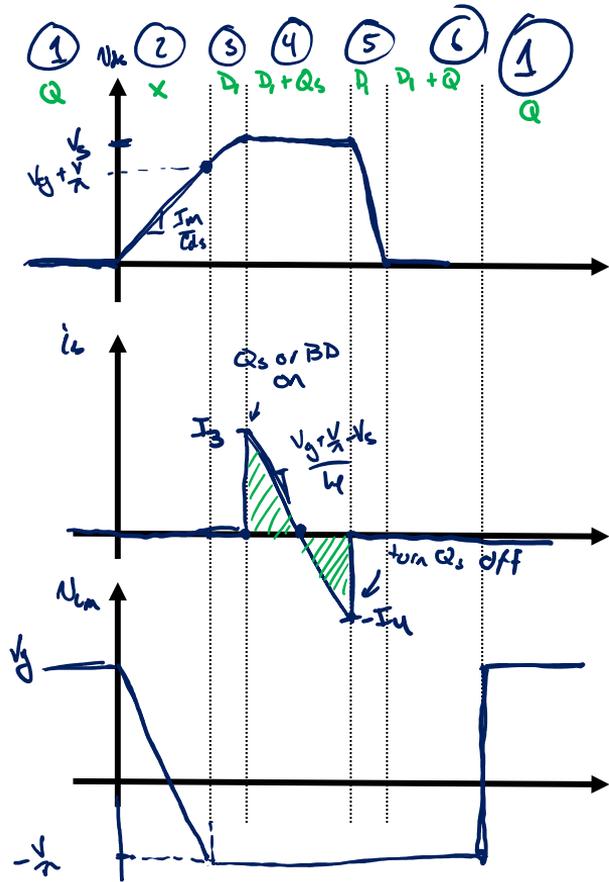$\approx n \frac{D_1 D}{D_1 - D} \rightarrow \text{CCM, small-ripple flyback solution}$



Average Output Current

Cap-Q balance on C

$$\int_0^{T_0} i_{C0} dt = \phi \quad \frac{1}{T_0} \int_0^{T_0} i_{C0} dt = I_{out}$$

$$n I_{out} = \frac{1}{T_0} \int_0^{T_0} (I_m - i_L) dt$$

$$n I_{out} = \frac{1}{T_0} [\cancel{g_1} + \cancel{g_2} + g_3 + g_4 + g_5 + g_6]$$

$$g_3 = I_m t_3 - C_{ds} (V_0 - V_g - \frac{V}{n})$$

$$g_4 = \frac{(I_m - I_4) + (I_m - I_5)}{2} t_4 = I_m t_4$$


$$g_5 = I_m t_5 + C_{ds} (\cancel{V_5})$$

$$g_6 = \frac{I_m + I_5}{2} t_6$$

$$\left(\frac{1}{I_{max}} \right) n I_{out} = \frac{1}{T_0} \left[I_m t_3 + C_{ds} (V_g + \frac{V}{n}) + I_m t_4 + I_m t_5 + \frac{I_m + I_5}{2} t_6 \right] \left(\frac{1}{I_{max}} \right)$$

$$n I_{out} = \frac{1}{T_0} \left[I_m (t_3 + t_4 + t_5 + \frac{t_6}{2}) + I_5 \frac{t_6}{2} + C_{ds} R_0 \right] \left(\frac{\omega_0}{\omega} \right) \rightarrow n I_{out} = \frac{F}{2\pi} \left[I_m \left(\delta + \theta_{u1} + \epsilon + \frac{\theta_6}{2} \right) + I_5 \frac{\theta_6}{2} + 1 \right]$$
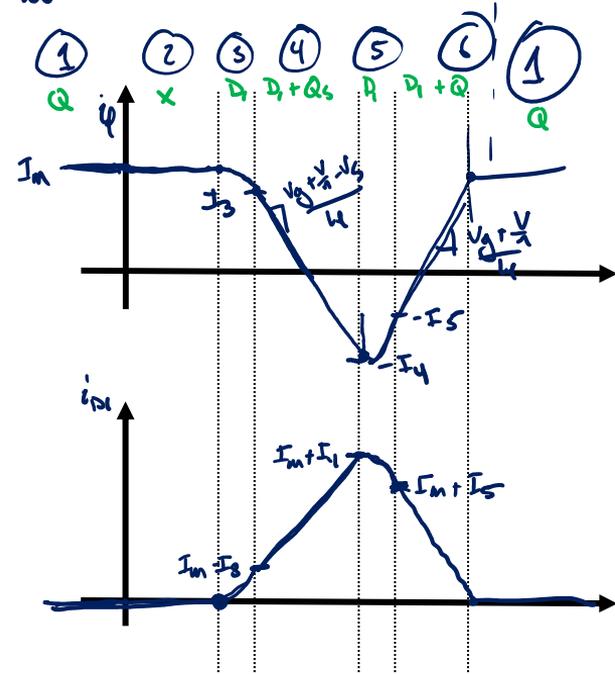
$$C_{ds} R_0 = C_{ds} \sqrt{\frac{L_1}{C_{ds}}} = \sqrt{L_1 C_{ds}} = \frac{1}{\omega_0}$$



Introduction to AC-link topologies

