
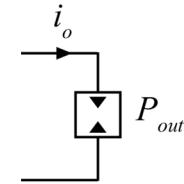


Analysis: Intervals 4-6


Analysis: Averaging

Average Output Current

Introduction to AC-link topologies

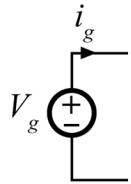

DC-Transformer (DCX)

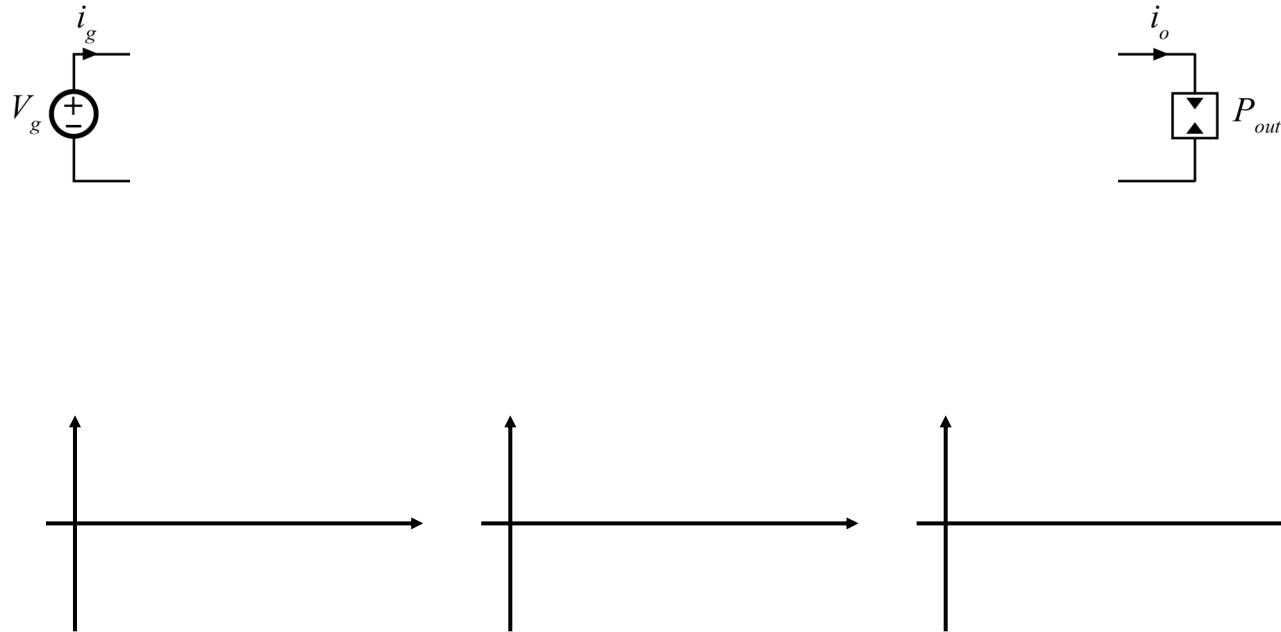

Dual Active Bridge

