

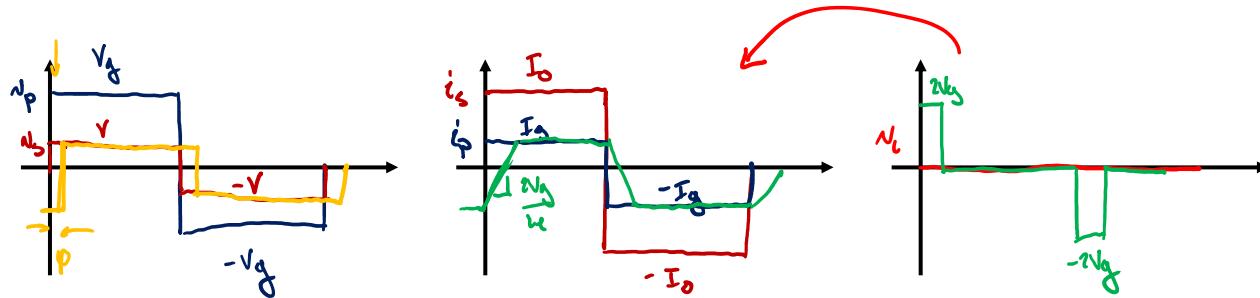


DC-Transformer (DCX)

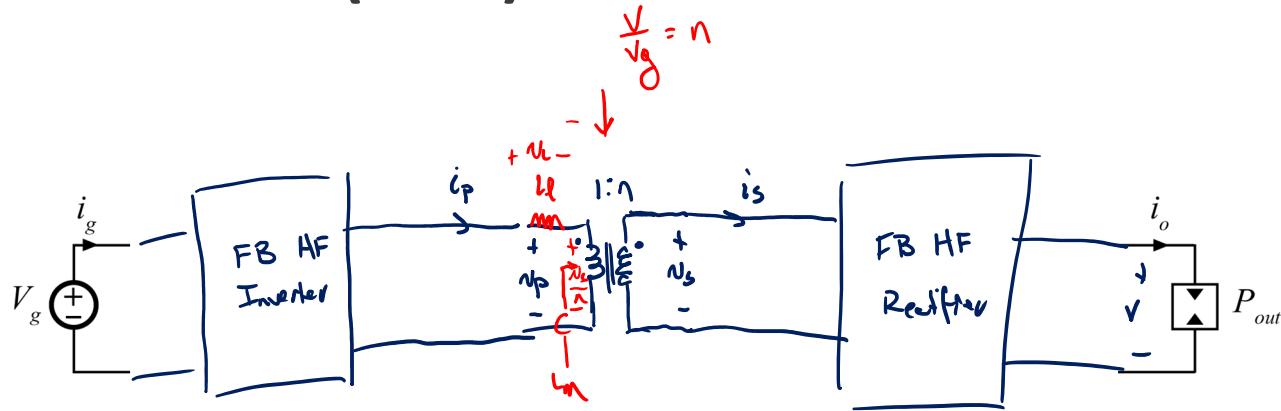


Dual Active Bridge

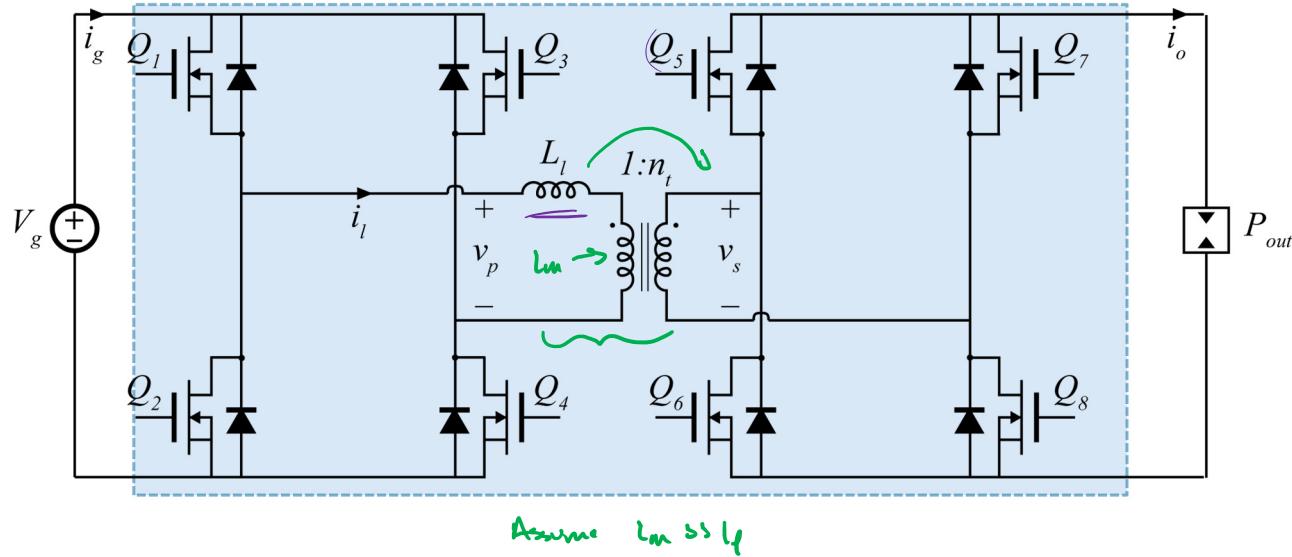


Switching Behavior (PSM)

Assume:

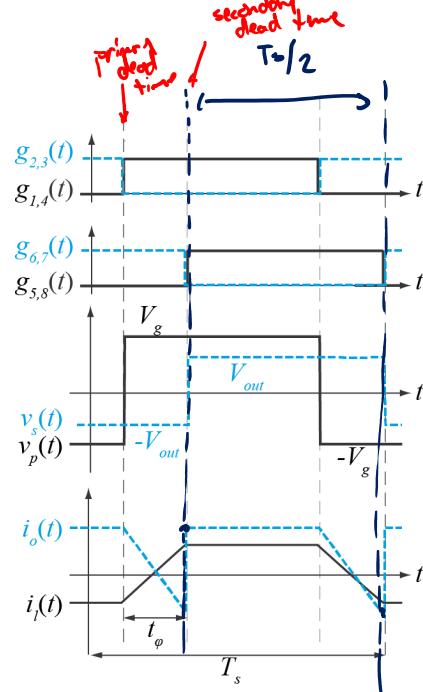
- ① Phase Shift Modulation
- ② $\frac{1}{\sqrt{g}} = n_t$




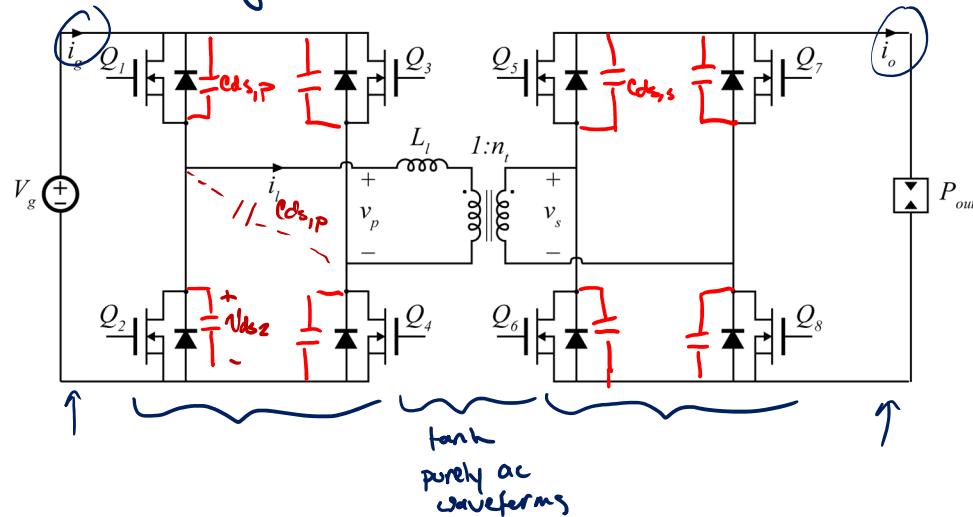
ac waveforms are half-period anti-symmetric
dc waveforms are half-period symmetric




Primary Dead time

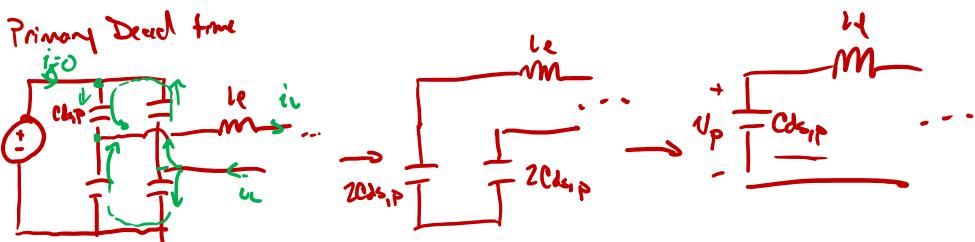

DAB Operation Analysis

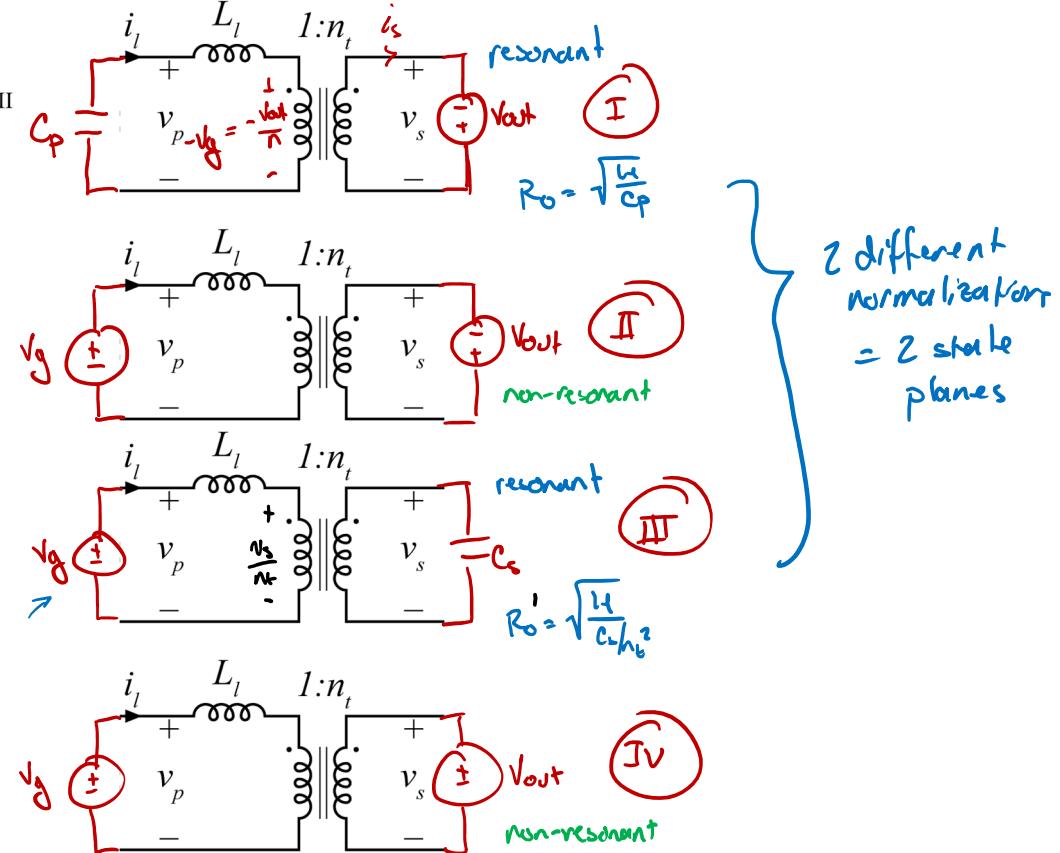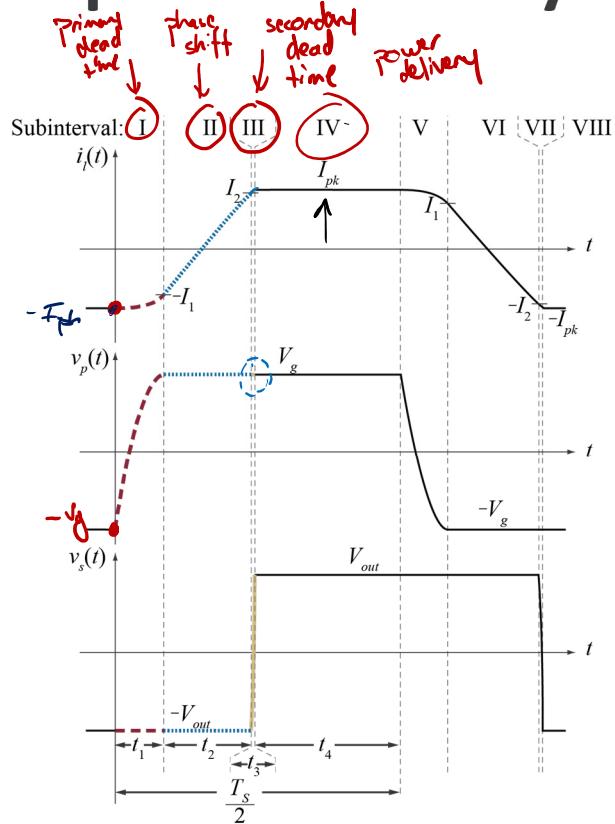


DAB State Plane

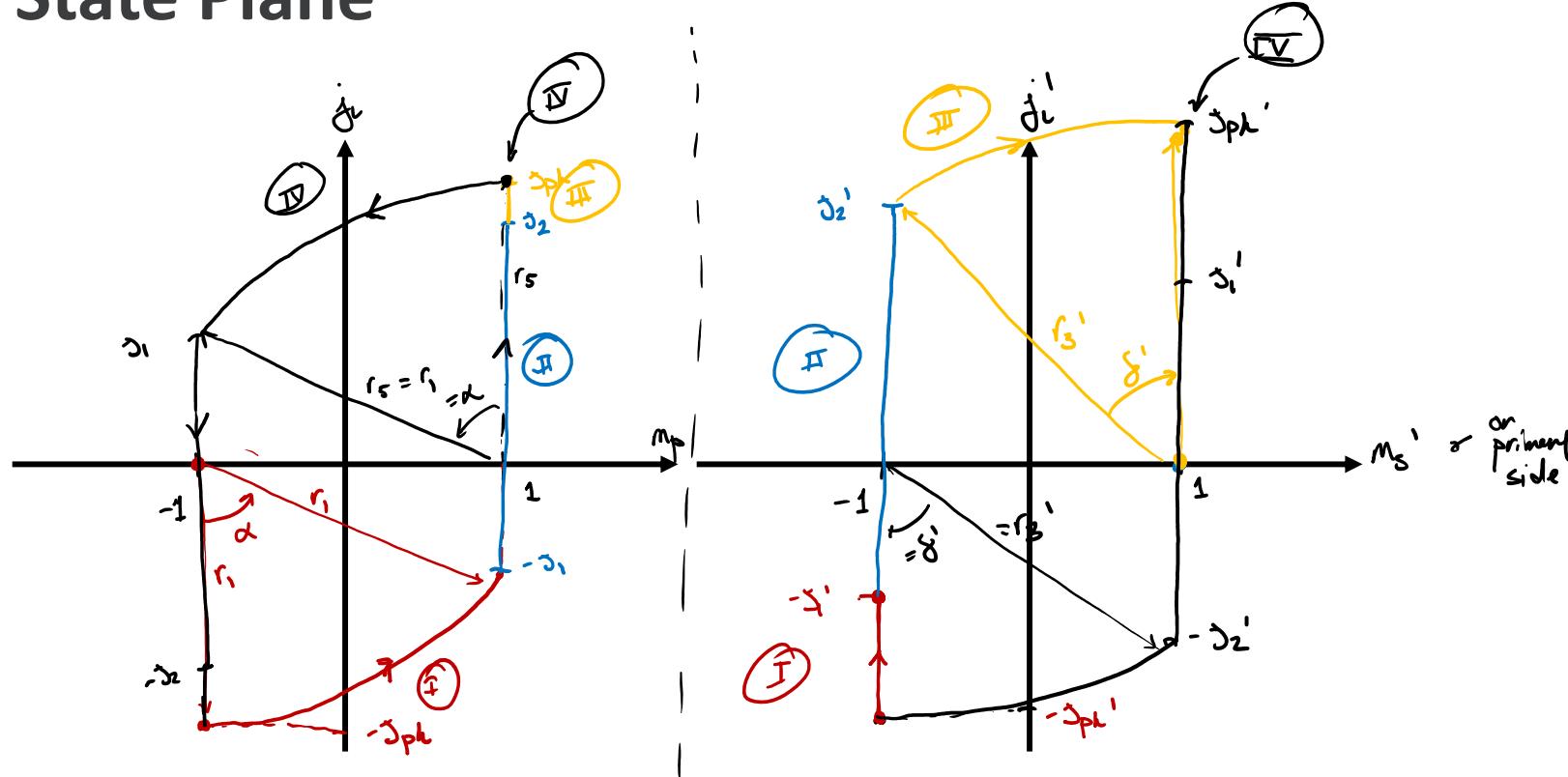


$$V_{base} = V_g \quad R_0 = \sqrt{\frac{u}{C_p}}$$

$$V_{base}' = V_g \cdot \frac{V_{0A}}{n_t} \quad R_0' = \sqrt{\frac{L_m^2}{C_s}}$$


State Plane Analysis of DAB Converter

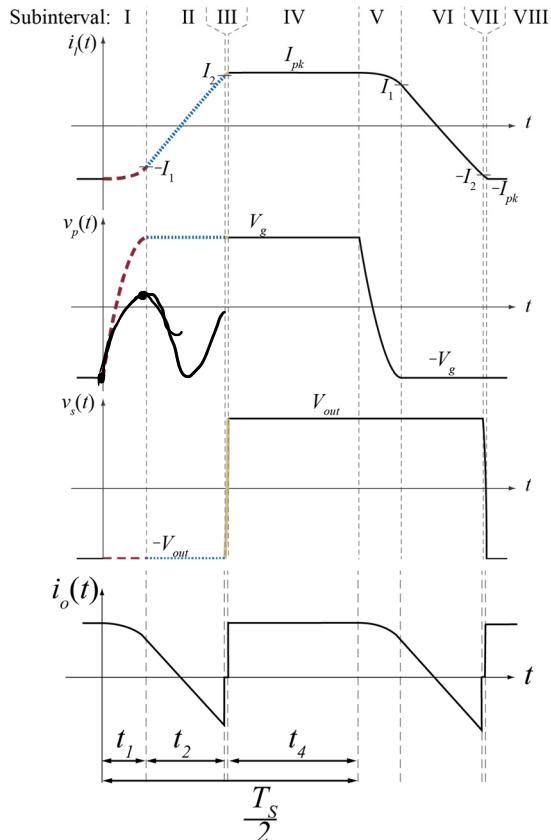

Primary

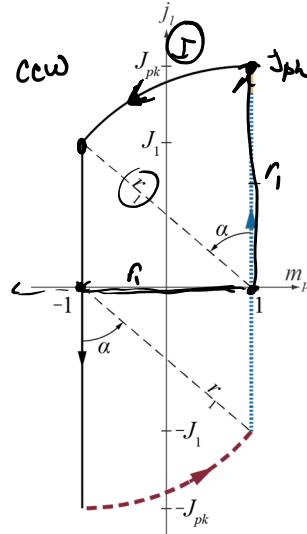

Secondary

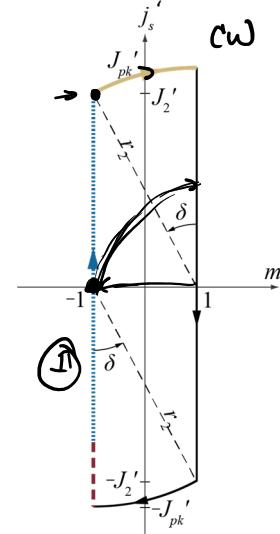

$$I_{base} = V_g \sqrt{\frac{C_p}{L_l}}$$

$$I_{base} = V_g \sqrt{\frac{C_s}{n_t^2 L_l}}$$

ZVS Condition

Primary

$$r_i > 2$$

$$I_{ph} > 2$$

$$I_{ph} > 2 I_{base} \Rightarrow I_{ph} > 2 V_g \sqrt{\frac{C_p}{L}}$$

$$\frac{1}{2} L_i I_{ph}^2 > \frac{1}{2} (2V_g)^2 C_p$$

Initial energy in L_i \downarrow Energy supplied to C_p

Secondary:

No constraint for this mode of operation