

State Plane Solution

$$\textcircled{I} \quad r_1^2 = \left| \mathbf{J}_{ph} \right|^2 = J_1^2 + 4$$

$$\alpha = \tan^{-1} \left(\frac{2}{J_1} \right)$$

$$\textcircled{II} \quad \frac{V_g + V_{out}}{I_e} t_2 = I_2 + I_1$$

$$2\theta_2 = J_2 + J_1$$

$$\textcircled{III} \quad r_2'^2 = \left| \mathbf{J}_{pk'} \right|^2 = (J_2')^2 + 4$$

$$\delta' = \tan^{-1} \left(\frac{2}{J_2'} \right)$$

$$\textcircled{IV} \quad \rightarrow X$$

$$\frac{T_o}{2} = t_1 + t_2 + t_3 + t_4$$


$$\frac{2\pi f_o}{2T_o} = \frac{\pi}{F} = \alpha + \theta_2 + \delta + \theta_4$$

$$M = \frac{V_{out}}{V_g} = n_t$$

changing to common
normalization
e.g.


$$\frac{J'}{\omega_0} = t_3$$

$$t_3 \omega_0 > \delta$$

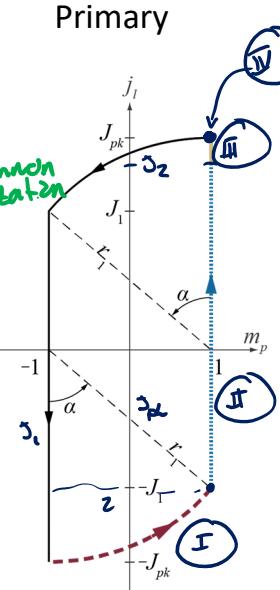

$$V_{base} = V_g$$
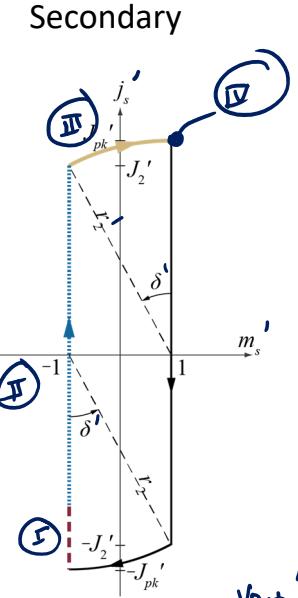
$$I_{base} = V_g \sqrt{\frac{C_p}{L_l}}$$



$$V_{base} = V_g \cdot \frac{V_{out}}{n_t}$$

$$I_{base} = V_g \sqrt{\frac{C_s}{n_t^2 L_l}}$$


Averaging Step

$$n_t I_{out} = \frac{2}{T_s} \int_0^{T_s/2} n_t i_o(t) dt = \frac{2}{T_s} \int_0^{T_s/2} i_L(t) dt$$

$$n_t I_{out} = \frac{2}{T_s} [q_1 + q_2 + q_3 + q_4]$$


$$\left(\frac{1}{I_{base}}\right) n_t I_{out} = \frac{2}{T_s} \left[C_p 2V_g + \frac{I_1 - I_2}{2} t_2 + \phi + I_{pk} t_4 \right] \left(\frac{1}{I_{base}}\right) \left(\frac{w_0}{w_0}\right)^{\frac{T_s}{2}}$$
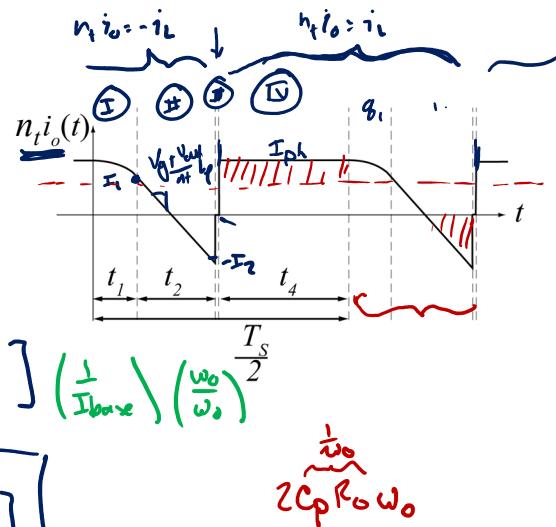
$$\boxed{n_t I_{out} = \frac{f}{\pi} \left[Z + \frac{J_1 - J_2}{2} \theta_2 + J_{ph} \theta_4 \right]}$$



Output Plane


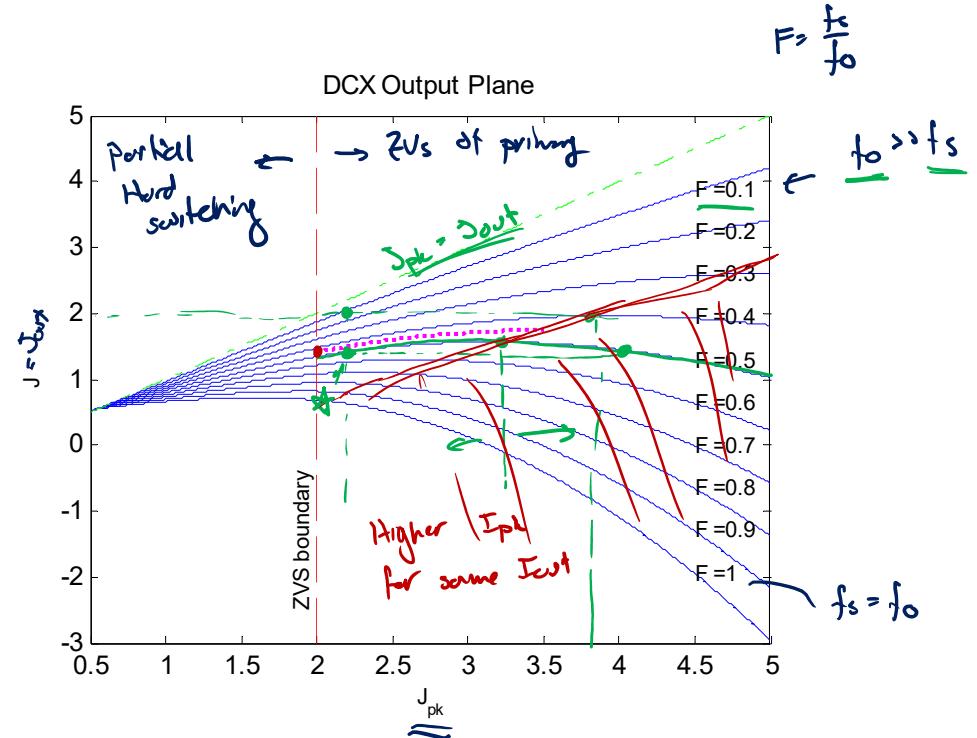
$$J = \frac{n\langle i_{out} \rangle}{I_{base}} = \frac{F}{\pi} \left[2 + \frac{1}{4} (J_1^2 - J_2^2) + J_p \left(\frac{\pi}{F} - \alpha - \theta_2 - \delta \right) \right]$$



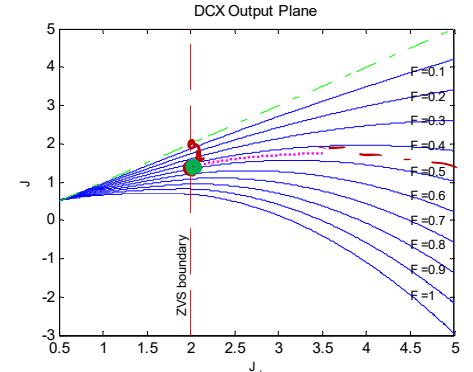
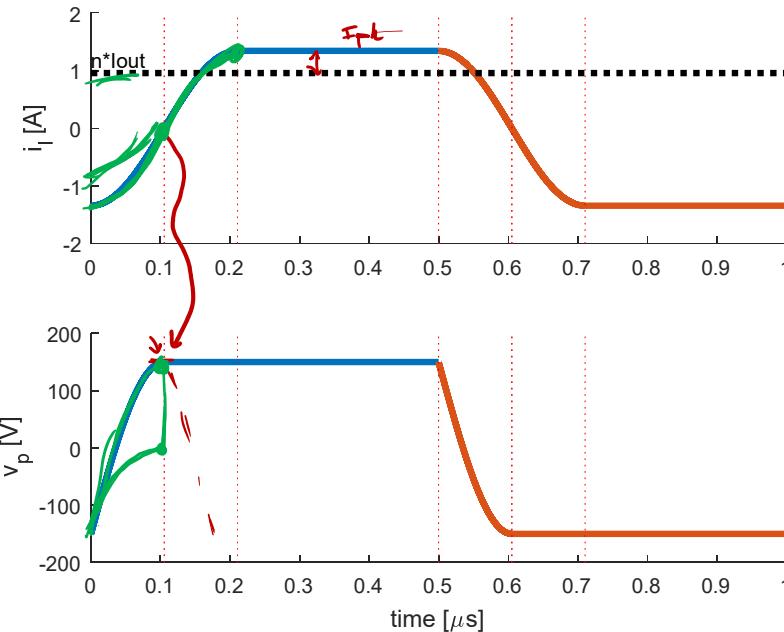
Example Waveforms

$$f_s = 1 \text{ MHz} \quad V_{out} > 12V \quad V_g = 150V$$



$$L_s = 15 \mu H \quad C_p = 300 \text{ pF} \quad C_s = \frac{C_p}{\pi^2}$$





Example Waveforms

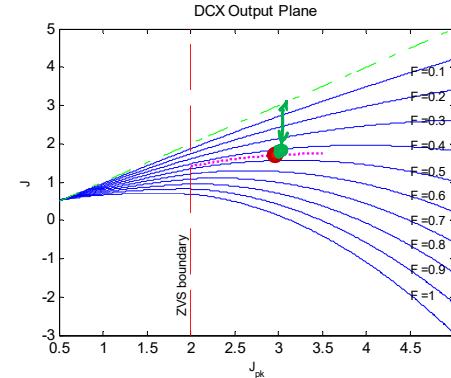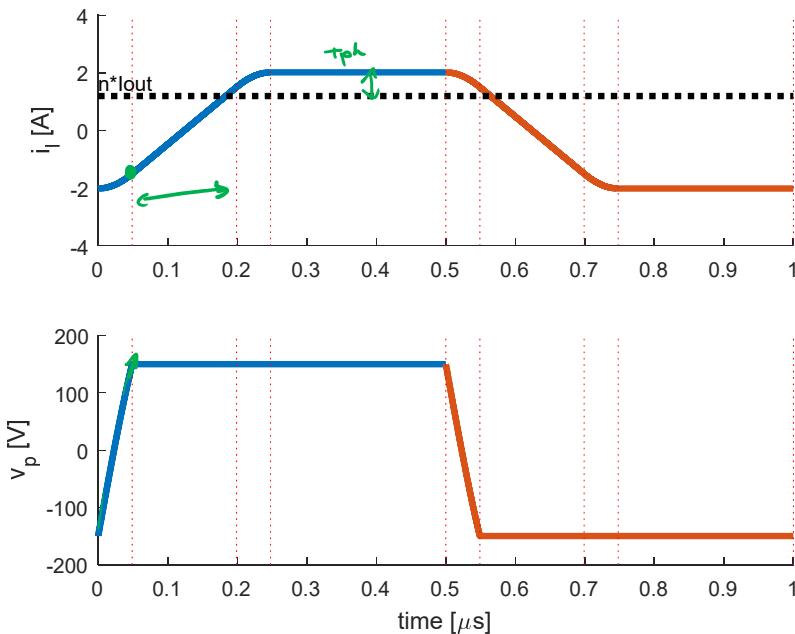



Example Waveforms

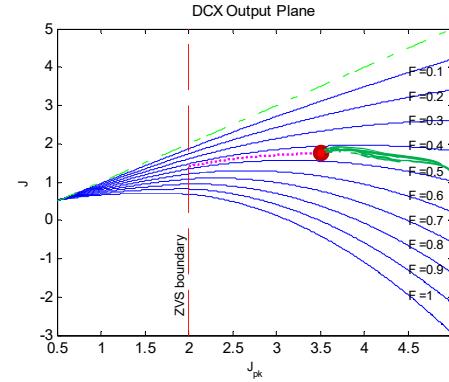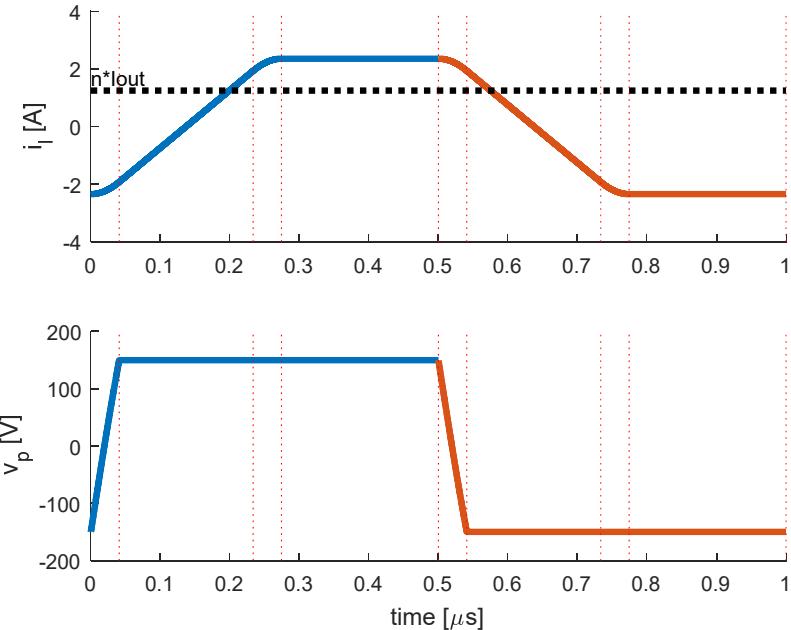


Example Waveforms

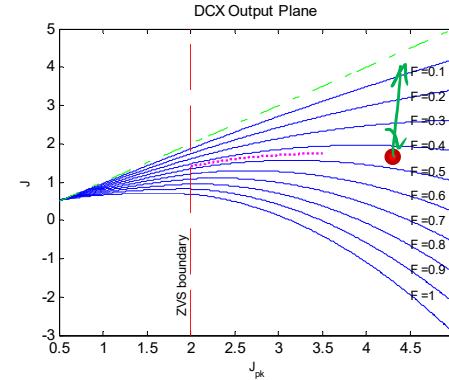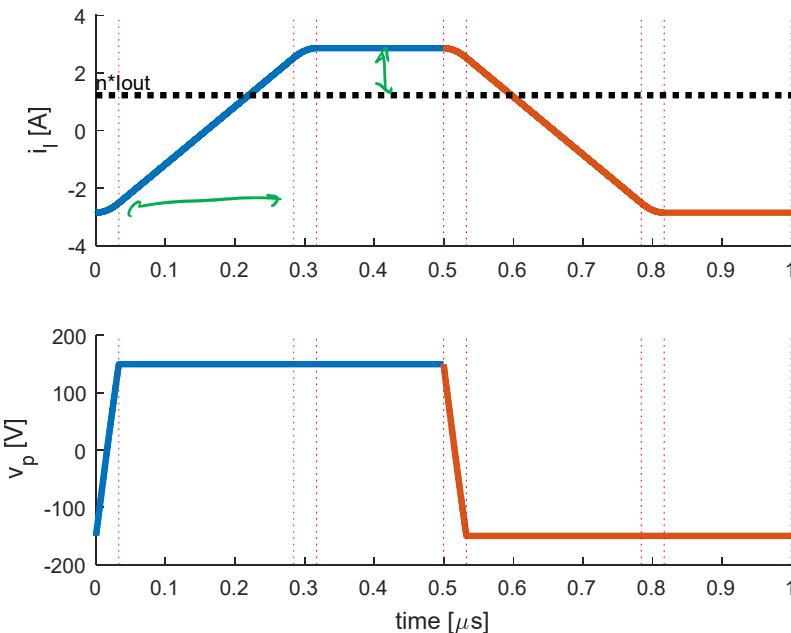



Example Waveforms

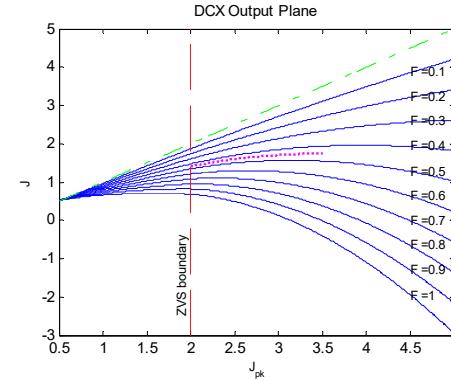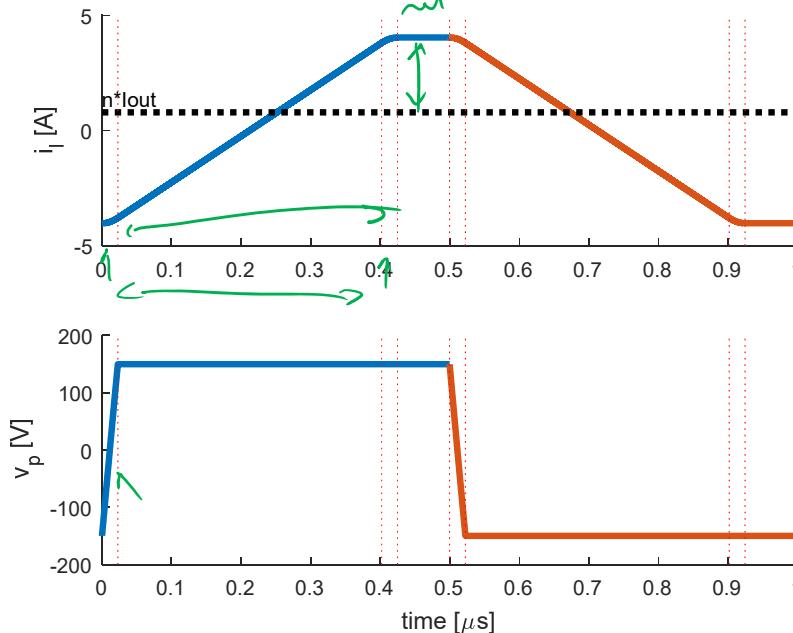


Output Current Vs. Inductance

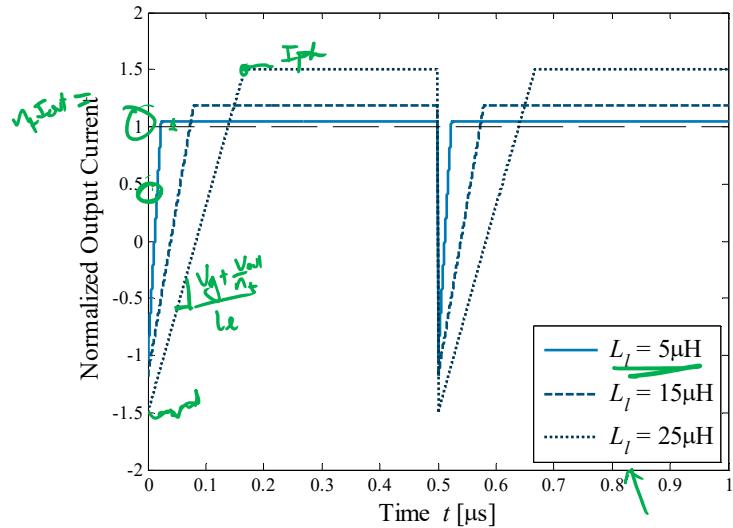


Output Current Vs. Inductance

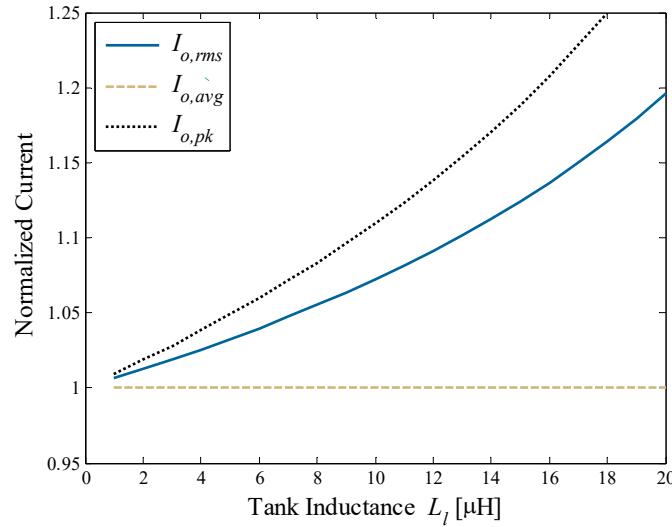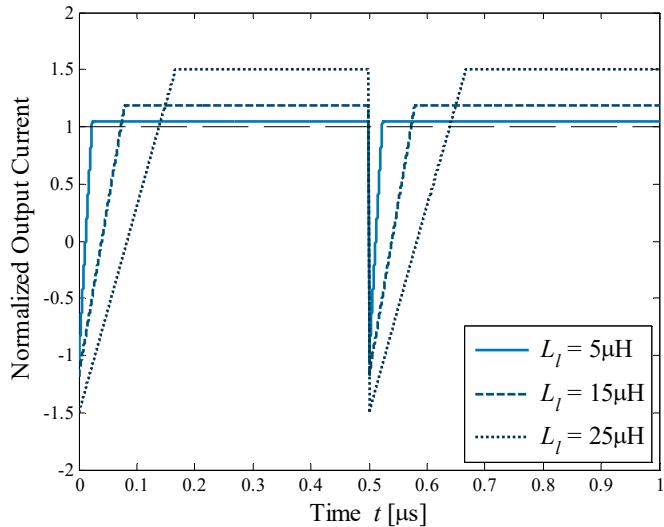

Constraints on Inductance


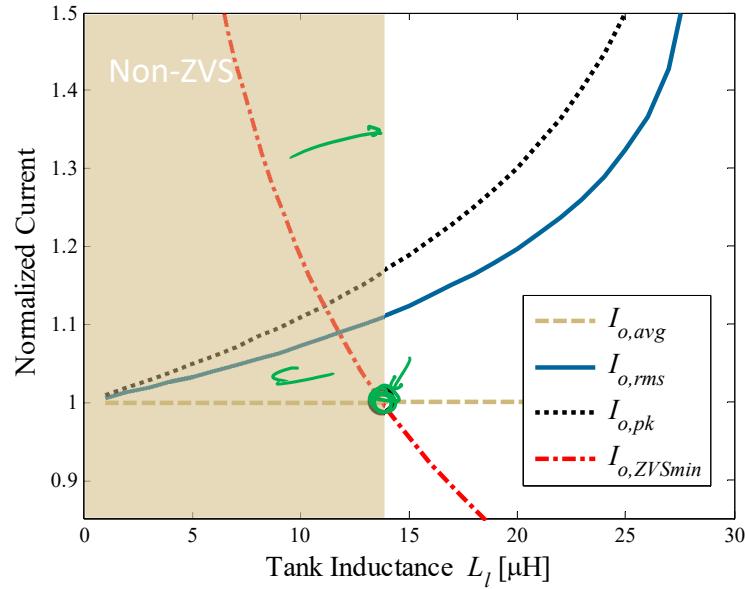


DAB: Experimental Results

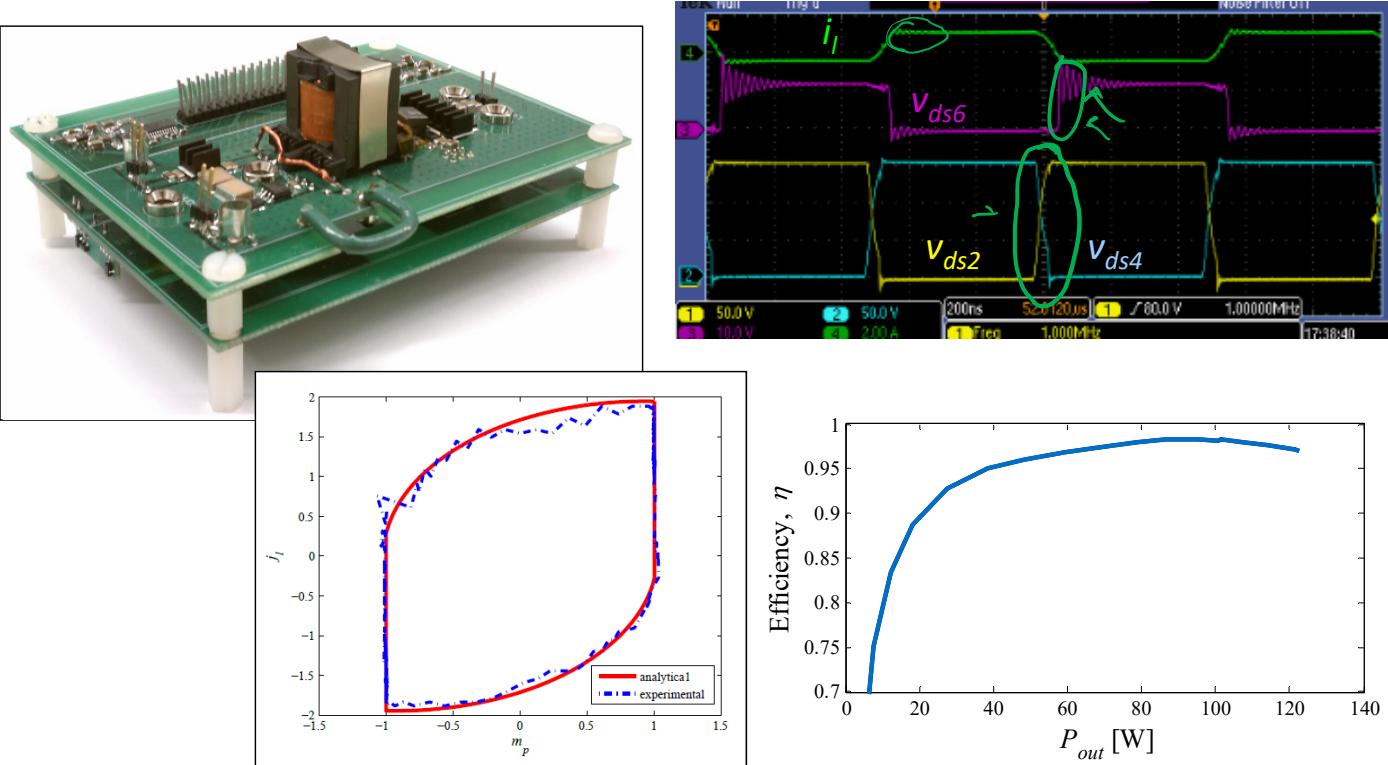

D. Costinett, D. Maksimovic, and R. Zane, "Design and control for high efficiency in high step-down dual active bridge converters operating at high switching frequency," IEEE Trans. Power Electron., vol. PP, no. 99, p. 1, 2012.

Operation with $V \neq nV_g$

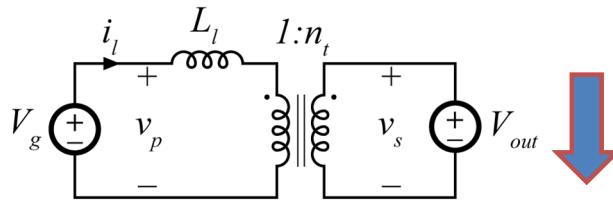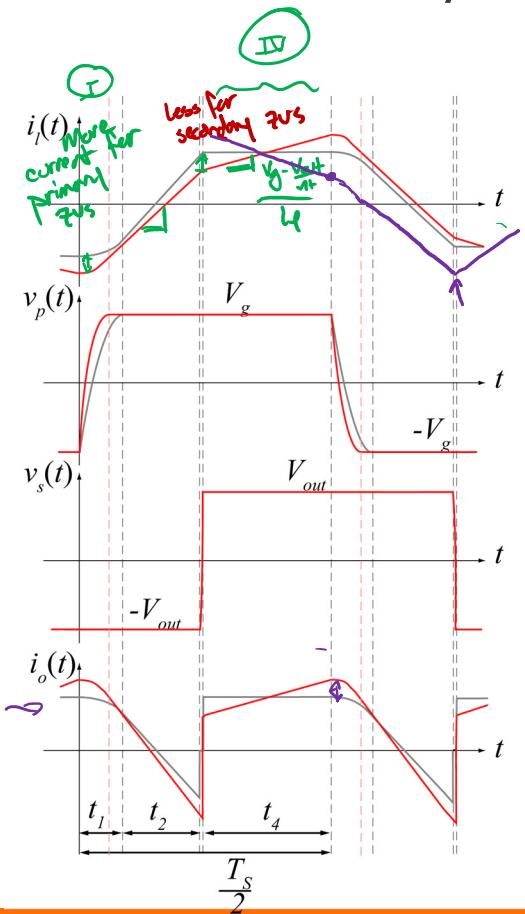

- E.g. Decrease to

$M < 1$

by decreasing output voltage

$M < 1$

if $M > 1$
opposite

- Current now ramping, causing more energy available for primary ZVS, but higher RMS currents
- Can use behavior to extend ZVS range of one bridge