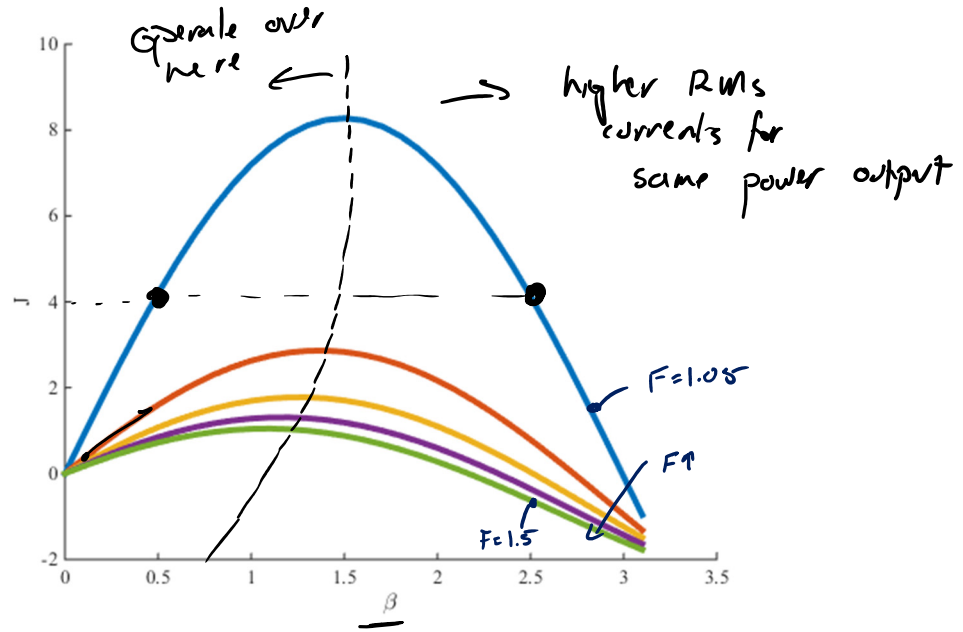


SRC Control Trajectory



Normally want to operate with $F \geq 1$
in SRC

$$F = \frac{f_s}{f_o} \geq 1 \quad f_s \geq f_o$$

→ Gives possibility of ZVS





SRC Current Stress

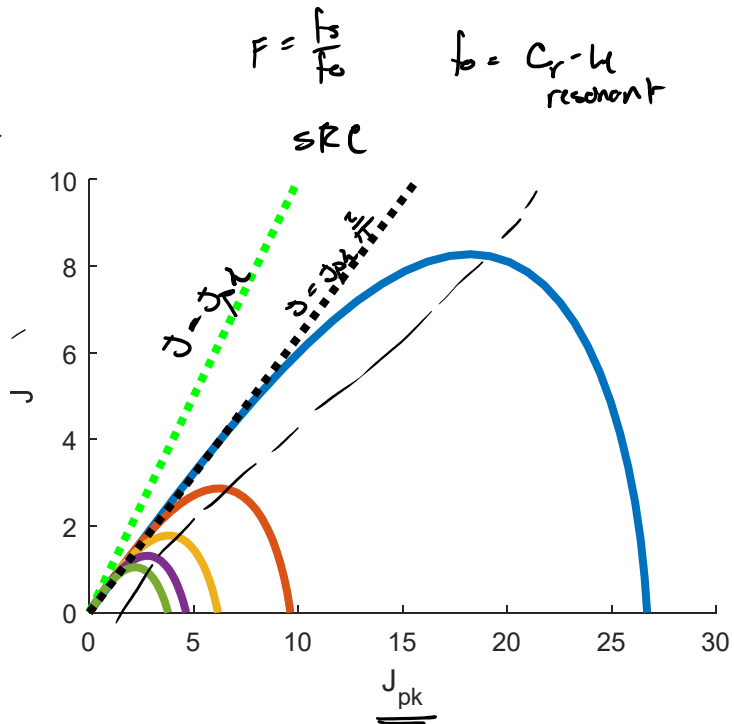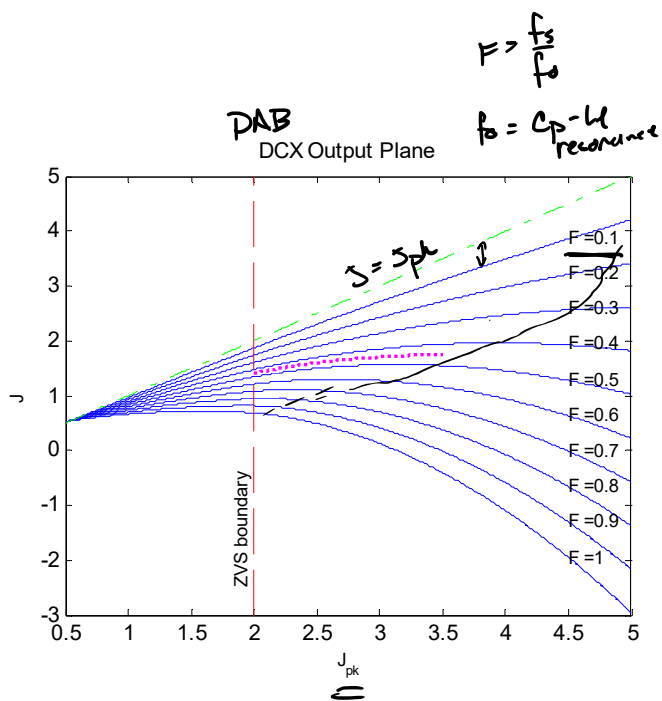


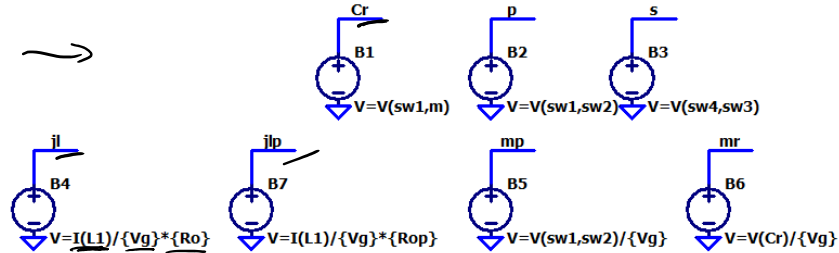
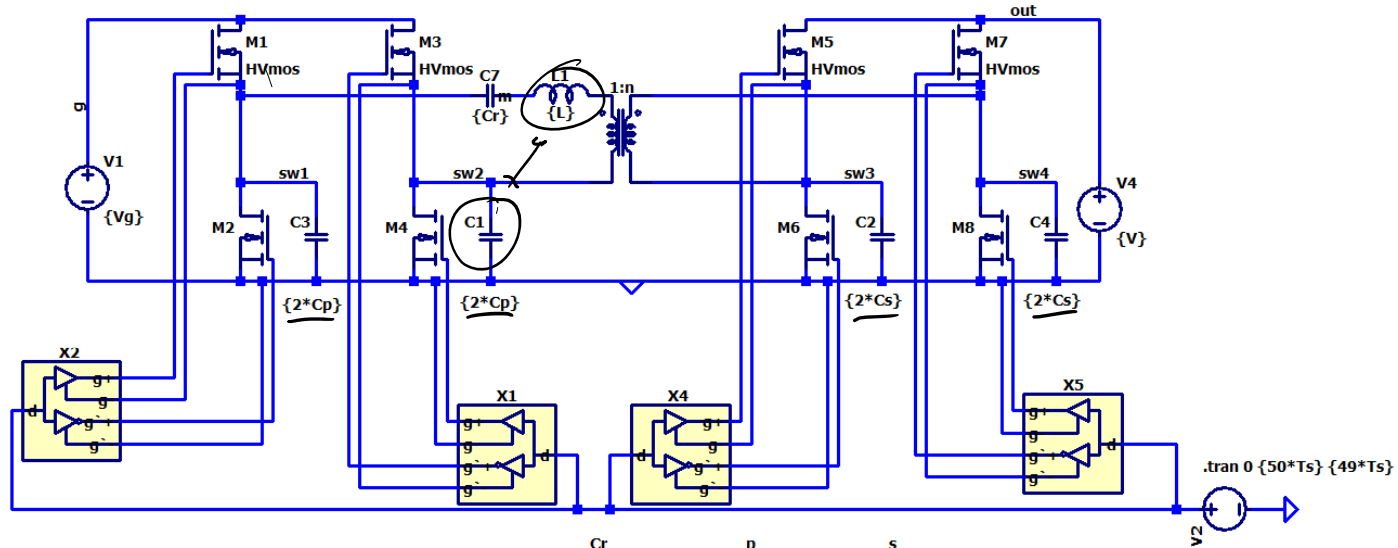
Example Simulation

```
.param Cr={150n} Ro={{L/Cr}*.5} td=70n phi={Ts/2+150n} Rop={{L/Cp}**.5}
.param fs=750k Ts={1/fs} Vg=100 V={Vg} C={100u} Cp=200p Cs={Cp} L={10u}
```



SRC Simulation
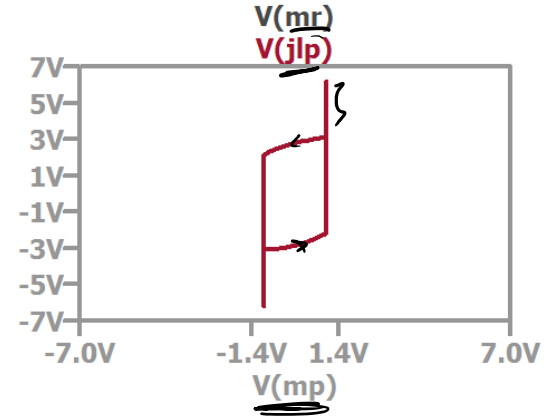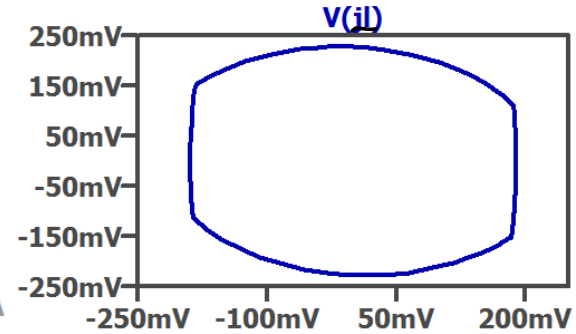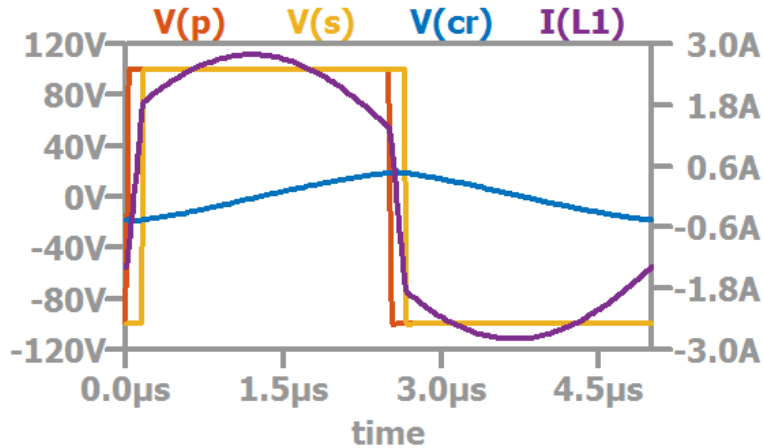
$$\left\{ \begin{array}{l} I_{out} = 2A \\ f_s = 200kHz \\ f_o = 130kHz \\ V_g = 100V \\ V_{out} = 100V \end{array} \right.$$



SRC Simulation




$$I_{out} = 6.5A$$

$$f_s = 200kHz$$

$$f_o = 130kHz$$

$$V_g = 100V$$

$$V_{out} = 100V$$

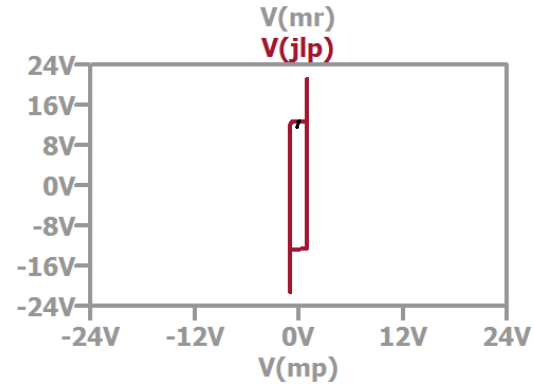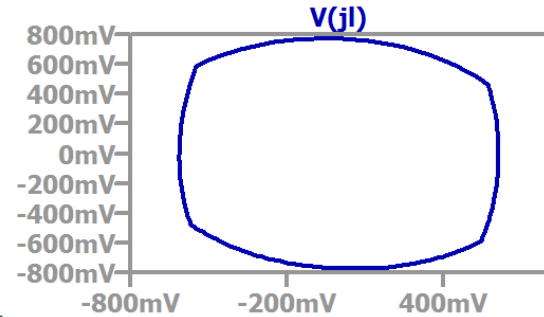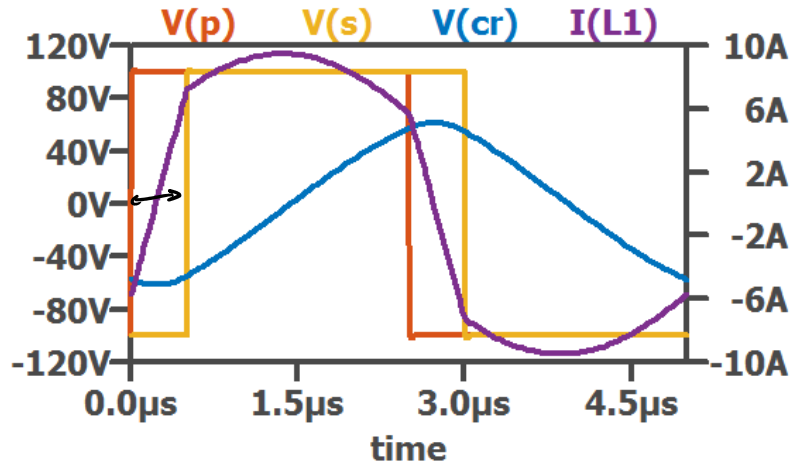

SRC Simulation




$$I_{out} = 500\text{mA}$$

$$f_s = 200\text{kHz}$$

$$f_o = 130\text{kHz}$$



$$V_g = 100\text{V}$$

$$V_{out} = 100\text{V}$$

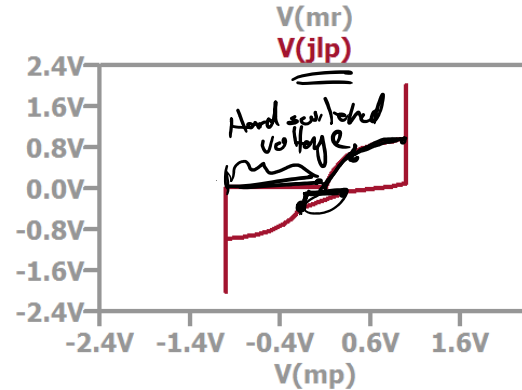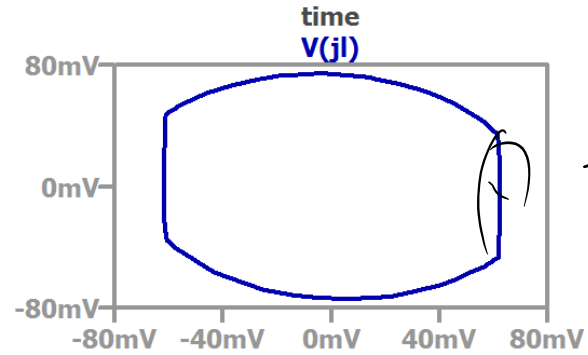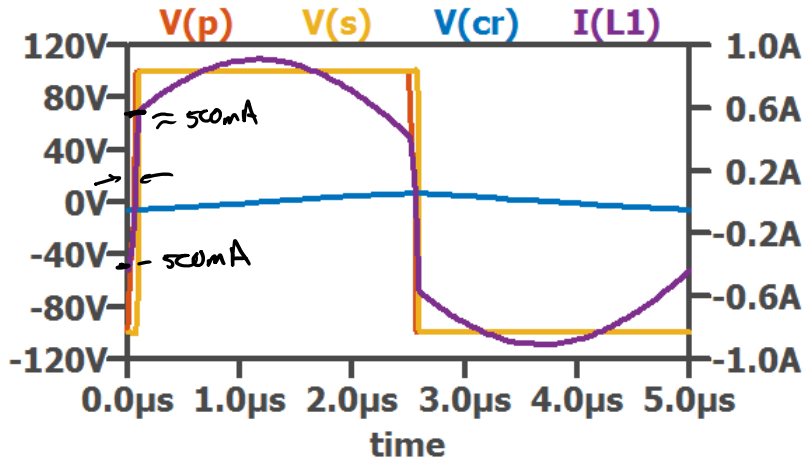




SRC Simulation

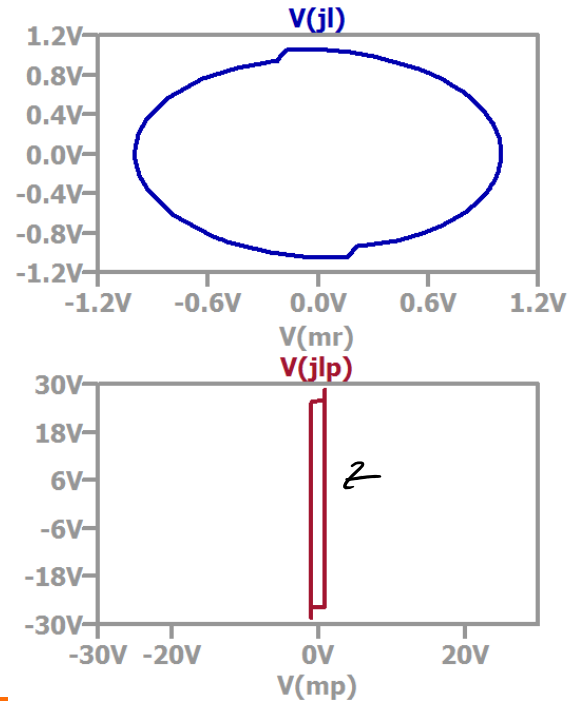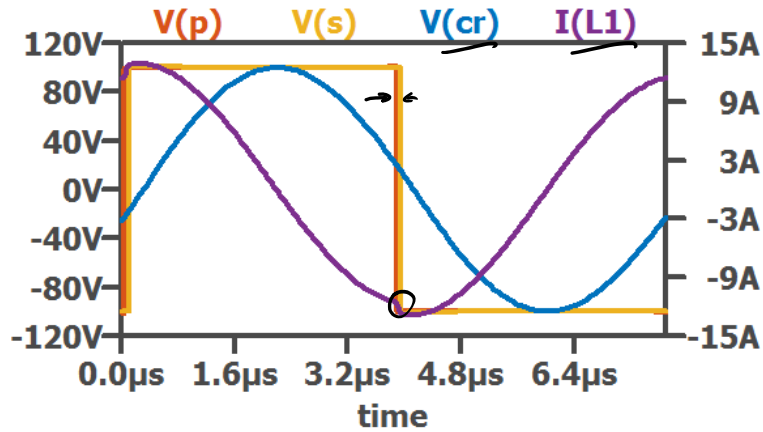$I_{out} = 1.2A$
→ $f_s = 130kHz$
 $f_o = 130kHz$ } $F = 1$
 $V_g = 100V$
 $V_{out} = 100V$






SRC Simulation

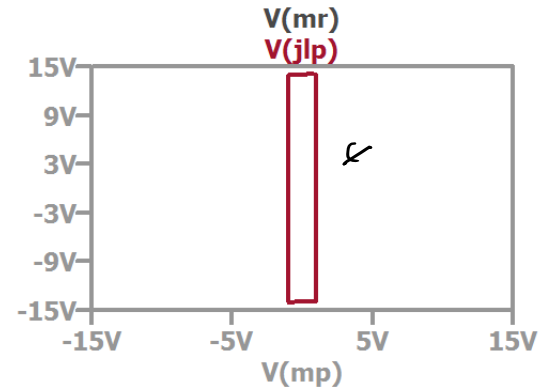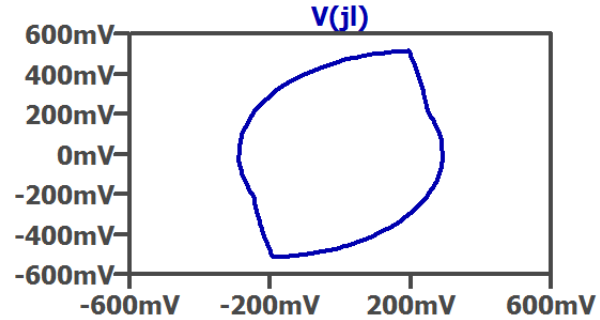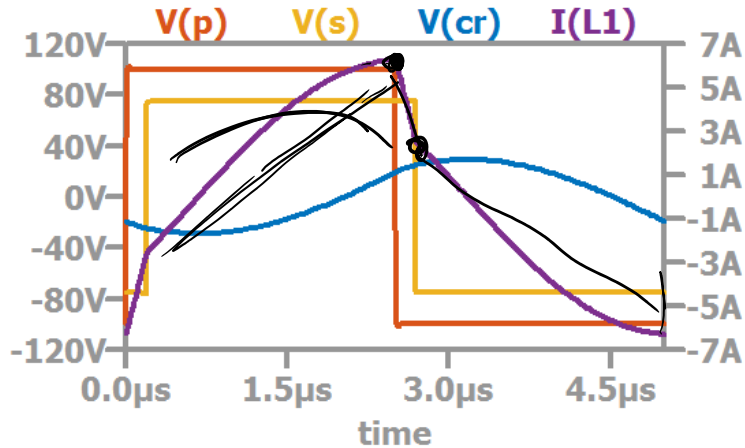$I_{out} = 3A$
 $f_s = 200kHz$
 $f_o = 130kHz$
 $V_g = 100V$
 $V_{out} = 75V$



SRC Simulation

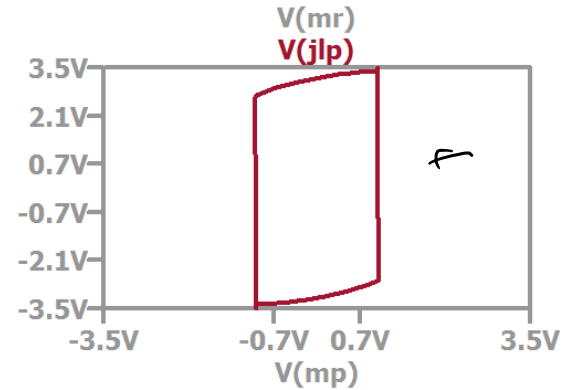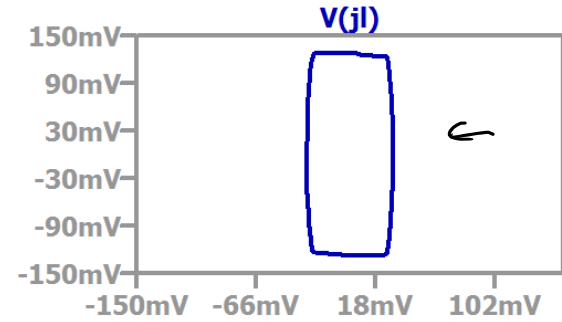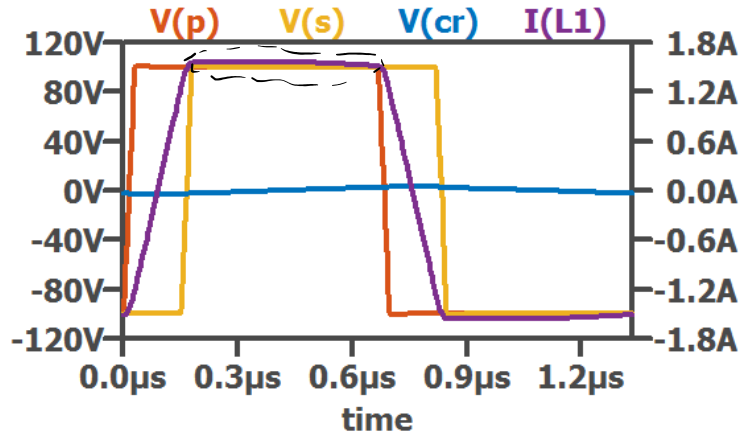$I_{out} = 1A$
→ $f_s = 750kHz$ $F \gg 1$
→ $f_o = 130kHz$
 $V_g = 100V$
 $V_{out} = 100V$



DAB vs SRC

$V_{out} = nV_g$


$V_{out} > nV_g$

$V_{out} > 5nV_g$

— $V_{in} = 1.0, V'_{out} = 1.0$ - - - $V_{in} = 1.0, V'_{out} = 1.2$ ····· $V_{in} = 1.0, V'_{out} = 1.4$


DAB

$\frac{1}{F} = f_r / f_s \rightarrow 0$

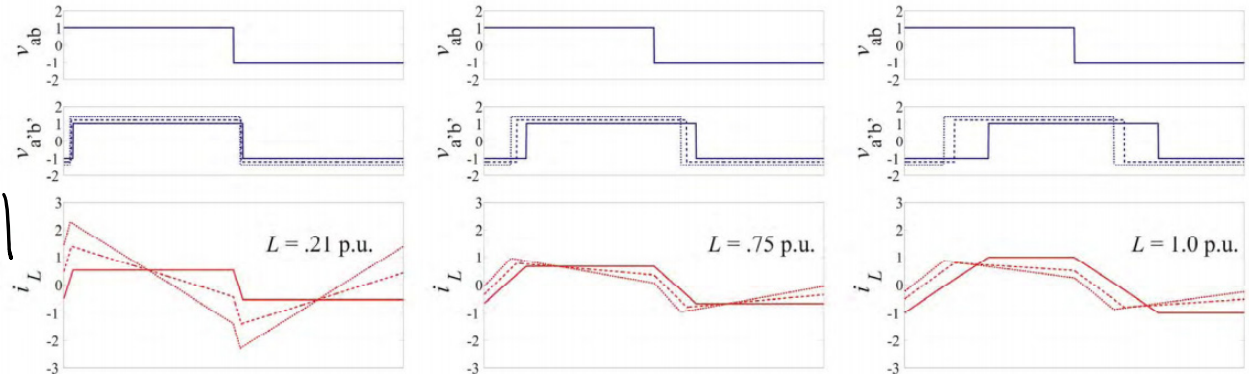

SRC

$\frac{1}{F} = f_r / f_s = 0.95$

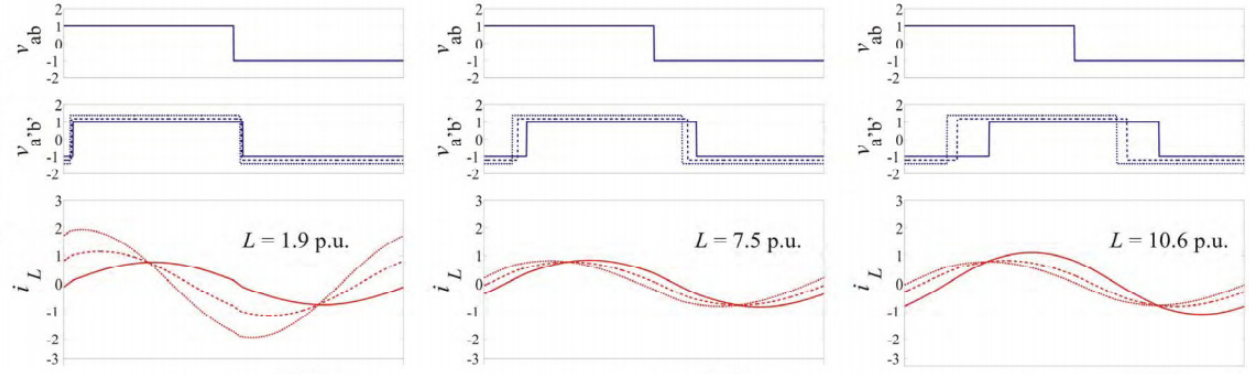

$\varphi_{1.0/1.0} = 10^\circ$

$\varphi_{1.0/1.0} = 45^\circ$

$\varphi_{1.0/1.0} = 90^\circ$



P_{out}

$S_T = V_T \cdot I_T$
(rms)

Normalized by P_{out}



















XF Voltage

RMS

$f_i/f_s = 0$ (DAB)

$f_i/f_s = .75$

$f_i/f_s = .95$

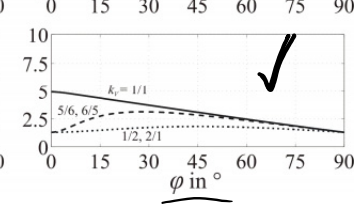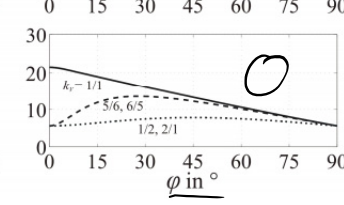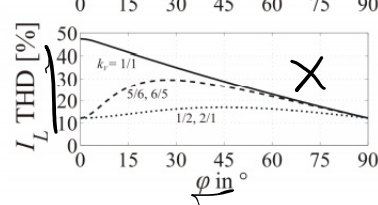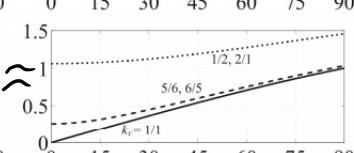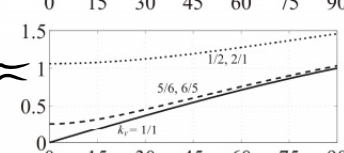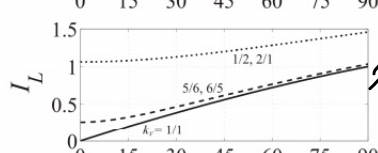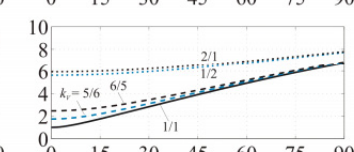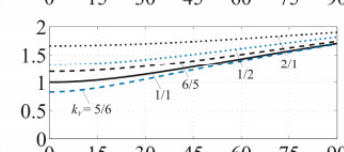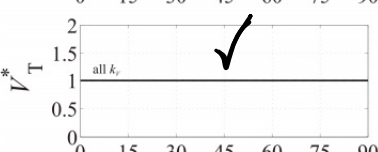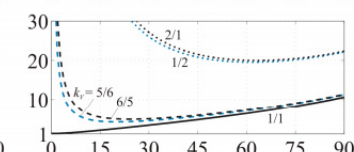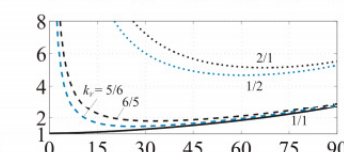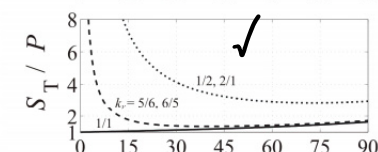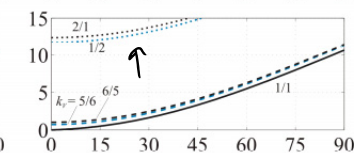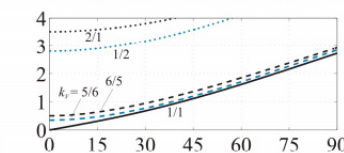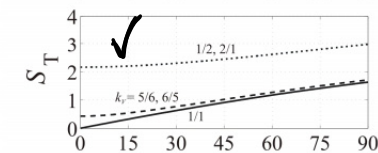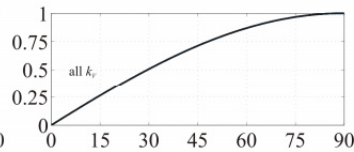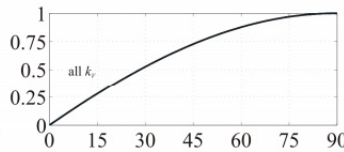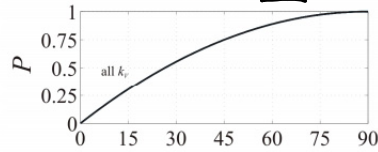

DAB vs SRC: Conclusions

DAB

- + Smaller resonant tank
- + Smaller RMS currents
- + Wider Soft-switching range

SRC

- + Can be designed with larger XF inductance
- + Lower AC winding losses
- + Reduced device turn-off losses

