

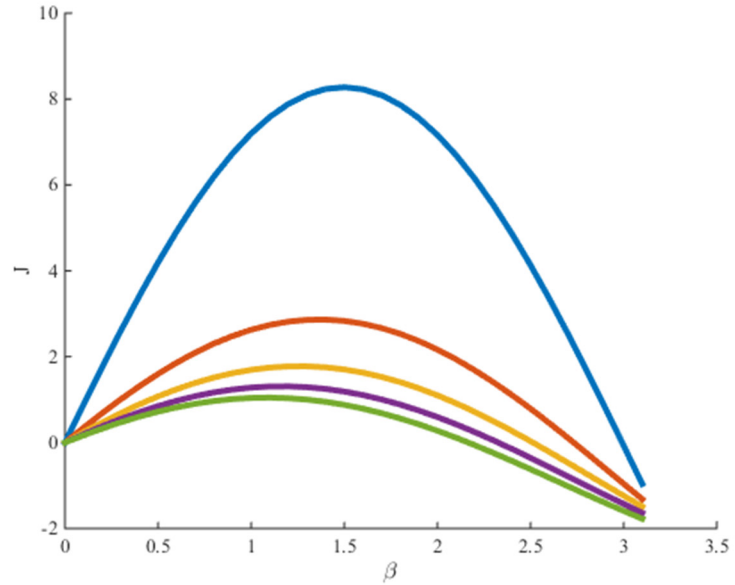


# SRC Control Trajectory

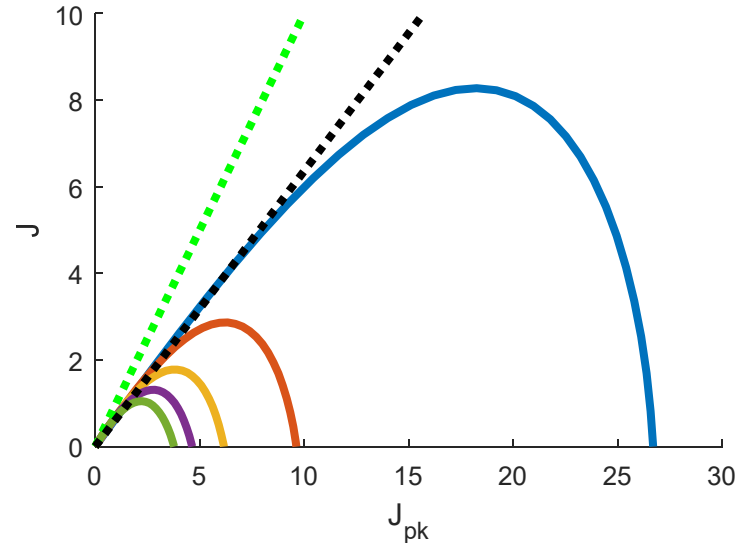


# SRC Current Stress

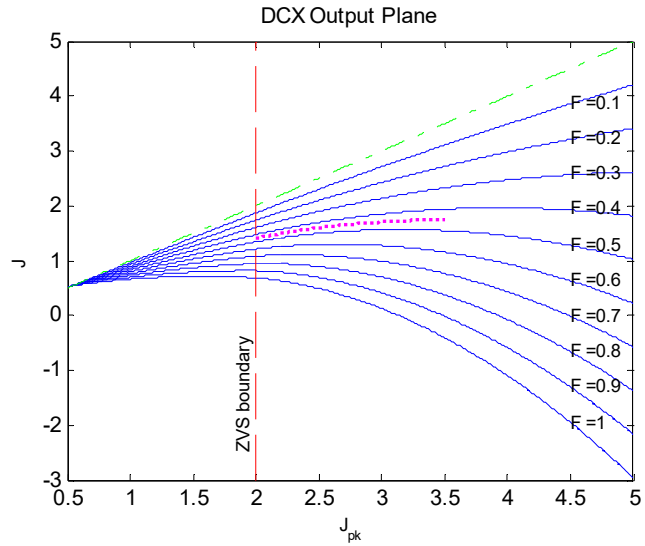



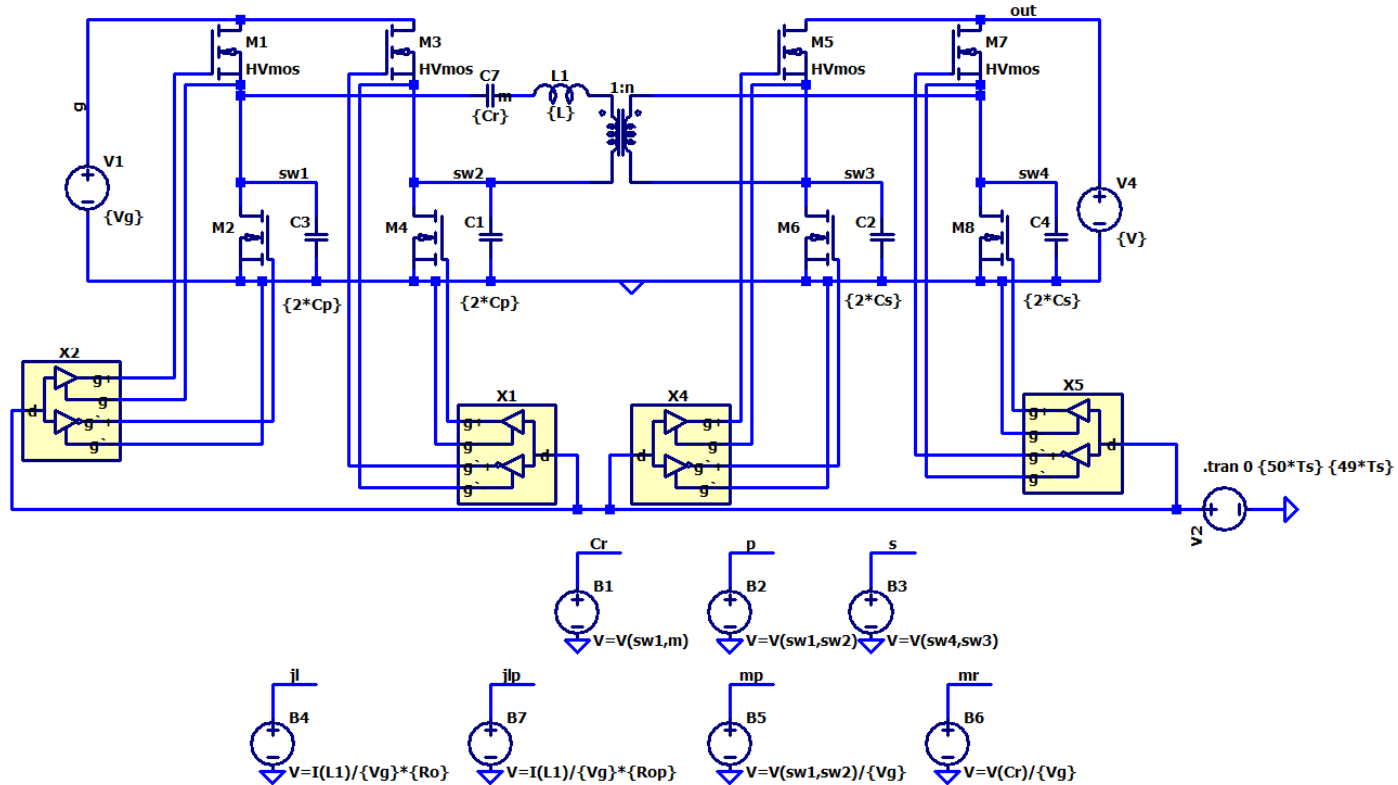
# Example Simulation

```
.param Cr={150n} Ro={{L/Cr}*.5} td=70n phi={Ts/2+150n} Rop={{L/Cp}**.5}
.param fs=750k Ts={1/fs} Vg=100 V={Vg} C={100u} Cp=200p Cs={Cp} L={10u}
```


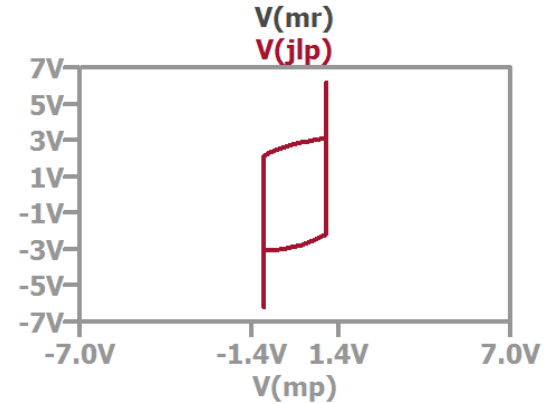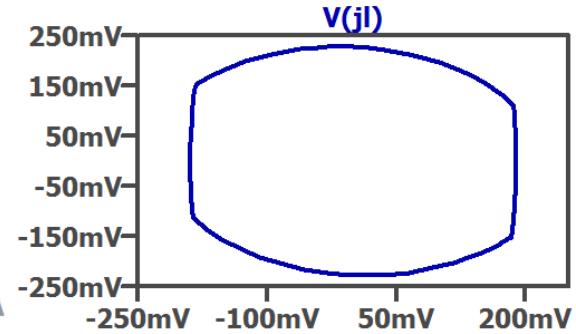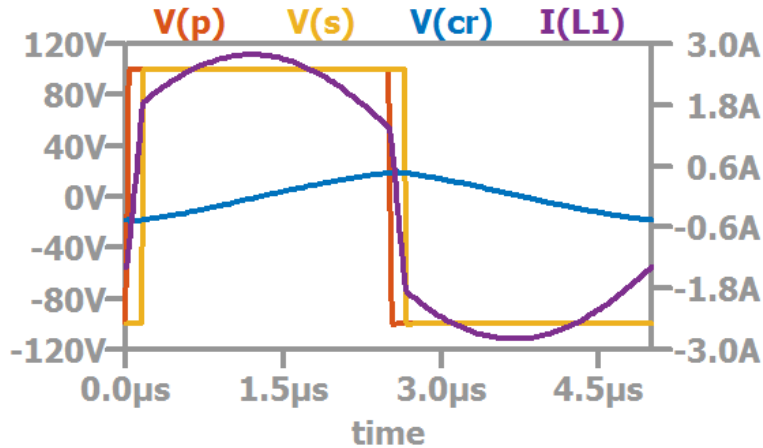
# SRC Simulation

$I_{out} = 2A$   
 $f_s = 200kHz$   
 $f_o = 130kHz$   
 $V_g = 100V$   
 $V_{out} = 100V$



# SRC Simulation




$$I_{out} = 6.5A$$

$$f_s = 200kHz$$

$$f_o = 130kHz$$

$$V_g = 100V$$

$$V_{out} = 100V$$

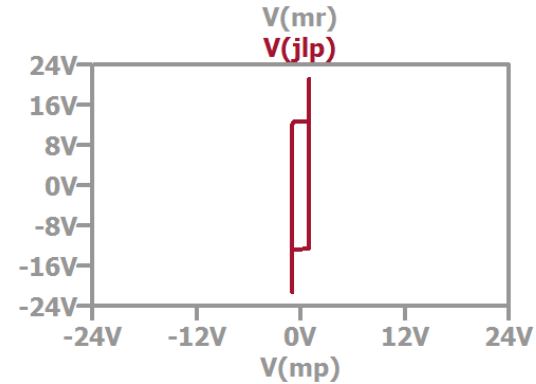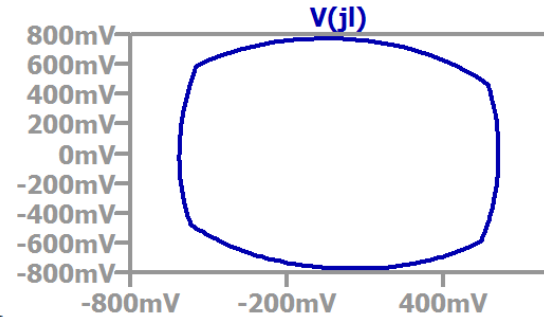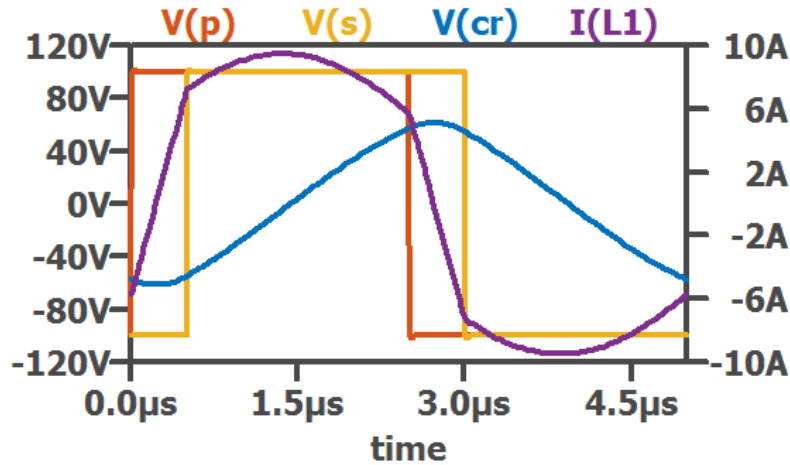

# SRC Simulation




$I_{out} = 500\text{mA}$

$f_s = 200\text{kHz}$

$f_o = 130\text{kHz}$

$V_g = 100\text{V}$

$V_{out} = 100\text{V}$

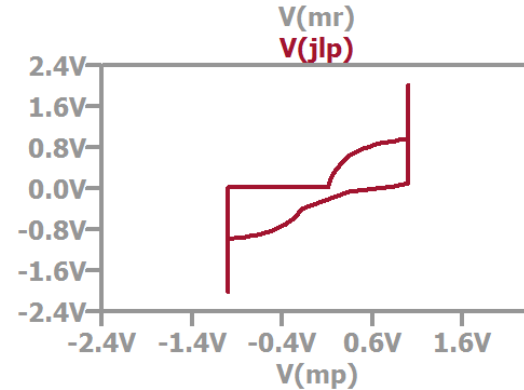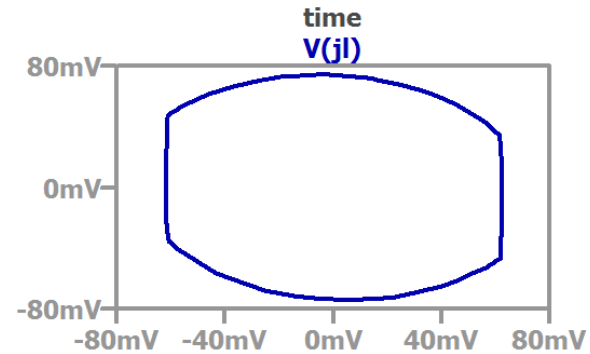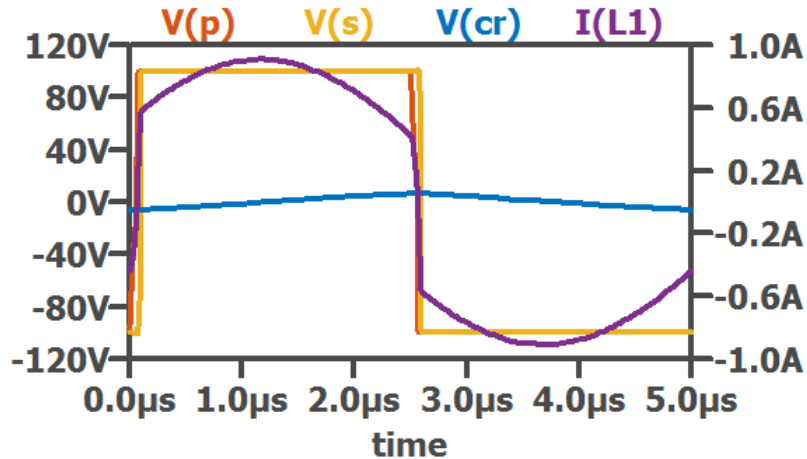

# SRC Simulation



$$I_{out} = 1.2A$$

$$f_s = 130kHz$$

$$f_o = 130kHz$$

$$V_g = 100V$$

$$V_{out} = 100V$$

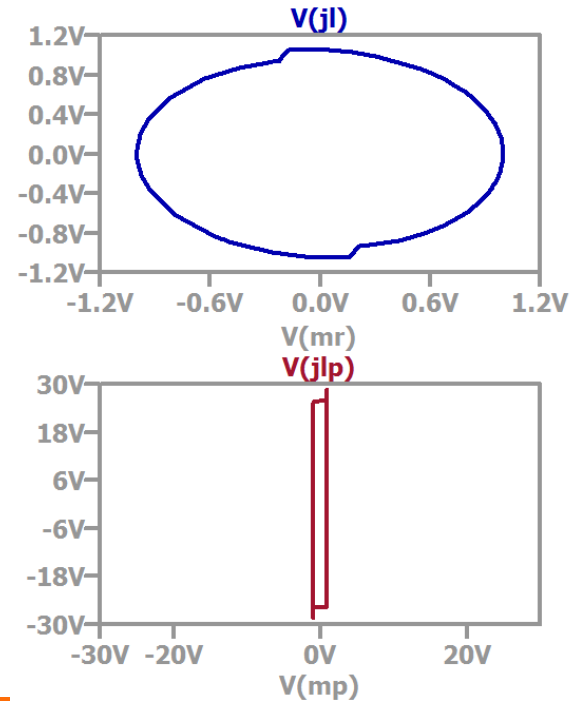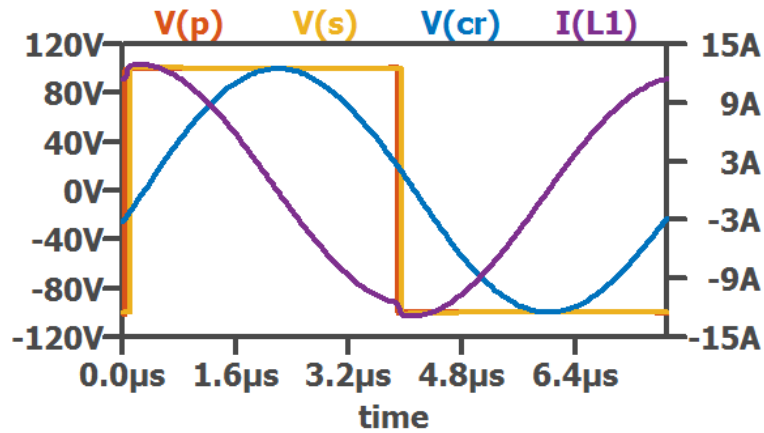

# SRC Simulation




$$I_{out} = 3A$$

$$f_s = 200kHz$$

$$f_o = 130kHz$$

$$V_g = 100V$$

$$V_{out} = 75V$$

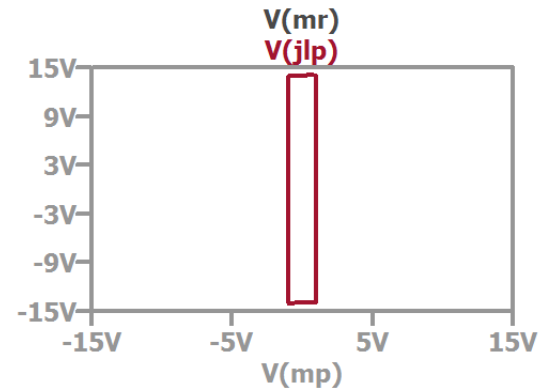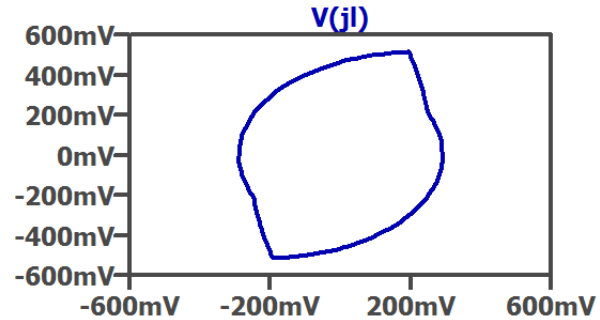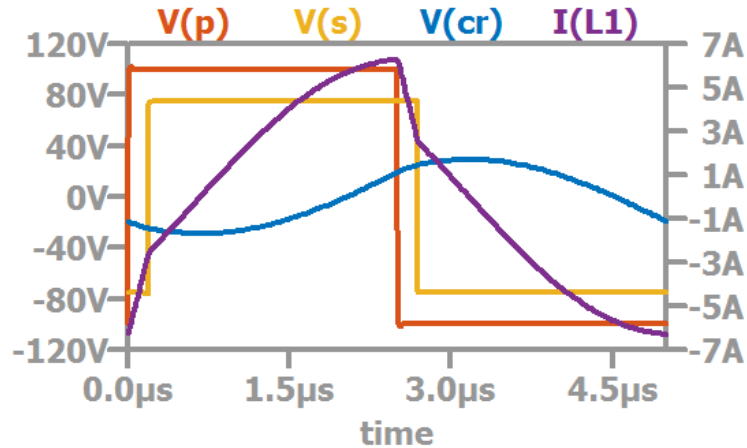



# SRC Simulation




$$I_{out} = 1A$$

$$f_s = 750kHz$$


$$f_o = 130kHz$$


$$V_g = 100V$$

$$V_{out} = 100V$$

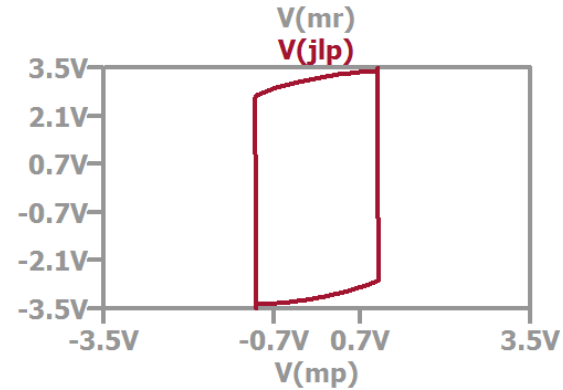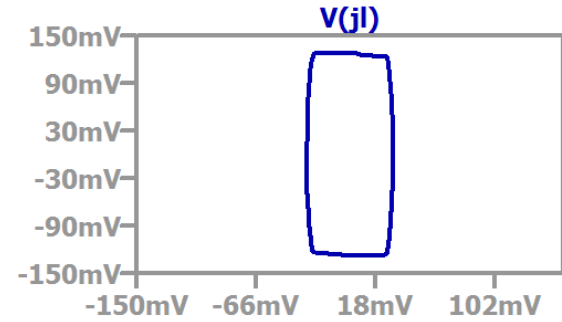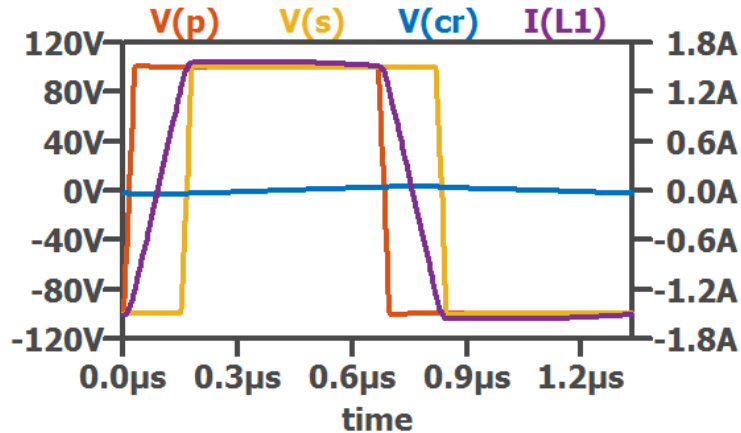

# DAB vs SRC

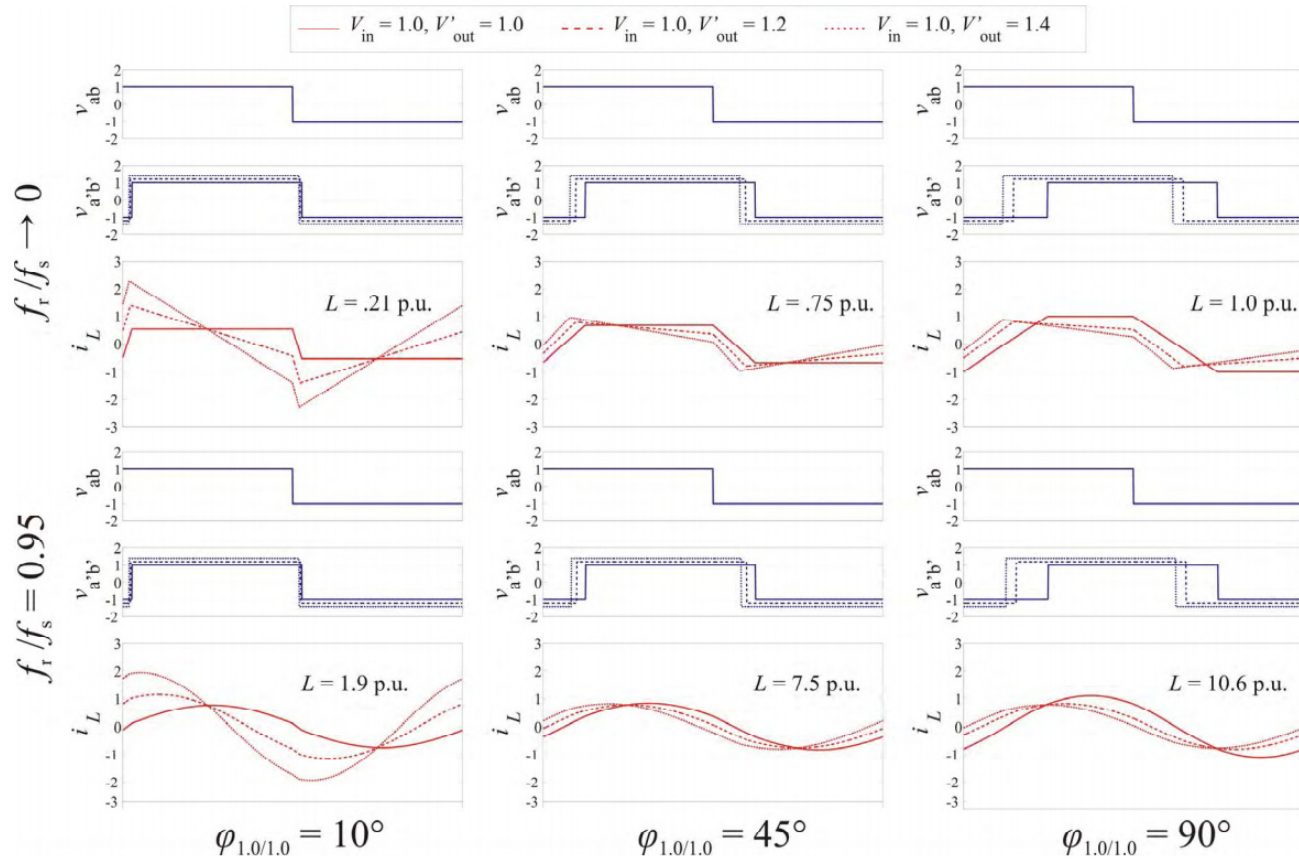

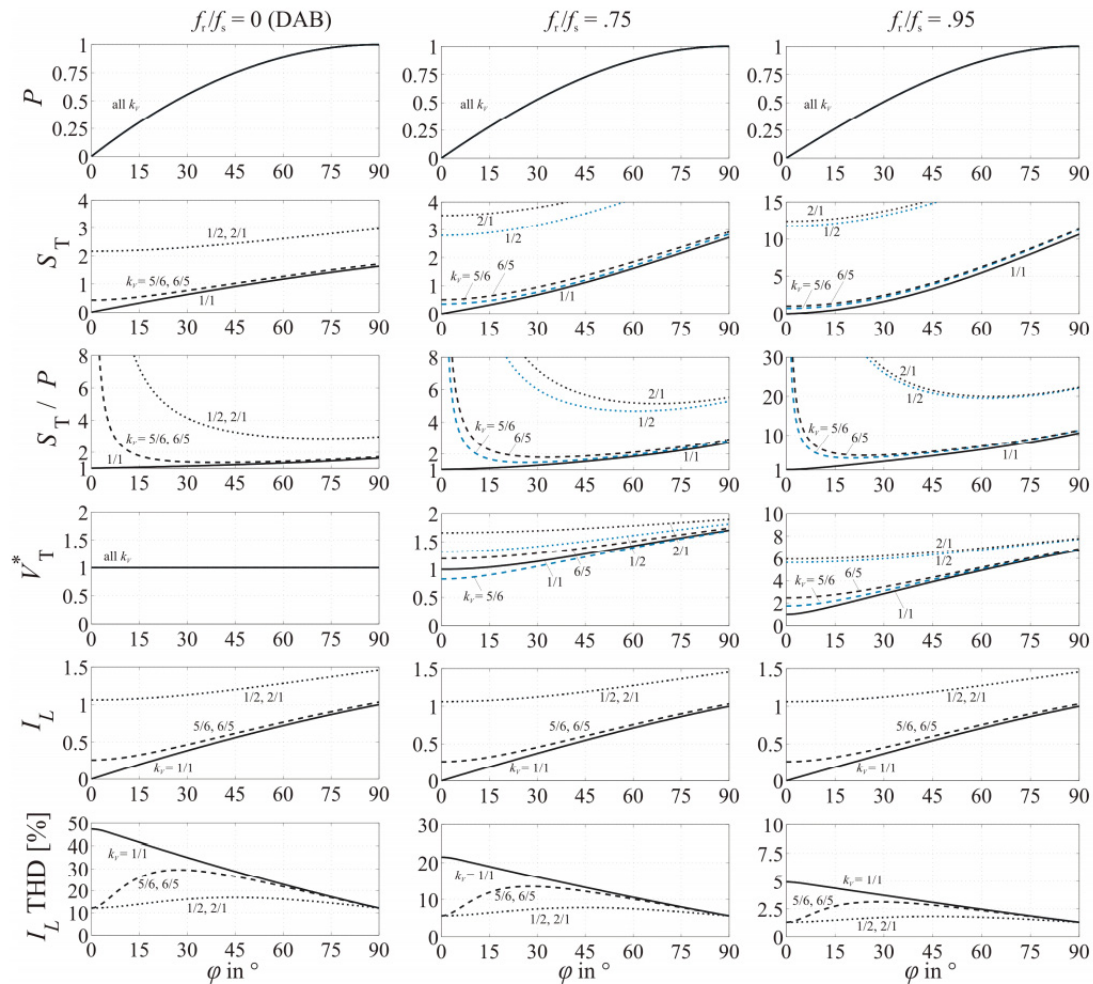

# DAB vs SRC: Conclusions

## DAB

- + Smaller resonant tank
- + Smaller RMS currents
- + Wider Soft-switching range

## SRC

- + Can be designed with larger XF inductance
- + Lower AC winding losses
- + Reduced device turn-off losses