
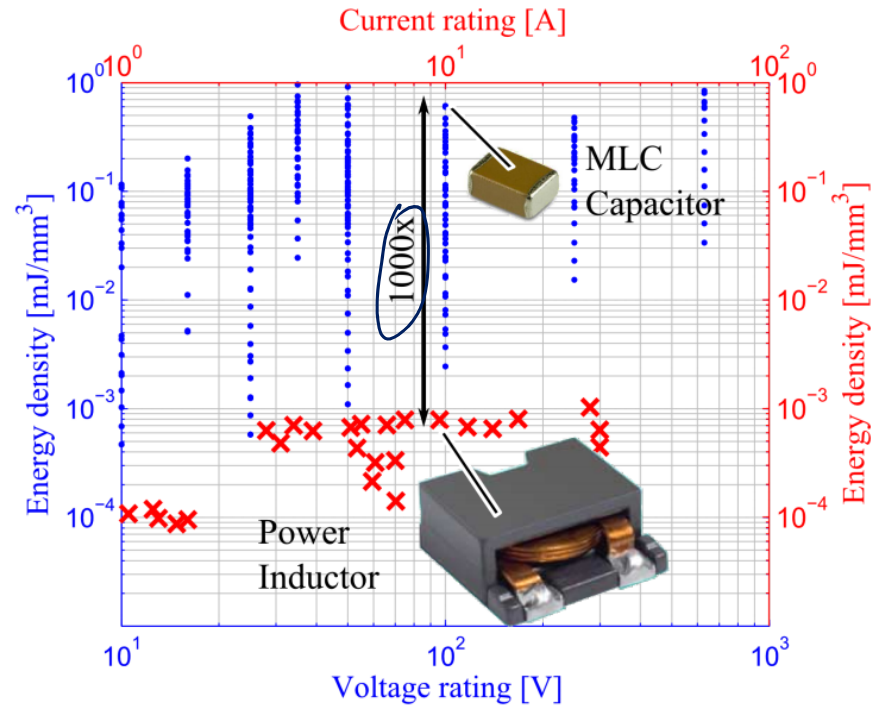


Switched Capacitor Converters

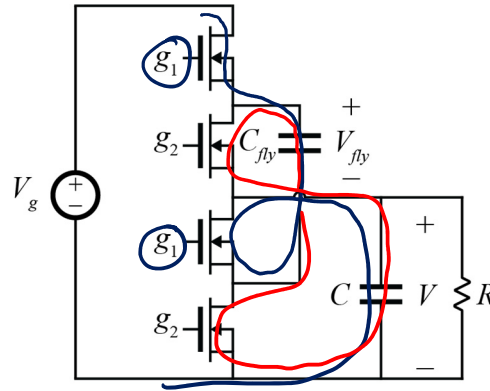

A 2:1 SC Converter



Assume:


- All C's are large, $V \approx \text{const}$
 $\rightarrow \underline{V_{fly} \approx \text{const}}$

- All time intervals long enough for any R-C time constants to converge to final value

(I) $V_g = V + V_{fly}$

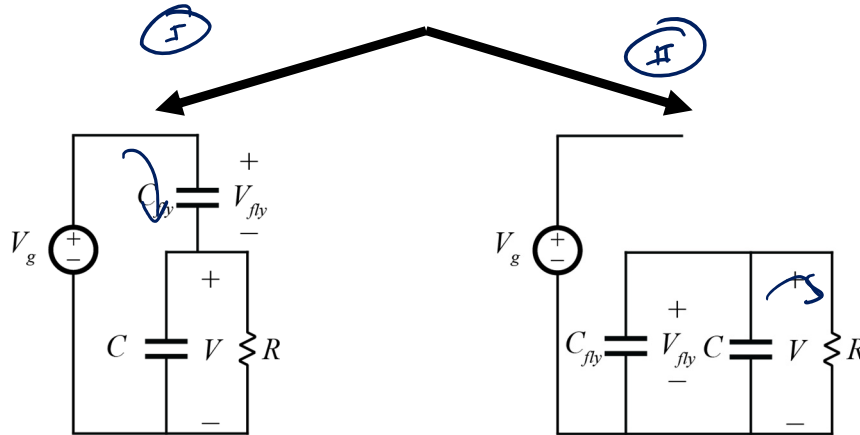(II) $V_{fly} = V$

$V_g = 2V \rightarrow \boxed{V = \frac{1}{2} V_g}$




SC Converters

- Fixed conversion ratio
 - Continuous regulation impossible¹ (except linear)
- Not lossless, even with ideal elements
- Can be very small, fully integrated
 - Discrete caps may be smaller & more energy dense than inductors
 - On-chip capacitors are significantly better than on-chip inductors
- Resonant versions can reduce loss
- Hybrid versions can allow regulation

¹D. Wolaver, "Fundamental study of dc to dc conversion systems," dissertation, 1969

Capacitor Charging: Voltage Source

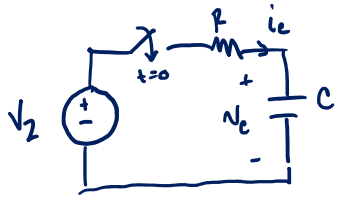

$$V_c(t=0) = V_1$$

At/after $t_c \gg RC$


$$\Delta E_c = \frac{1}{2} C V_2^2 - \frac{1}{2} C V_1^2$$

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2)$$

$$\Delta E_W = \int_0^{t_c} V_2 i_c dt = V_2 \int_{V_1}^{V_2} C dV_c = \overbrace{V_2 C (V_2 - V_1)}^{\Delta E_C} = \Delta E_W$$

$$\begin{aligned} E_{loss} &= \Delta E_W - \Delta E_c = C V_2 (V_2 - V_1) - \frac{1}{2} C (V_2^2 - V_1^2) \\ &= C V_2^2 - C V_2 V_1 - \frac{1}{2} C V_2^2 + \frac{1}{2} C V_1^2 \\ &= \frac{1}{2} C V_2^2 + \frac{1}{2} C V_1^2 - (2) \frac{1}{2} C V_2 V_1 \end{aligned}$$
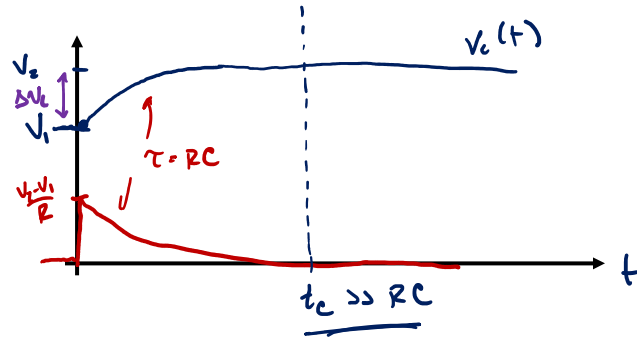
$$E_{loss} = \frac{1}{2} C (V_2 - V_1)^2 = \frac{1}{2} (\Delta V_c)^2$$



$$v_2 - v_1 = \Delta v_c$$

$$\eta = \frac{\Delta E_c}{\Delta E_v} = \frac{\frac{1}{2} \cancel{v_2^2} - \frac{1}{2} v_1^2}{v_2 \cancel{v_2} - v_2 v_1} = \frac{\frac{1}{2} v_2^2 - \frac{1}{2} v_1^2}{v_2^2 - v_2 v_1}$$

$$= \frac{1}{2} \frac{v_c^2 - (v_2 - \Delta v_c)^2}{v_2^2 - v_2 (v_2 - \Delta v_c)} = \frac{1}{2} \frac{\cancel{v_2^2} - \cancel{v_2^2} - (\Delta v_c)^2 + 2 v_2 \Delta v_c}{\cancel{v_2^2} - \cancel{v_2^2} + v_2 \Delta v_c}$$

$$= \frac{1}{2} \left(2 - \frac{\Delta v_c}{v_2} \right)$$


$$\boxed{\eta = 1 - \frac{\Delta v_c}{2v_2}} \rightarrow$$

↑ ↑

if $\Delta v_c \ll v_2 \rightarrow$ high efficiency possible

No dependence on R
except $t_c \gg RC$


Capacitor Charging: Current Source

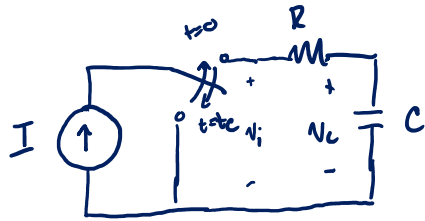

$$V_c(t=0) = V_1$$

$$\frac{I}{C} t_c = (V_2 - V_1)$$

$$t_c = \frac{C(V_2 - V_1)}{I}$$

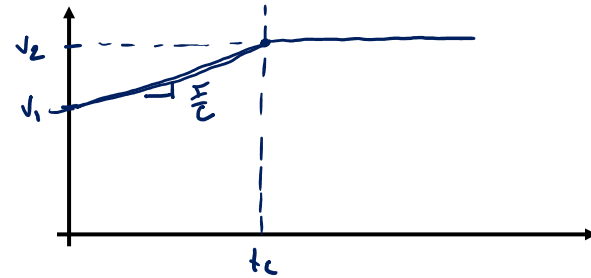

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2) \quad (\text{same})$$

$$\Delta E_I = \int_0^{t_c} V_c I dt = \int_0^{t_c} (V_c + IR) I dt = I \left[\frac{V_2 + V_1}{2} t_c + IR t_c \right]$$

$$= \cancel{I} \frac{V_2 + V_1}{2} \frac{C(V_2 - V_1)}{\cancel{I}} + I \cancel{R} \frac{C(V_2 - V_1)}{\cancel{I}}$$

$$= \frac{1}{2} C (V_2^2 - V_1^2) + IRC (V_2 - V_1)$$

$$= \frac{1}{2} C (V_2^2 - V_1^2) + RC \left[C \frac{V_2 - V_1}{t_c} \right] (V_2 - V_1) =$$

$$\boxed{\frac{1}{2} C (V_2^2 - V_1^2) + \frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}}$$


Eloss
ΔEc
Extra in V-src case
Add'l scale factor

V-src charging	:	$E_{loss} = \frac{1}{2} C (V_2 - V_1)^2$
I-src charging	:	$E_{loss} = \frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}$

if $t_c \gg RC$ ← Current source charging has lower loss

if $t_c \not\gg RC$ → Don't know, V-src charging analysis is only valid for $t_c \gg RC$

Capacitor Charging: Resonant

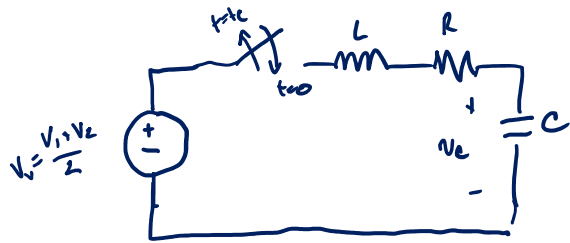

$$v_c(t=0) = V_1$$

$$i_c(t=0) = 0$$

High-efficiency approx: Assume we can use waveforms with $R = 0$ then calculate losses afterwards

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2) \quad (\text{same})$$



$$E_{\text{loss}} = I_{\text{rms}}^2 R t_c = \frac{I_{c, \text{pk}}^2}{2} R t_c$$

$$= \frac{1}{2} R \frac{1}{R_0^2} \frac{(V_2 - V_1)^2}{4} t_c$$

$$= \frac{1}{2} R \frac{1}{R_0^2} \frac{\pi}{\omega_0} \frac{1}{4} (V_2 - V_1)^2$$

$$= \frac{1}{8} \frac{R \pi}{R_0} C (V_2 - V_1)^2 = \frac{1}{2} C (V_2 - V_1)^2 \cdot \frac{R \pi}{4 R_0}$$

Loss in wave comp

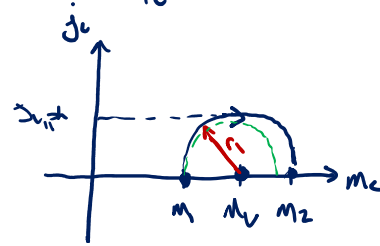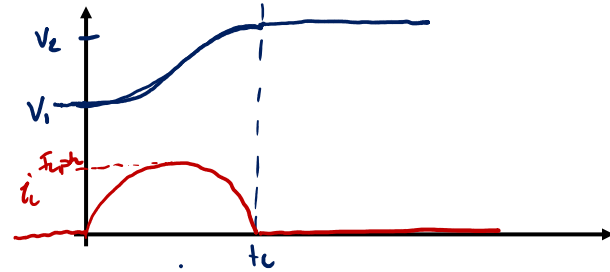

$$\alpha = \pi$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$t_c = \frac{\pi}{\omega_0}$$

$$\Delta q_{\text{pk}} = q_1 = m_2 - m_1$$

$$I_{c, \text{pk}} = \frac{1}{R_0} \left(\frac{V_1 + V_2}{2} - V_1 \right)$$

$$= \frac{1}{R_0} \left(\frac{V_2 - V_1}{2} \right)$$

$$\frac{1}{R_0} \frac{1}{\omega_0} = \sqrt{\frac{C}{L}} \sqrt{LC} = C$$