

Resonant Charging

$$E_{\text{loss}} = \frac{1}{2} C (V_2 - V_1)^2 \frac{R}{R_0} \frac{\pi}{4} \rightarrow \frac{R}{R_0} \rightarrow \text{High-Q resonance for low loss}$$


$$\frac{1}{R_0} = \sqrt{\frac{C}{L}} = \frac{1}{\sqrt{LC}} \cdot C = C \omega_0 = \underline{\underline{C \frac{\pi}{t_c} = \frac{1}{R_0}}}$$

$$E_{\text{loss}} = \frac{1}{2} C (V_2 - V_1)^2 \frac{RC \pi^2}{4 t_c}$$

→

$$t_c \gg RC \text{ for low loss (still)}$$
$$\frac{\pi^2}{4} \approx \underline{\underline{2.5}}$$

Cap-Cap Charging

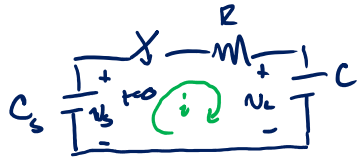

$$v_C(t=0) = v_1$$

$$v_s(t=0) = v_3$$

charge conservation

$$v_3 C_s + v_1 C = (C + C_s) v_2$$


$$v_3 = \left(\frac{C}{C_s} + 1\right) v_2 - \frac{C}{C_s} v_1 = \frac{C}{C_s} (v_2 - v_1) + v_2$$

$$\Delta E_C = \frac{1}{2} C (v_2^2 - v_1^2) \quad (\text{same})$$

$$\Delta E_s = \frac{1}{2} C_s (v_3^2 - v_2^2)$$

$$= \frac{1}{2} C_s \left[(v_2 - v_1)^2 \left(\frac{C}{C_s}\right)^2 + \cancel{v_2^2} + 2 \frac{C}{C_s} v_2 (v_2 - v_1) - \cancel{v_2^2} \right]$$
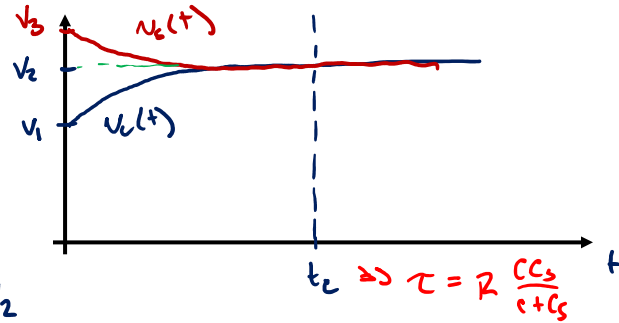
$$= \frac{1}{2} C_s \left[\left(\frac{C}{C_s}\right)^2 (v_2^2 + v_1^2 - 2v_1 v_2) + 2 \frac{C}{C_s} (v_2^2 - v_1 v_2) \right]$$



$$\begin{aligned}
E_{\text{loss}} &= \Delta E_s - \Delta E_c \\
&= \frac{1}{2} \frac{c^2}{c_s} (v_2^2 + v_1^2 - 2v_1 v_2) + c(v_2^2 - v_1 v_2) - \frac{1}{2} c v_2^2 + \frac{1}{2} c v_1^2 \\
&= \left(\frac{1}{2} \frac{c^2}{c_s} + \frac{1}{2} c \right) v_2^2 + \left(\frac{1}{2} \frac{c^2}{c_s} + \frac{1}{2} c \right) v_1^2 + \left(-\frac{c^2}{c_s} - c \right) v_1 v_2 \\
&= \frac{1}{2} c \left[\left(\frac{c}{c_s} + 1 \right) v_2^2 + \left(\frac{c}{c_s} + 1 \right) v_1^2 - 2 \left(\frac{c}{c_s} + 1 \right) v_1 v_2 \right]
\end{aligned}$$

$$E_{\text{loss}} = \frac{1}{2} c \left(\frac{c}{c_s} + 1 \right) (v_2 - v_1)^2$$

↳ Add'l term relative to v-src changing

if $c_s \gg c \rightarrow$ back to v-src changing solution

if $c_s = c \rightarrow$ 2x losses from v-src changing

if $c_s \ll c \rightarrow$ high losses

Comparison of Capacitor Charging

for charging C from V_1 to V_2 in time t_c

Loss

Voltage source

$$\frac{1}{2} C (V_2 - V_1)^2$$

Assumptions

$$\underline{\underline{t_c \gg RC = \tau}}$$

Current source

$$\frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}$$

X

Resonant

$$\frac{1}{2} C (V_2 - V_1)^2 \frac{\pi^2 RC}{4 t_c}$$

High-Q resonance

$$R_0 \gg R \rightarrow t_c \gg \pi RC$$

Cap - Cap


$$\frac{1}{2} C (V_2 - V_1)^2 \left(\frac{C}{C_s} + 1 \right)$$

$$t_c \gg R \frac{C C_s}{C + C_s} = \tau$$






2:1 SC Revisited

Remove small-ripple on C_{fly}

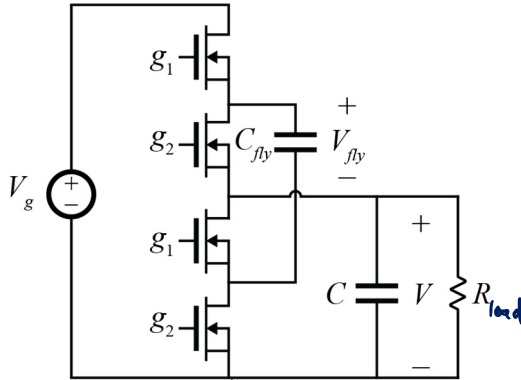

(I) (II)

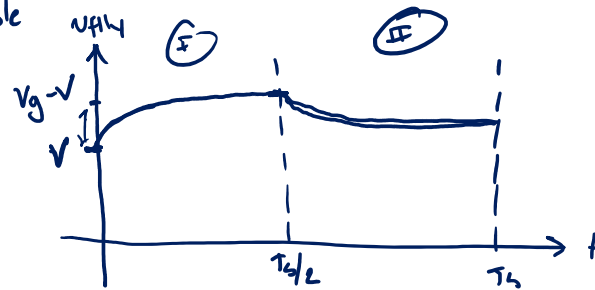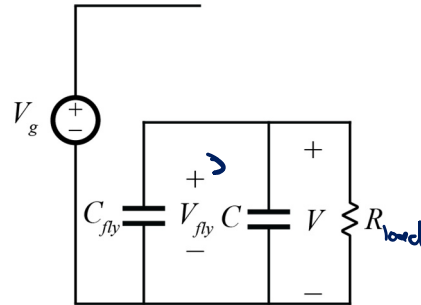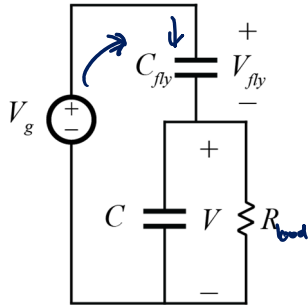

Assume $T_{d/2} \gg RC_{fly}$
 $R = \text{equivalent resistance}$
 $= ESR_{eff} + 2R_{on}$

Energy loss:

$$\begin{cases} \text{(I)} & E_{loss} = \frac{1}{2} C_{fly} (V_g - V - v)^2 \\ \text{(II)} & E_{loss} = \frac{1}{2} C_{fly} (V_g - V - v)^2 \end{cases}$$


$$P_{loss} = C_{fly} (V_g - 2V)^2 f_s$$

$$P_{in} = V_g C_{fly} (V_g - 2V) f_s$$


Equivalent Circuit Model

$$P_{loss} = \underbrace{C_{fly} f_s}_{\text{green}} (V_g - 2V)^2$$
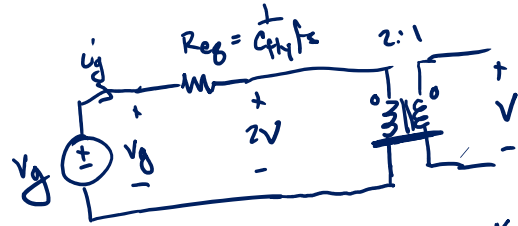
$$P_{in} = V_g \underbrace{C_{fly} f_s}_{\text{green}} (V_g - 2V)$$



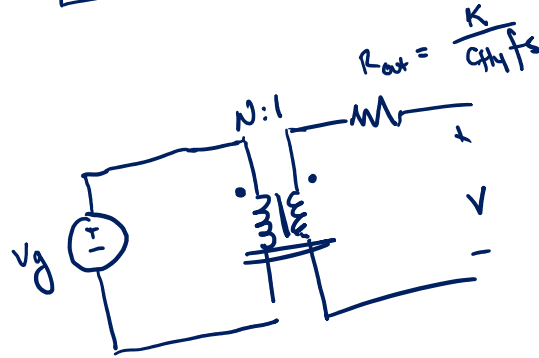($\frac{1}{4C_{fly}f_s}$ in the 2:1 case)




For high η , want small R_{out}

- Large C_{fly}
- High f_s

can continue ch until $\frac{T_s}{2} = t_c \gg R_{out} C_{fly}$

2:1 – Current Loaded

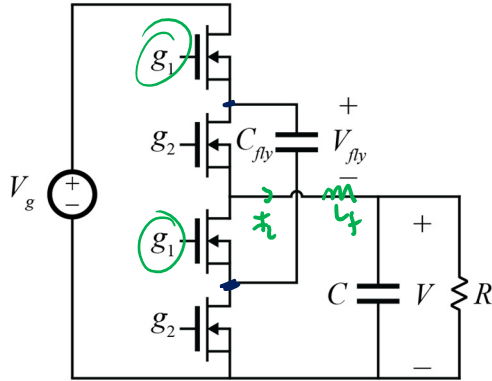

2:1 SC, current loaded

3-level Buck converter @ $D = 50\%$

2:1 : FCML converter

Add $L_f \rightarrow$ large, filter element with small ripple

$$\begin{aligned} \textcircled{I} \quad E_{\text{loss}} &= \frac{1}{2} C_{fly} (V_2 - V_1)^2 \frac{2RCf_{th}}{t_c} \\ \textcircled{II} \quad E_{\text{loss}} &= \frac{1}{2} C_{fly} (V_2 - V_1)^2 \frac{2RCf_{th}}{t_c} \end{aligned} \quad \left. \vphantom{\begin{aligned} \textcircled{I} \\ \textcircled{II} \end{aligned}} \right\} t_c = \frac{T_s}{2}$$

$$\text{total loss} = C_{fly}^2 (V_2 - V_1)^2 \frac{4R}{T_s} f_s$$

$$\left[C_{fly} (V_2 - V_1) \right]^2 = (DQ_{fly})^2 = \left(I_L \frac{T_s}{2} \right)^2$$

$$P_{\text{loss}} = I_L^2 \frac{T_s}{4} \left(4R \frac{1}{T_s} \right) = \underline{\underline{I_L^2 R}}$$

$$R = ESR_c + 2R_{\text{ont}} R_c + \dots$$