
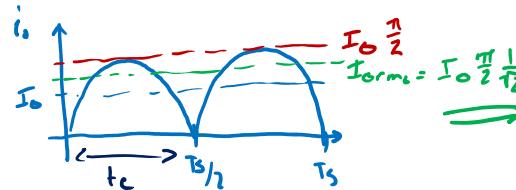
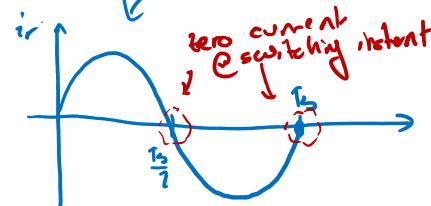


2:1 – Resonant Implementation

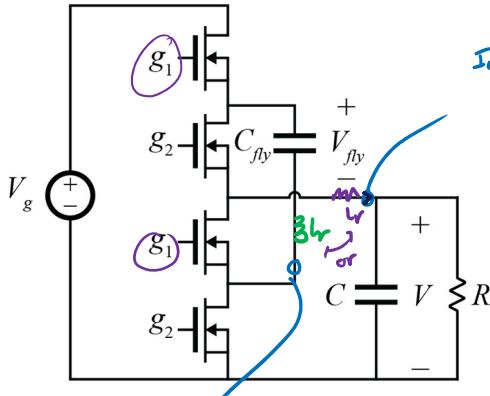

$$E_{loss} = 2 \cdot \frac{1}{2} C (V_2 - V_1)^2 \frac{\pi^2 f_c^2}{2 T_s}$$

$$\begin{aligned} P_{loss} &= C^2 (V_2 - V_1)^2 \frac{\pi^2}{2} f_c^2 R \\ &= \Delta Q^2 \end{aligned}$$

$$\Delta Q = I_o \frac{T_s}{2}$$


$$P_{loss} = \left(\frac{\Delta Q \pi f_s}{T_s^2} \right)^2 R$$

$$= \left(\frac{I_o T_s \pi f_s}{2 T_s^2} \right)^2 R$$

$$\underline{P_{loss} = \underline{I_{o,rms}}^2 R}$$




$$R = ESR_c + 2R_{on} + R_L$$

Slow and Fast Switching Limits

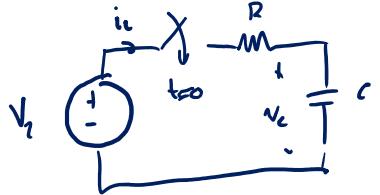

$$V_c(t=0) = V_1$$
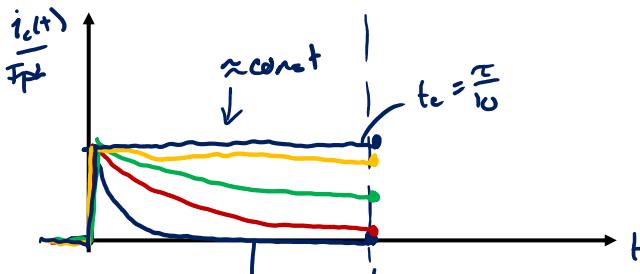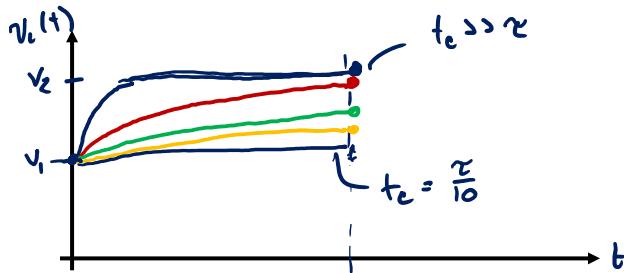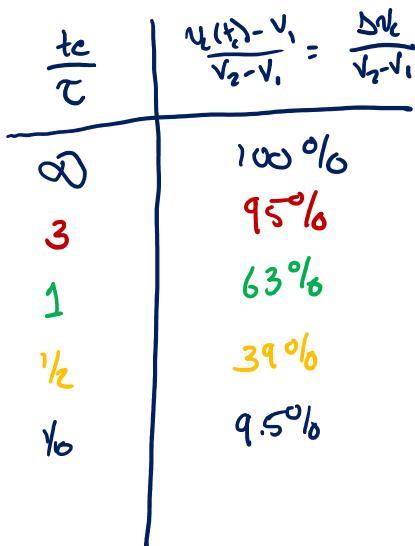
$$V_c(t \gg 0) = V_1 + (V_2 - V_1) (1 - e^{-\frac{t}{RC}})$$



$t_c \gg T \rightarrow V_c(t_c) \rightarrow V_2 \quad i_c \rightarrow 0$ before end of period

Slow switching limit (SSL)

$t_c \ll T \rightarrow$ Current \approx constant through entire interval
Fast switching limit (FSL)

$$\Delta V_c \ll V_2 - V_1$$

2:1 SC – FSL Model


FSL : assume $t_c = \frac{T_3}{2} \ll RC = T$

$$P_{out} = V \cdot I_0$$


$$= V \cdot \frac{1}{T_3} \int_0^{T_3} i_0(t) dt$$

$$= V \cdot \frac{1}{T_3} \left[\frac{V_g - V_{fhy} - V}{R} \cdot \frac{T_3}{2} + \frac{V_{fhy} - V}{R} \frac{T_3}{2} \right]$$
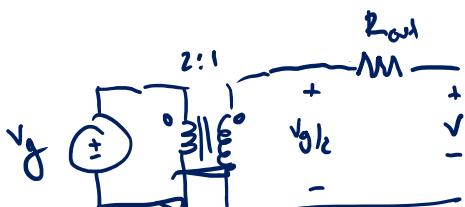
$$= V \cdot \frac{1}{2} \left[\frac{V_g - 2V}{R} \right] = V \cdot \underbrace{\left[\frac{V_g / R - V}{R} \right]}_{I_0}$$




$$R_{out} = ESR_c + 2R_{dn} + \dots$$

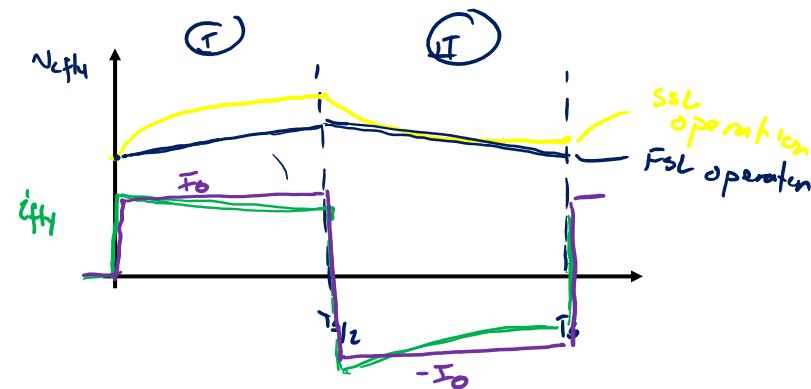

$$\begin{cases} R_{out,SSL} = \frac{1}{4C_{fhy} f_s} \\ R_{out,FSL} = ESR_c + 2R_{dn} \end{cases}$$

SC Output Resistance

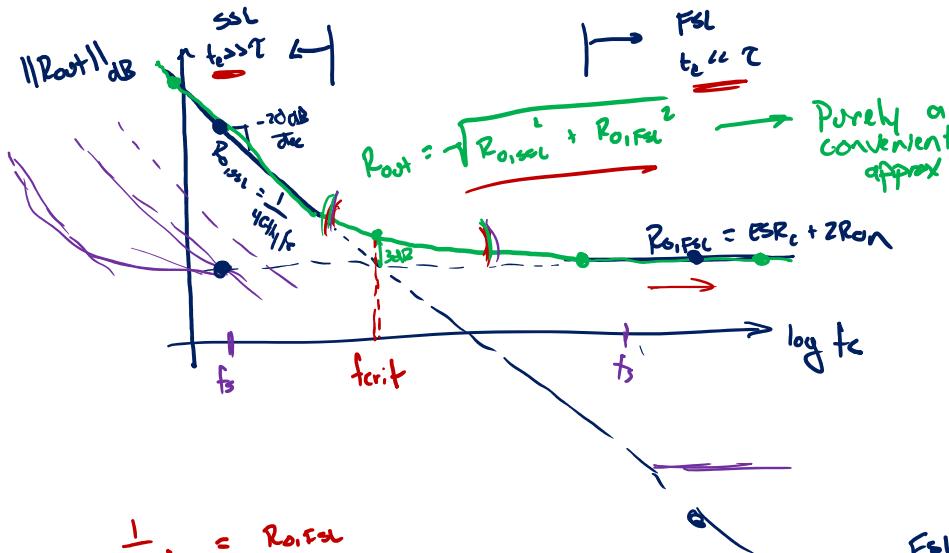

$$\frac{1}{4CfL}f_{crit} = R_{0,SSL}$$

$$f_{crit} = \frac{1}{4CfL R_{0,FCL}}$$

$$\frac{1}{T_B} = \frac{1}{4CfL R_{0,FCL}}$$

$$\frac{1}{2\tau_c} = \frac{1}{4CfL R_{0,SSL}}$$

$$\underline{t_c = 2CfL R = 2\tau_c}$$

$\rightarrow R_{out} \downarrow @ \text{higher } f_s$

want high f_s for small "conduction" losses
But switching losses aren't included

FCL + SSL equivalent model:

$$R_{out} \approx \sqrt{\left(\frac{k}{CfL f_s}\right)^2 + (R_{eq})^2}$$

