

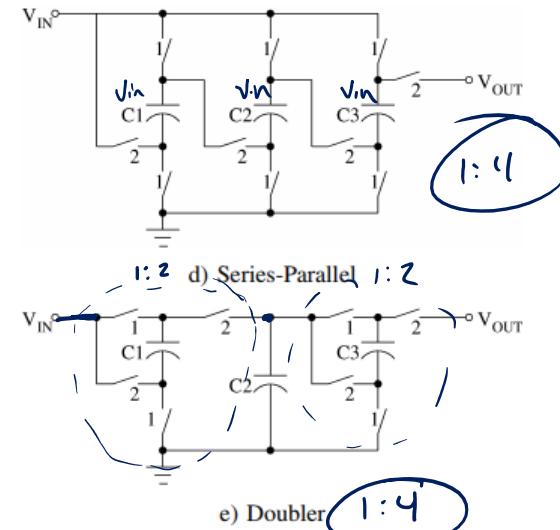


SC Converter Topologies

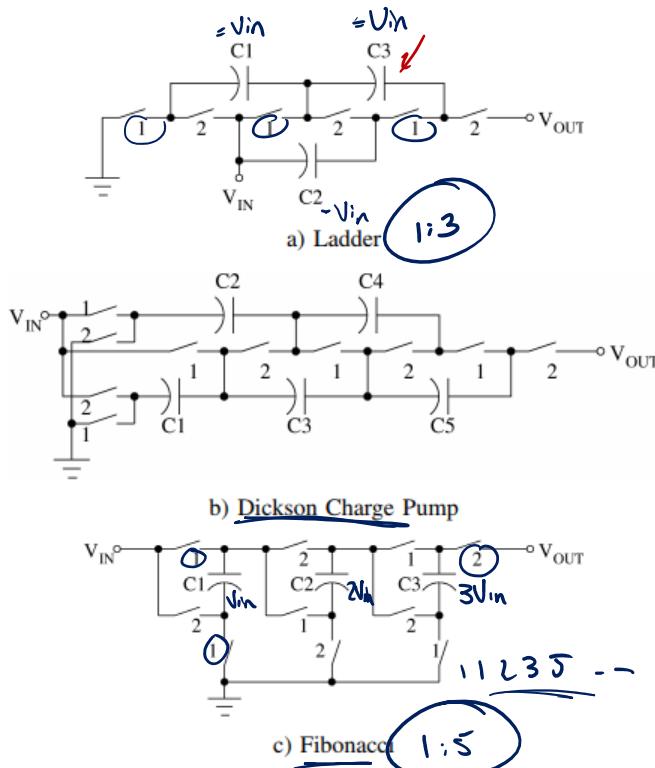


Dickson Converter

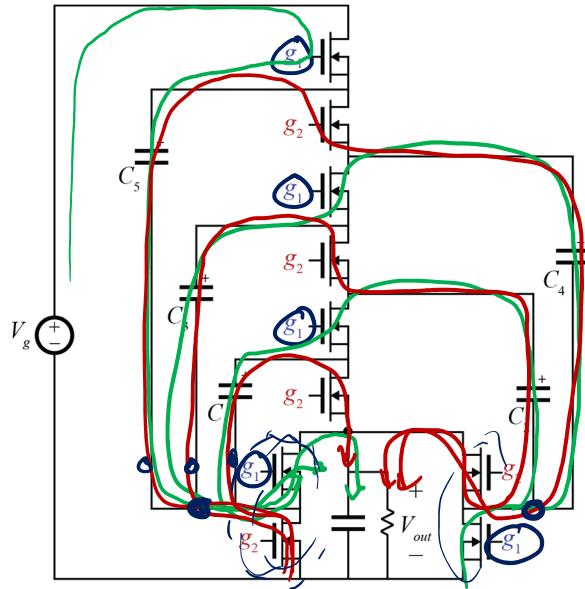

Dickson Subintervals

Ideal analysis → neglect any capacitor voltage ripples

①

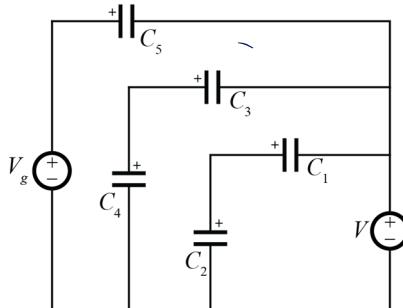


$$\sqrt{V_g} = 6V$$


$$\sqrt{V_{c1}} = 4V$$

$$\sqrt{V_{c2}} = 2V$$

this is a 6:1 Dickson converter

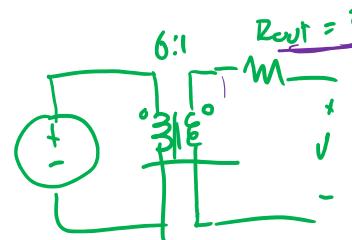

②

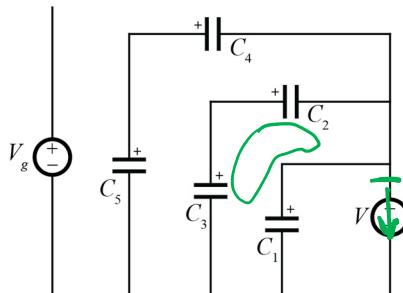


$$\sqrt{V_{c5}} = 5V$$


$$\sqrt{V_{c3}} = 3V$$

$$\sqrt{V_{c1}} = V$$

Dickson Converter Variants

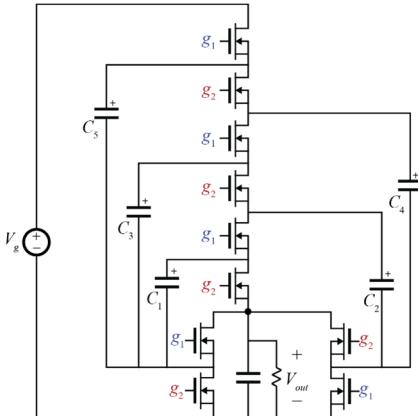


Standard Dickson Converter

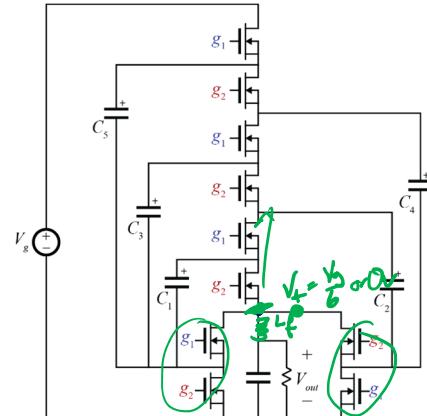

Hybrid Dickson Converter

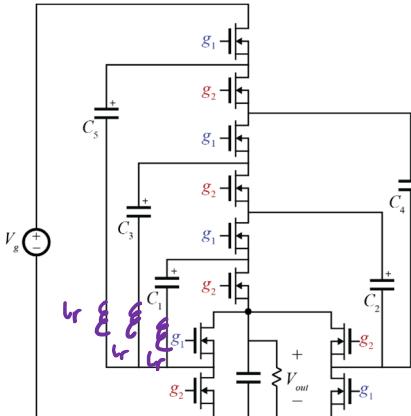- On its own it allows some current source type charging
- Can add PWM regulation for $V_{out} \leq \frac{1}{2}V_g$



Switched Tank Converter

- Unregulated, high η
- Resonant charging of all capacitors

Y. Lei, R. May, and R. Pilawa-Podgurski, "Split-Phase Control: Achieving Complete Soft-Charging Operation of a Dickson Switched-Capacitor Converter," 2016

Y. Li, X. Lyu, D. Cao, S. Jiang and C. Nan, "A 98.55% Efficiency Switched-Tank Converter for Data Center Application," 2018.

Charge Vector Analysis: Notation

Find N & k for arbitrary switched cap converter

- Applies cap-Q balance to every capacitor in the circuit

q_x^I = charge into element x in subinterval I ($q_{ci}^I \rightarrow$ charge in C_i in I)

$a_x^I = \frac{q_x^I}{q_{out}}$ → Charge normalized by total output charge over all subintervals

$$q_{out} = q_{out}^I + q_{out}^{II} + \dots$$

$$\bar{a}_c^I = [q_{in}^I, \underbrace{a_{c_1}^I, a_{c_2}^I, \dots, a_{c_N}^I}_{\text{All capacitors}}, q_{out}^I]$$

$\overbrace{\hspace{10em}}$

Input source All capacitors Output port

$N =$ total number of flying caps
in the circuit

$$\bar{V}^I = [V_g, V_{c_1}^I, V_{c_2}^I, \dots, V_{c_N}^I, V]$$

$V_{c_x}^I$ = Voltage on C_x at the end of subinterval I (assumed SSL)

Charge Vector Analysis: Rules


- KVL \nrightarrow KCL apply

- for all caps $\int_0^{t_0} i_{cx} dt = \sum_{all\ int} q_{cx} = \phi$ (cap-charge balance)

for a 2-subinterval converter
same is true for q_{ax}

$$q_{cx}^I + q_{cx}^{II} = \phi \rightarrow q_{cx}^I = -q_{cx}^{II}$$

2:1 Converter Charge Vector Analysis

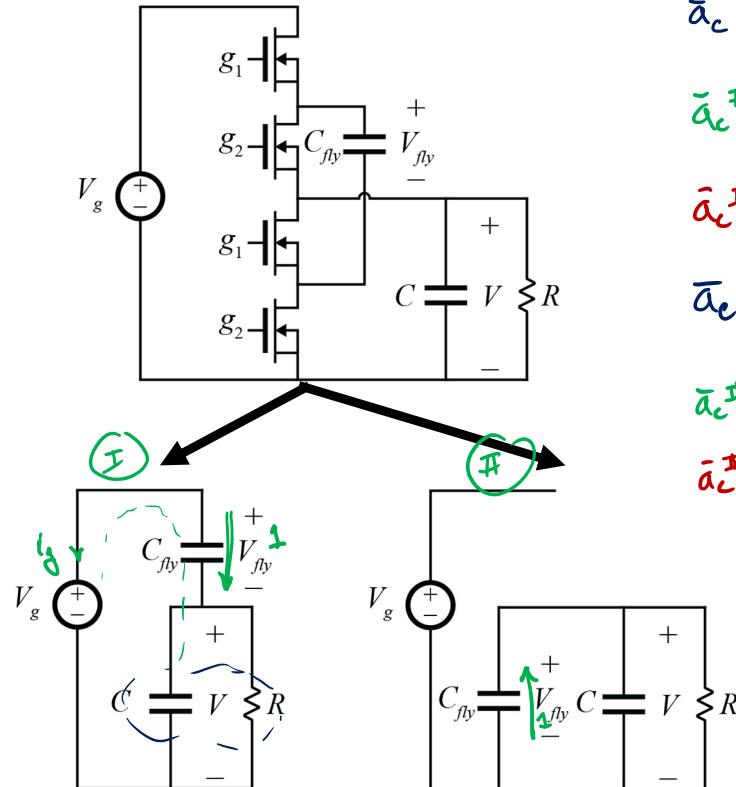

$$\bar{a}_c^I = \begin{bmatrix} g_{in}^I & g_{fly}^I & g_{out}^I \end{bmatrix} / g_{out}$$

$$\bar{a}_c^{\text{II}} = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix} / g_{out} \rightarrow g_{out} = g_{out}^I + g_{out}^{\text{II}}$$

$$\bar{a}_c^I = \begin{bmatrix} -\frac{1}{2} & \frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$\bar{a}_c^{\text{II}} = \begin{bmatrix} g_{in}^{\text{II}} & g_{fly}^{\text{II}} & g_{out}^{\text{II}} \end{bmatrix} / g_{out}$$

$$\bar{a}_c^{\text{II}} = \begin{bmatrix} \phi & -1 & 1 \end{bmatrix} / g_{out}$$

$$\bar{a}_c^{\text{II}} = \begin{bmatrix} \phi & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

Normalized $g_{out} = 1$ always

$$a_{in} = -\frac{1}{2}$$

$$V_g = 2V \rightarrow \text{equivalent circuit}$$

$$M = \frac{V}{V_g} = \frac{-a_{in}}{a_{out}} = -a_{in}$$

Tellegen's Theorem

For any valid circuit (will be seen apply)

$$\sum_{i \in \text{elements}} V_i I_i = \phi$$

$V_i \rightarrow$ Voltage across,

$I_i \rightarrow$ current through

Passive sign convention held on all elements

For our 2-interval SC converter

$$\bar{a}^I \bar{v}^I + \bar{a}^{II} \bar{a}^{II} = \phi \quad \nmid \quad \bar{a}^{I+I} = \bar{a}^{II-II} = \phi$$