

Charge Vector Analysis: Rules


- KVL & KCL apply

- for all caps $\int_0^{t_s} i_{cx} dt = \sum_{\text{all in's}} q_{cx} = \phi$ (cap-charge balance)

for a 2-subinterval converter
same is true for q_{cx}

$$q_{cx}^I \rightarrow q_{cx}^{\#} = \phi \rightarrow q_{cx}^I = -q_{cx}^{\#}$$

To find R_{out} :

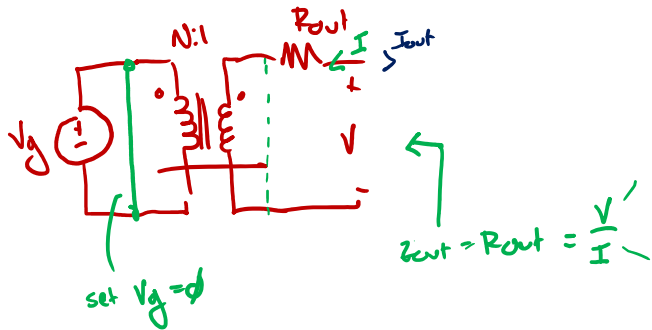

Tellegen's Theorem

For any valid circuit (KVL & KCL apply)

$$\sum_{\text{elements}} V_i I_i = \phi$$

$V_i \rightarrow$ Voltage across i

$I_i \rightarrow$ current through i

Passive sign convention held on all elements

For our 2-terminal SC converter

$$\underline{\bar{a}^I \bar{v}^I} + \underline{\bar{a}^{\text{II}} \bar{v}^{\text{II}}} = \phi$$

$$\bar{a}^I \bar{v}^I = \bar{a}^{\text{II}} \bar{v}^{\text{II}} = \phi$$

$$\cancel{V_g (a_{in}^I + a_{in}^{\text{II}})}$$

set $V_g = \phi$ to find R_{out}

$$+ a_{c1}^I v_{c1}^I + a_{c1}^{\text{II}} v_{c1}^{\text{II}} + \dots$$

$$V_{out} (a_{out}^I + a_{out}^{\text{II}}) = \phi$$

= 1

by our normalization

SSL Output Resistance

$$a_{c1}^I v_{c1}^I + a_{c1}^{II} v_{c1}^{II} + \dots = -V_{out}$$

any other caps

$$\sum_{i \in \text{all caps}} a_{ci}^I v_{ci}^I + a_{ci}^{II} v_{ci}^{II} = -V_{out} = \sum_{i \in \text{caps}} a_{ci}^I (v_{ci}^I - v_{ci}^{II})$$

For a 2-subinterval converter $a_{ci}^I = -a_{ci}^{II}$

$$\Delta v_{ci} = \frac{\beta_{ci}}{C_i} = \left(\frac{\beta_{ci}}{g_{out}} \right) \frac{g_{out}}{C_i} = a_{ci}^I \frac{g_{out}}{C_i}$$


$$\left(\frac{1}{g_{out}} \frac{1}{f_s} \right) -V_{out} = \sum_{i \in \text{caps}} (a_{ci}^I)^2 \frac{g_{out}}{C_i} \left(\frac{1}{g_{out}} \frac{1}{f_s} \right)$$

$$\frac{-V_{out}}{g_{out} f_s} = \sum_{i \in \text{caps}} (a_{ci}^I)^2 \frac{1}{C_i f_s}$$

$$\frac{-V_{out}}{I_{out}} = R_{out} = \sum_{i \in \text{caps}} (a_{ci}^I)^2 \frac{1}{C_i f_s}$$

for 2-subinterval converters

Output Resistance

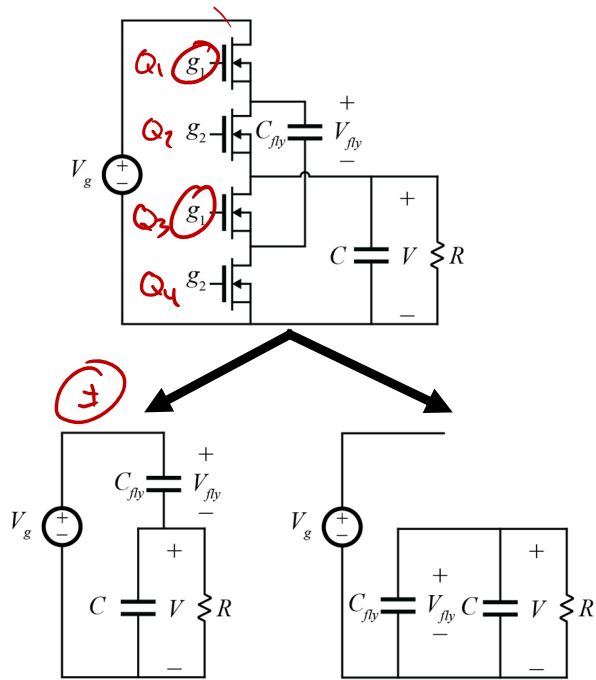

$$\bar{a}^I = \begin{bmatrix} -\frac{1}{2} & \frac{1}{2} & \frac{1}{2} \\ a_{in} & a_{fly} & a_{out} \end{bmatrix} \quad \bar{a}^{II} = \begin{bmatrix} 0 & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$R_{out} = \sum_{caps} (a_c)^2 \frac{1}{C_i f_s}$$

$$= \left(\frac{1}{2}\right)^2 \frac{1}{C_{fly} f_s} = \frac{1}{4 C_{fly} f_s} = R_{o,SSL}$$

In FSL: $\bar{a}_r = \begin{bmatrix} a_{g1} & a_{g2} & a_{g3} & a_{g4} \\ 1/2 & 1/2 & 1/2 & 1/2 \end{bmatrix}$


$$R_{o,FSL} = \sum_{i \in FETs} 2 (a_{ri})^2 R_{on,i}$$

$$R_{o,FSL} = 2 R_{on}$$

$$(R_{on,i} = R_{on})$$

Dickson Charge Vector Analysis

I

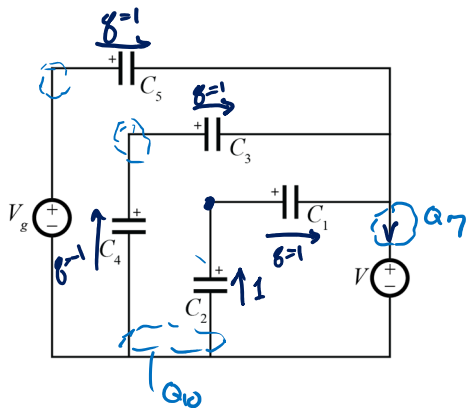

$$a^I = \begin{bmatrix} g_{in} & g_{c1} & g_{c2} & g_{c3} & g_{c4} & g_{c5} & g_{out} \\ -1 & 1 & -1 & 1 & -1 & 1 & 3 \end{bmatrix} / g_{out}$$

$$a^I = \begin{bmatrix} \frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & \frac{1}{2} \end{bmatrix}$$


\bar{a}_c

$$a^I = \begin{bmatrix} \emptyset & -1 & 1 & -1 & 1 & -1 & 3 \end{bmatrix} / g_{out}$$

$$a^{II} = \begin{bmatrix} \emptyset & \frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{2} \end{bmatrix}$$

$g_{out} = 6$

II

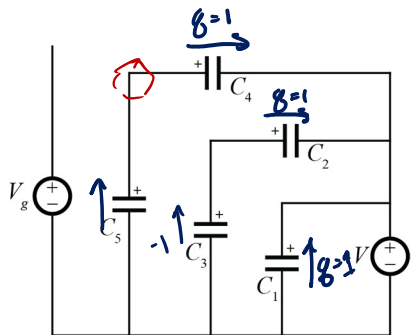

$$a_{in} = -\frac{1}{6} \quad a_{out} = 1$$

$M = \frac{1}{6}, 6:1$ Dickson converter

Dickson Output Resistance

$$R_{out} = \sum_{i \in caps} (a_{ci})^2 \frac{1}{C_i f_s}$$


Assume all $C_i = C_{TH}$

$$R_{out} = \frac{5}{36} \frac{1}{C_{TH} f_s}$$

In FSL

$$a_r = [$$

Dickson Converter

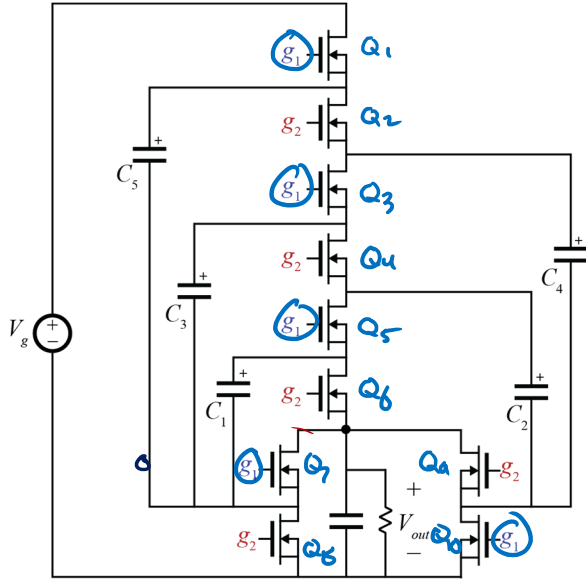

$$a^I = \begin{bmatrix} -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & \frac{1}{2} \end{bmatrix}$$

$$a^{II} = \begin{bmatrix} \phi & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{2} \end{bmatrix}$$


$$a_r = \begin{bmatrix} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 \\ \frac{1}{6} & \frac{1}{6} & \frac{1}{6} & \frac{1}{6} & \frac{1}{6} & \frac{1}{6} & \frac{1}{2} & \frac{1}{2} & \frac{1}{3} & \frac{1}{3} \end{bmatrix}$$

$$R_{o,fsl} = \sum_{i \neq rts} (a_{ri})^2 R_{on,i} \cdot 2$$

$$R_{on,i} = R_{on}$$

$$= 2R_{on} \left(\frac{1}{6} + \frac{1}{2} + \frac{2}{9} \right)$$
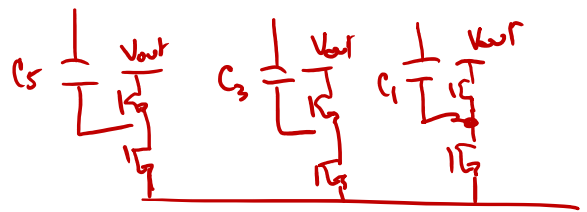
$$R_{o,fsl} = 2R_{on} \left(\frac{16}{18} \right) = R_{on} \frac{32}{18} = \boxed{R_{on} \frac{16}{9}}$$



Charge Vector Analysis in FSL

$$\vec{a}_r = \frac{\vec{g}_r}{g_{out}}$$

where g_{ri} are charges through transistors (or any resistances)

For a 2-subinterval converter transistor only has nonzero g_{ri} in one of the subintervals

a_{ri} found as some linear combination of a_{ci}

$R_{o,FSL}$ found by:

i_{ri} = current in transistor i when conducting \rightarrow Assumed constant in FSL

$$i_{ri} = g_{ri} \left(\frac{2}{T_s} \right) \rightarrow \text{Assume 2-subinterval converter w/ } D=50\%$$

$$P_{ri} = (i_{ri})^2 R_{on,i} \cdot \frac{1}{2} = \left(g_{ri} \frac{2}{T_s} \right)^2 R_{on,i} \cdot \frac{1}{2}$$

$$P_{ri} = (a_{ri})^2 4 \cdot \frac{1}{2} f_s^2 R_{on,i} g_{out}^2$$

$$P_{ri} = I_{out}^2 (a_{ri})^2 R_{on,i} \cdot 2$$

$$P_{tot} = I_{out}^2 \sum_{i \in FETS} 2(a_{ri})^2 R_{on,i} \rightarrow$$

$$R_{o,FSL} = \sum_{i \in FETS} 2(a_{ri})^2 R_{on,i}$$