

Tellegen's Theorem

For any valid circuit (will be seen apply)

$$\sum_{i \in \text{elements}} V_i I_i = \phi$$

$V_i \rightarrow$ Voltage across,

$I_i \rightarrow$ current through


Passive sign convention held on all elements

For our 2-interval SC converter

$$\bar{a}^I \bar{v}^I + \bar{a}^{II} \bar{a}^{II} = \phi \quad \nmid \quad \bar{a}^{I+I} = \bar{a}^{II-II} = \phi$$


SSL Output Resistance

Output Resistance


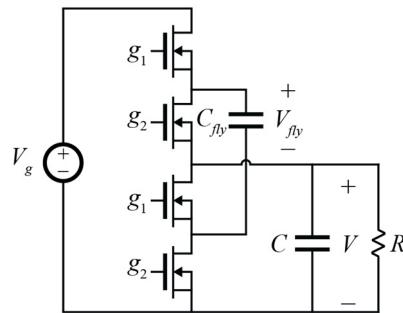


$$\bar{a}^I = \left[-\frac{1}{2} \quad \frac{1}{2} \quad \frac{1}{2} \right]$$
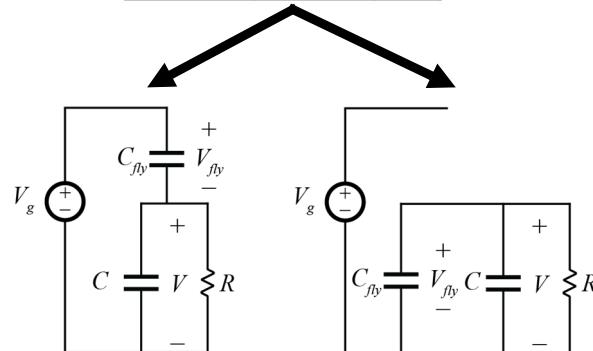
$$\bar{a}^{II} = \left[0 \quad -\frac{1}{2} \quad \frac{1}{2} \right]$$




Dickson Charge Vector Analysis

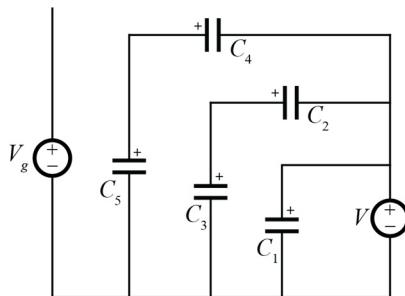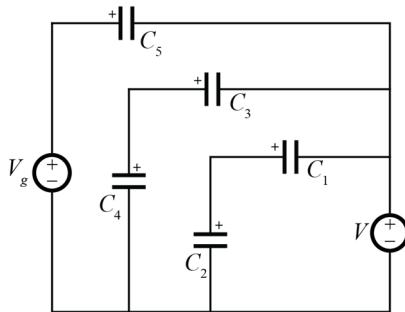

Dickson Output Resistance


Charge Vector Analysis in FSL

6:1 Dickson Converter Simulation

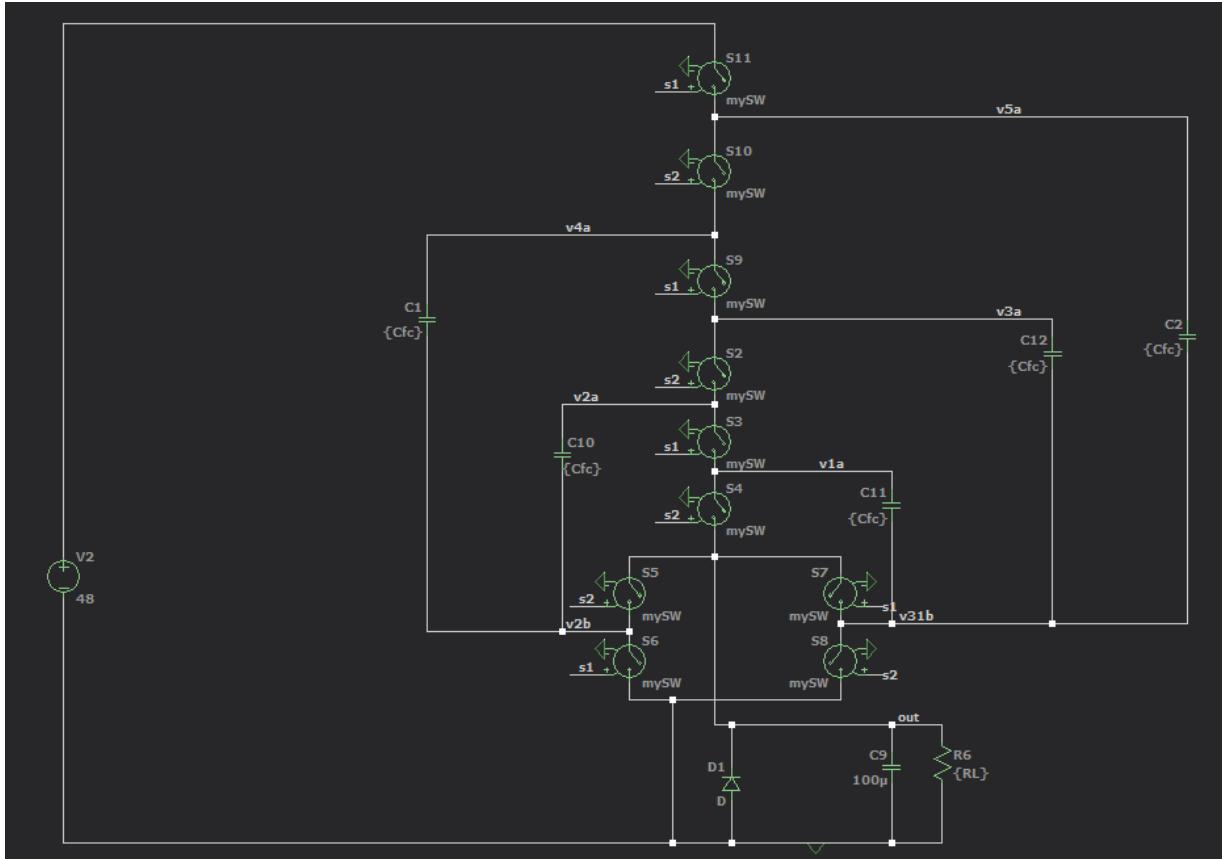

Simulation Comparison to Model

fixed $f_s = 1\text{MHz}$

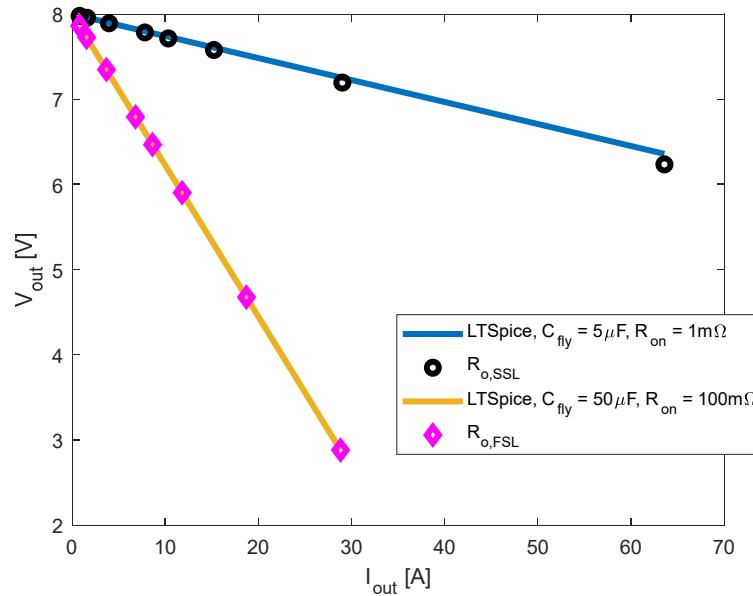

R_o vs Switching Frequency

fixed $R_{on} = 10\text{m}\Omega$, $C_{fly} = 5\mu\text{F}$

