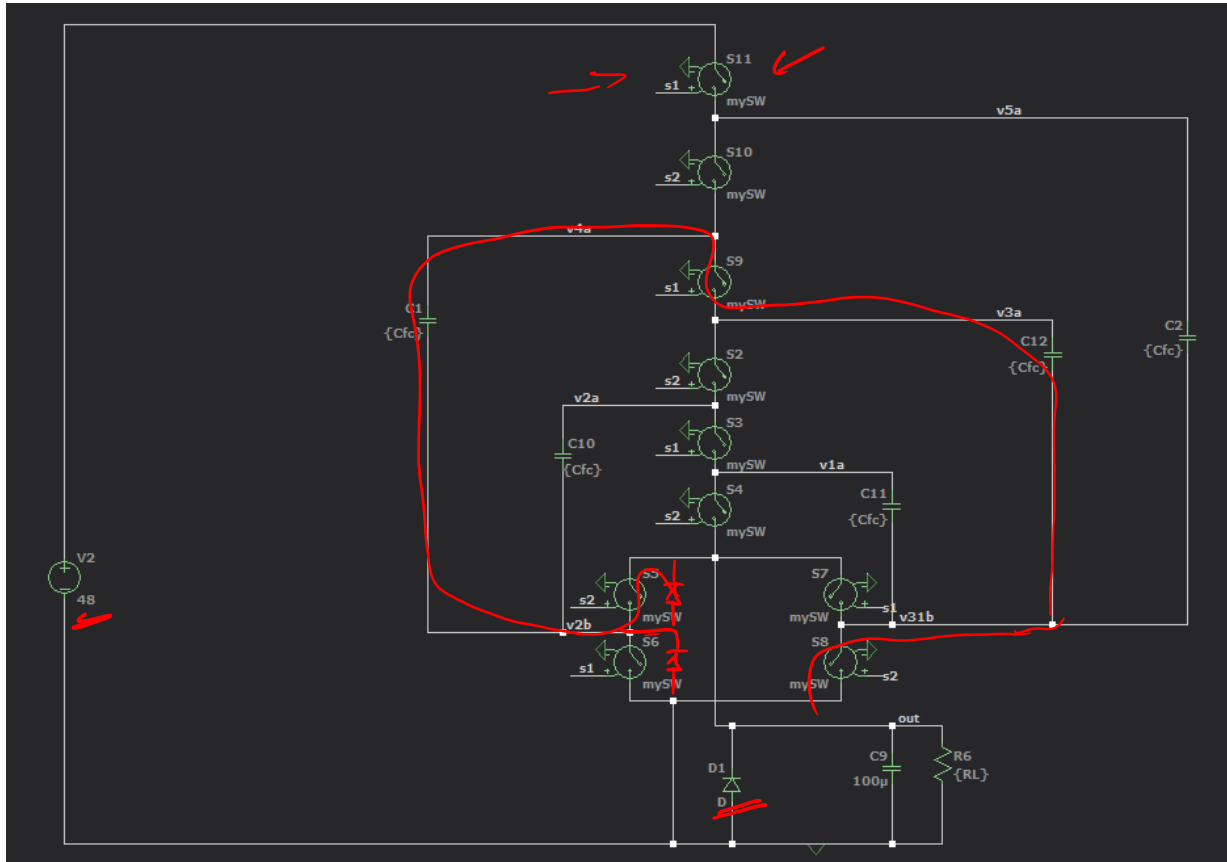




# 6:1 Dickson Converter Simulation


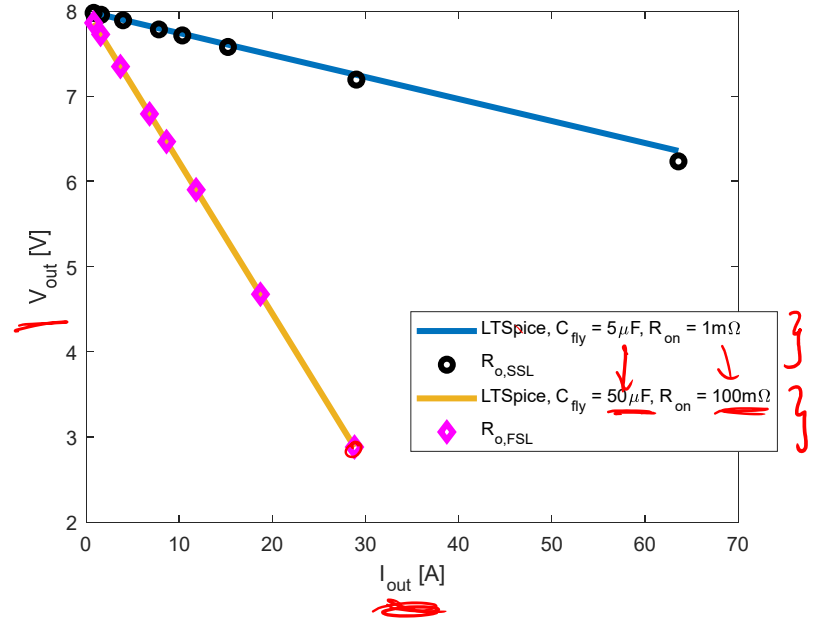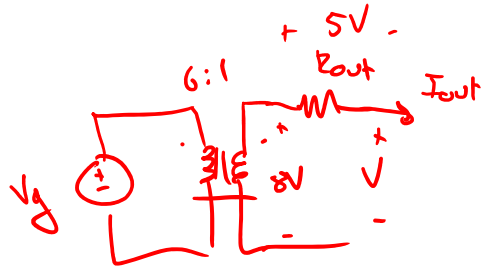
# Simulation Comparison to Model

fixed  $f_s = 1\text{MHz}$


$$f_x = \frac{1}{2\pi R_{on} C_{fly}} = \begin{cases} 300\text{kHz} & R_{on} = 100\text{m}\Omega \\ 30\text{MHz} & R_{on} = 1\text{m}\Omega \end{cases}$$


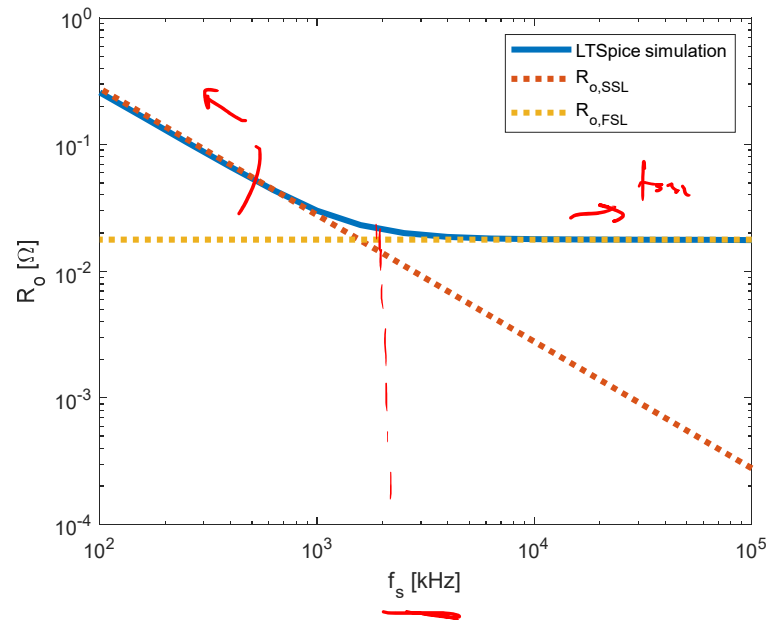
# $R_o$ vs Switching Frequency

fixed  $R_{on} = 10\text{m}\Omega$ ,  $C_{fly} = 5\mu\text{F}$


$$R_{out} \approx \sqrt{R_{o,SSL}^2 + R_{o,FSL}^2}$$


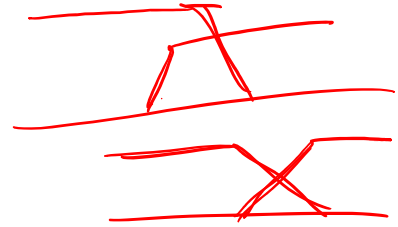
# Switching Losses in SC Converters

In SSL

- Full Cross loss @ every FET turn-on
- $\approx \emptyset$  turn-off loss
- Minimal ( $\approx \emptyset$ )  $P_{\text{ov}}$  loss  $\rightarrow$  some in FET but much less than in L-loaded HB  
may need to carefully look @  $L_{\text{par}}$



Hybrid / Resonant Implementation

- $L_f$  or  $L_r$  added
- May have FETs with  $\omega_{\text{th}}$   $P_{\text{ov}} = \emptyset$   $\$ P_{\text{ov}} = \frac{1}{2} V I_c t_{\text{ov}} f_s$

# Charge Sharing Loss and Soft Charging


Charge sharing:

Loss that occurs from C-C or C-V type charging  
 $E = \frac{1}{2} (V_2 - V_1)^2$

Soft Charging:


Remove losses associated with charge sharing beyond base conduction loss

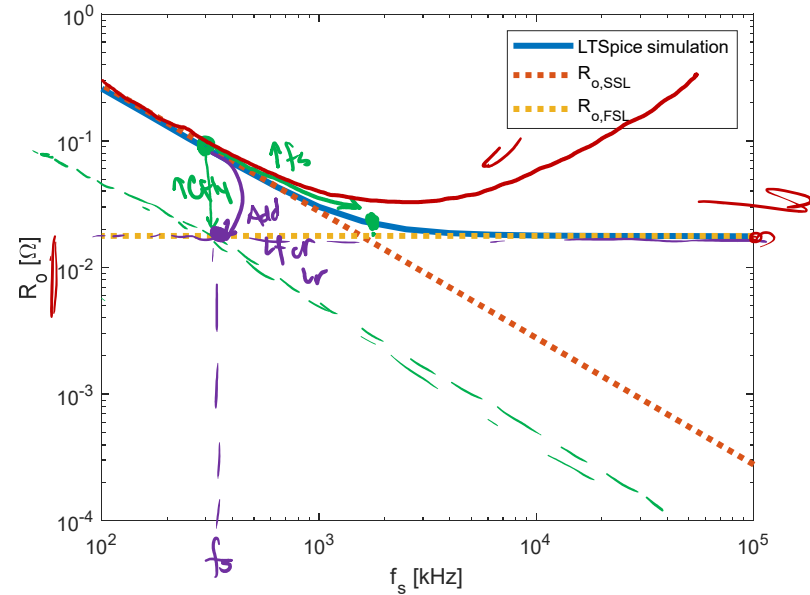- 1: Use current source type charging
- 2: Make sure caps are at same voltage before starting them.




# Hybrid Dickson Converter


I

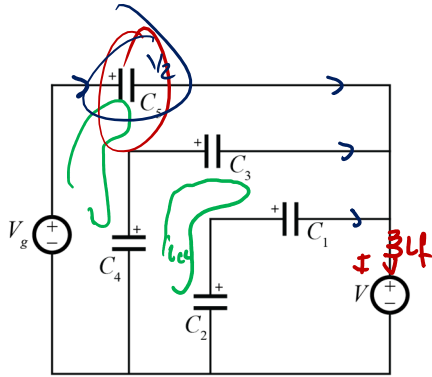

II

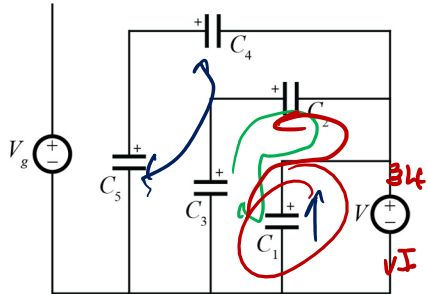

In either subinterval  
ac-equiv

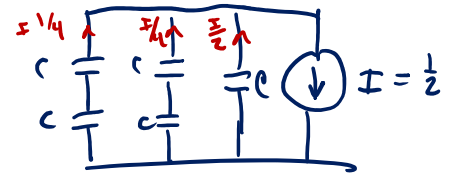

Assuming no charge-sharing current

$$\bar{a}^I = \begin{bmatrix} -\frac{1}{4} & \frac{1}{8} & -\frac{1}{8} & \frac{1}{8} & -\frac{1}{8} & \frac{1}{4} & \frac{1}{2} \end{bmatrix}$$

$$\bar{a}^{II} = \begin{bmatrix} 0 & -\frac{1}{4} & \frac{1}{8} & -\frac{1}{8} & \frac{1}{8} & \frac{1}{8} & \frac{1}{2} \end{bmatrix}$$

so it could be true that everything is  
current source charging