

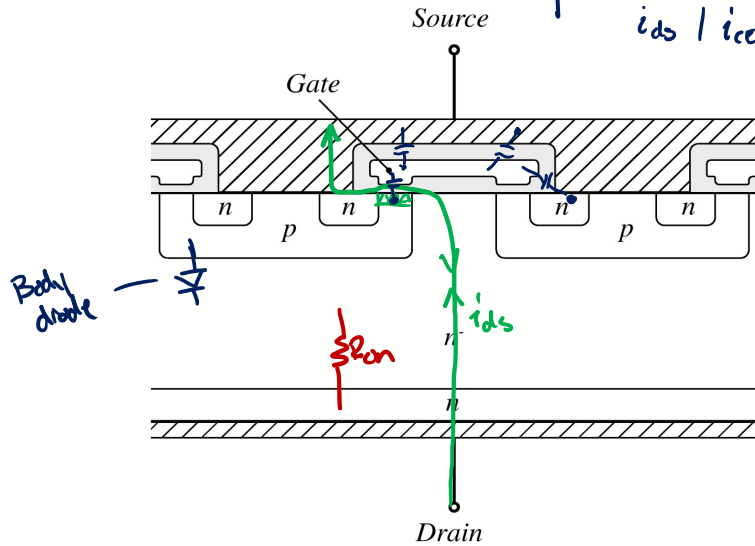


Charge Storage

MOSFET
Majority carrier

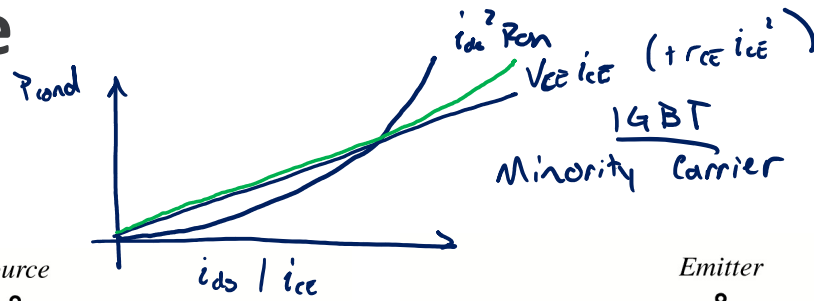


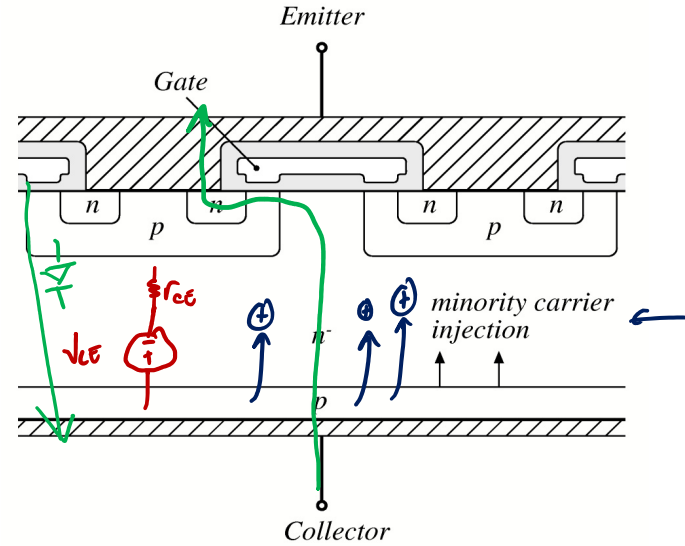- R_{on} fixed by doping density
- + No stored minority charge



- + Conductivity modulation
- Stored minority charge


IGBT Current Tailing

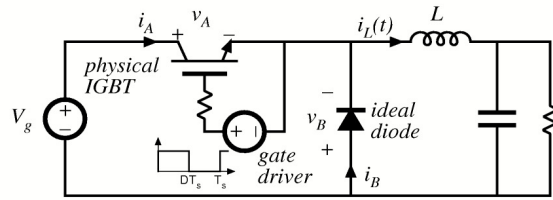


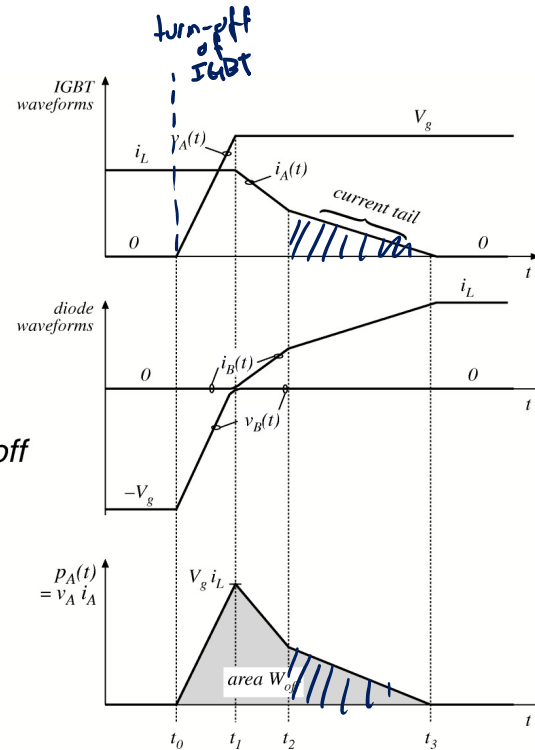
Example: buck converter with IGBT

transistor turn-off transition

$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$



Schottky Diode

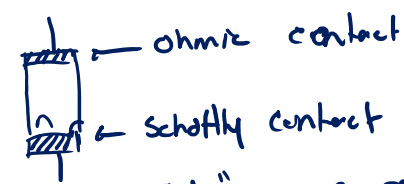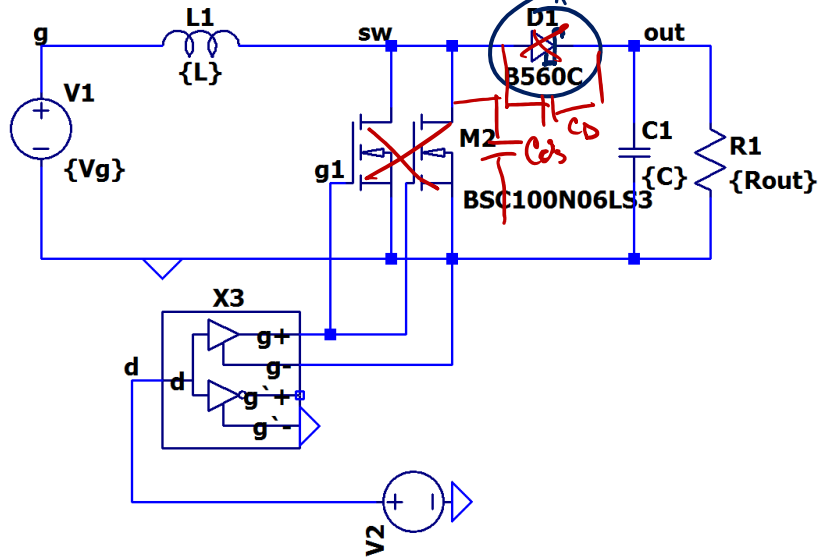


- "No" reverse recovery
- limited HV performance in Si
New, Good SiC HV Schottky diodes



L	C_{out}	f_s	Diode	η (Sim)
22uH	22uF	202k	Si (FR)	93.9%
22uH	22uF	202k	Si Schottky	95.8%

~ 2% increase in η
 (But was hoping for 3%)


Simulation Waveforms

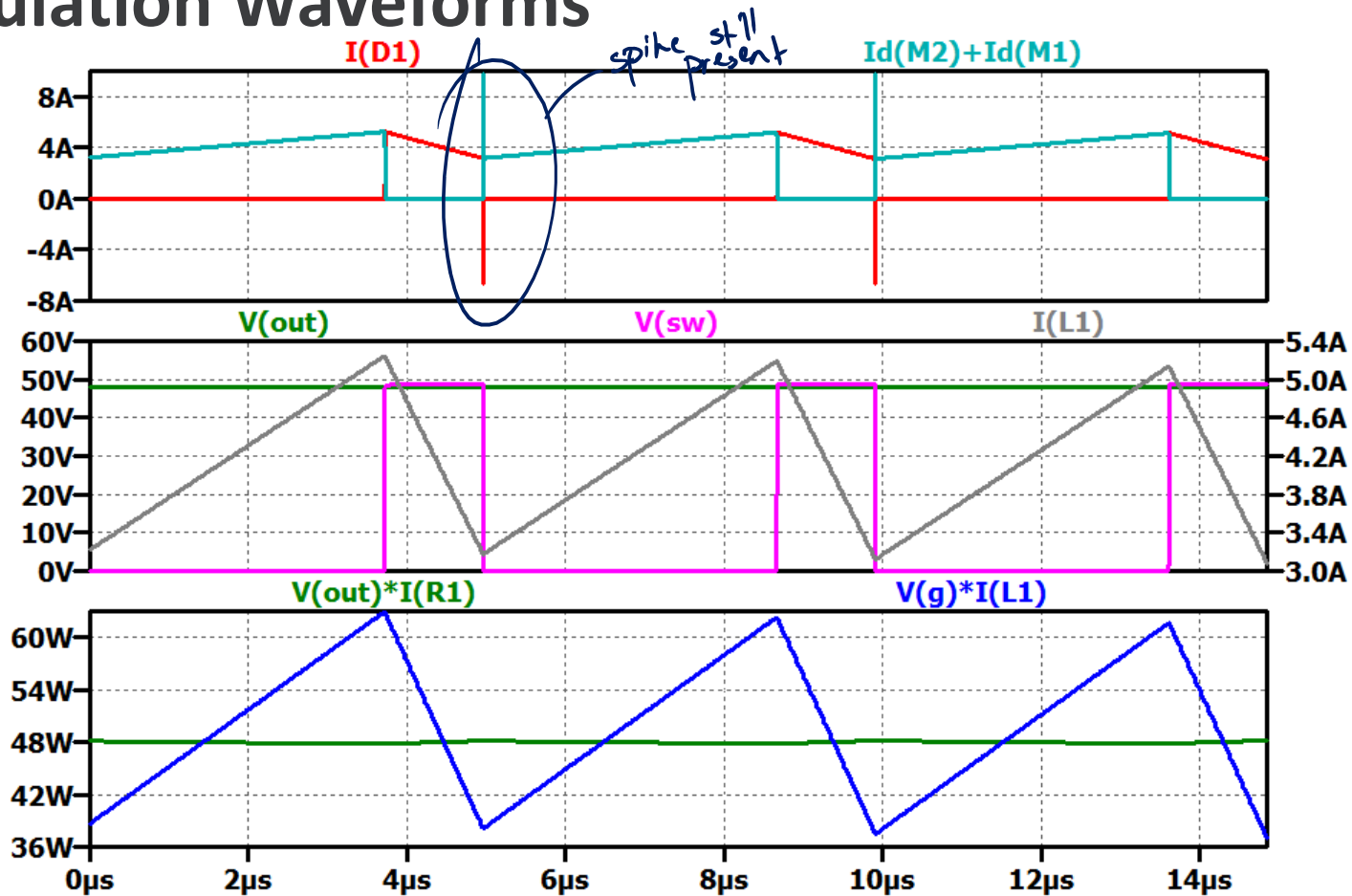

Switching Transition – FET turn ON

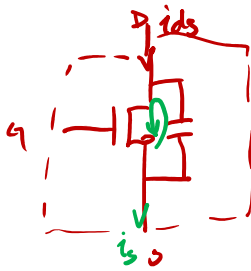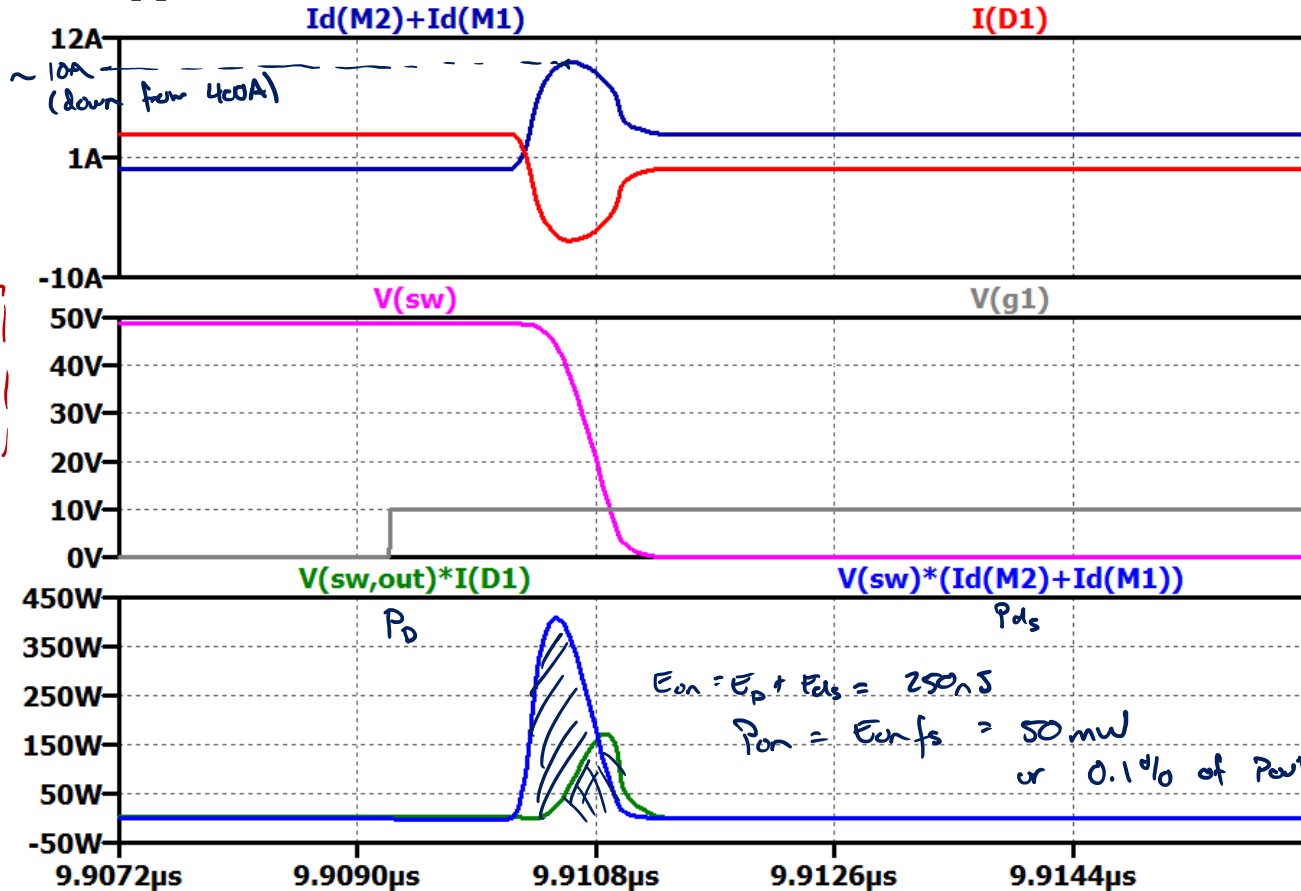

Switching Transition – FET turn OFF

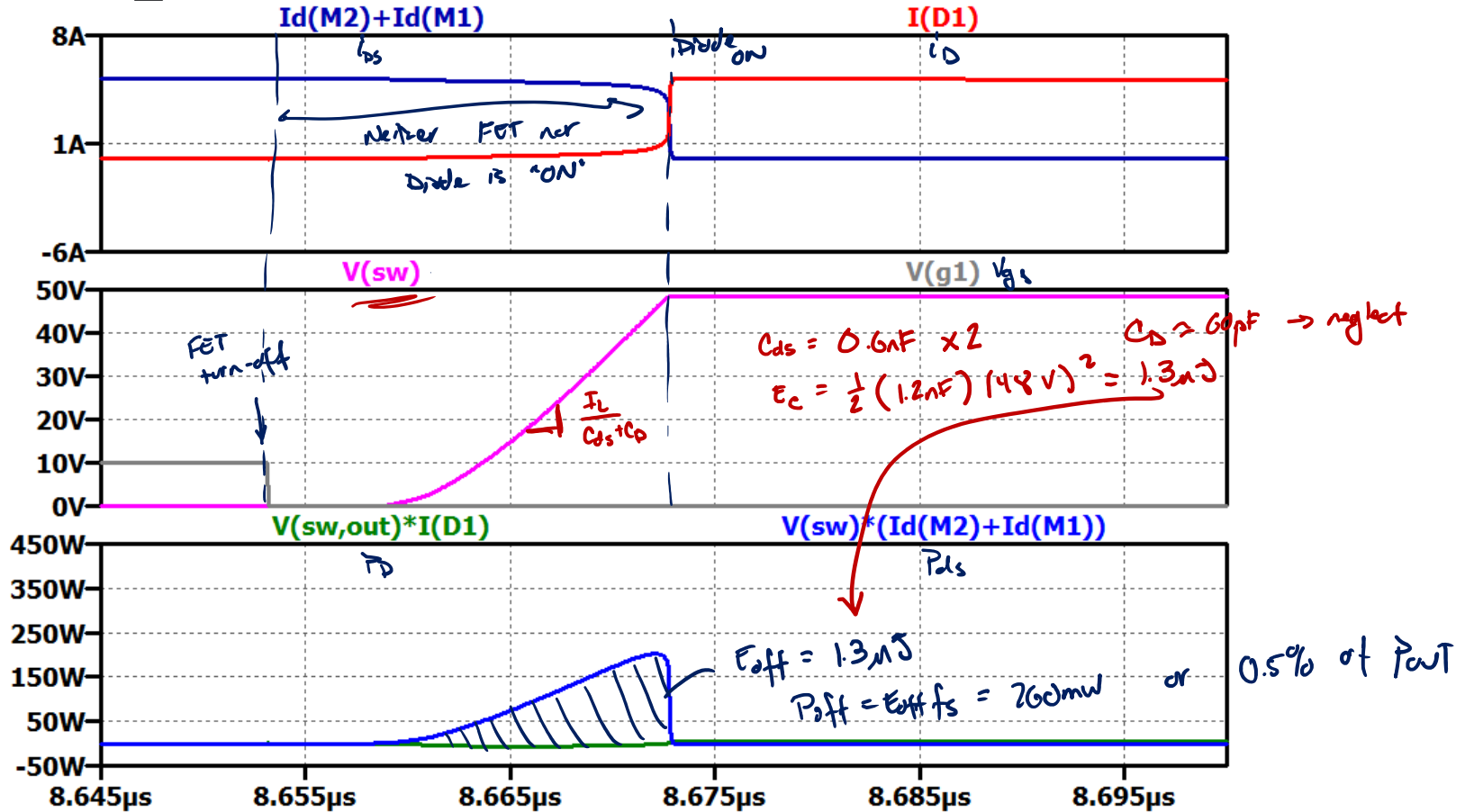


MOSFET Switching Behaviors

First: static

5 Typ. output characteristics

$$I_D = f(V_{DS}); T_j = 25^\circ\text{C}$$


parameter: V_{GS}

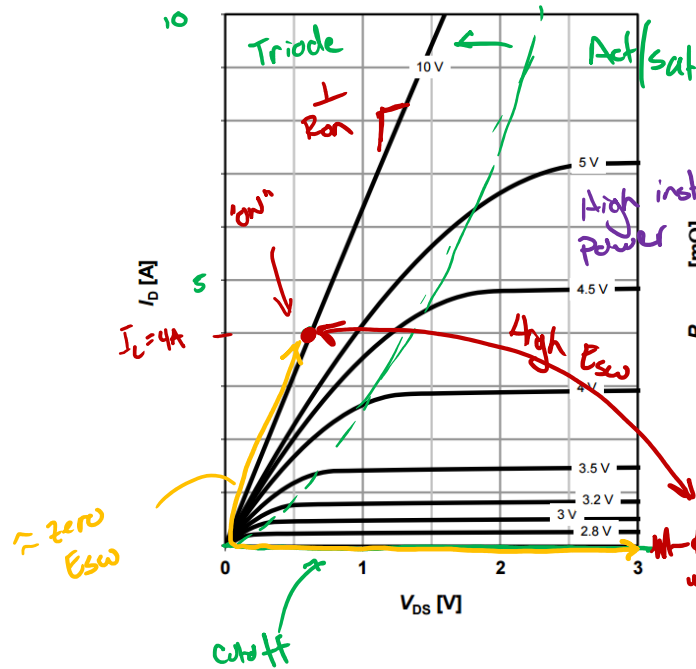

6 Typ. drain-source on resistance





$$R_{DS(on)} = f(I_D); T_j = 25^\circ\text{C}$$

parameter: V_{GS}

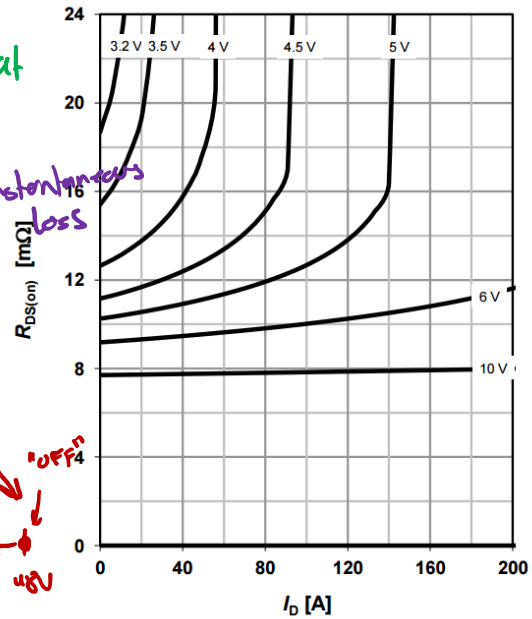

MOSFET Stored Charge

Then: Dynamic

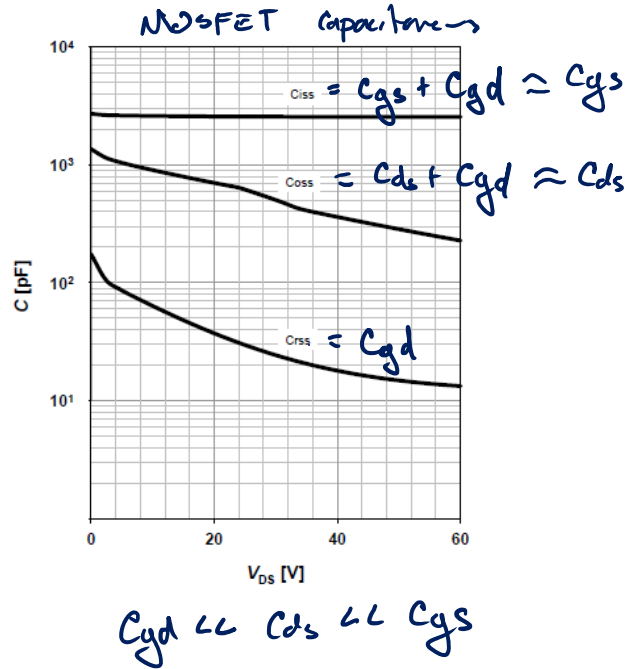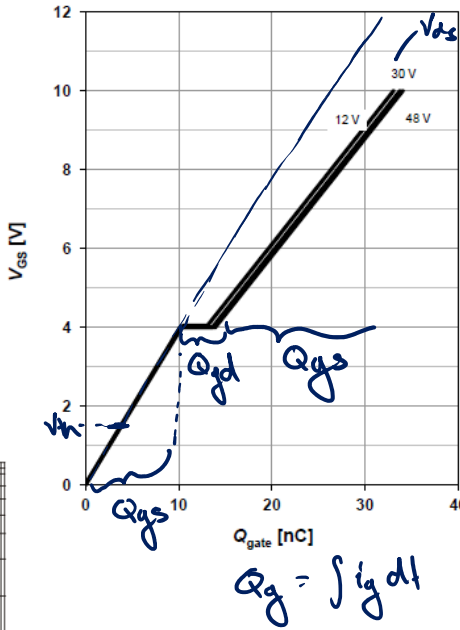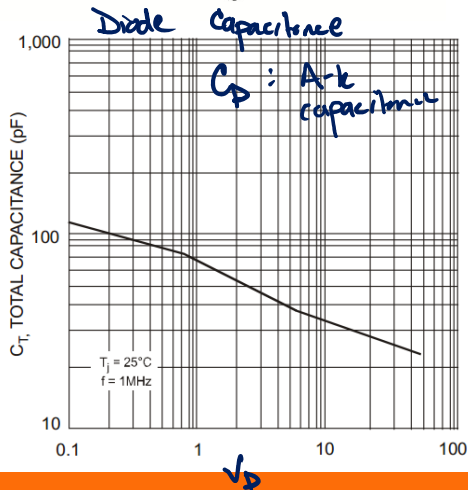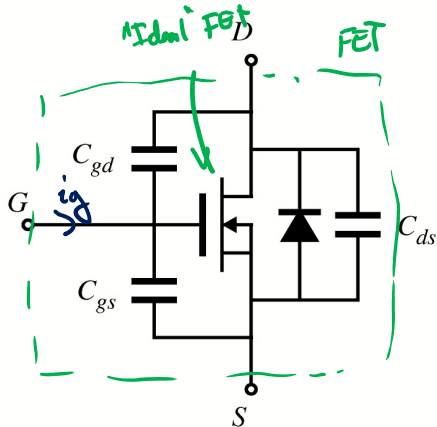

$$C_{gd} \ll C_{ds} \ll C_{gs}$$