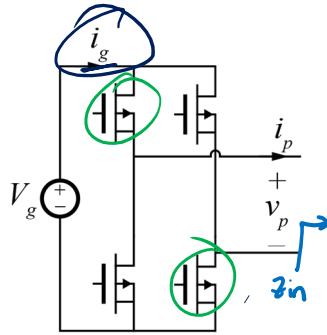


Switch Network Sinusoidal Analysis



Fourier Series:

$$b_1 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(x) dx$$

for $v_p(t)$:

$$b_1 = \frac{2}{T_s} \int_0^{T_s} v_p(t) \sin(2\pi f_s t) dt$$

$$\theta = 2\pi f_s t$$

$$d\theta = 2\pi f_s dt$$



$$= 2 \left(\frac{2}{T_s} \right) \int_0^{T_s/2} V_g \sin(2\pi f_s t) dt$$

$$= \frac{4}{T_s} V_g \int_0^{\pi} \sin \theta \frac{1}{2\pi f_s} d\theta$$

$$= \frac{4}{T_s} V_g \frac{1}{2\pi f_s} [-\cos \theta] \Big|_0^{\pi}$$

$$= \frac{4}{T_s} V_g \frac{1}{2\pi f_s} (2) = \boxed{\frac{4}{\pi} V_g} = b_1$$

$\frac{4}{\pi} \approx 1.27$

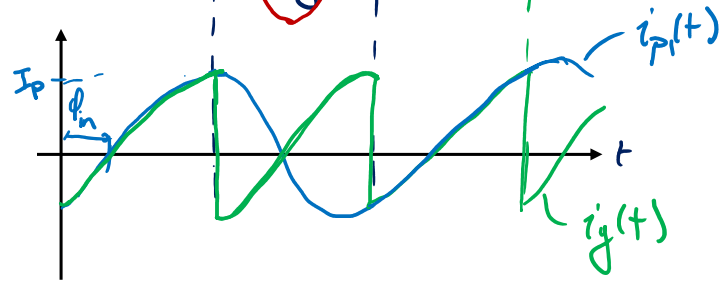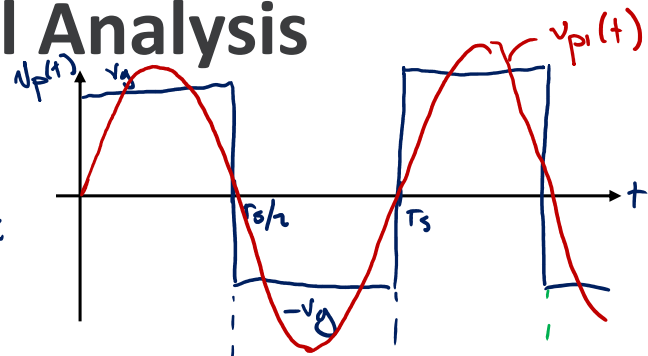

Input Current

say $i_p(t) = I_p \sin(2\pi f_s t - \phi_{in})$

then the DC input current is

$$I_g = \langle i_g(t) \rangle_{T_s} = \frac{2}{T_s} \int_0^{T_s/2} i_p(t) dt$$

$$= \frac{2}{T_s} \int_0^{T_s/2} I_p \sin(2\pi f_s t - \phi_{in}) dt$$

$$= \frac{2}{T_s} I_p \int_{-\phi_{in}}^{\pi - \phi_{in}} \sin(\theta) \frac{1}{2\pi f_s} d\theta$$

$$= \frac{2}{T_s} I_p \frac{1}{2\pi f_s} \left[-\cos(\theta) \right]_{-\phi_{in}}^{\pi - \phi_{in}}$$


$$= \frac{2}{T_s} I_p \frac{1}{2\pi f_s} 2 \cos(\phi_{in})$$

$$\boxed{I_g = \frac{2}{\pi} I_p \cos(\phi_{in})}$$

$$\theta = 2\pi f_s t - \phi_{in}$$

$$d\theta = 2\pi f_s dt$$

Switch Network Equivalent Circuit

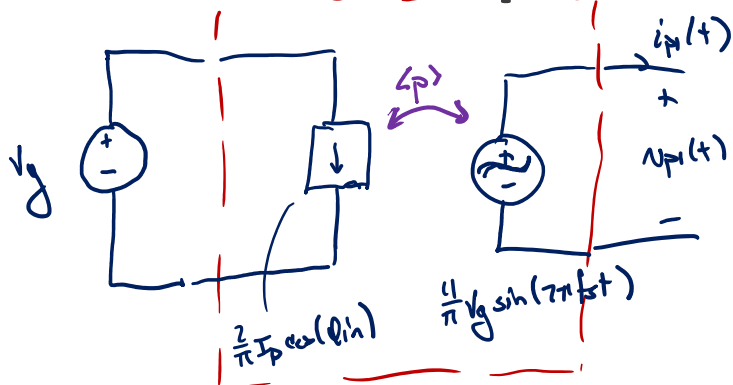

$$P_g = v_g I_g = v_g \frac{2}{\pi} I_p \cos(\phi_{in})$$

$$P_{ac} = \langle i_p \cdot v_p \rangle_{T_s}$$

$$= \frac{1}{T_s} \int_0^{T_s} I_p \sin(2\pi f_s t - \phi_{in}) \frac{4}{\pi} v_g \sin(2\pi f_s t) dt$$

Phasor mode!


$$I_p = I_p \angle -\phi_{in}$$

$$V_p = \frac{4}{\pi} v_g \angle \phi$$

$$P = \frac{1}{2} I_p \frac{4}{\pi} v_g \cdot \cos(\phi_{in}) \checkmark$$

Diode Rectifier Sinusoidal Analysis

Assume

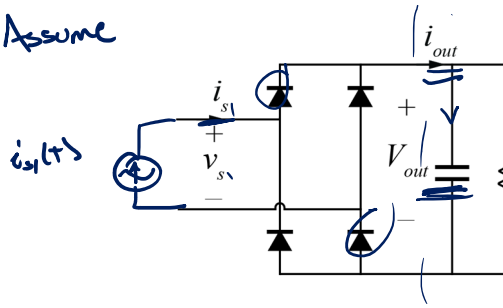


$$i_s(t) = I_s \sin(2\pi f_s t - \phi_{ps})$$

$$v_s(t) = \frac{4}{\pi} V_{out} \sin(2\pi f_s t - \phi_{ps})$$


(same derivation as inverter)

$$I_{out} = (i_{out})|_{T_s} = \boxed{\frac{2}{\pi} I_s = I_{out}}$$
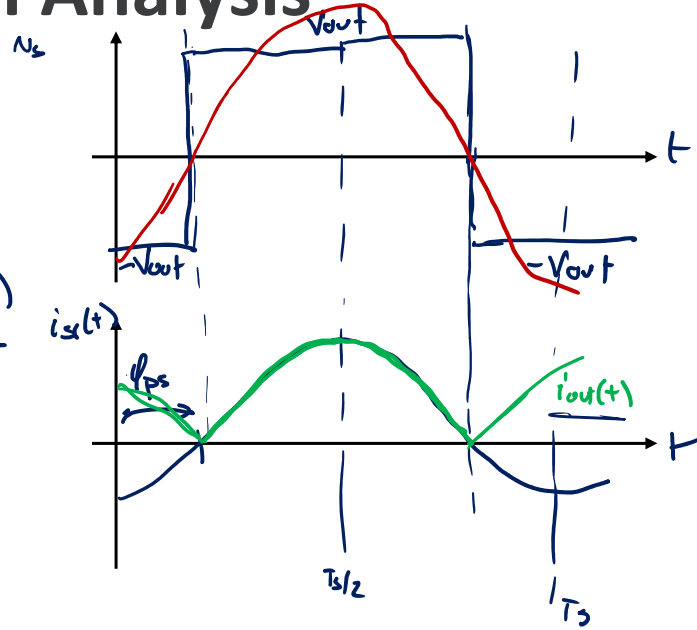
$$V_{out} = I_{out} R = \frac{2}{\pi} I_s R$$




Diode Rectifier Equivalent Circuit

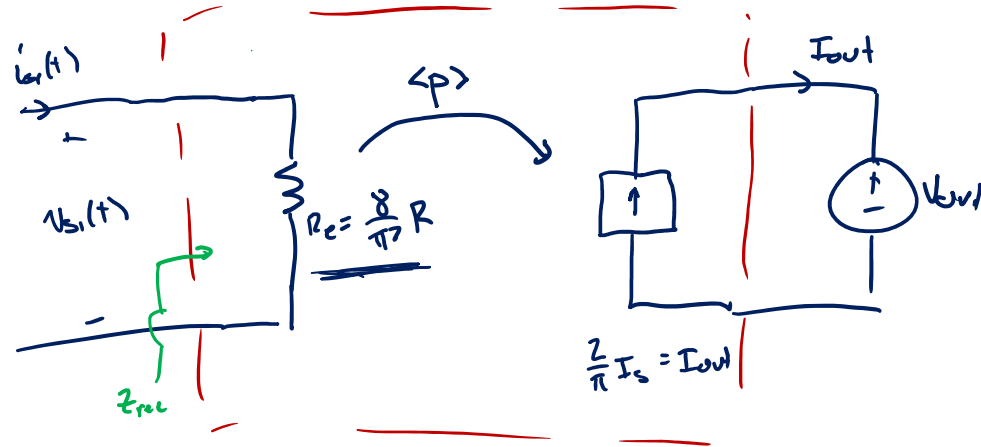


$$Z_{rec} = \frac{V_{s1}}{I_{s1}} = \frac{\frac{4}{\pi} V_m \sin(2\pi f t - \phi_c)}{I_s \sin(2\pi f t - \phi_c)} = \frac{\frac{4}{\pi} V_m}{I_s} = \frac{\frac{4}{\pi} V_m}{\frac{\pi}{2} I_{out}} = \frac{8}{\pi^2} \frac{V_m}{I_{out}} = \underline{\underline{\frac{8}{\pi^2} R}}$$

Other Implementations

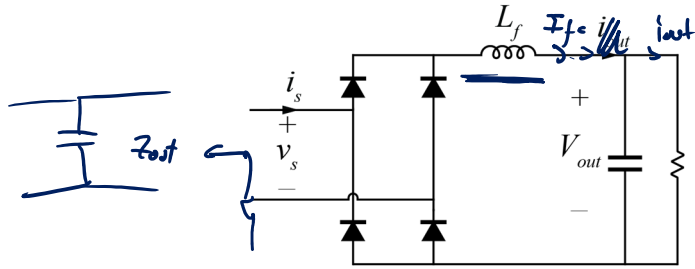

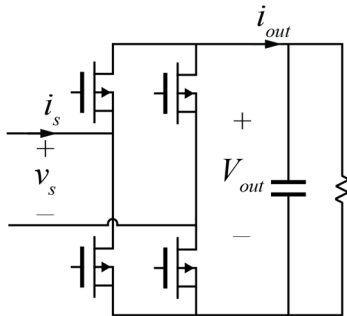large $L_f \rightarrow I_f \approx \text{constant}$
 $i_c(t) =$




Synchronous Rectifier

ϕ_{s-v_s} is not necessarily zero

$$Z_e = R_e' + jX_e$$

can also control duty cycle

Complete Equivalent Circuit

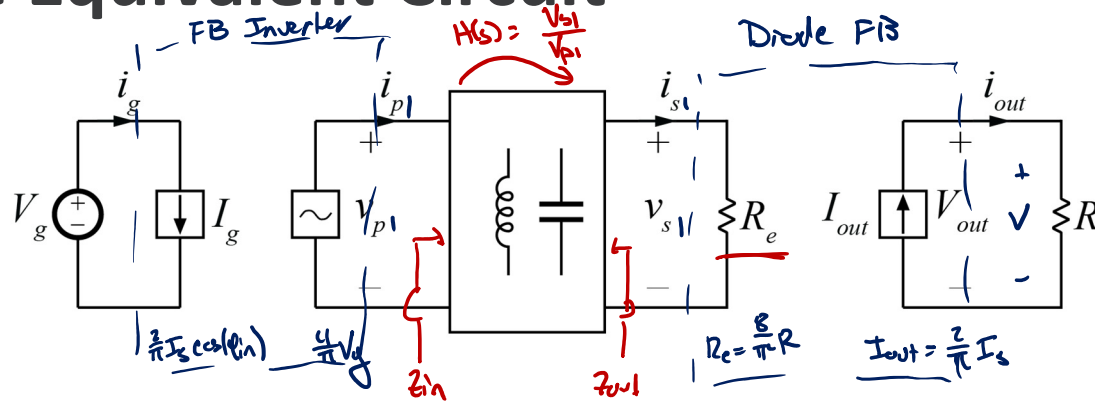

For FB Inverter, FB Diode Rectifier

$$M = \frac{V}{V_g} = \frac{V_{out}}{I_{out}} \cdot \frac{I_{out}}{I_s} \cdot \frac{I_s}{V_s} \cdot \frac{V_s}{V_p} \cdot \frac{V_p}{V_g}$$

$$= \cancel{R} \cdot \cancel{\frac{2}{\pi}} \cdot \cancel{\frac{\pi^2}{8} \frac{1}{R}} \cdot \|H(s)\| \cdot \cancel{\frac{4}{\pi}}$$

$$M = \|H(s)\|$$