
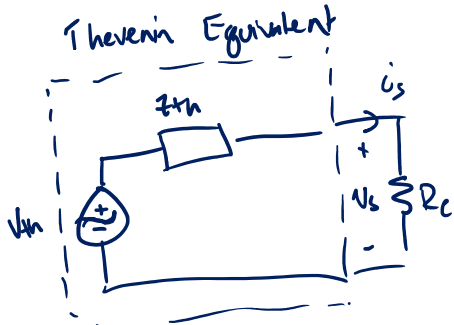
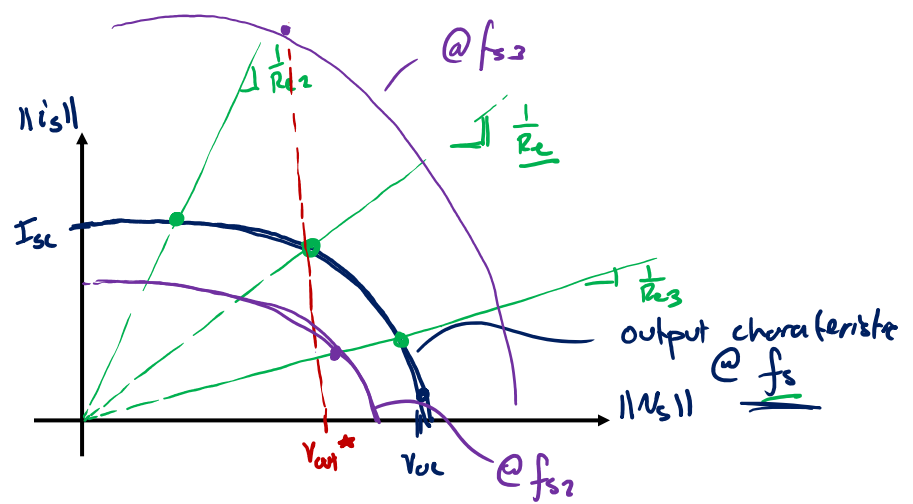


Announcements

- TBC PCB and components ordering
 - Once approved e-mail to eeecs-orders@utk.edu
 - Include description (for course design competition)
 - Actionable orders
 - cc Daniel.Costinett@utk.edu

Output Characteristic

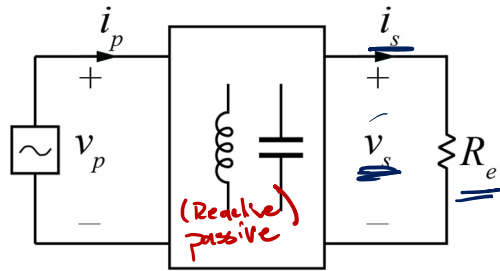

$$V_{th} = V_{oc}$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} \leftarrow$$

$$V_s = V_{th} \frac{R_e}{R_e + Z_{th}} \quad \text{if } Z_{th} \text{ is dominantly reactive}$$

$$\|V_s\|^2 = V_{oc}^2 \frac{R_e^2}{R_e^2 + \|Z_{th}\|^2}$$


$$\frac{\|V_s\|^2 R_e^2}{V_{oc}^2 R_e^2} + \frac{\|V_s\|^2 \|Z_{th}\|^2}{V_{oc}^2 R_e^2} = 1$$

$$\frac{\|V_s\|^2}{V_{oc}^2} + \frac{\|i_s\|^2}{I_{sc}^2} = 1$$

Equation for ellipse

Construction of Tank Transfer Function

SFC as an example $H(s)$

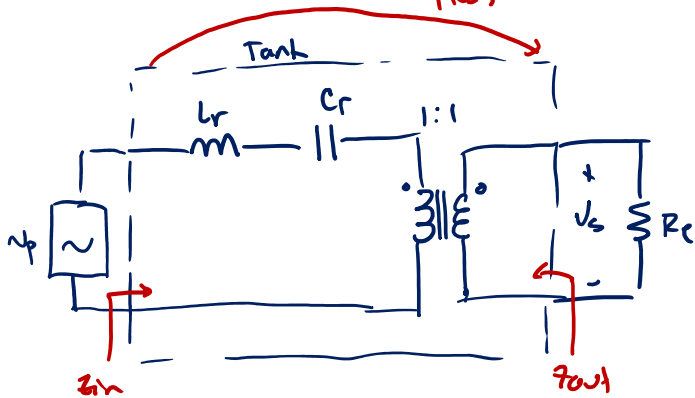

$$Z_{in} = sL_r + \frac{1}{sC_r} + R_e$$

$$Z_{out} = sL_r + \frac{1}{sC_r}$$

$$A(s) = \frac{R_e}{Z_{in}}$$

$$A(s) = \frac{sR_eC_r}{s^2L_rC_r + sC_rR_e + 1}$$

in standard form

$$A(s) = \frac{s/(Q_e\omega_0)}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q_e\omega_0} + 1}$$

$$\omega_0 = \frac{1}{\sqrt{L_rC_r}}$$

$$R_0 = \sqrt{\frac{L_r}{C_r}}$$

$$Q_e = \frac{R_0}{R_e}$$

Q_e = "effective" or loaded quality factor

$$M = \|A(s)\| = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{1}{P} - F\right)^2}}$$

Tank Input Impedance


SRC example

$$z_{in} = sL_r + \frac{1}{sC_r} + R_e$$


$$H(s) = \frac{R_e}{z_{in}}$$

@ f_0 : $|H(s)|_{dB} = 0dB$ for all R_e

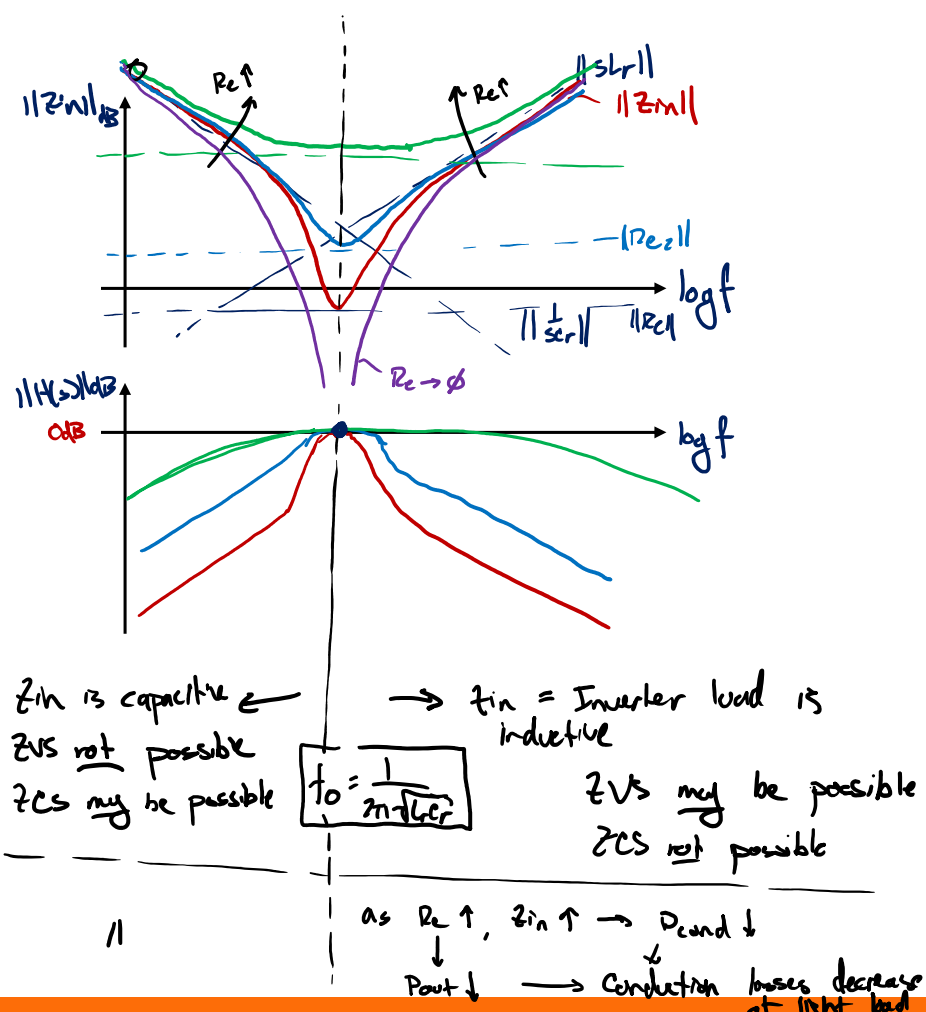
- as $R_e \rightarrow \phi$ $z_{in} \rightarrow \phi$
- cannot tolerate output short circuit
- z_{in} is resistive



Series Resonant Tank

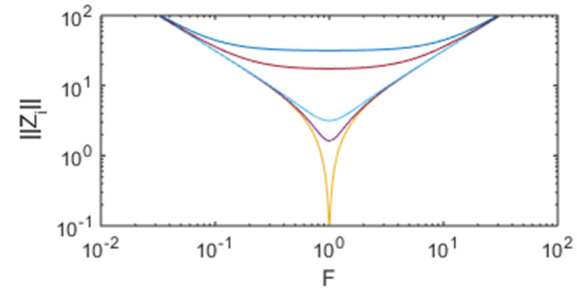

not log scale \rightarrow

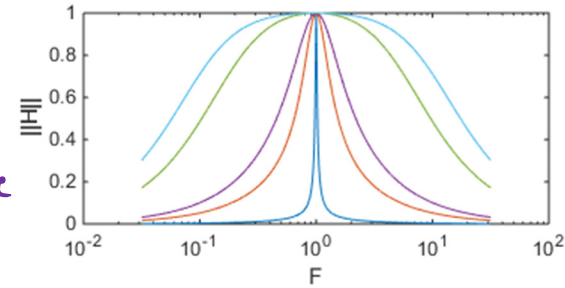

Parallel Resonant Converter

