

Tank Input Impedance


SRC example

$$z_{in} = sL_r + \frac{1}{sC_r} + R_e$$


$$H(s) = \frac{R_e}{z_{in}}$$

@ f_0 : $|H(s)|_{0dB} = 0dB$ for all R_e

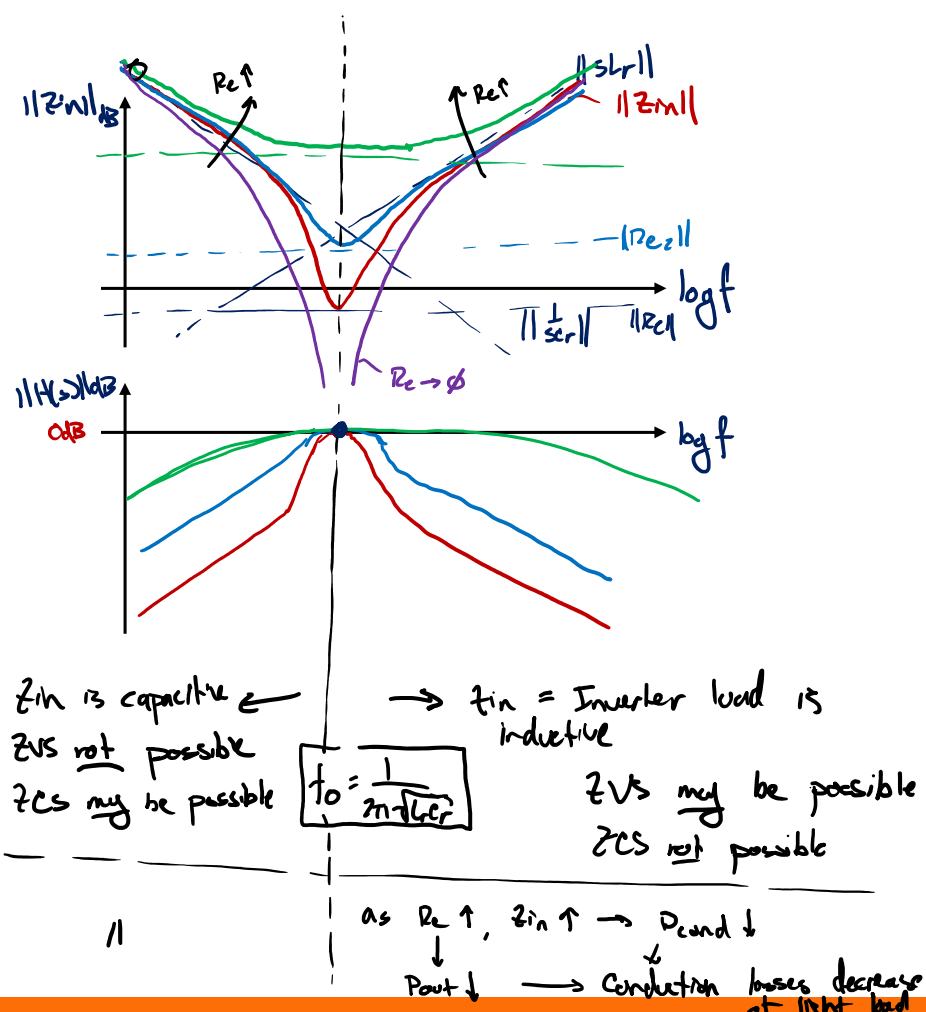
- as $R_e \rightarrow \phi$ $z_{in} \rightarrow \phi$
- cannot tolerate output short circuit
- z_{in} is resistive




Series Resonant Tank

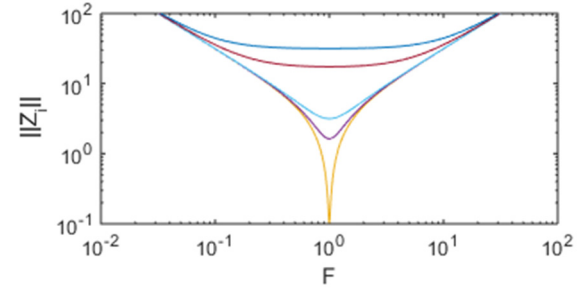


not log scale \rightarrow

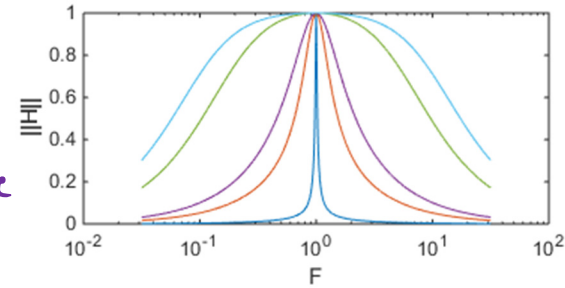

Parallel Resonant Converter

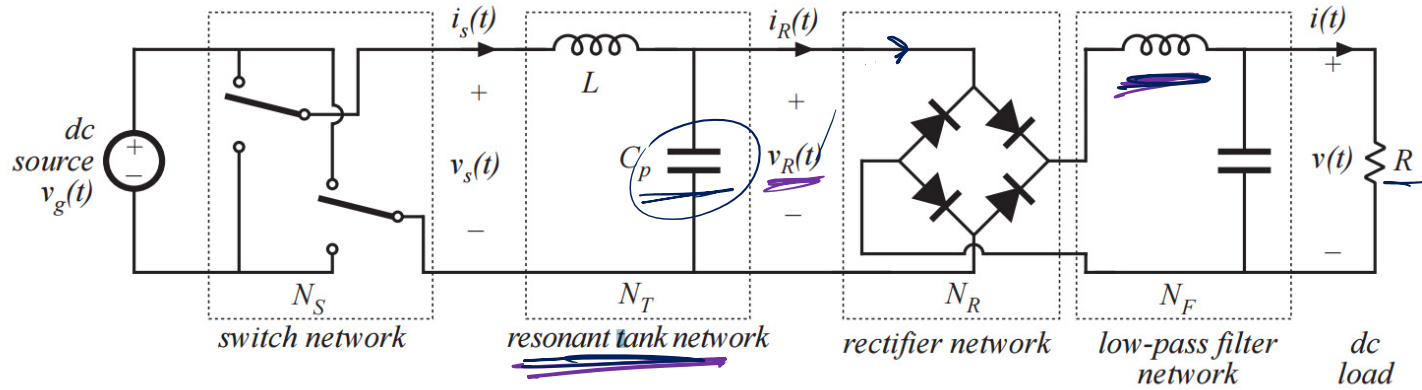


PRC Tank Input Impedance

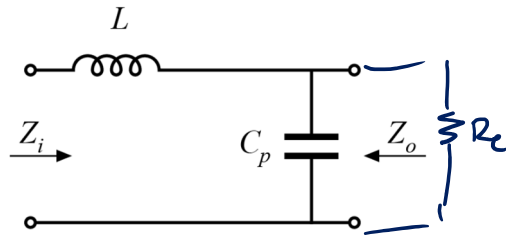

$$Z_{in} = sL + \frac{1}{sC_p} \parallel R_e$$

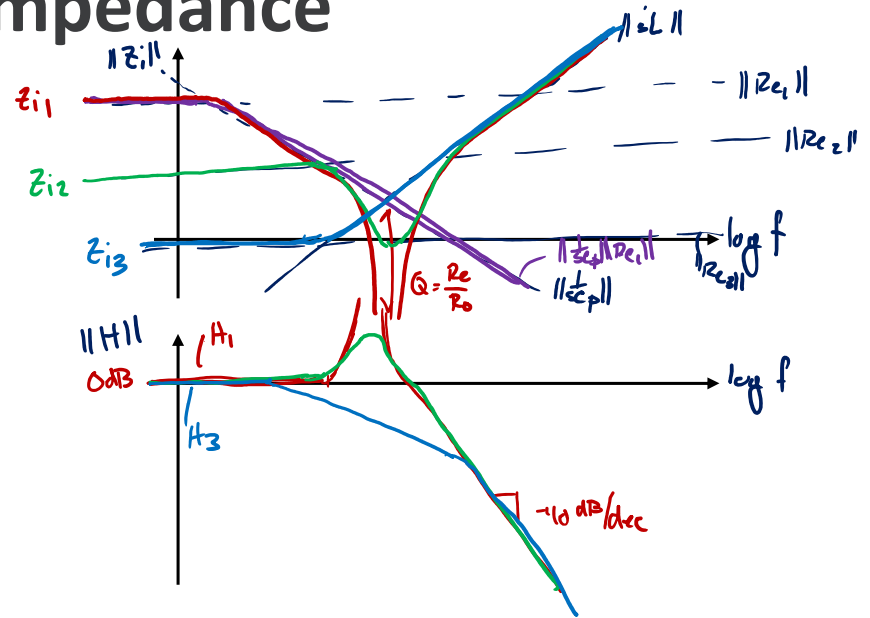
$$H(s) = \frac{\frac{1}{sC_p} \parallel R_e}{Z_{in}}$$





PRC Tank

Textbook Theorem 1



- 19.4.2 in 2nd Edition
- 22.4 in 3rd Edition
- If tank is purely reactive $\|Z_i(j\omega)\|$ is a purely monotonic function of R_e
- Only need to look at $Z_{i\infty} = Z_i|_{R_e \rightarrow \infty}$ and $Z_{i0} = Z_i|_{R_e \rightarrow 0}$; all other curves are monotonically decreasing/increasing in between

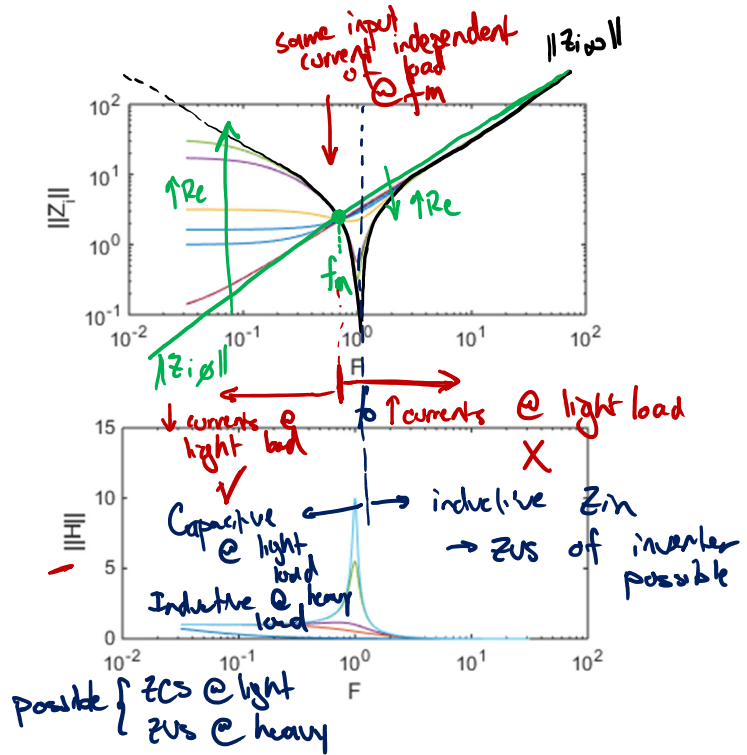

LCC

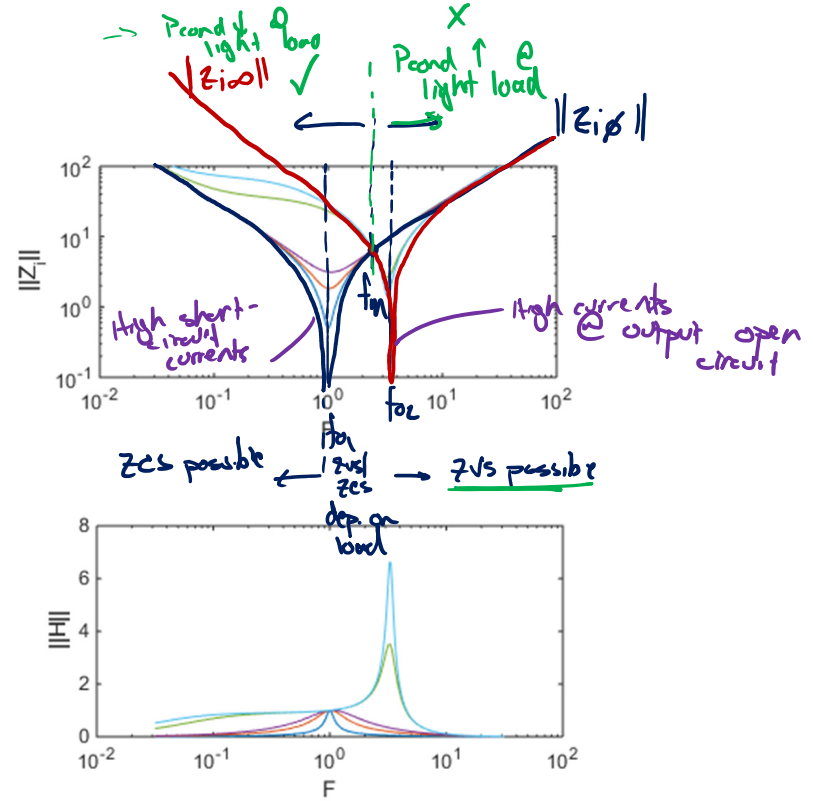
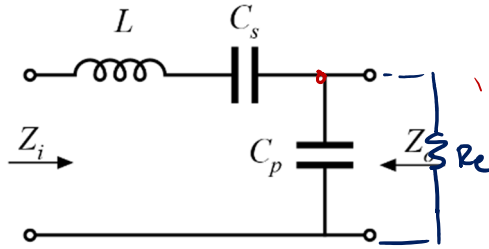


LLC

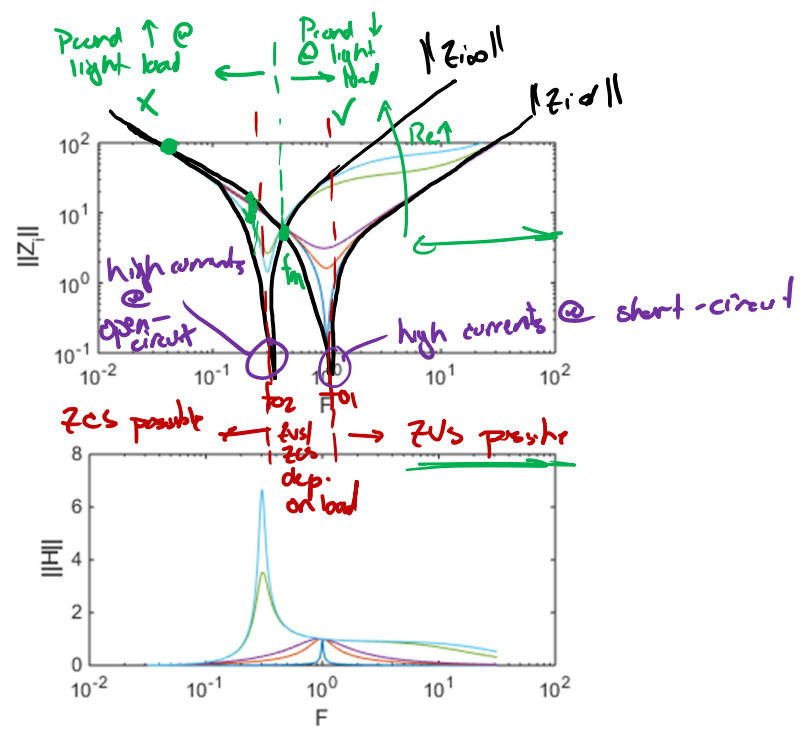
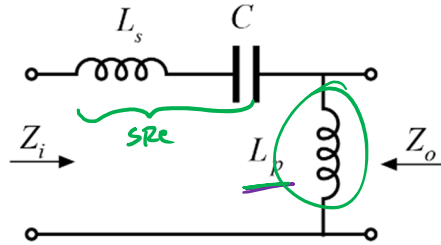


Tank Summary (1/2)

Series

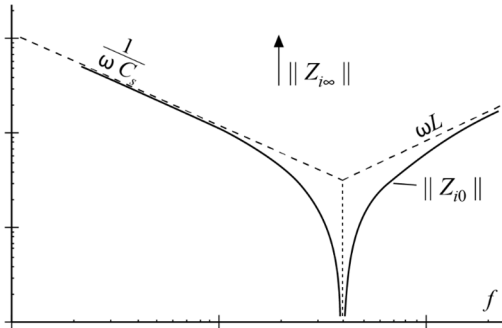
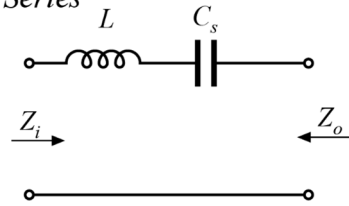


Parallel

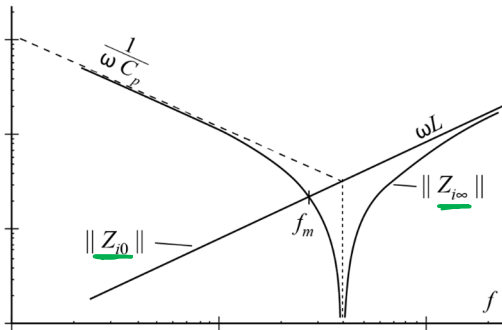
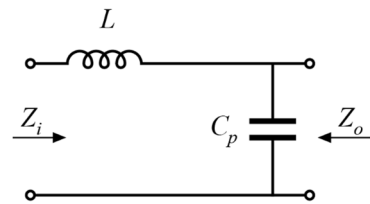


Tank Summary (2/2)


LCC

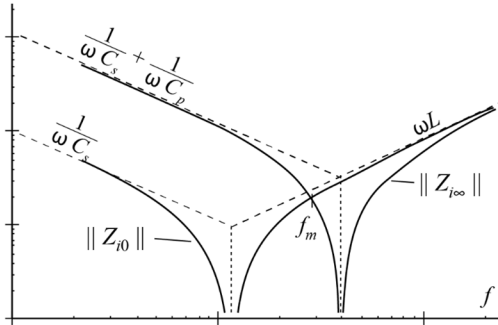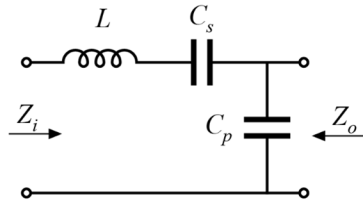


LLC

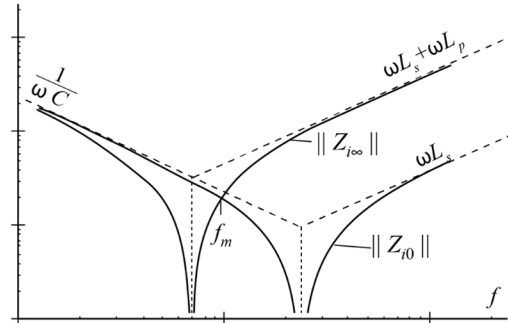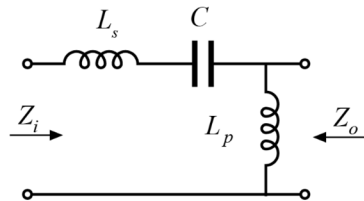



Series Resonant Tank – Subharmonic Modes

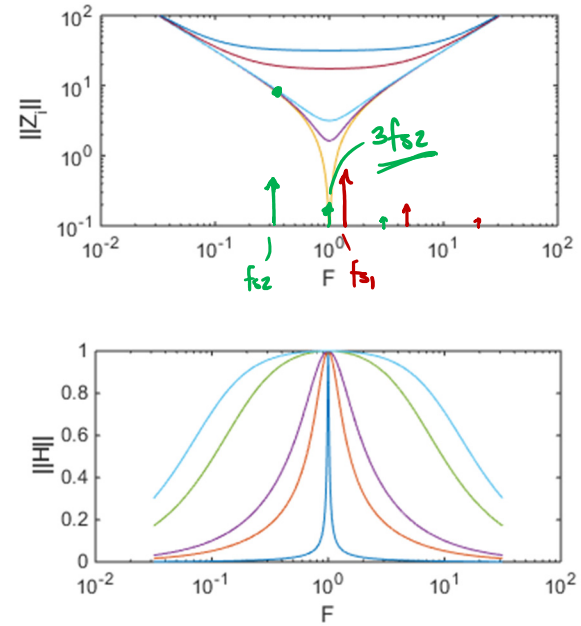


Subharmonic Modes - High Q

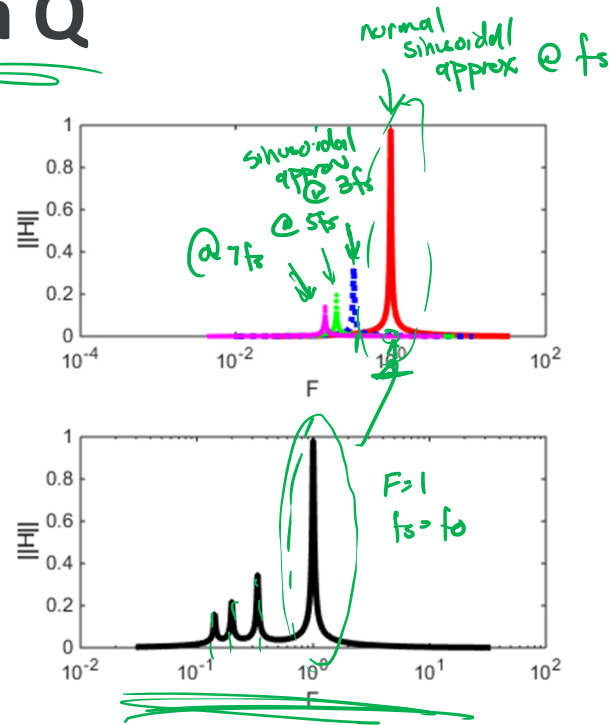

Subharmonic Modes – Low Q

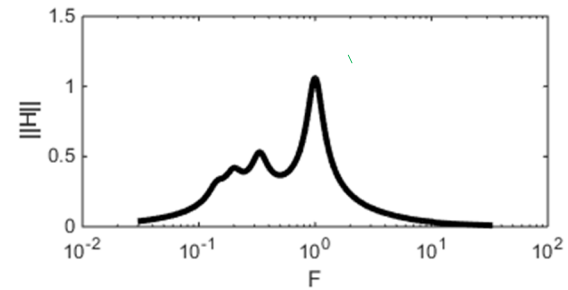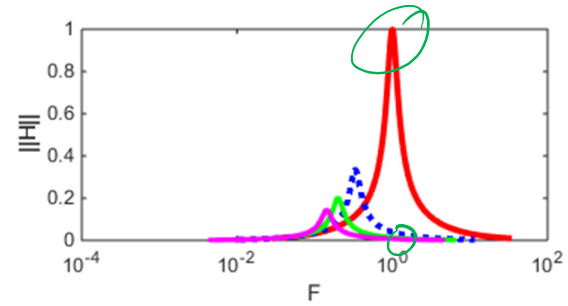

SRC Control Plane

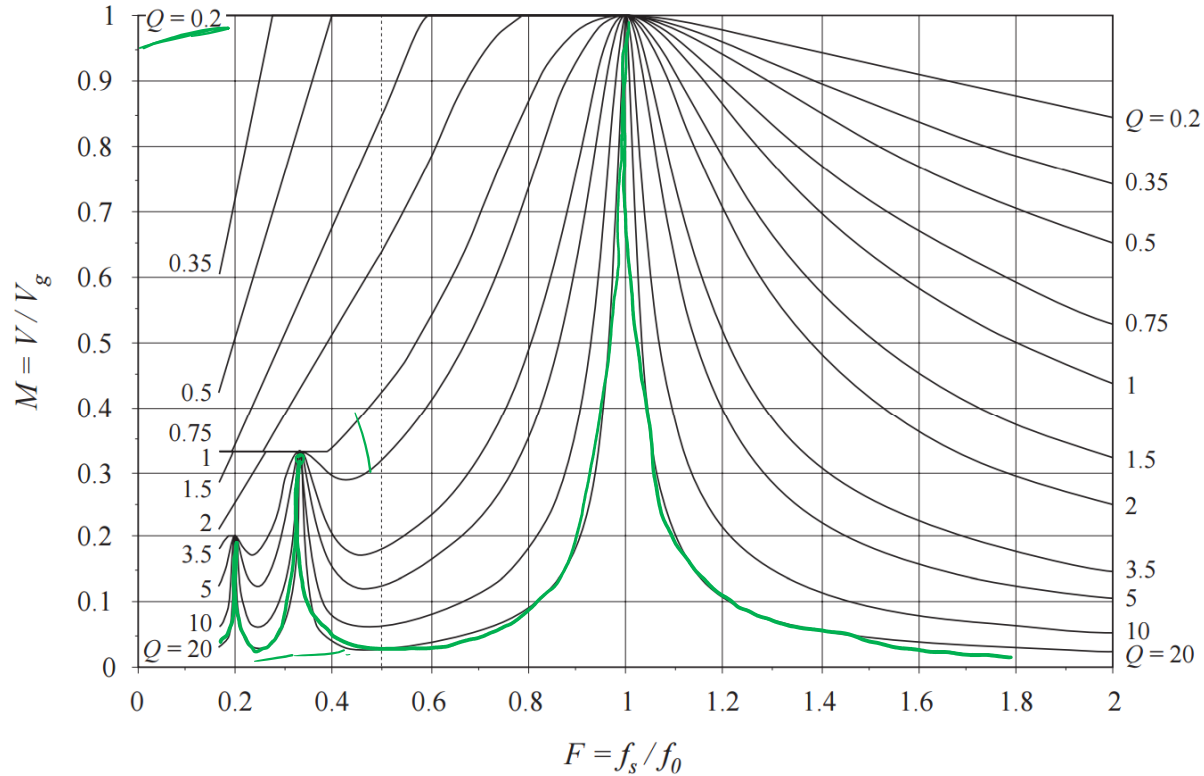

SRC Mode Boundaries

